



# CSCI 150

## Introduction to Digital and Computer System Design

### Lecture 2: Combinational Logical Circuits I



Jetic Gū

# Overview

- Focus: Boolean Algebra
- Architecture: Combinatory Logical Circuits
- Textbook v4: Ch2 2.1 2.2; v5: Ch2 2.1 2.2
- Core Ideas:
  1. Logical Gates
  2. Introduction to LogicWorks

# Logic Gates


And, Or, Not Gates, LogicWorks

# What is a Logic Gate?




- A basic circuit unit implemented using transistors and interconnections
- We when analysing a digital circuit, are not concerned with the internals of a gate, but only it's external properties
- Performs a single logical operation  
operate on one or more binary input signals to produce an output signal
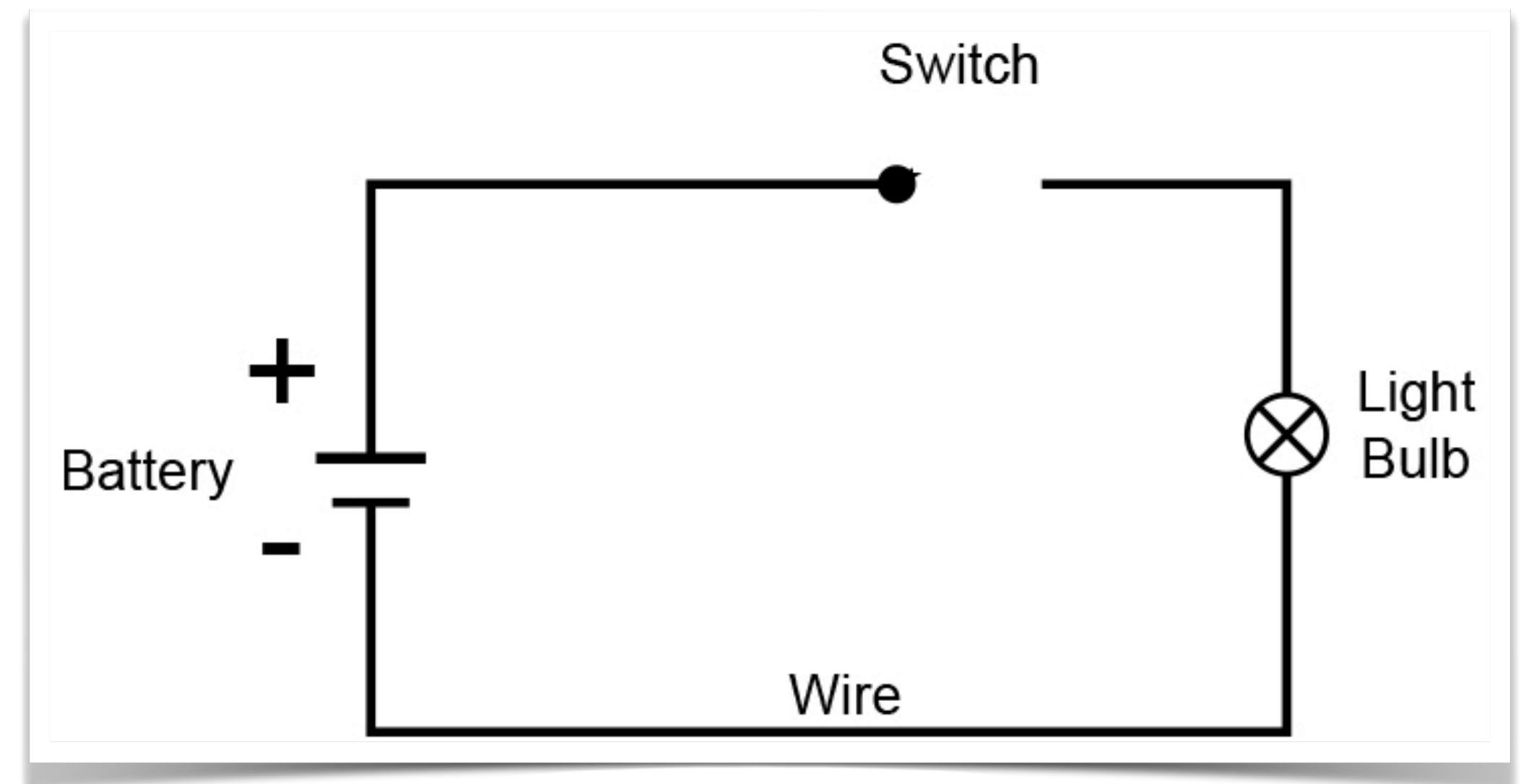
# What is a Logic Gate?


- Similar to in electric circuit design, we are not concerned with the design of the lightbulb or battery, but we know what it does.
- A logic gate is like that, we know it's external logic properties, that's enough.




# First 3 Gates

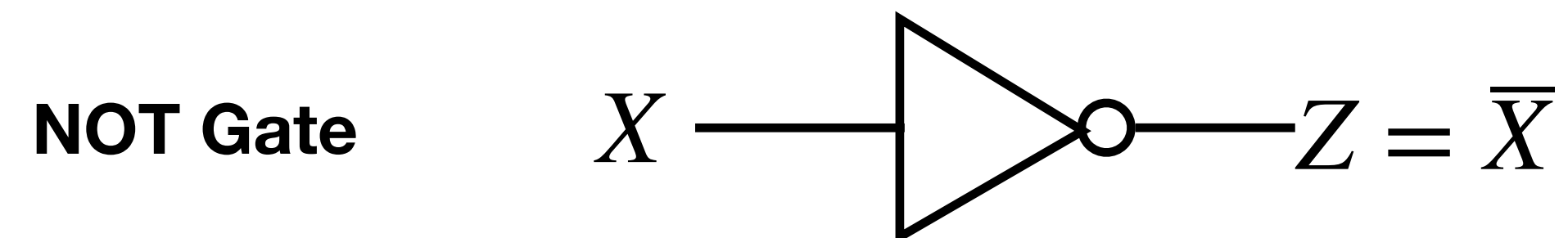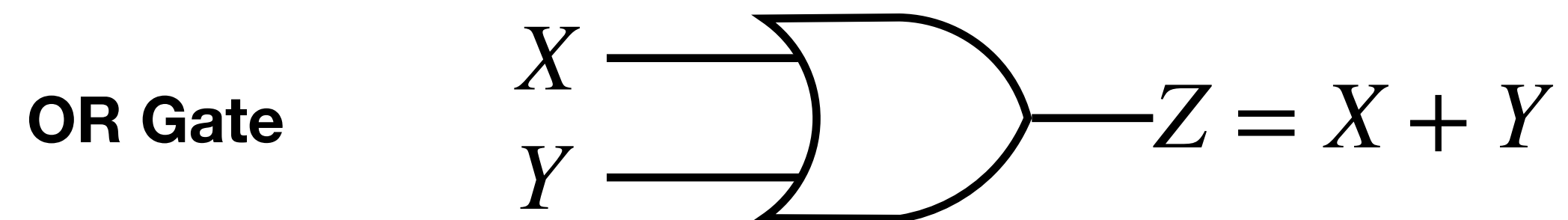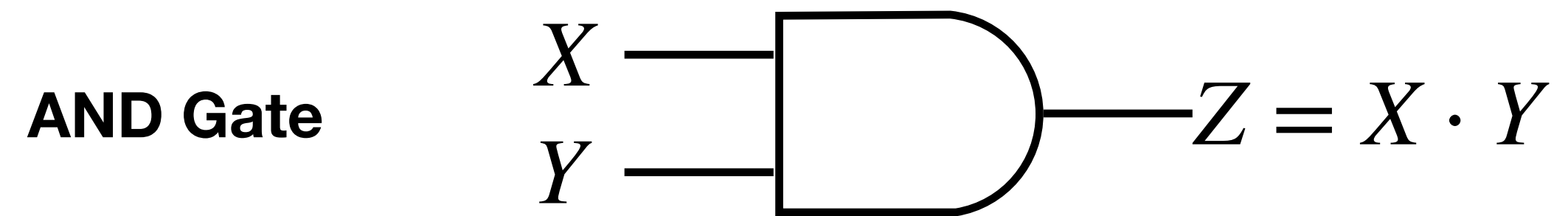

# First 3 Gates

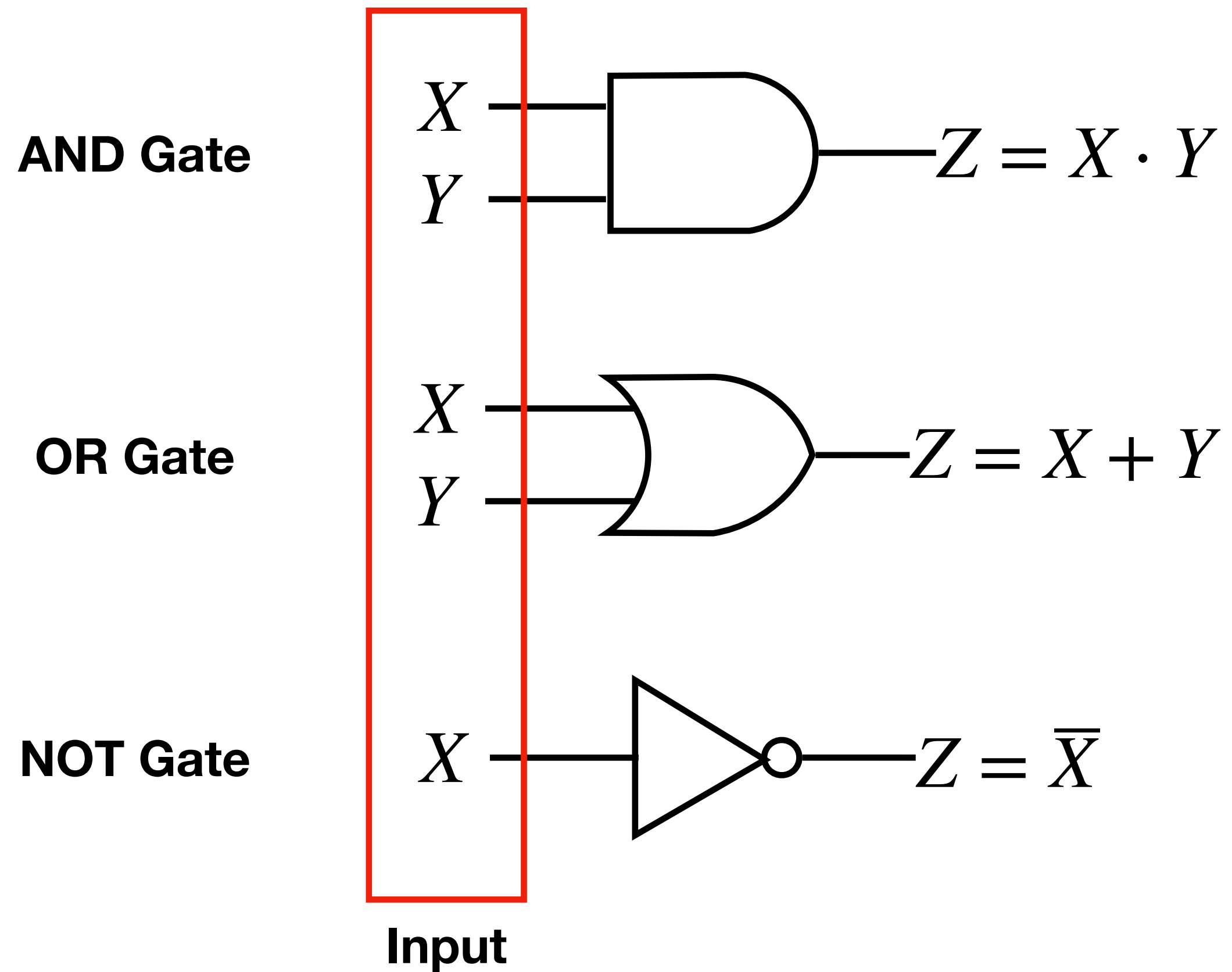


# First 3 Gates

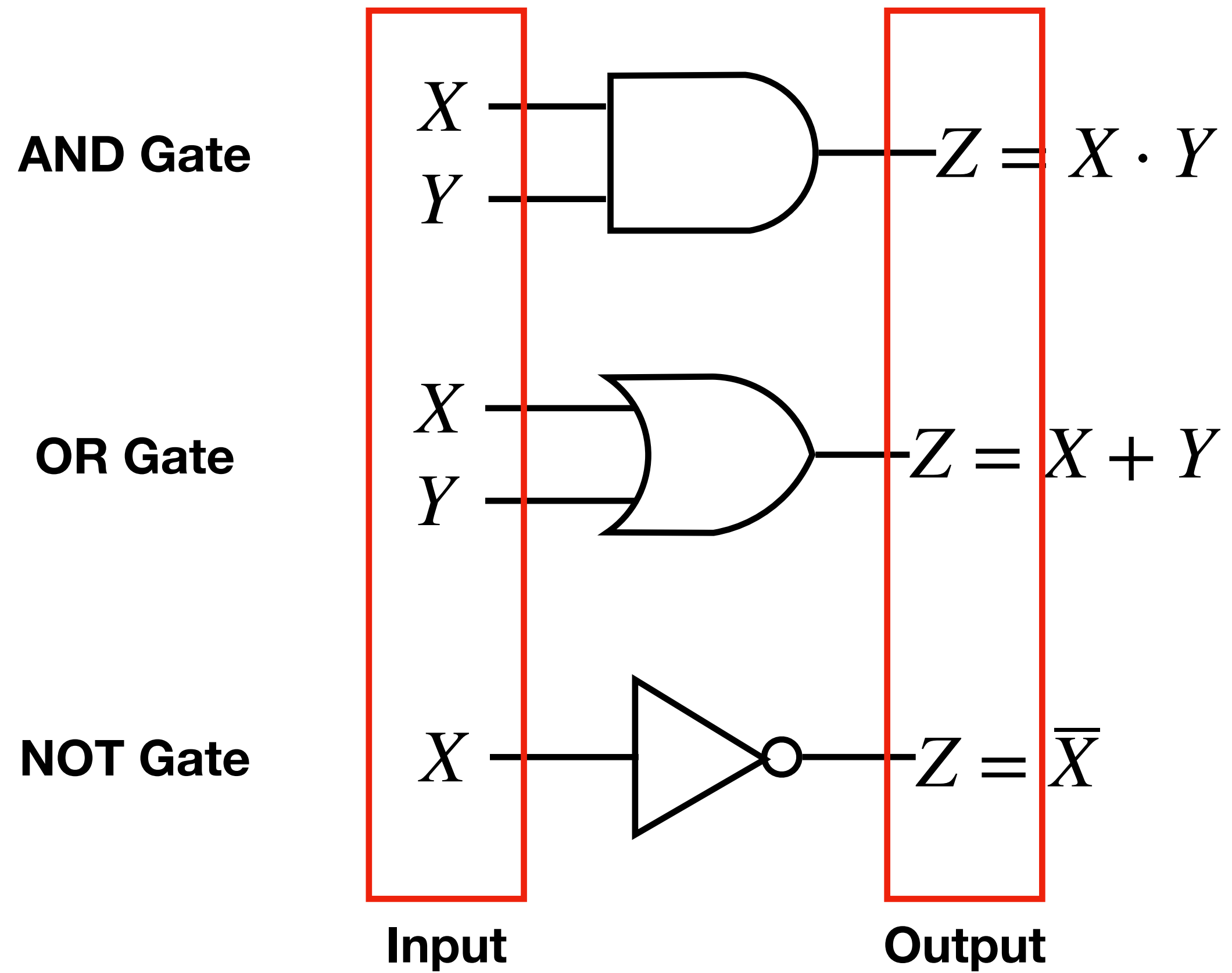



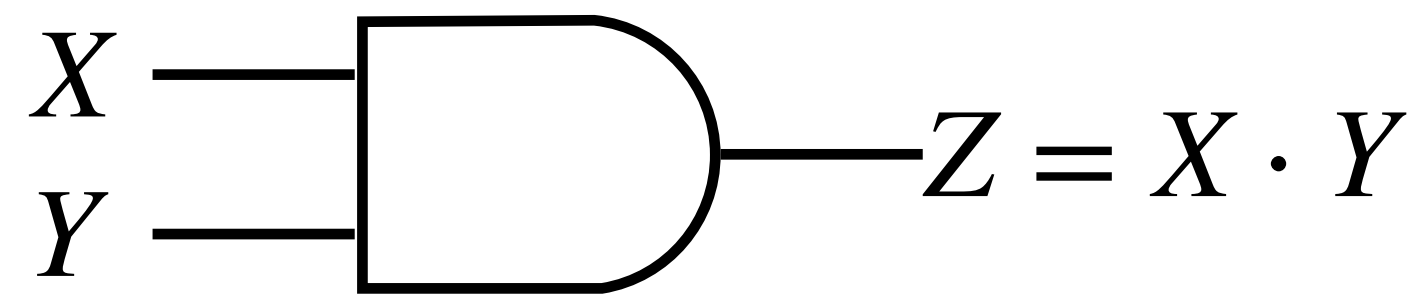
# AND Operator and Boolean Algebra / Binary Logic



- Boolean Algebra
  - Each variable can only have one of two values:
    - TRUE/ON/1
    - False/OFF/0
  - AND:  $Z$  is equal to  $X$  AND  $Y$ 
    - Operator:  $\cdot$  (`\cdot`)

# AND Operator and Boolean Algebra

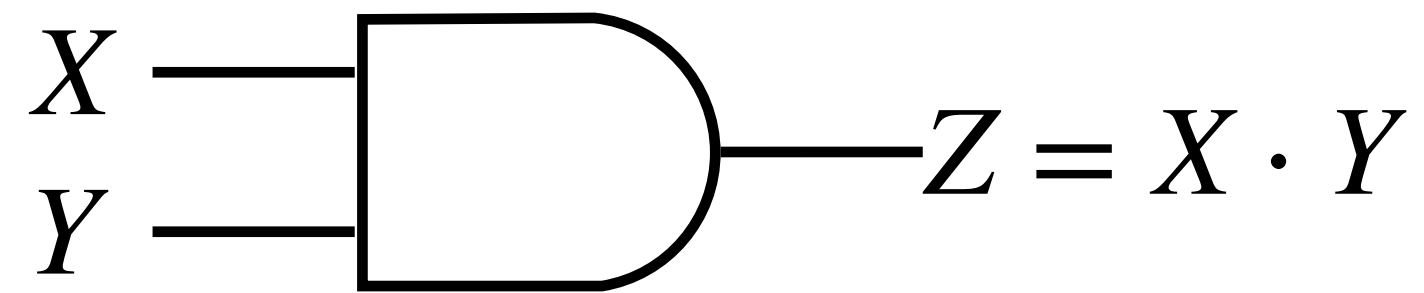


AND Truth Table

$X$	$Y$	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

- AND:  $Z$  is equal to  $X$  AND  $Y$
- Operator:  $\cdot$  (`\cdot`)
- Truth Table
  - Left: all combinations of input values
  - Right: corresponding output values

# OR Operator

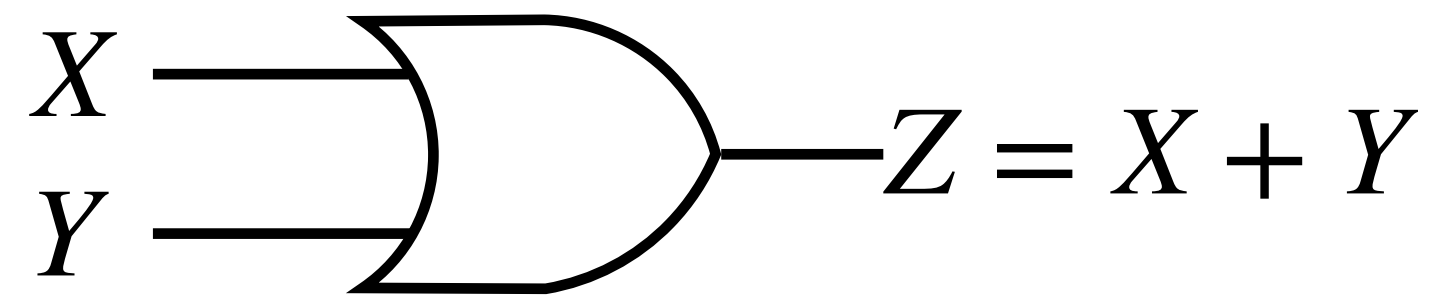


OR Truth Table

$X$	$Y$	$Z = X + Y$
0	0	0
0	1	1
1	0	1
1	1	1

- OR:  $Z$  is equal to  $X$  or  $Y$
- Operator:  $+$

# NOT Operator

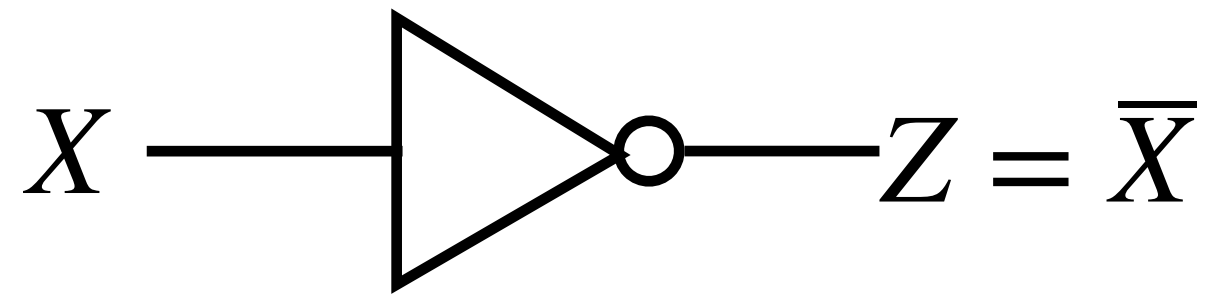

NOT Truth Table

$X$	$Z = \bar{X}$
0	1
1	0

- NOT:  $Z$  is equal to NOT  $X$
- Operator:  $\bar{X}$  ( $\overline{X}$ )
- Also called: *Complement* operation;  
*Inverter* gate

# Logic Gate and Boolean Algebra

- Logic Gates
  - AND Gate, OR Gate, NOT Gate
  - Actual physical components
- Boolean Algebra Operators
  - AND ( $\cdot$ ), OR ( $+$ ), NOT ( $\bar{X}$ )
  - Mathematical Representations



**THEY HAVE  
DIFFERENCES!**

# Digital Logical Gates

- In math, everything happens simultaneously
- An equation like  $250 + 760 = 1010$  doesn't change with time/location
- In digital circuits, we have **electrons as 'messengers'**. They travel at about 2,200 kilometres per second
- Logic gates are tiny circuits, which means they still have internal components: even slower
- This means: there will be tiny delays called **Gate Delay**



# Digital Logical Gates

Timing Diagram

 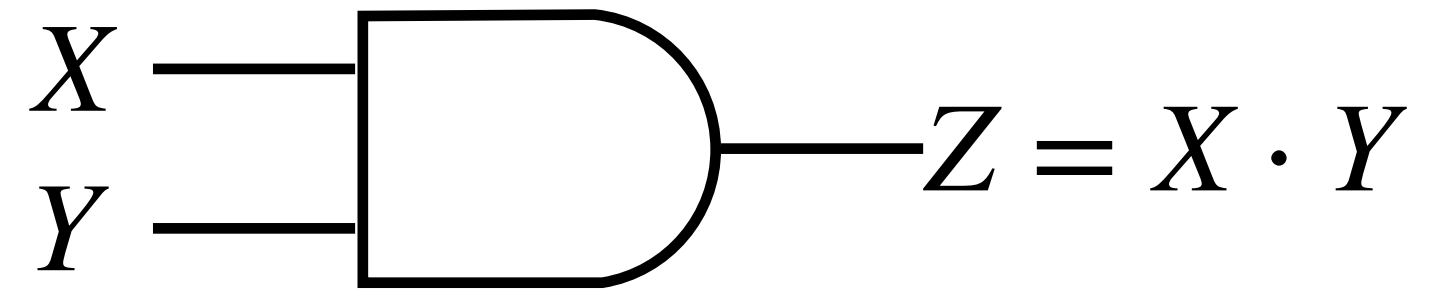

# Digital Logical Gates



Timing Diagram

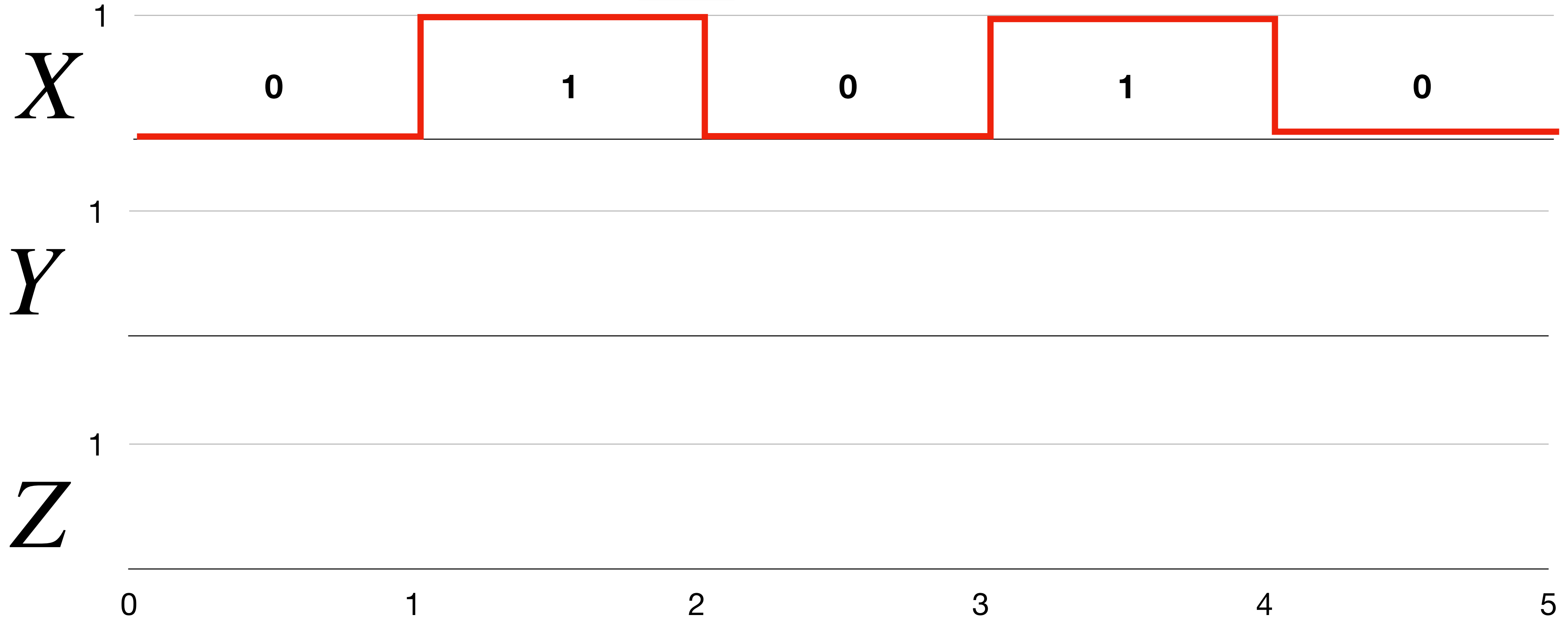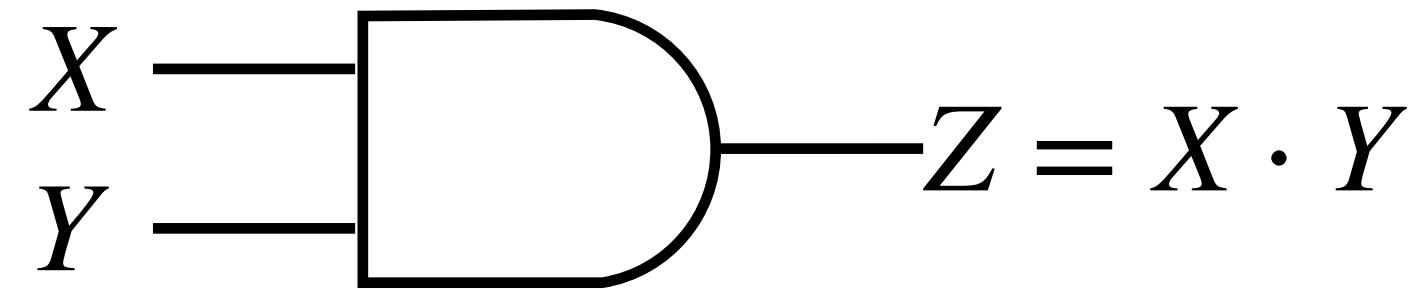





# Digital Logical Gates

Timing Diagram

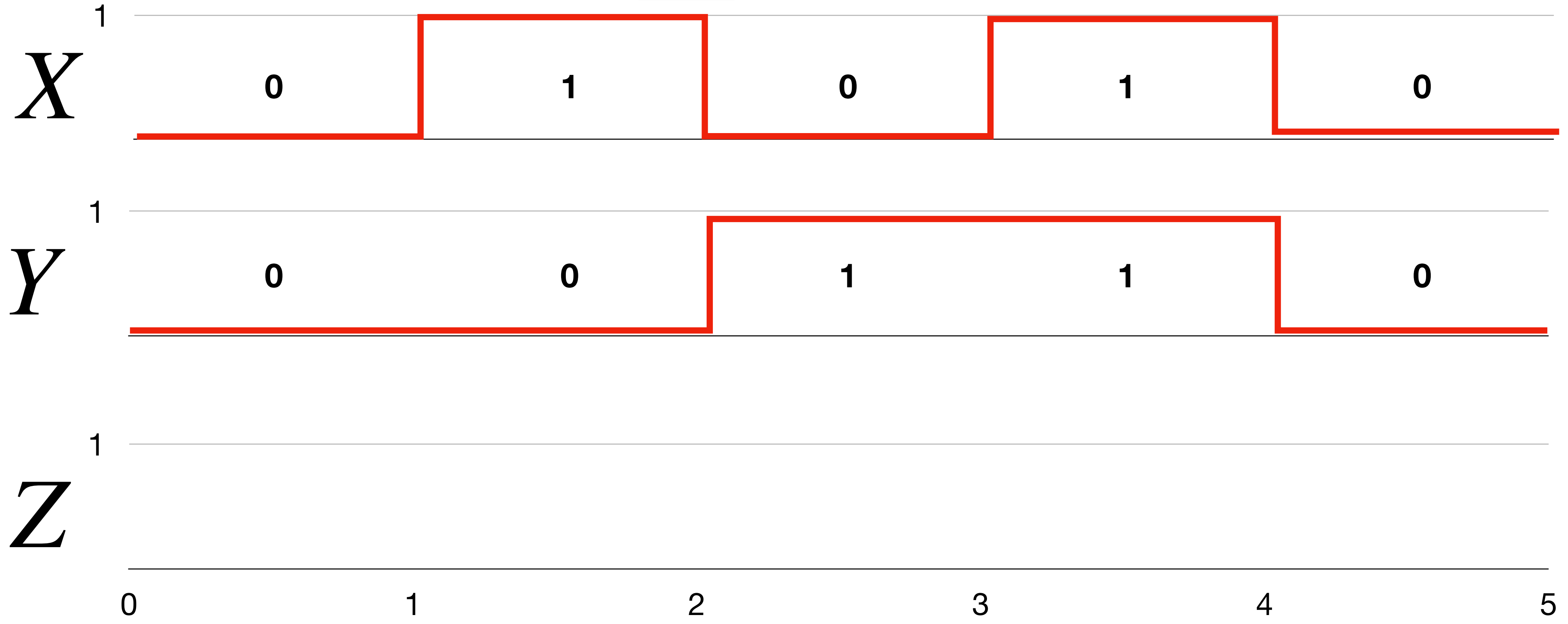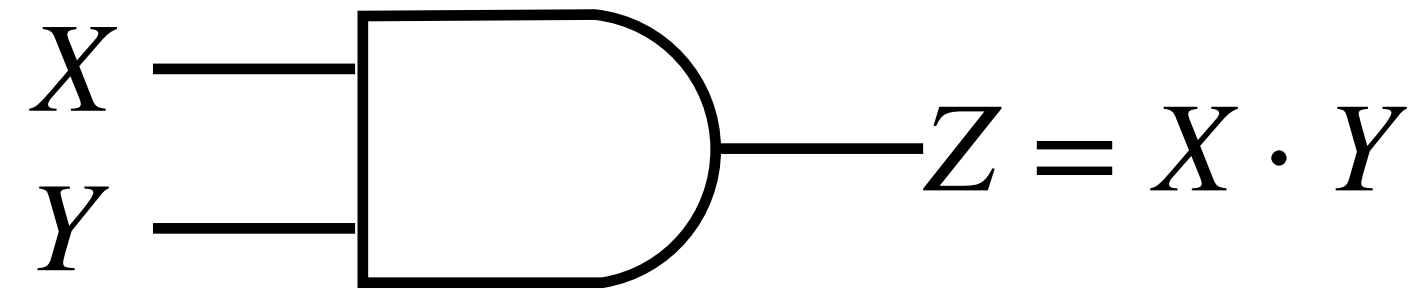



# Digital Logical Gates

Timing Diagram

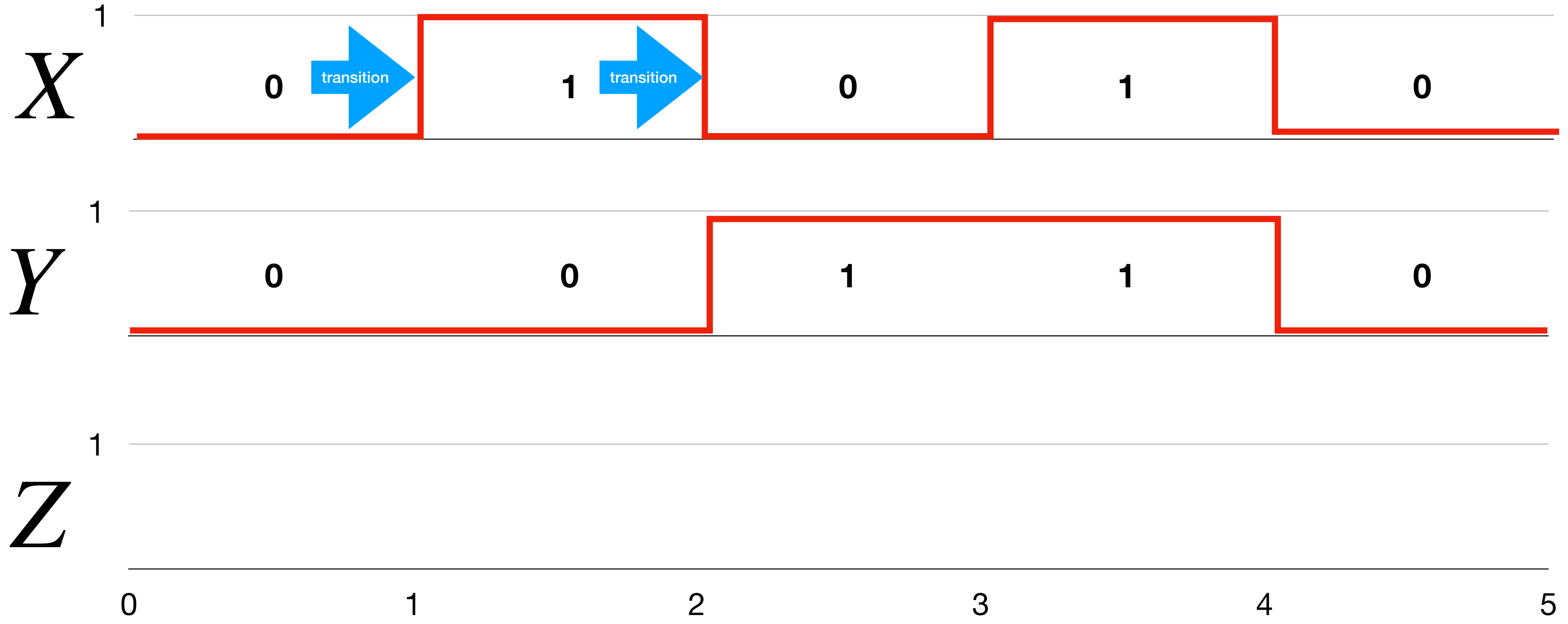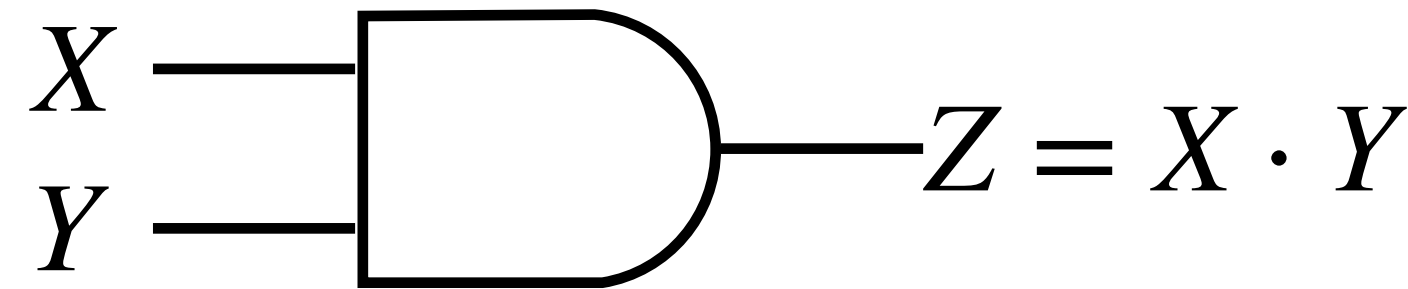



# Digital Logical Gates

Timing Diagram

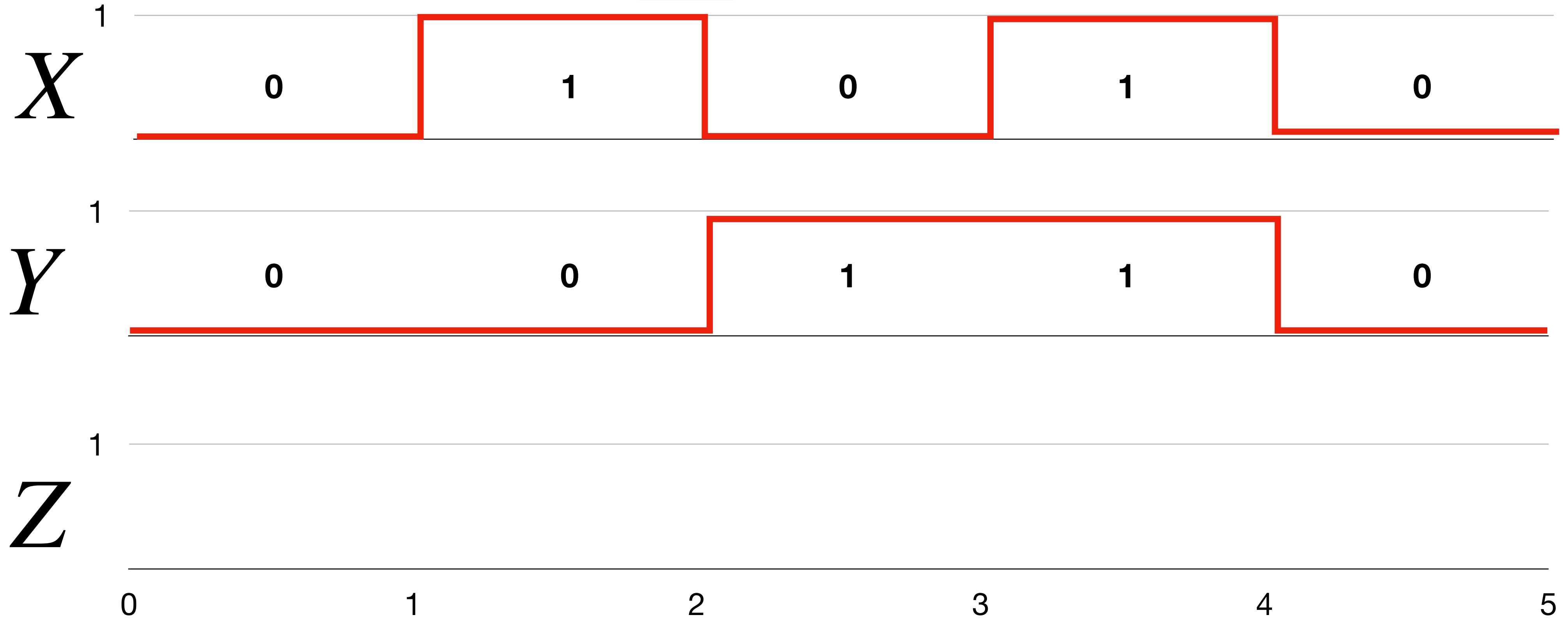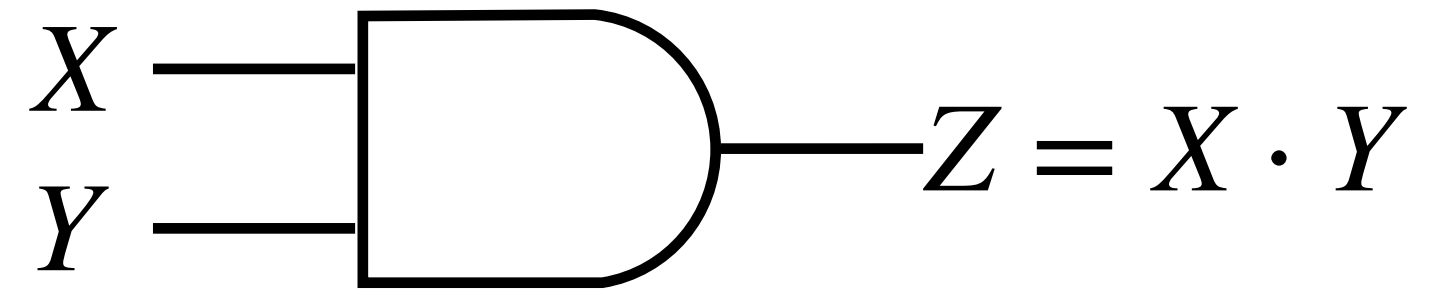




# Digital Logical Gates

Timing Diagram (**IDEAL**)

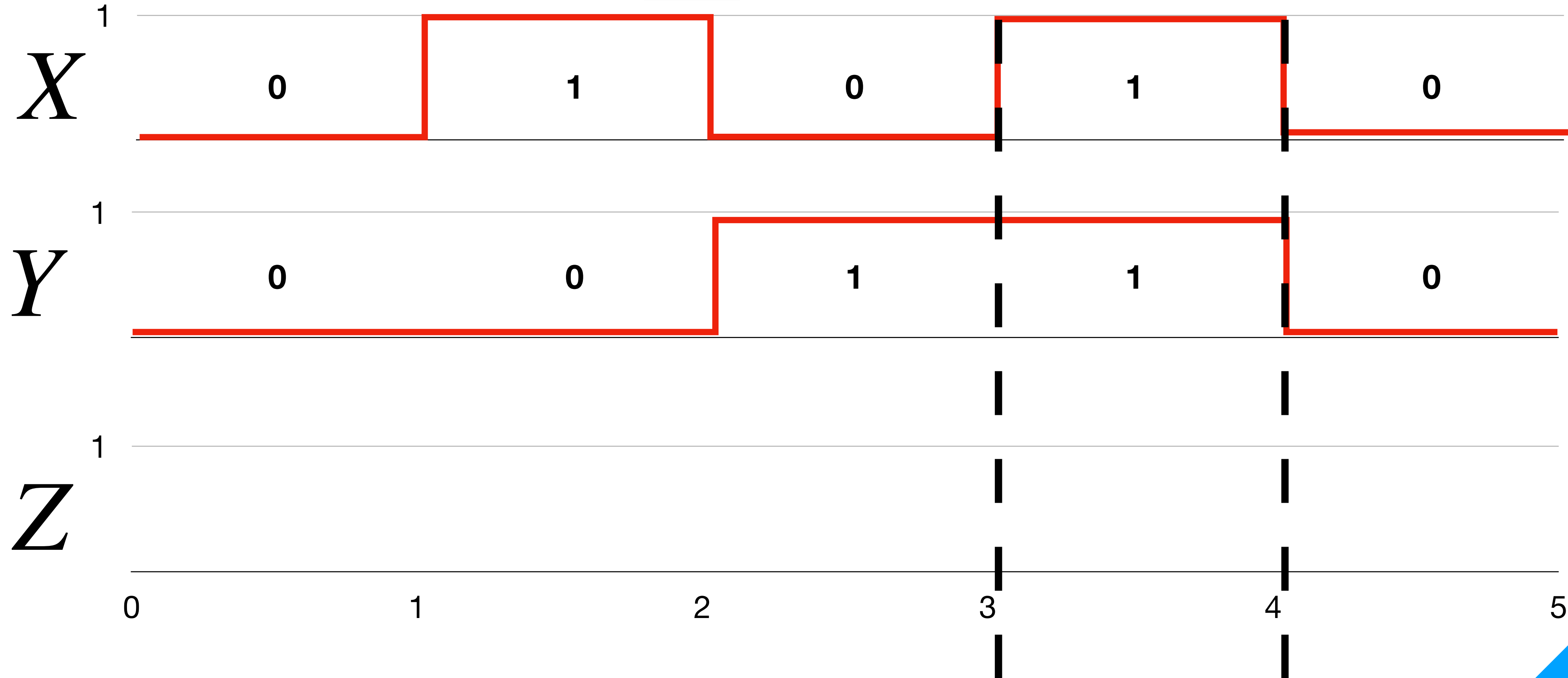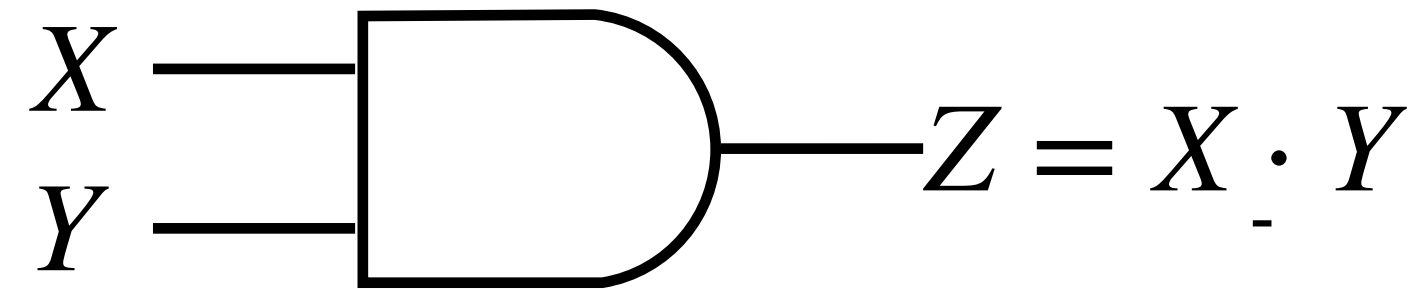



# Digital Logical Gates

Timing Diagram (**IDEAL**)

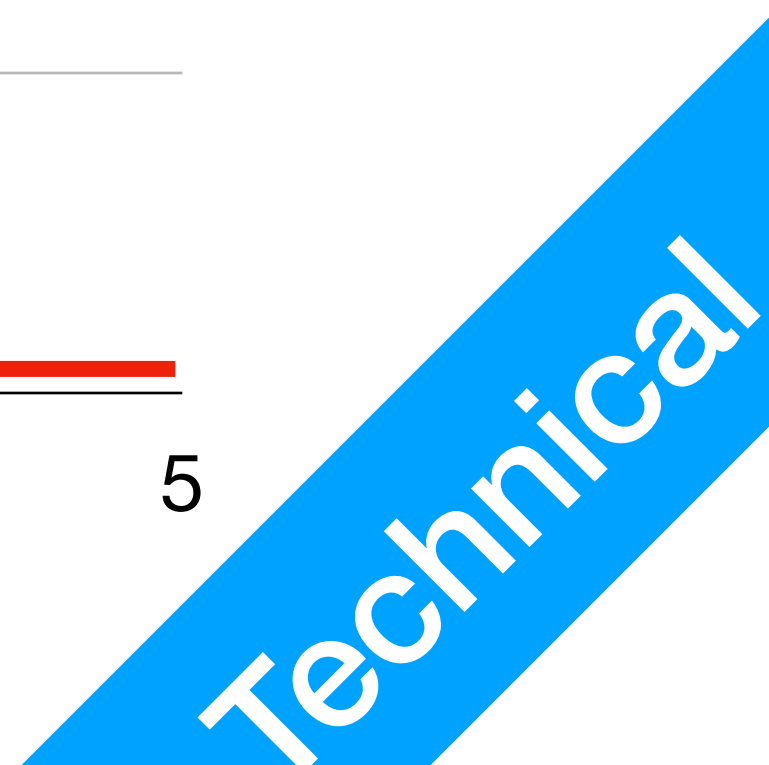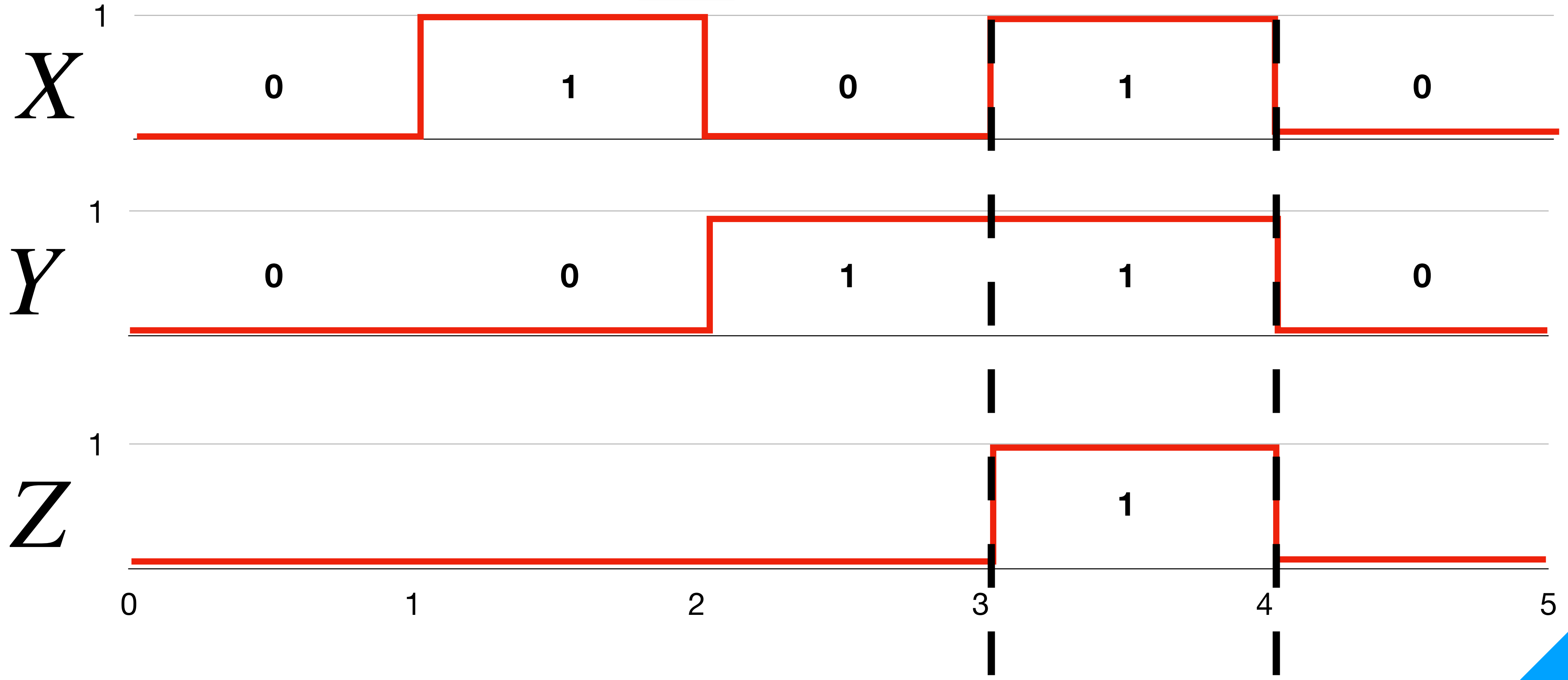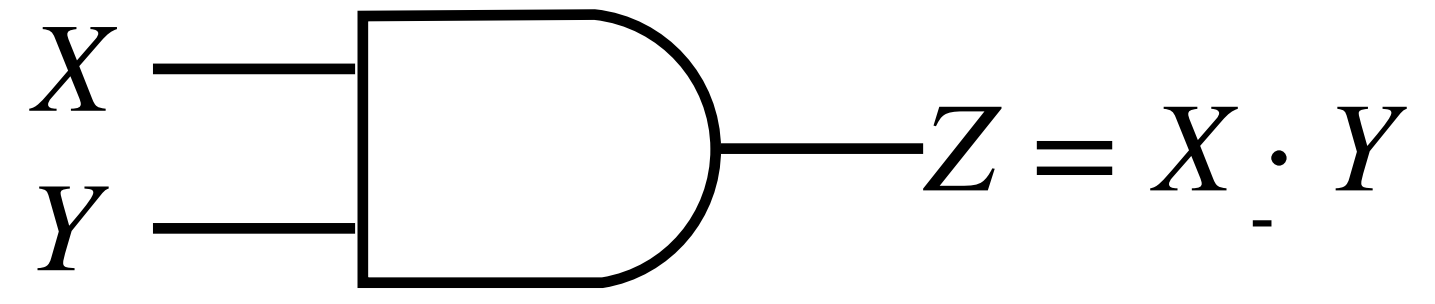




# Digital Logical Gates

Timing Diagram (**REALITY**)

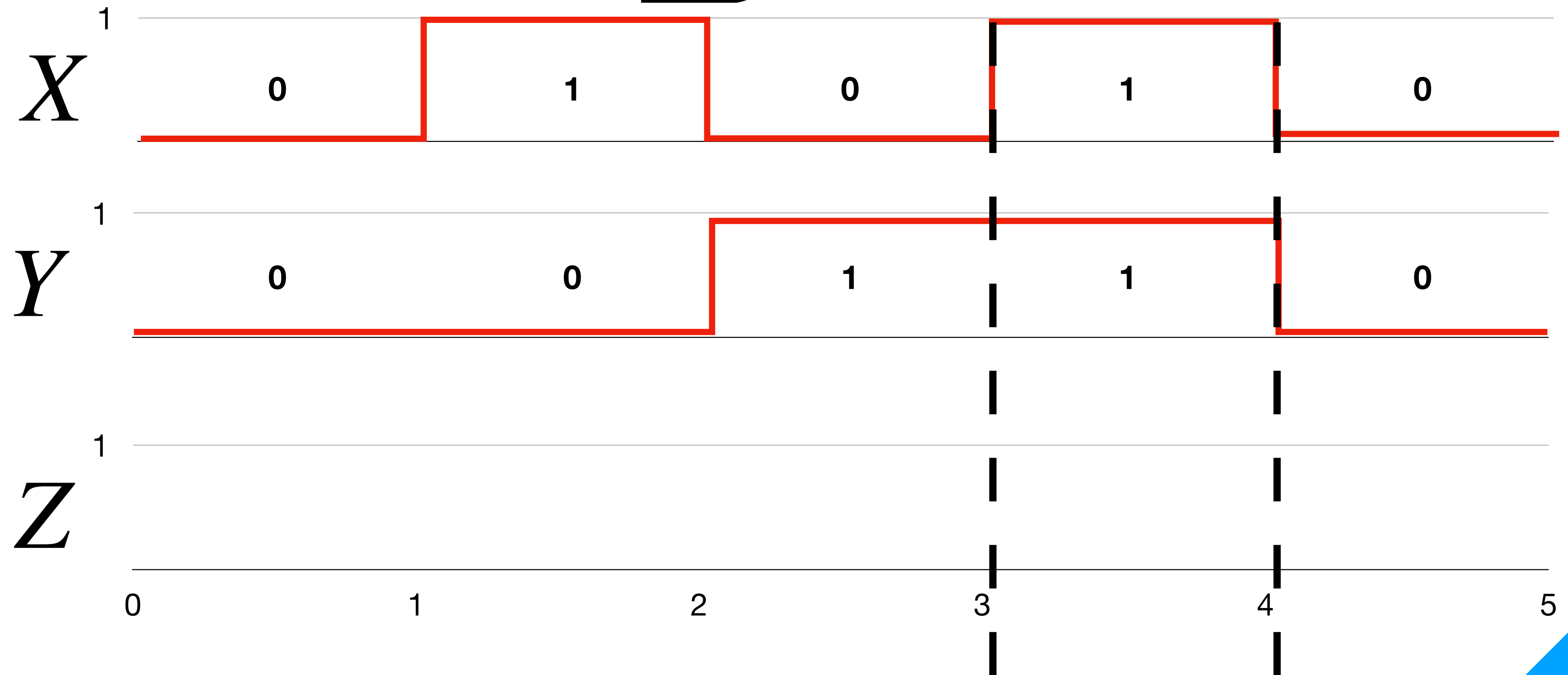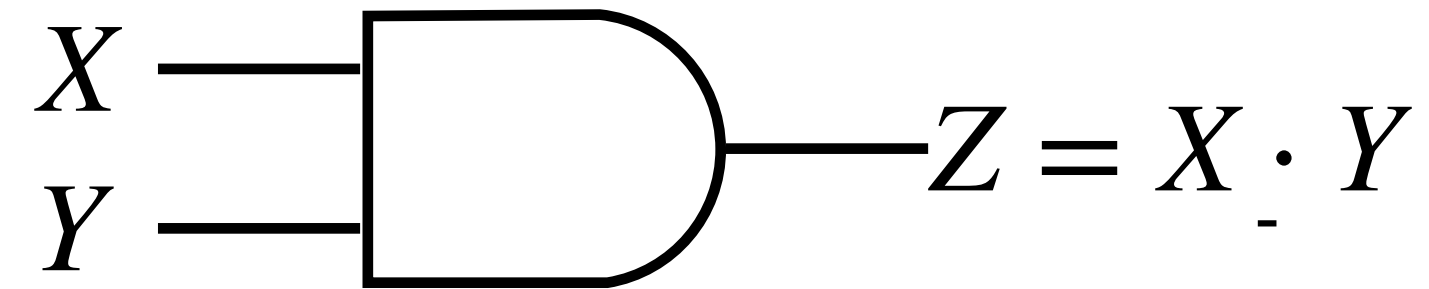



# Digital Logical Gates

Timing Diagram (**REALITY**)

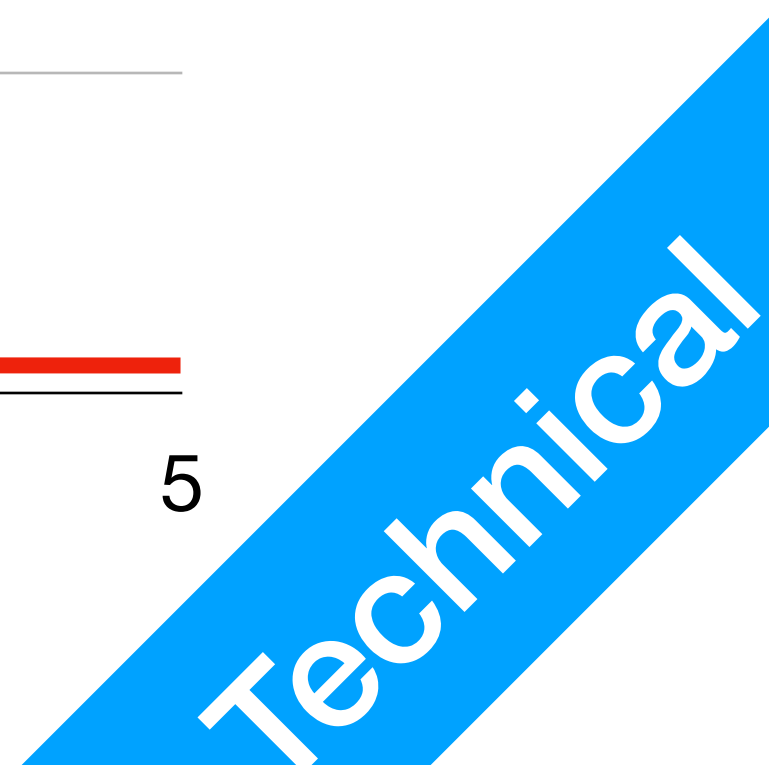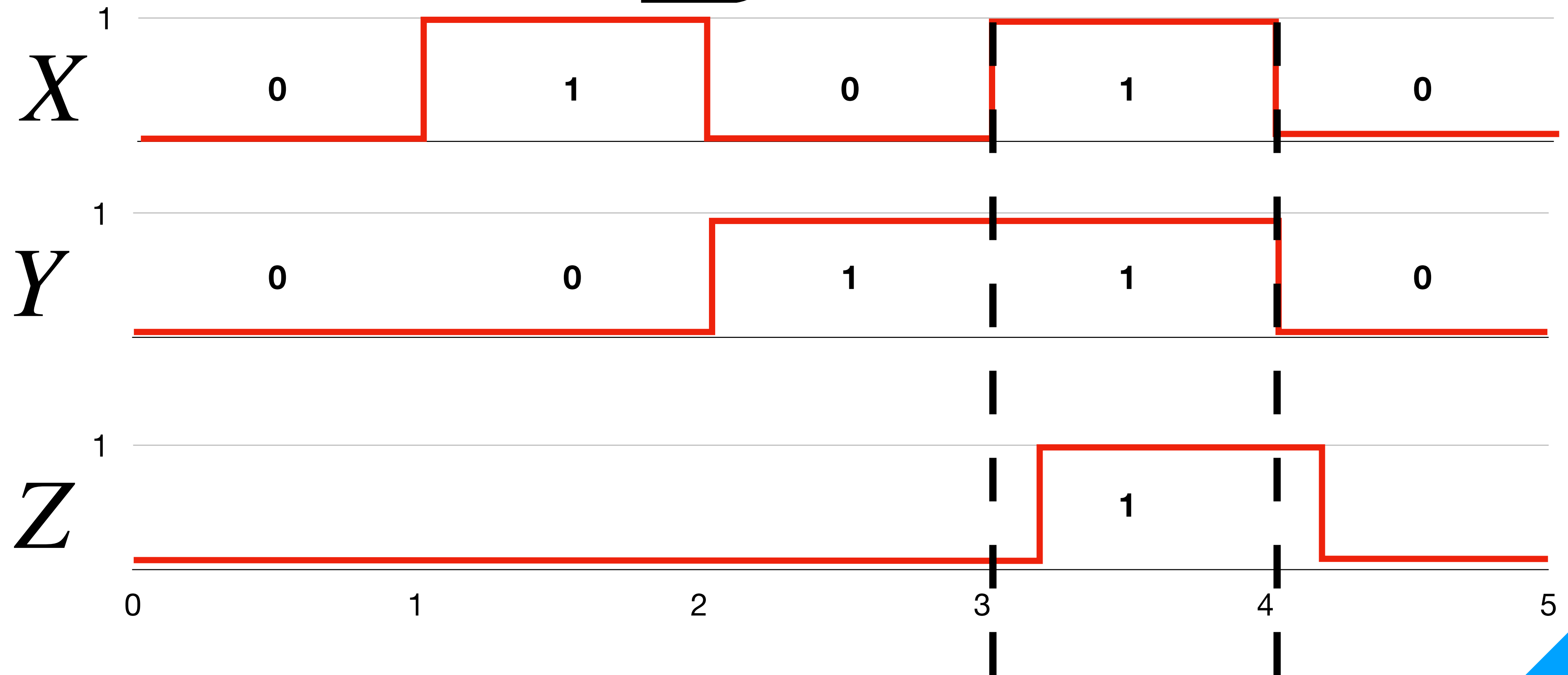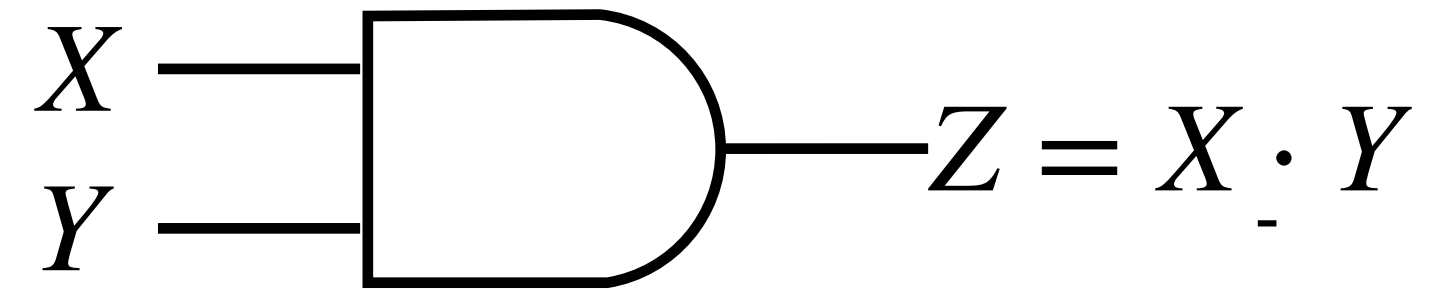

# Digital Logical Gates

Timing Diagram (**REALITY**)

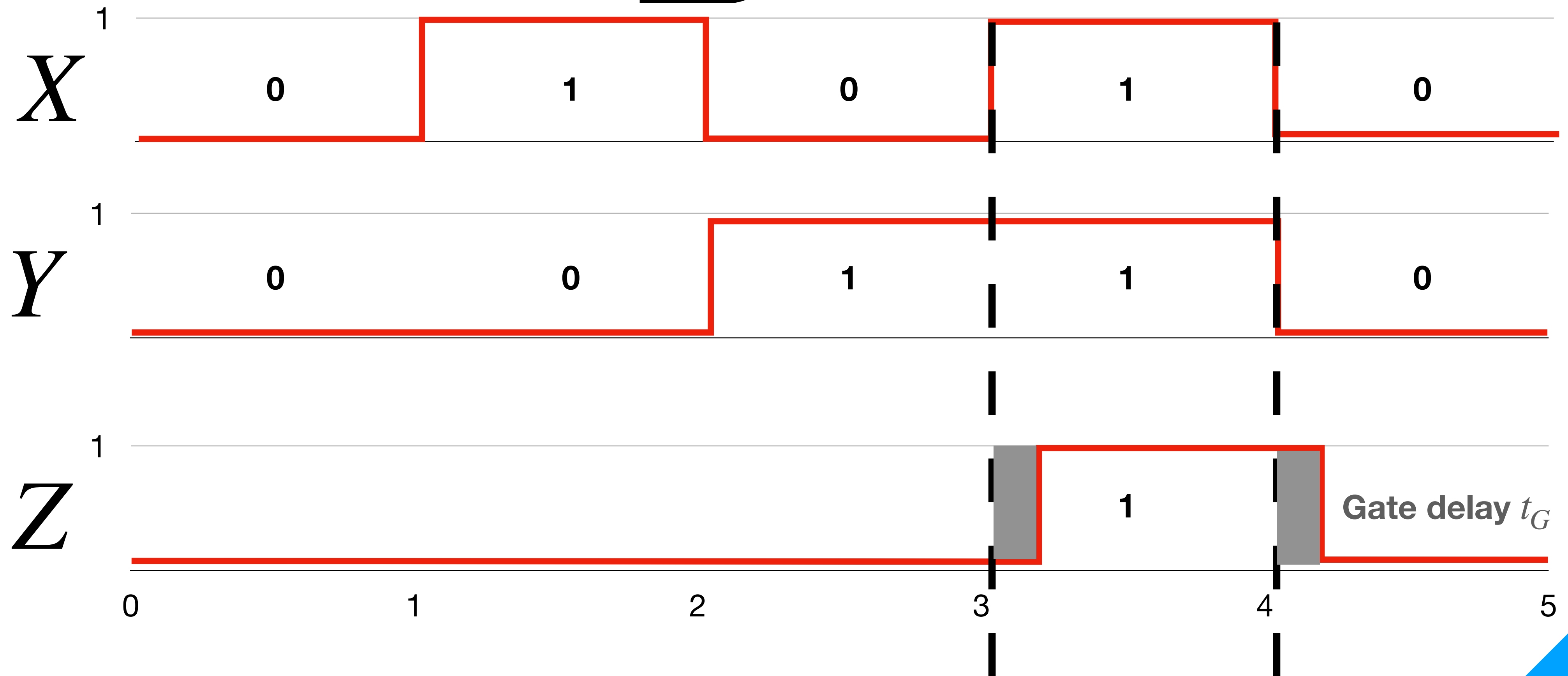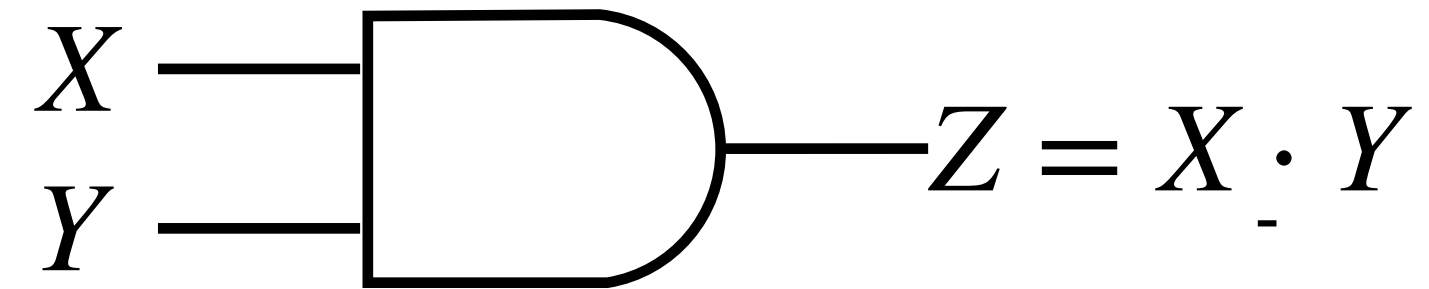




# Gate Delay

- Gate delay are small, but not ignorable in practice
  - for simulation, you can ignore it for now
- Gate delay differs for different types and implementations of Gates

# Simulation 1

Truth Table


$X$	$Y$	$Z$
0	0	
0	1	
1	0	
1	1	

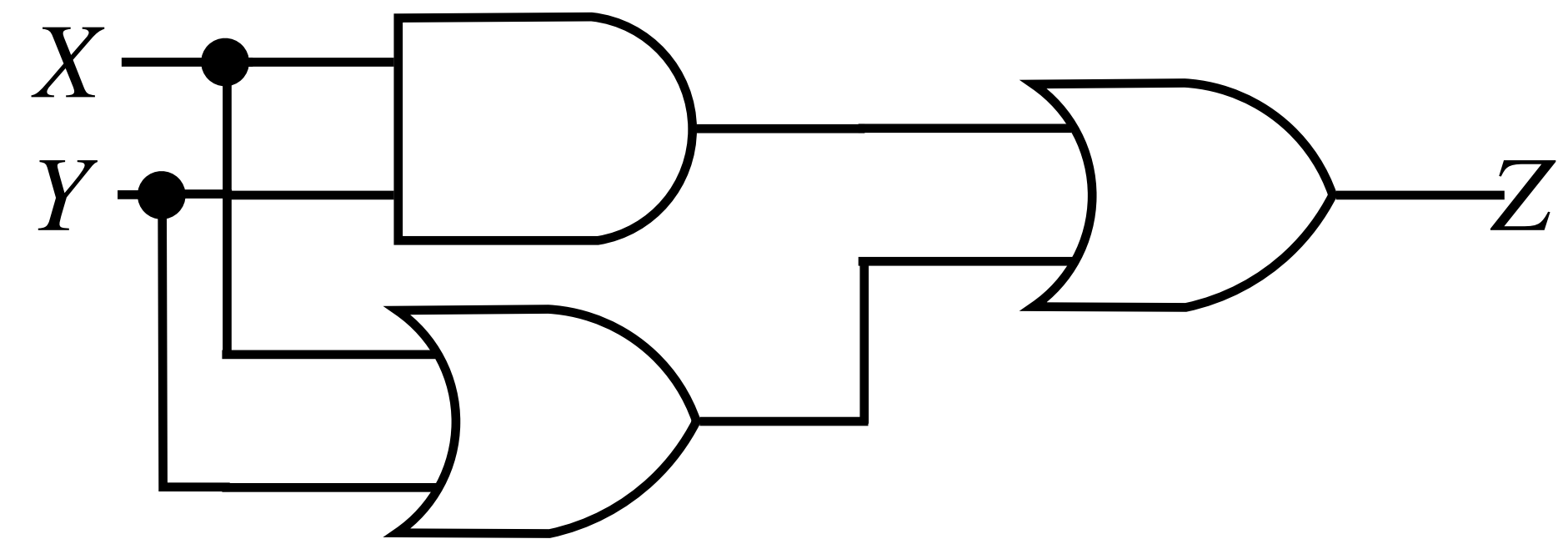

# Simulation 1

Truth Table


$X$	$Y$	$Z = (X \cdot Y) + (X + Y)$
0	0	
0	1	
1	0	
1	1	

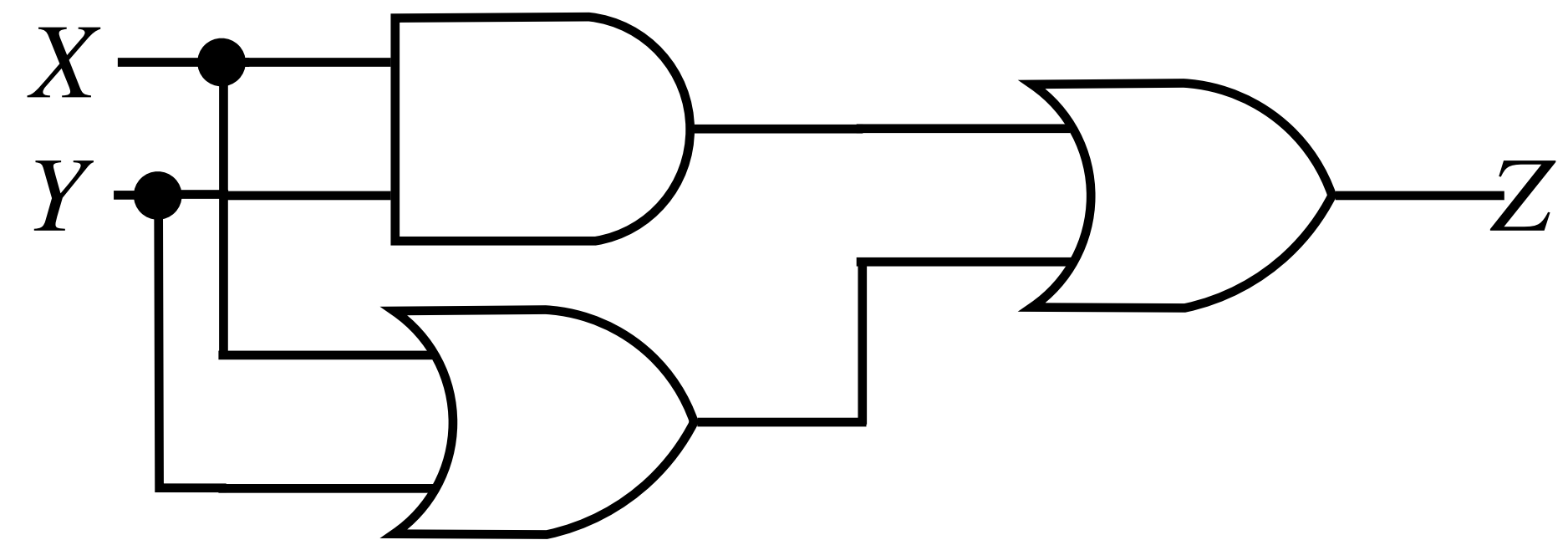

# Simulation 2

Truth Table


$X$	$Y$	$Z$	$F$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

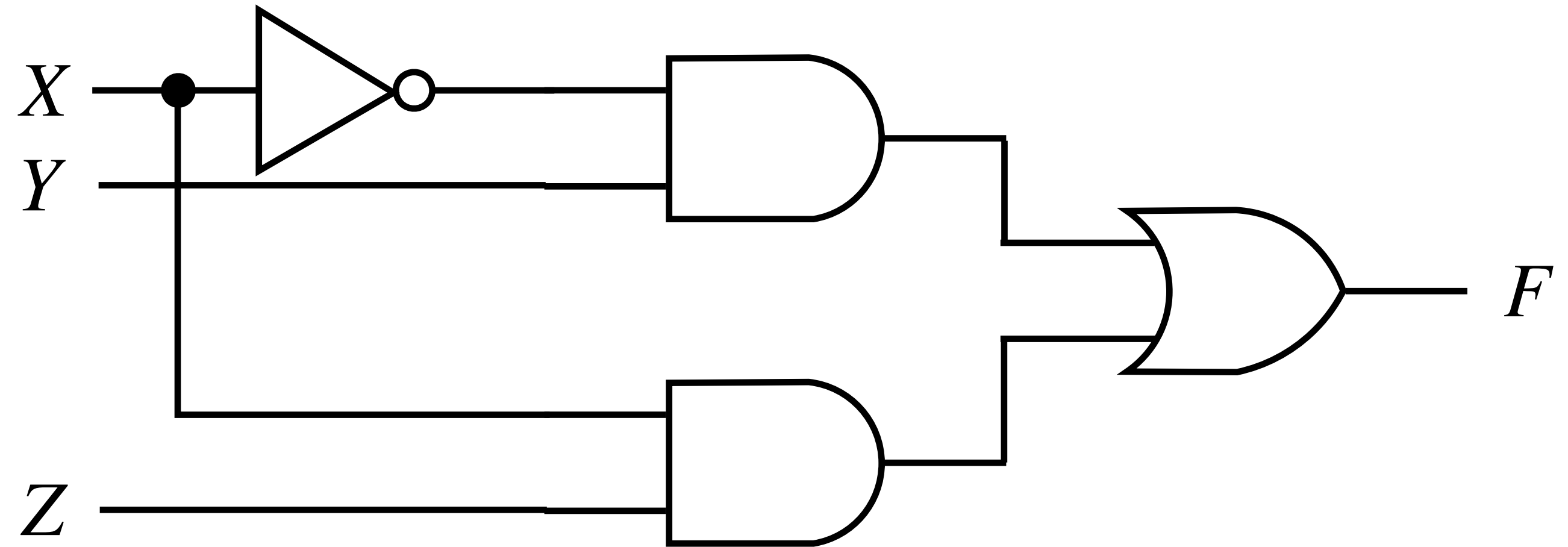

# Simulation 2

Truth Table


$X$	$Y$	$Z$	$F = (\bar{X}Y) + (XZ)$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

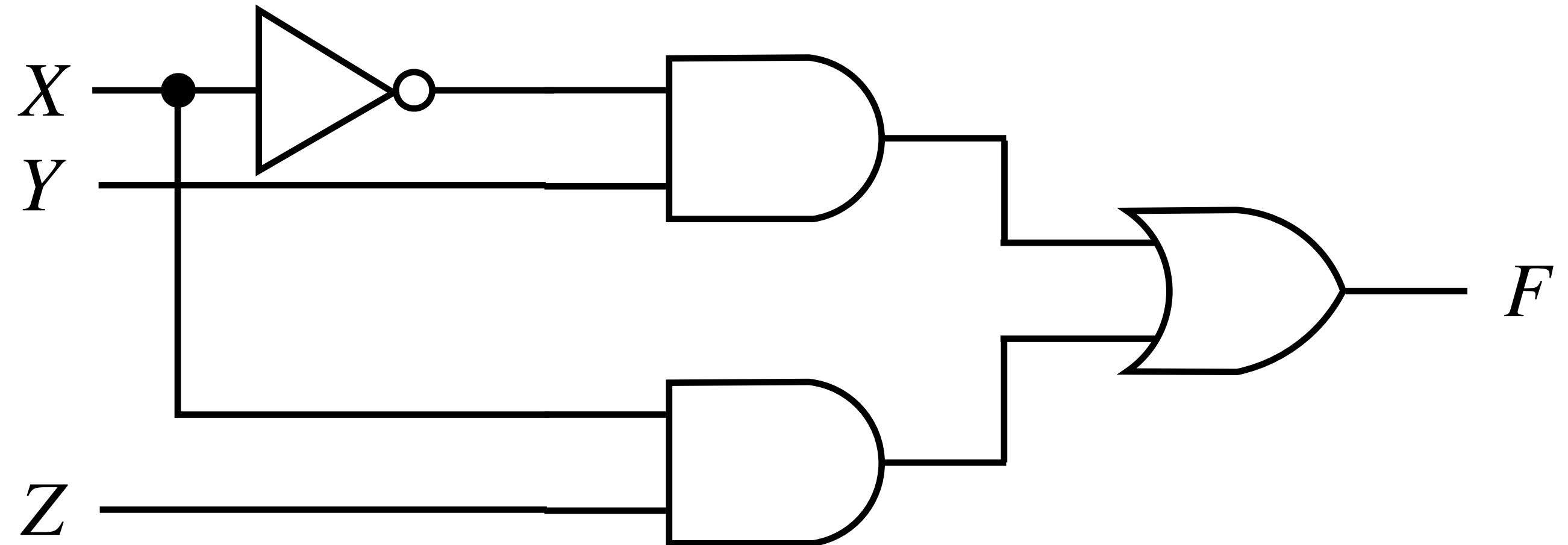

# Simulation 3

Truth Table


$X$	$Y$	$Z$	$F$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

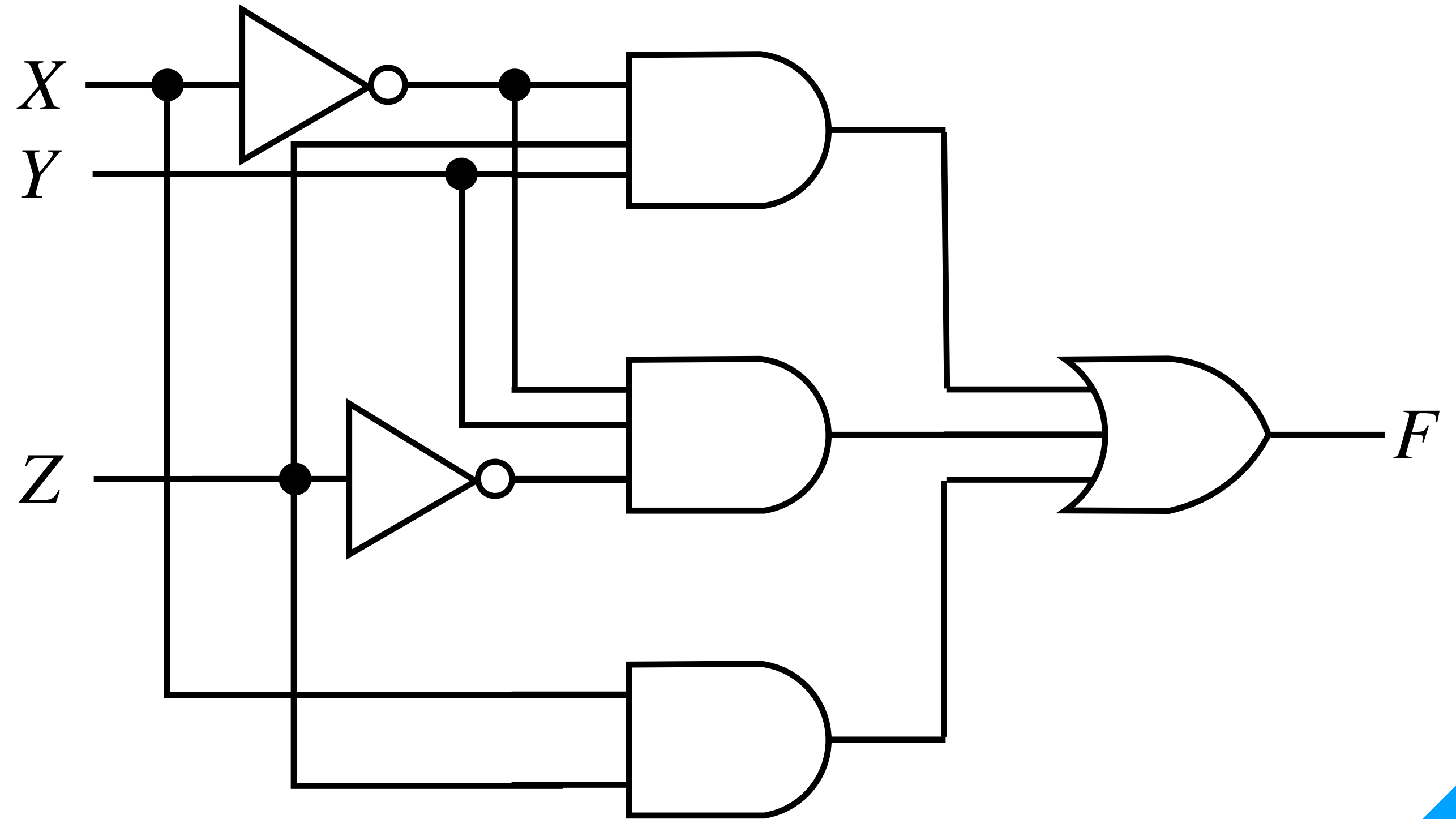

# Simulation 3

Truth Table

$X$	$Y$	$Z$	$F = \bar{X}YZ + \bar{X}Y\bar{Z} + XZ$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

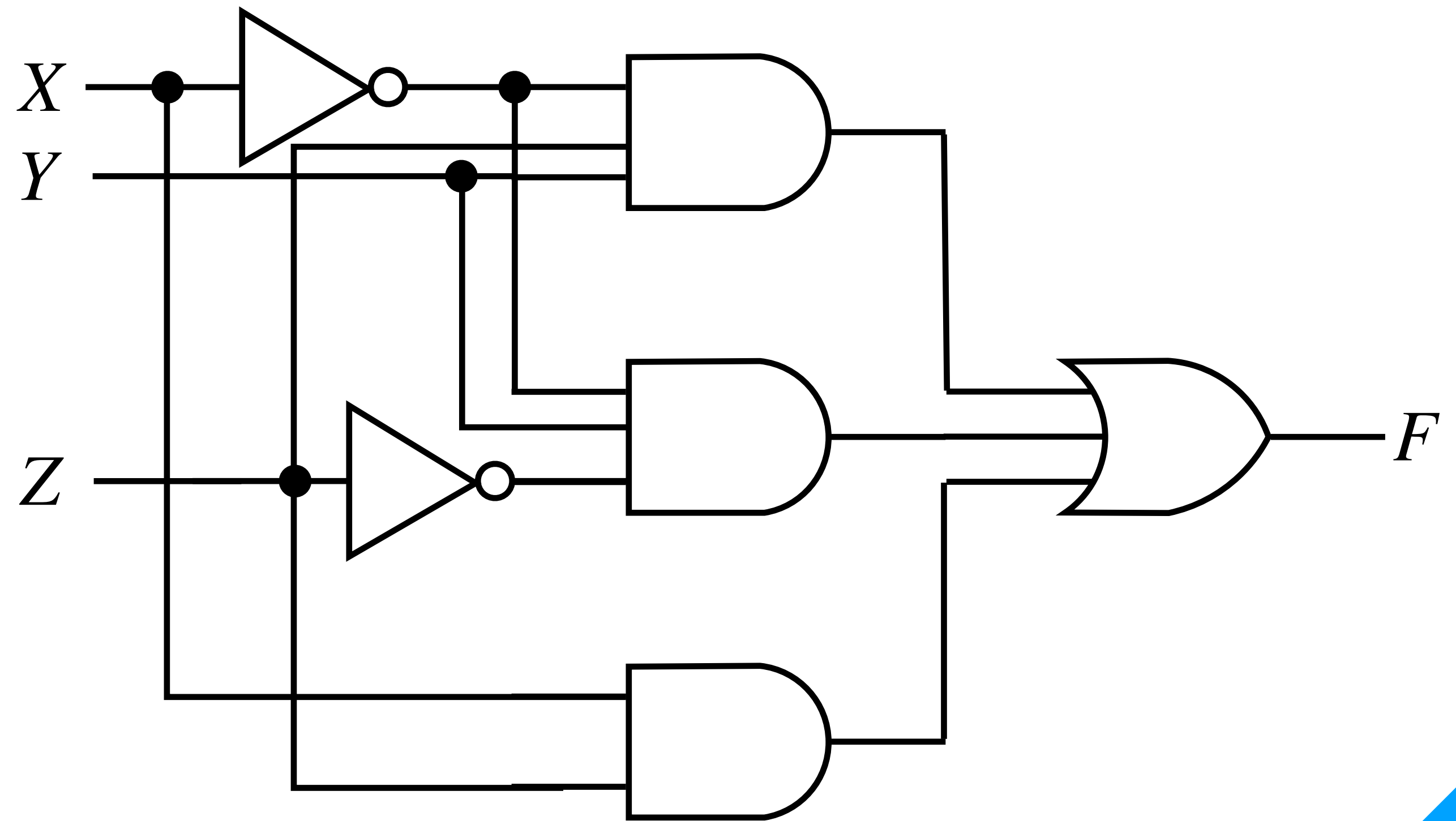


# Summary

- AND, OR, NOT Operators
- Logic Gates
- Timing diagram
- Truth Table
- Gate Delay




# LogicWorks

Fire up your computer please!

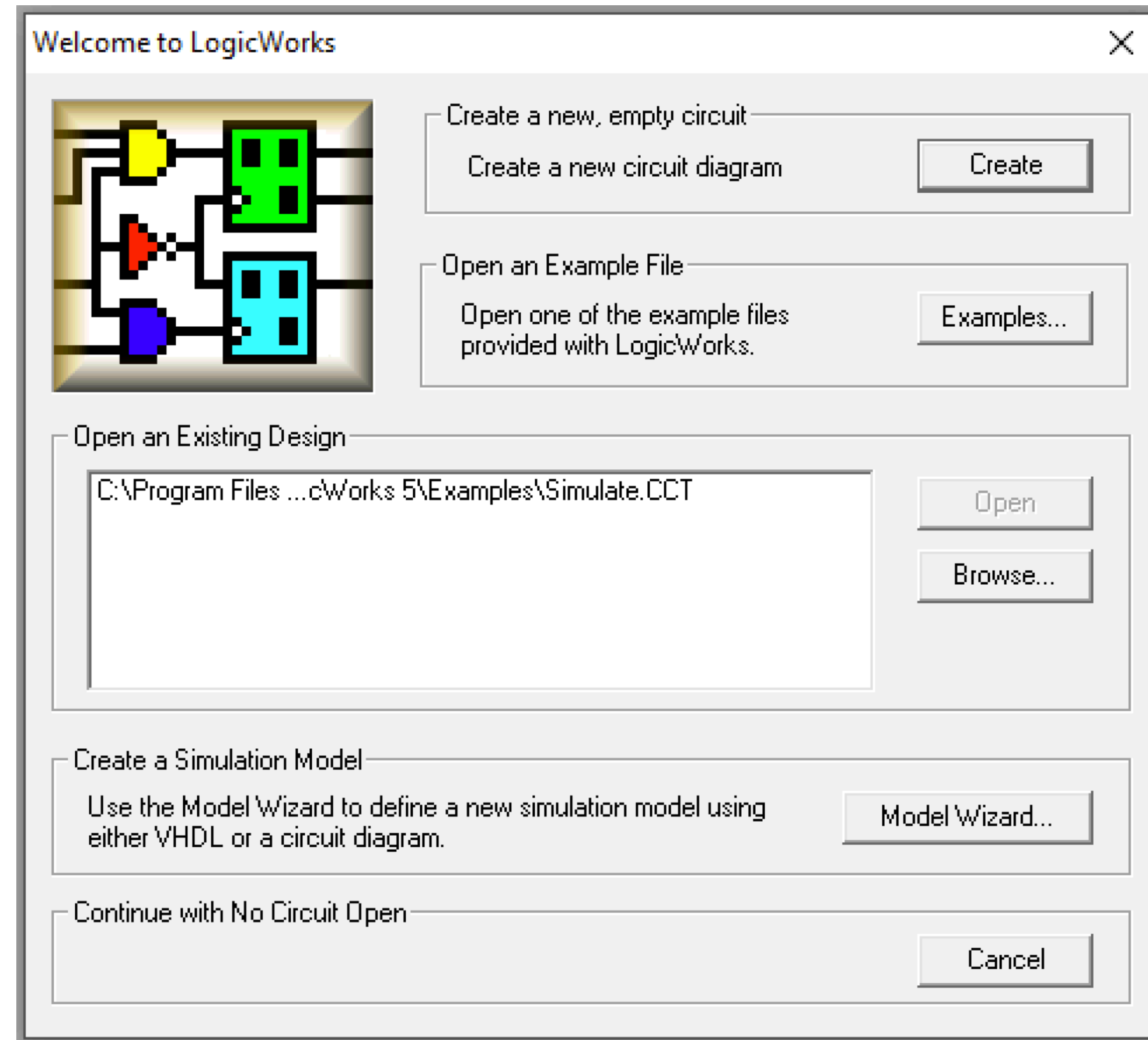


# P2 Tutorial

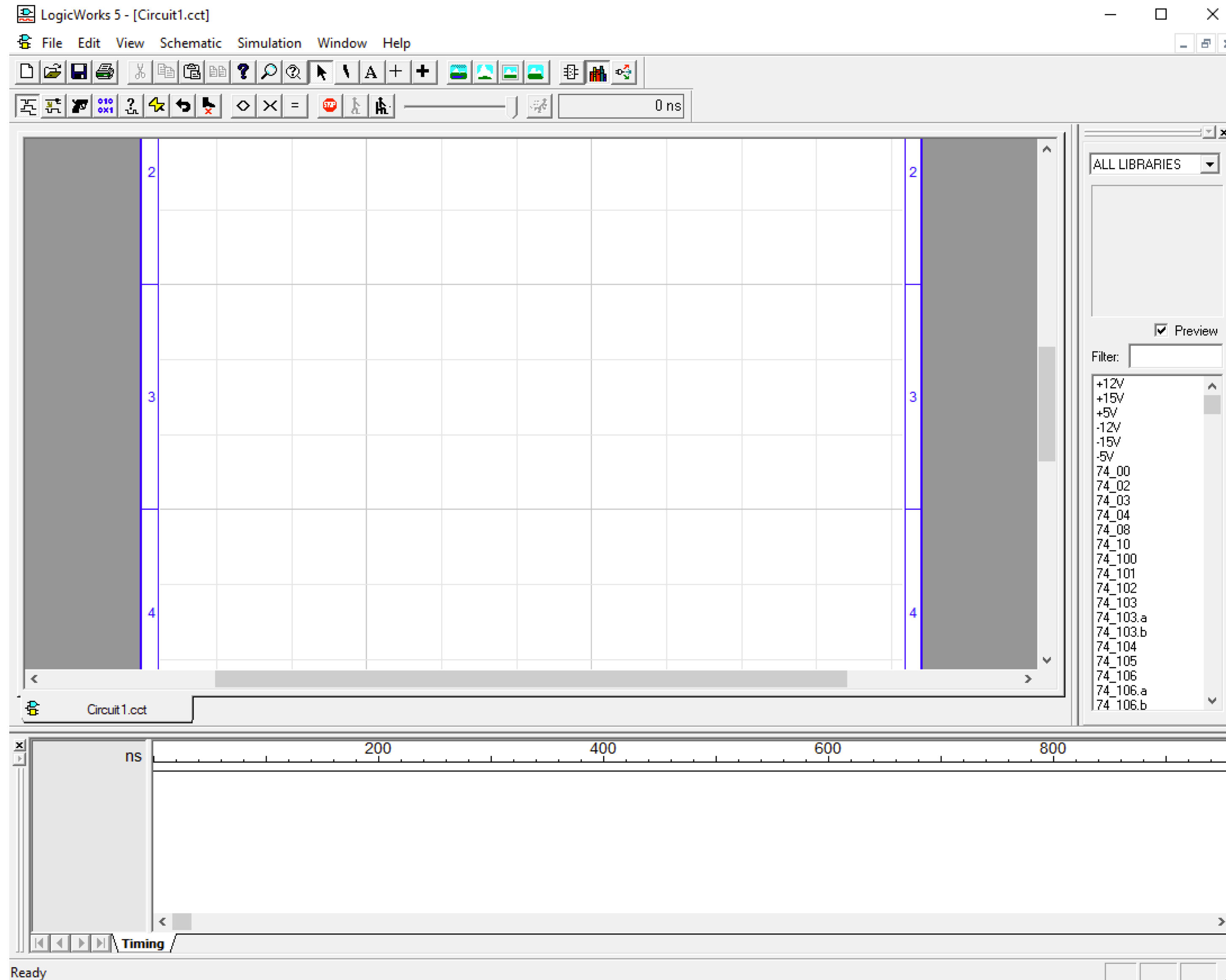

1. This is the main interface

Technical


# P2 Tutorial

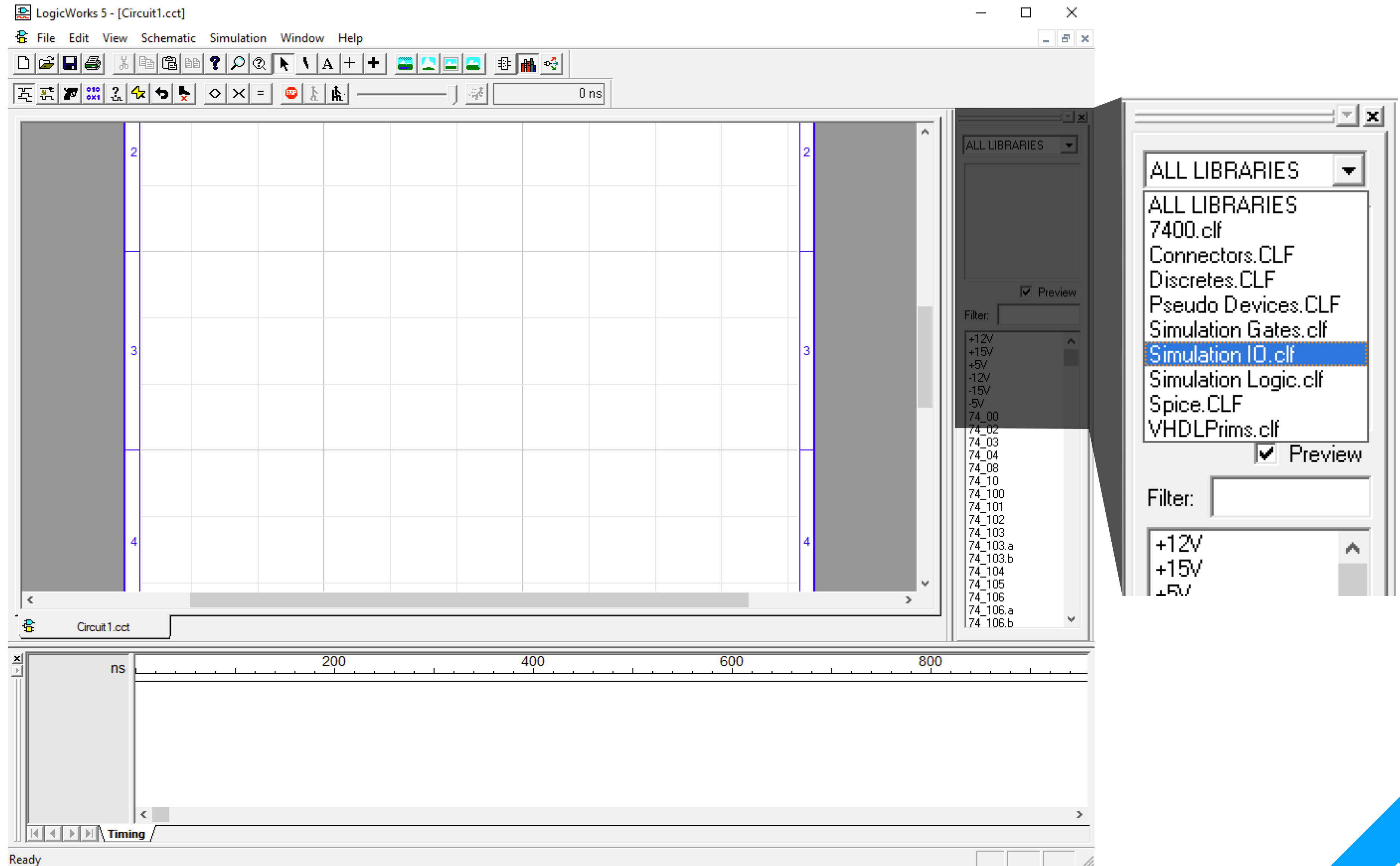

1. Select Simulation IO from the Parts Palette

Technical

P2  
Tutorial

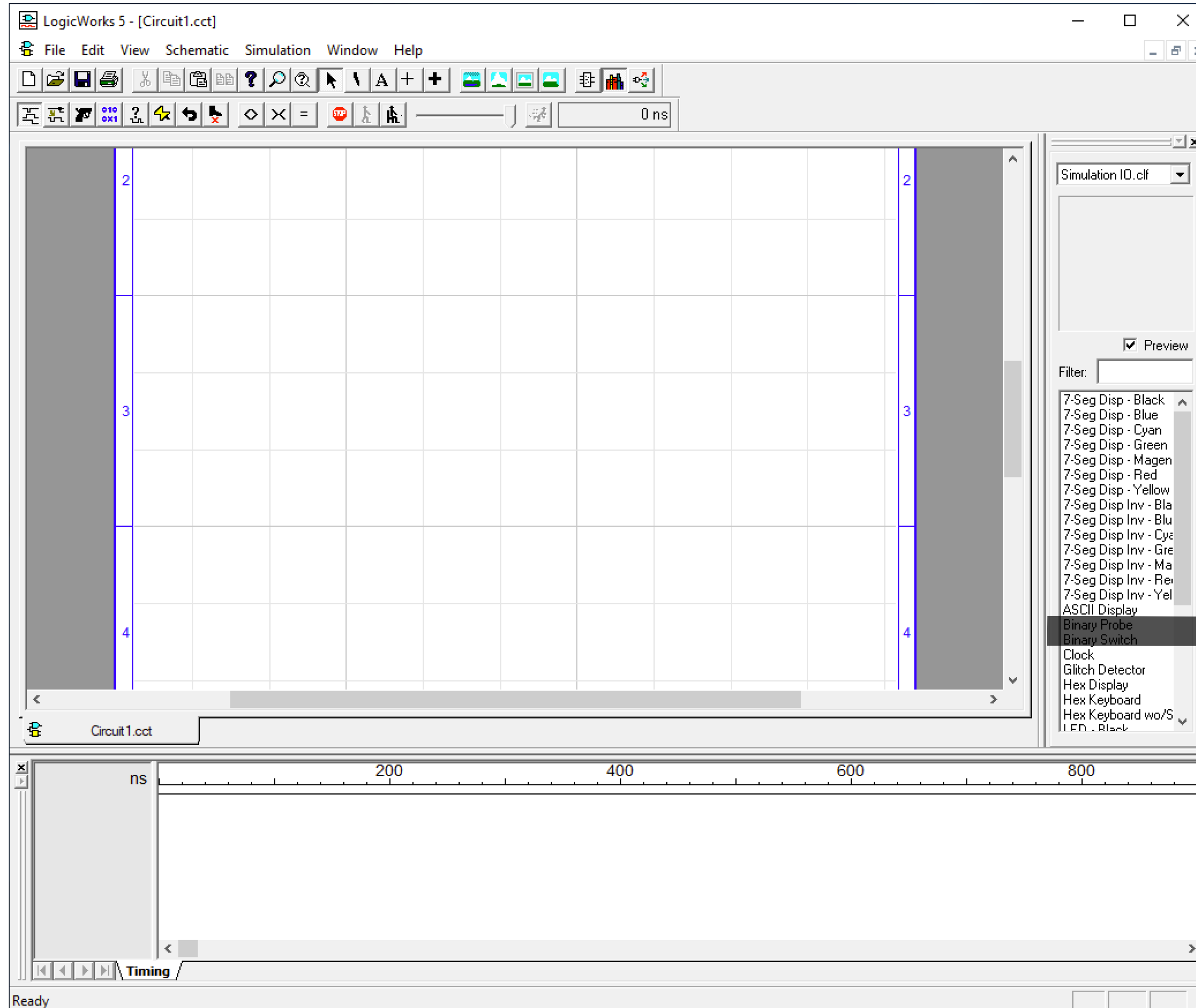


Binary Probe  
Binary Switch

Technical

1. Pay Attention to Binary Probe and Binary Switch


P2  
Tutorial

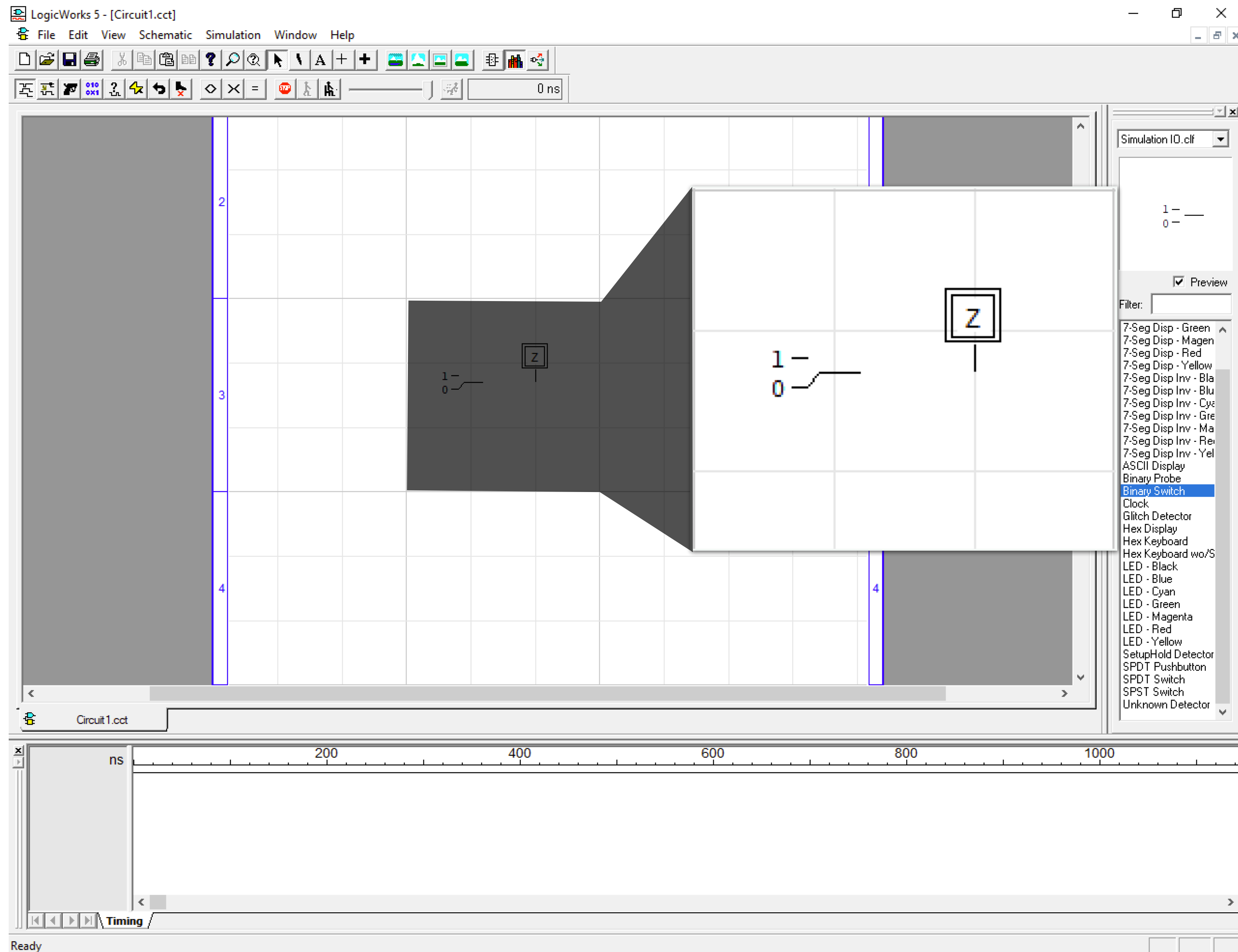

Technical

1. Double click and place one of each on the main board


P2  
Tutorial

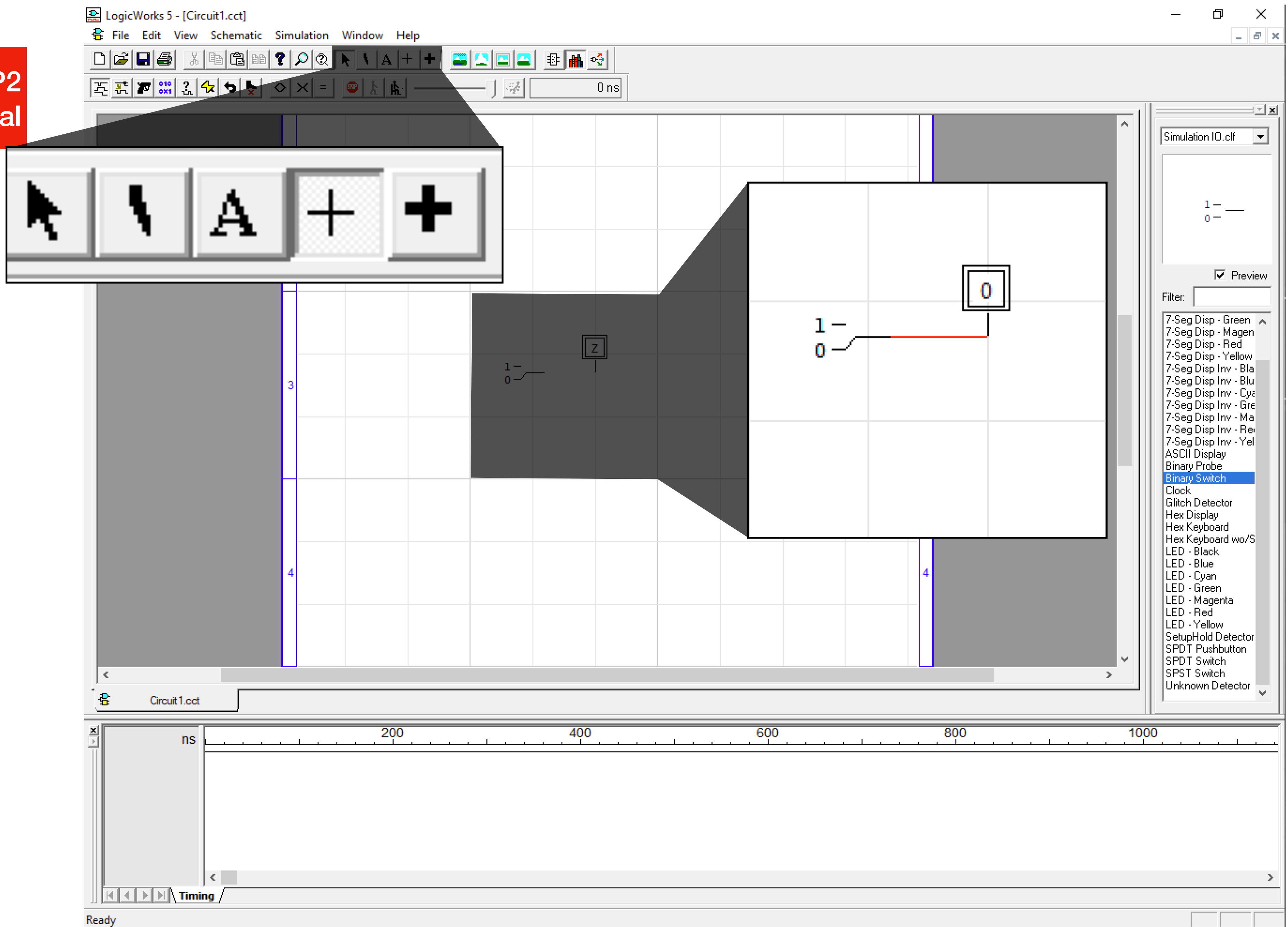

1. Use the 'Draw Signal' tool to connect the two parts

Technical

P2  
Tutorial


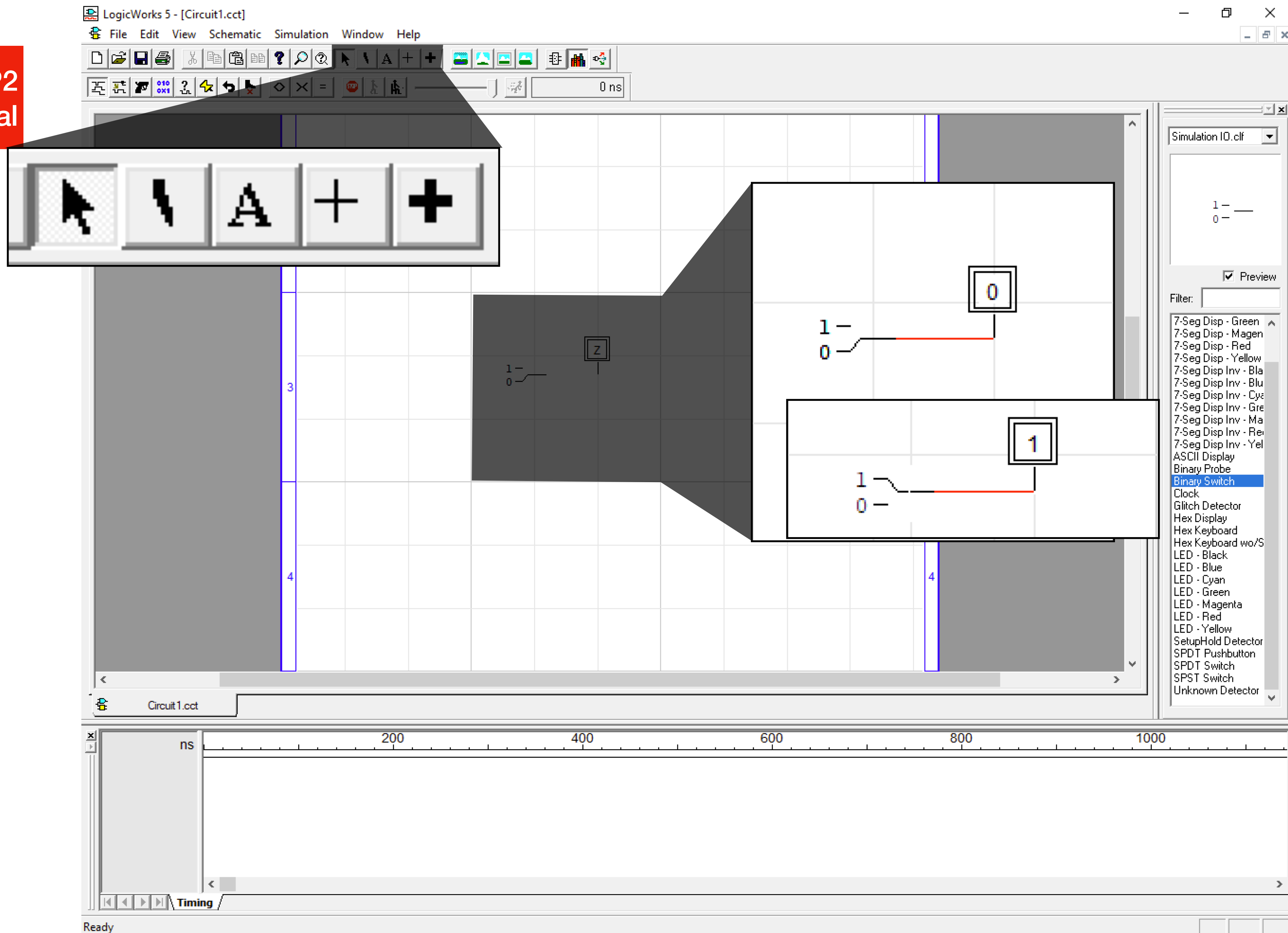


1. Switch back to the **Cursor** mode, now click on the switch and you can change the signal value

Technical



P2  
Tutorial

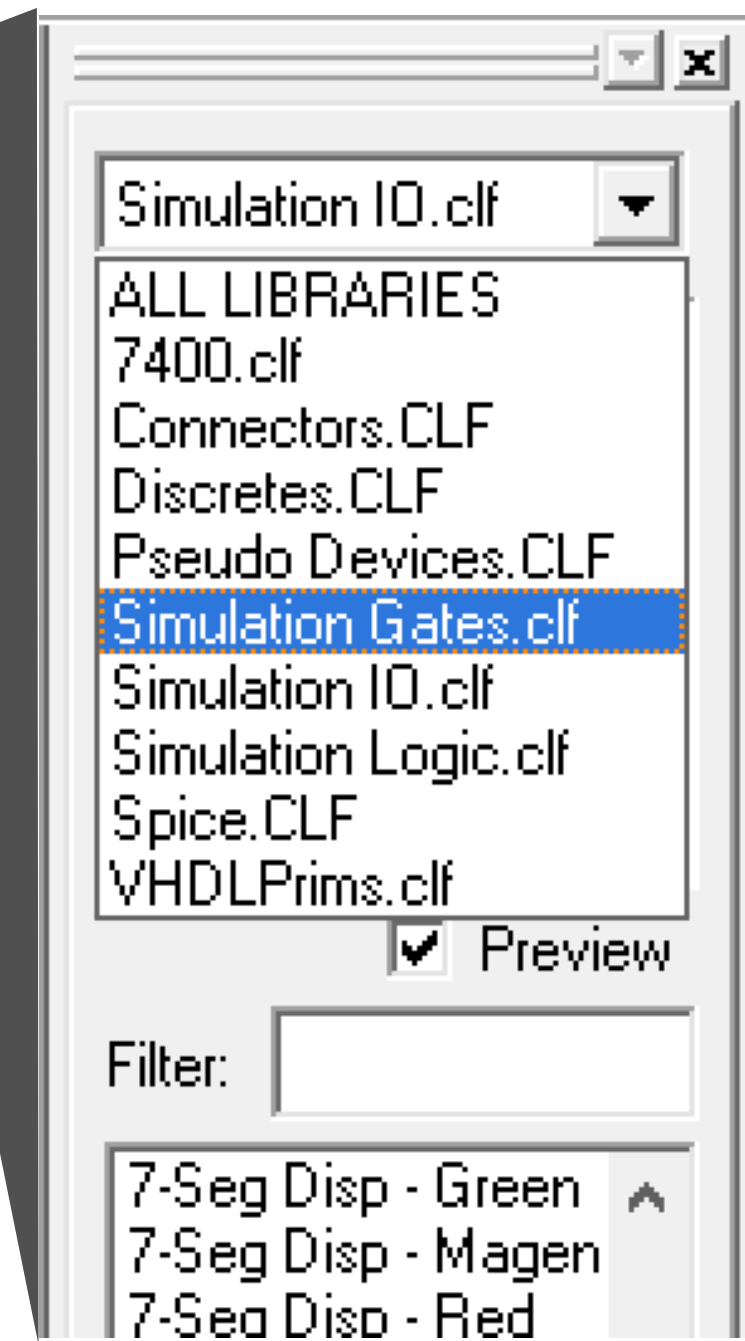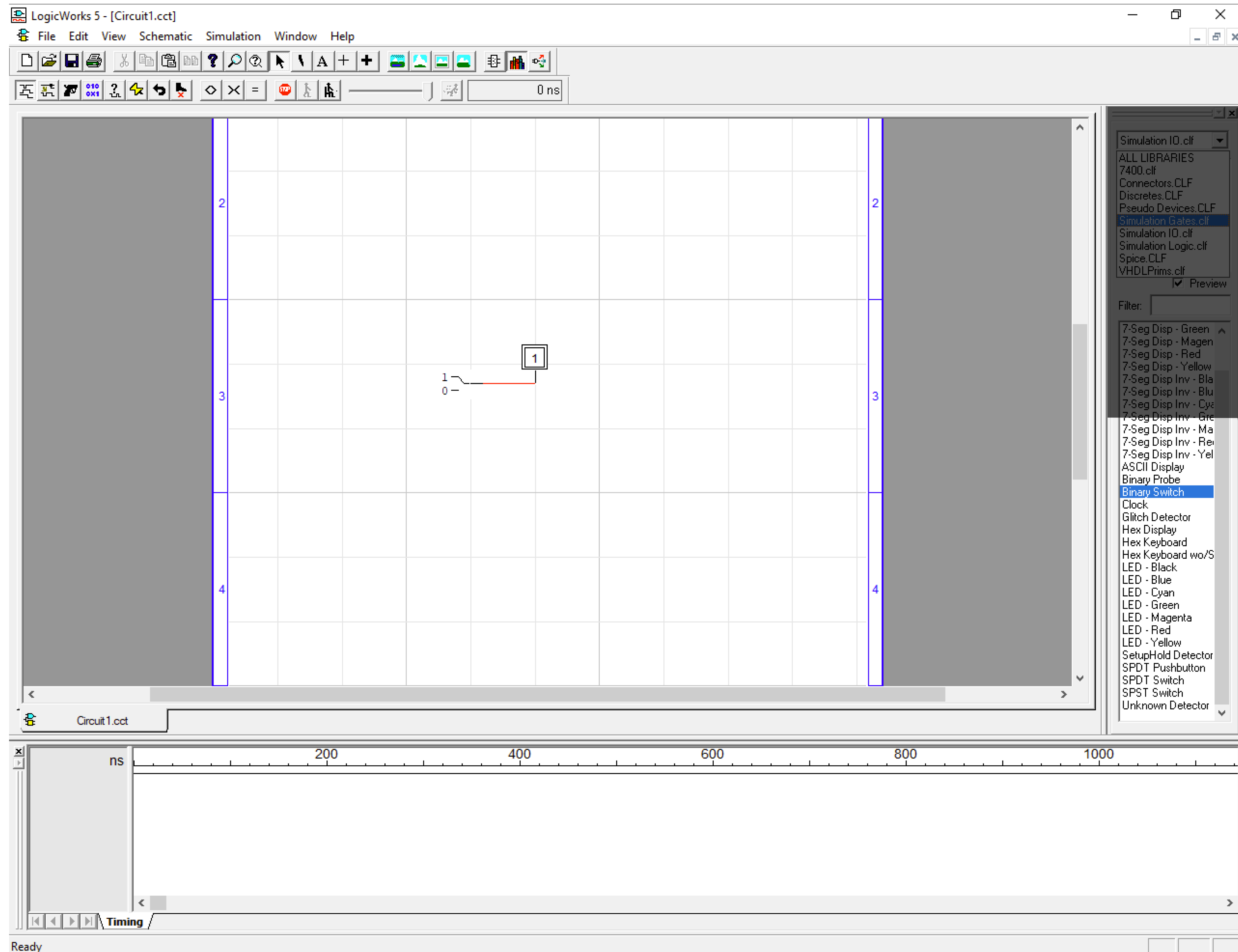

1. Select Simulation Gates

Technical

P2  
Tutorial

The screenshot displays the LogicWorks 5 interface. The main workspace shows a circuit diagram with a 2-bit bus on the left, a 2-bit bus on the right, and a 4-bit bus at the bottom. The circuit includes a 2-to-1 multiplexer, an AND gate, and two output indicators labeled '1' and '0'. The AND gate's inputs are connected to the outputs of the multiplexer. The output of the AND gate is connected to the indicator labeled '0'. The indicator labeled '1' is connected to a constant '1' signal. The simulation window on the right shows a list of components, with 'AND-2' selected. The timing diagram at the bottom shows a signal that is high from 0 to 200 ns and low from 200 to 1000 ns.

1. Select **AND-2**, then complete the above diagram

Technical

P2  
Tutorial

The screenshot displays the LogicWorks 5 interface. The main workspace shows a circuit diagram with a clock source (square wave), an AND gate, and two binary switches. The top toolbar contains various editing tools. The right-hand side features a 'Simulation IO.clf' window with a list of components, where 'Clock' is highlighted. Below this is a 'Timing' window showing a square wave signal over time. The status bar at the bottom indicates 'Ready'.

1. Select **Clock** from **Simulation IO**, then replace the lower **Binary Switch** with it. A **Clock** is a device that generates a 1 at a certain frequency

Technical


P2  
Tutorial

The screenshot displays the LogicWorks 5 interface. The main workspace shows a circuit diagram with a clock source (square wave), a binary switch (set to 1), an AND gate, and two LEDs (one labeled '1' and one labeled '0'). The simulation IO window is open on the right, showing a list of components. The 'Clock' component is selected in the list. The timing diagram at the bottom shows a 3 ns scale.

1. Select **Clock** from **Simulation IO**, then replace the lower **Binary Switch** with it

Technical

P2  
Tutorial

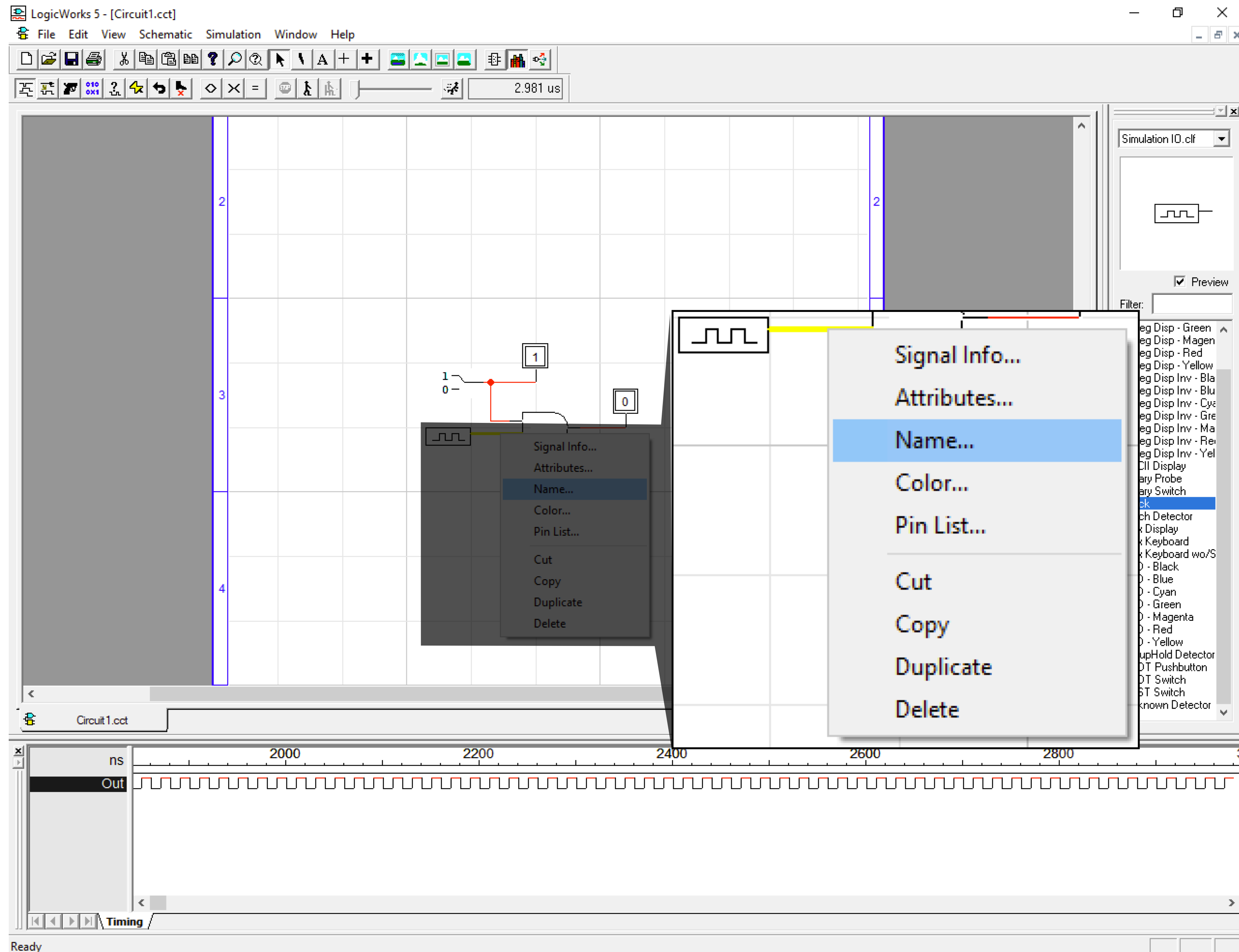

1. Right click the **Red Wire**, select **Name**

Technical

P2  
Tutorial

The screenshot displays the LogicWorks 5 interface for a circuit simulation. The main workspace shows a schematic diagram with a callout box highlighting a specific section. The callout shows a clock source connected to the In1 input of an AND gate. The other input of this AND gate is connected to a logic '1' source. The output of this AND gate is connected to the In1 input of a second AND gate. The second AND gate's other input is also connected to a logic '1' source, and its output is labeled 'Out'. The 'Out' signal is connected to an LED. A timing diagram at the bottom shows the waveforms for In1, In2, and Out over time. The In1 signal is a square wave, In2 is a constant logic '1', and the Out signal is a square wave that is high only when In1 is high. A toolbar with various icons is visible on the left side of the schematic area.

1. Complete the diagram like above, then click **Reset Simulation**

Technical

P2  
Tutorial

LogicWorks 5 - [Circuit1.cct]

File Edit View Schematic Simulation Window Help

2.981 us

190 ns

ns 200 400

In1  
In2  
Out

Timing

Reset simulator

Simulation IO.clf

Preview

Filter:

- 7-Seg Disp - Green
- 7-Seg Disp - Magen
- 7-Seg Disp - Red
- 7-Seg Disp - Yellow
- 7-Seg Disp Inv - Bla
- 7-Seg Disp Inv - Blu
- 7-Seg Disp Inv - Cya
- 7-Seg Disp Inv - Gre
- 7-Seg Disp Inv - Ma
- 7-Seg Disp Inv - Re
- 7-Seg Disp Inv - Yel
- ASCII Display
- Binary Probe
- Binary Switch
- Clock
- Glitch Detector
- Hex Display
- Hex Keyboard

Technical

1. Use the Simulation Panel to control the speed of simulation, then you will see the Timing Diagram!

# Exe 1

- Curtain Motor Control
  - Button1: 1 when user wants to open the curtain
  - Button2: 1 when user wants to close the curtain
  - Output1: 1 to make the motor open the curtain
  - Output2: 1 to make the motor close the curtain
  - Light: motor is active



- When both buttons are pressed, motors do nothing



# Exe 2

- Curtain Motor Control
  - **Sensor1: 1 when curtain is fully closed**
  - **Sensor2: 1 when curtain is fully open**
  - Button1: 1 when user wants to open the curtain
  - Button2: 1 when user wants to close the curtain
  - Output1: 1 to make the motor open the curtain
  - Output2: 1 to make the motor close the curtain
  - Light: motor is active



- Stop the motor when the curtain is already fully opened/  
closed

# Summary

- Simulation in LogicWorks
- Binary Probe / Binary Switch in LogicWorks
- Gates in LogicWorks
- Clocks in LogicWorks
- Timing Diagram in LogicWorks