



# CSCI 150

## Introduction to Digital and Computer System Design

### Lecture 3: Combinational Logic Design VI



Jetic Gū

# Overview


- Focus: Arithmetic Functional Blocks
- Architecture: Combinatory Logical Circuits
- Textbook v4: Ch4 4.3, 4.7; v5: Ch2 2.9, Ch3 3.10
- Core Ideas:
  1. Subtraction I
  2. VHDL

# Review



Unsigned Binary Adder
 
# 1-bit Half Adder

- Half adder  
input  $X$ ,  $Y$   
output  $S$ ,  $C$





# 1-bit Half Adder

  
  
# 1-bit Full Addder

- Full addder  
input  $X$ ,  $Y$ ,  $Z$ ;  
output  $S$ ,  $C$




# 1-bit Full Adder

- Full adder  
input  $X, Y, Z$ ;  
output  $S, C$


- Half adder1  
input  $X, Y$   
output  $S', C'$
- Half adder2  
input  $S', Z$   
output  $S, C''$

$$C = C' + C''$$

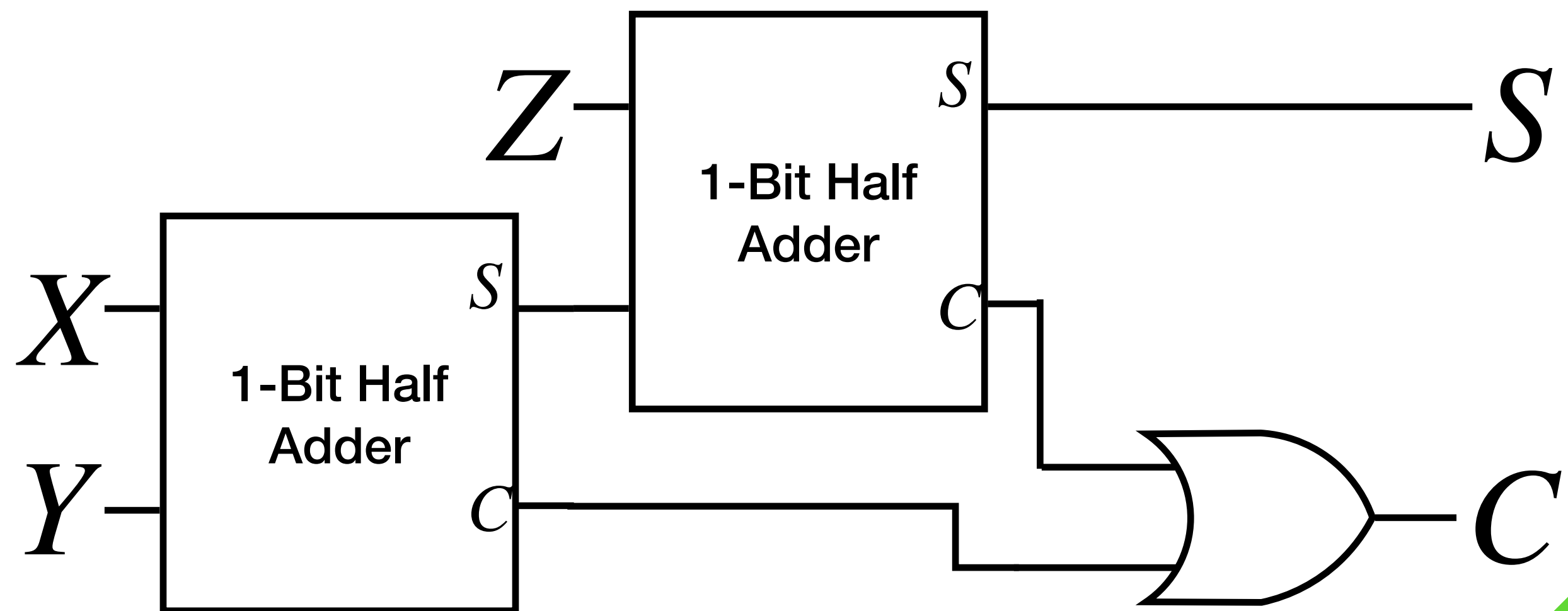

# n-bit Full Adder

- Ripple Carry Adder

 



# Unsigned Binary Subtraction I

# Unsigned Binary Subtraction

- Input: Minuend and Subtrahend  
Previous borrow
- Output: Last borrow, difference

Borrows	0
Minuend	10110
Subtrahend	<u>−10011</u>
Difference	

# Unsigned Binary Subtraction

- Input: Minuend and Subtrahend  
Previous borrow
- Output: Last borrow, difference

Borrows	000110	Input Output
Minuend	10110	
Subtrahend	– 10011	
Difference	00011	

This method works when the Minuend is greater than the Subtrahend!

# Unsigned Binary Subtraction

$$X > Y, F = X - Y$$

- We learned to perform subtraction, by subtracting the smaller number from the greater number

# Unsigned Binary Subtraction


- Input: Minuend and Subtrahend  
Previous borrow
- Output: Last borrow, difference

Borrows	000110	<b>Input</b> <b>Output</b>
Minuend	10110	
Subtrahend	−10011	
Difference	00011	

# Unsigned 1-bit Binary Subtraction

- Input: Minuend  $X$  and Subtrahend  $Y$   
Previous borrow  $Z$
- Output: Last borrow  $B$ , difference  $D$


	$B$	$Z$
Borrows	1	0
Minuend $X$		0
Subtrahend $Y$	-	1
Difference $D$		1

 

# Unsigned 1-bit Binary Subtraction

- Input: Minuend  $X$  and Subtrahend  $Y$   
Previous borrow  $Z$
- Output: Last borrow  $B$ , difference  $D$


	$B$	$Z$
Borrows	1	0
Minuend $X$	0	
Subtrahend $Y$	-1	
Difference $D$	1	

 

$X$	$Y$	$Z$	$B$	$D$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1
 
# Unsigned 1-bit Binary Subtraction

- Implementation using 3-to-8 Decoder
  - $B = \Sigma m(1,2,3,7)$
  - $D = \Sigma m(1,2,4,7)$





# Unsigned Binary Subtraction

Technology

- 1 bit Unsigned Subtractor

- Input: Minuend and Subtrahend  
Previous borrow
- Output: Last borrow, difference


	<i>B</i>			<i>Z</i>	
Borrows	0	0	0	1	1
Minuend <i>X</i>	1	0	1	1	0
Subtrahend <i>Y</i>		–	1	0	0
Difference <i>D</i>	0	0	0	1	1

Input  
Output

# Unsigned Binary Subtraction

Technology

- 1 bit Unsigned Subtractor

 

	<i>B</i>		<i>Z</i>
Borrows	0	0011	0
Minuend $X_{0:n-1}$	1	0110	
Subtrahend $Y_{0:n-1}$	-	10011	
Difference $D_{0:n-1}$		00011	

Input  
Output



# Hardware Description Language

VHDL (VHSIC-HDL): Very High Speed Integrated  
Circuit Hardware Description Language




# What is HDL

- Designing complex circuits using logic circuit diagrams is inefficient
- Hardware Description Language
  - Like programming language, describes hardware structures and behaviours
  - More efficient
  - Common languages
    - Verilog
    - VHDL

# Creating a AND1INV model

 
 


# Creating a AND1INV model

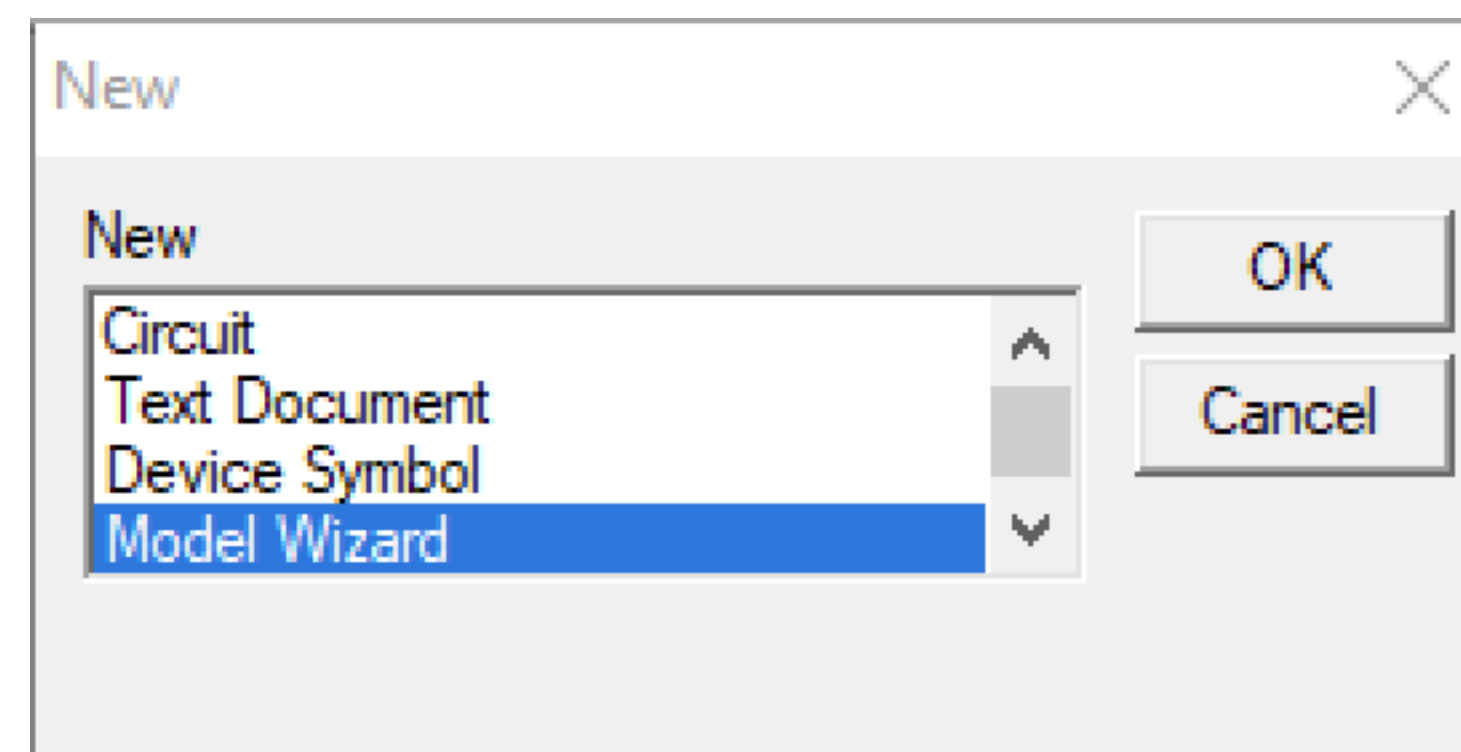
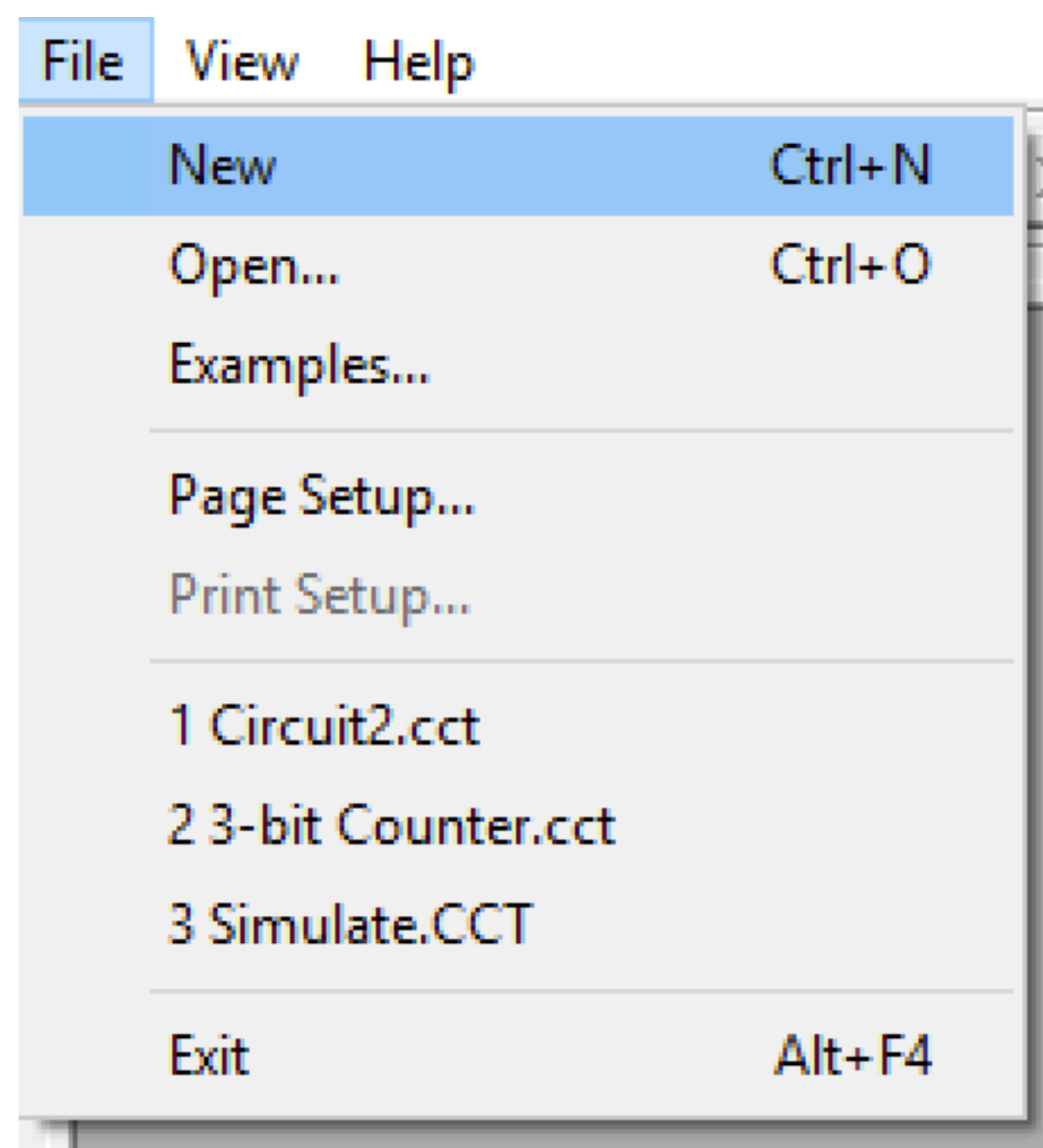
 


1. Go to the File menu, select New command. Select Model Wizard and click OK

# Creating a AND1INV model

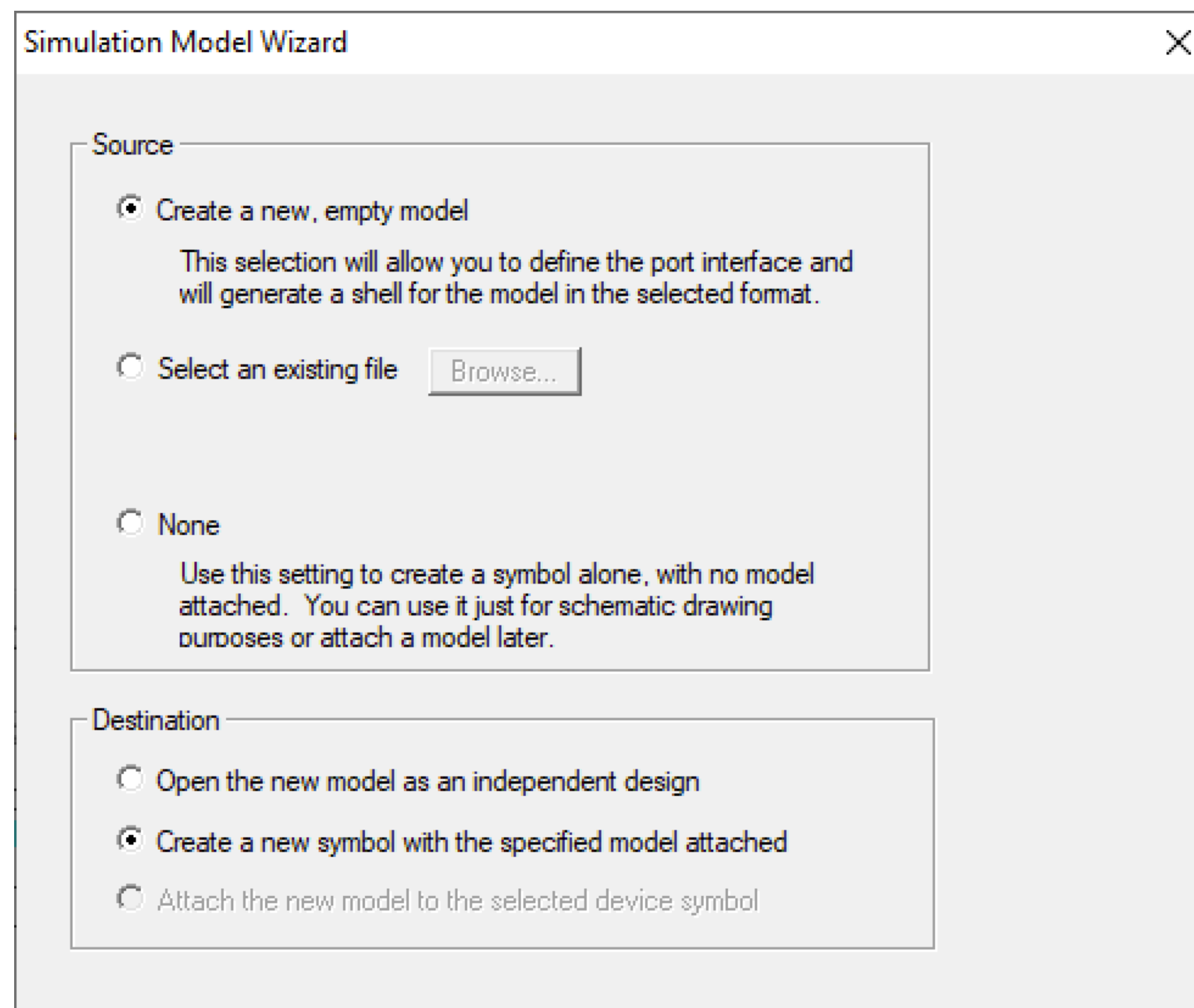 


# Creating a AND1INV model

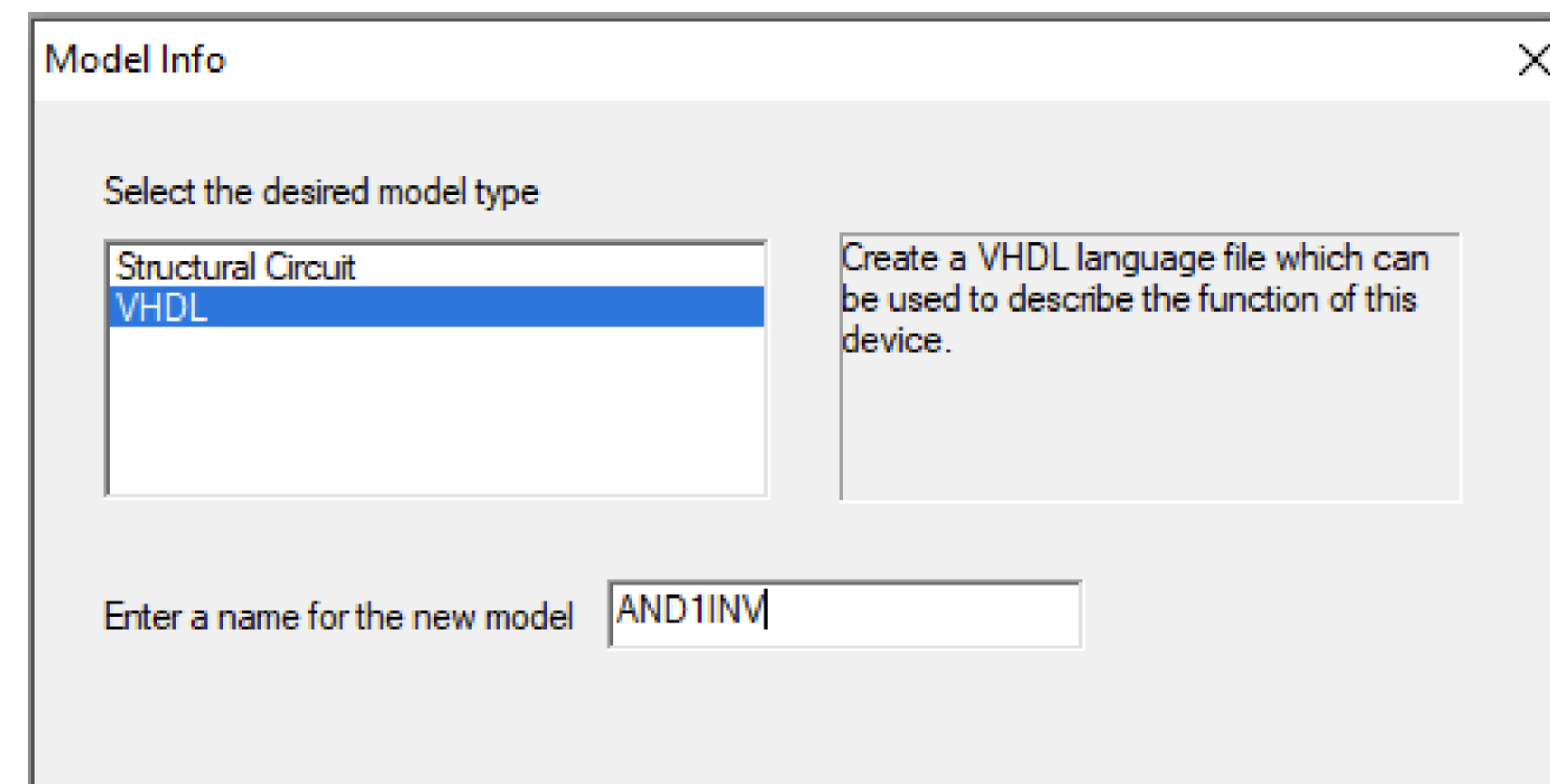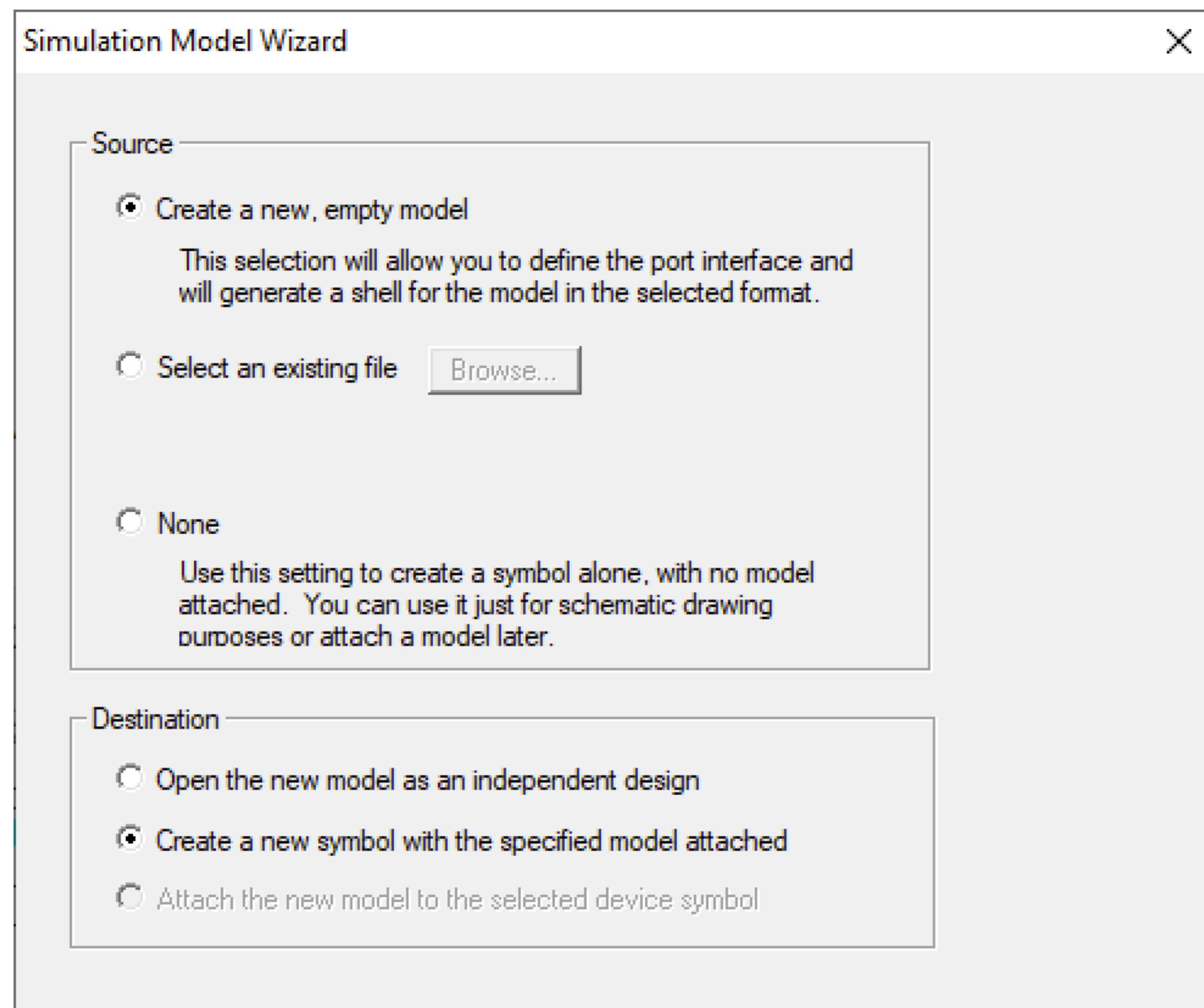 



# Creating a AND1INV model

 

- This is where you define all inputs and outputs
  - Input: POS
  - Input: NEG
  - Output: Out1

Model Port Interface

Use the controls at right to add pins to the interface list. NOTE: If you are attaching this model to an existing device symbol, the interface list must exactly match the pins on the symbol.

Name	Func	Left	Right
------	------	------	-------

Function

Input  
 Output  
 Bidirectional

Name

<< Add Single Bit

Vector

Left Bit Number


Right Bit Number

<< Add Vector


>> Remove

Drag and drop to re-order items in the list


# Creating a AND1INV model

 

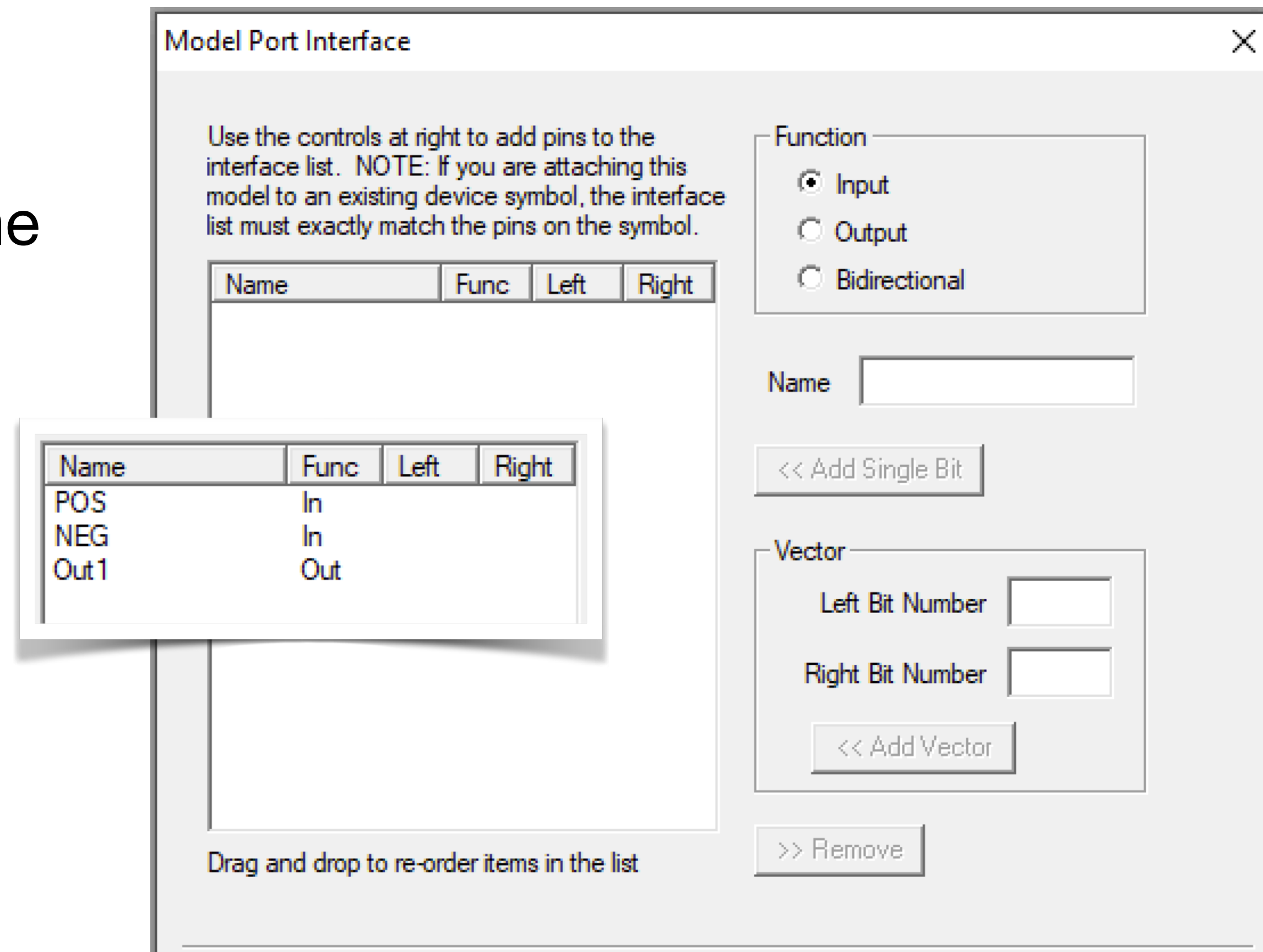- This is where you define all inputs and outputs
- Input: POS
- Input: NEG
- Output: Out1



# Creating a AND1INV model

 


Pin Locations ×


You can now specify where on the symbol you would like the pins to be placed. To move pins, just drag and drop between the boxes representing the left, top, right and bottom of the symbol.

Left pins	Top pins (left to right)	Right pins
NEG POS		Out1
	Bottom pins (left to right)	Symbol Label
		AND1INV

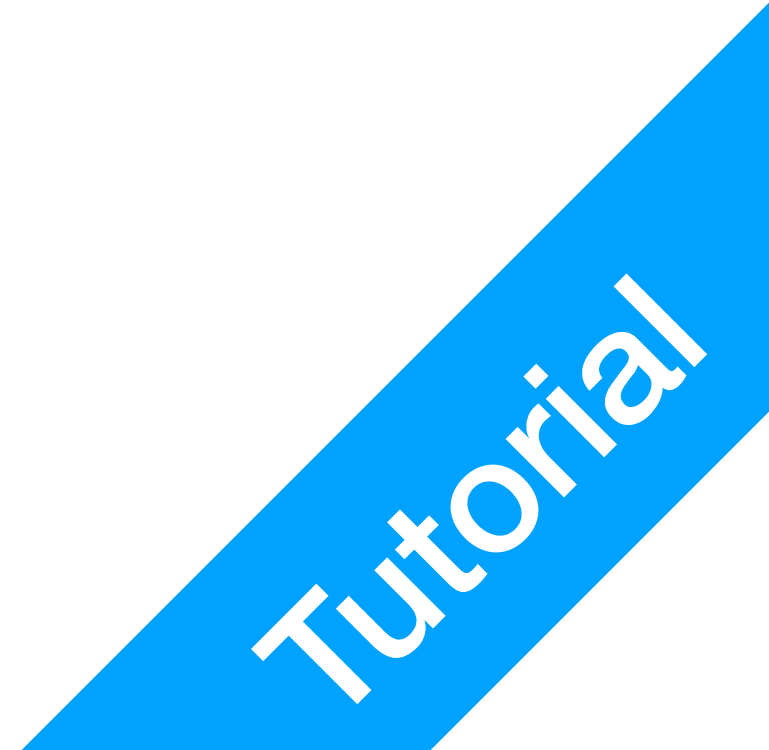4. The programme will ask you for Pin Location assignment. Just click Next.



# Creating a AND1INV model

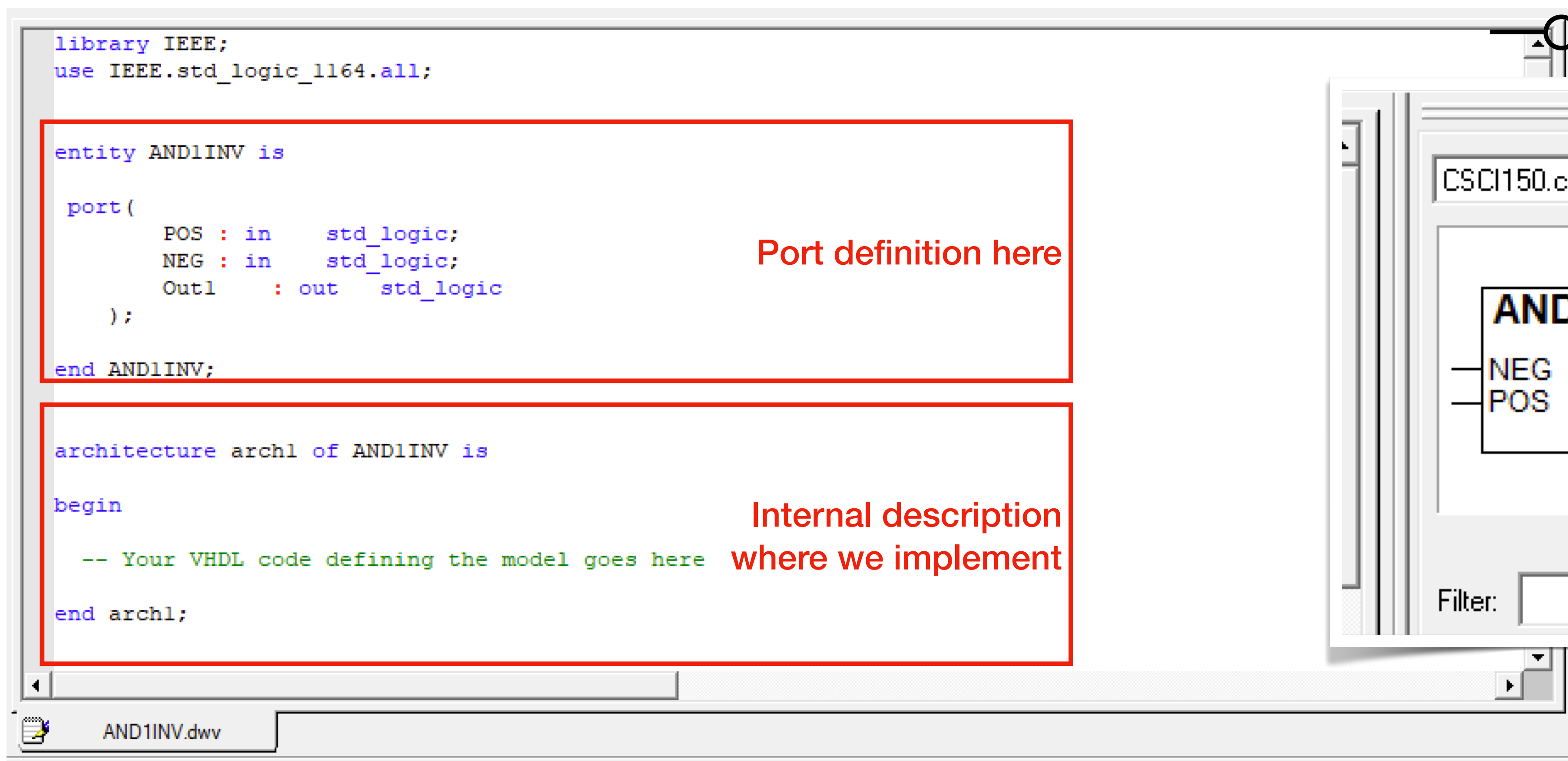

The screenshot shows a VHDL editor window with the following code:

```
library IEEE;
use IEEE.std_logic_1164.all;

entity AND1INV is
  port(
    POS : in    std_logic;
    NEG : in    std_logic;
    Out1 : out  std_logic
  );
end AND1INV;

architecture arch1 of AND1INV is
begin
  -- Your VHDL code defining the model goes here
end arch1;
```

Red annotations highlight the port definition and the internal description area.

Port definition here

Internal description where we implement

AND1INV.dvw


CSCI150.clf

AND1INV


NEG POS Out1

Preview

Filter:

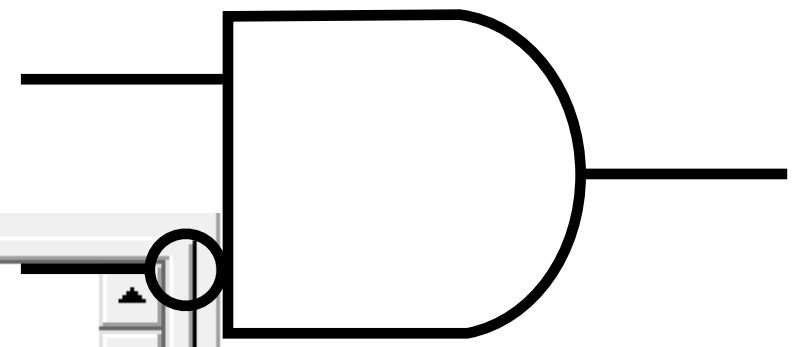


# Creating a AND1INV model

 



```
library IEEE;
use IEEE.std_logic_1164.all;

entity AND1INV is
  port (
    POS : in    std_logic;
    NEG : in    std_logic;
    Out1 : out  std_logic
  );
end AND1INV;

 architecture arch1 of AND1INV is
begin
  OUT1 <= POS AND NOT NEG AFTER 1NS;
end arch1;
```



# Creating a AND1INV model

 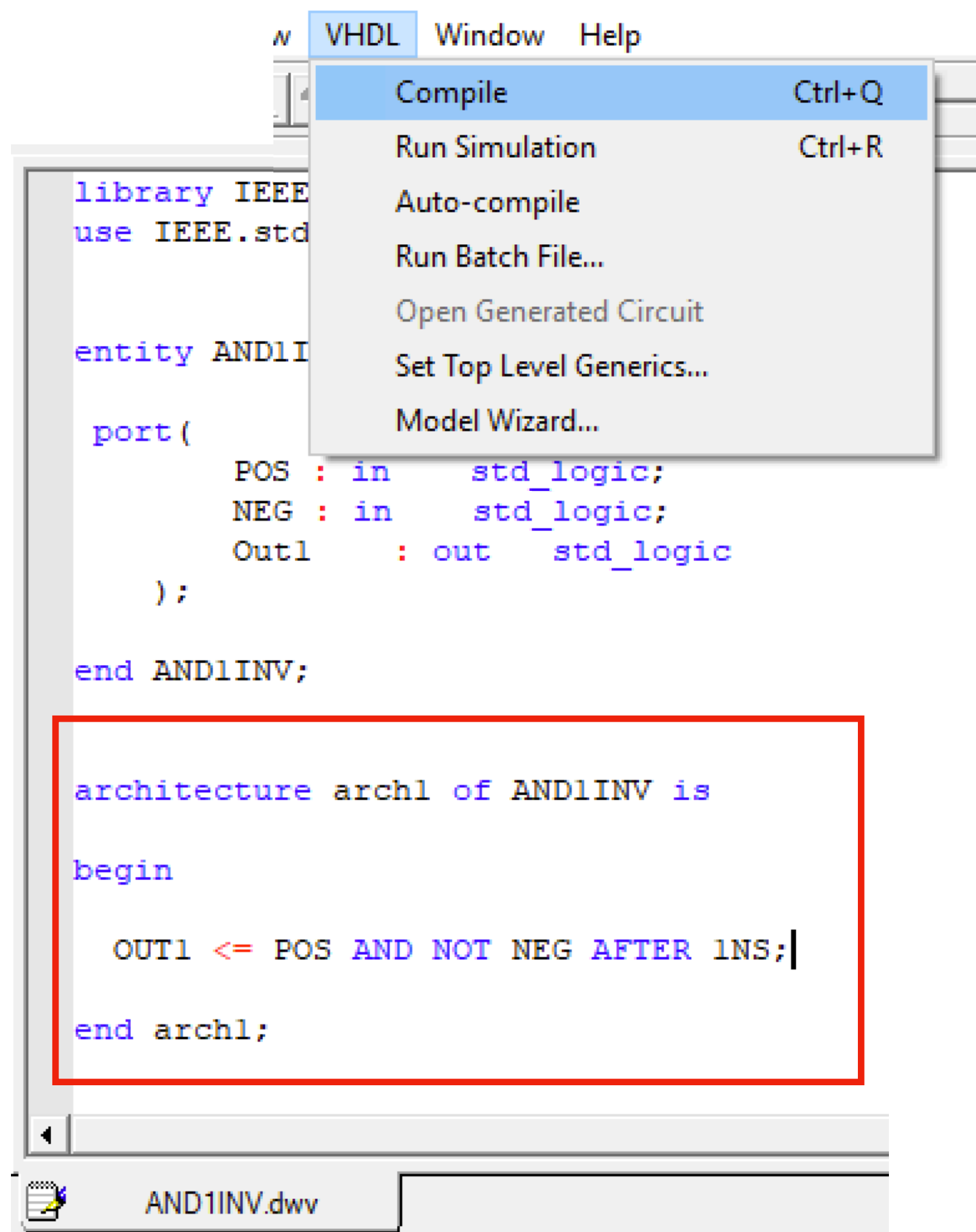



OUT1 <= POS **AND NOT** NEG **AFTER** 1NS;

↑  
Transferring

↙ ↘  
Boolean Operators

↙ ↘  
Things do not happen simultaneously

# Run Simulation

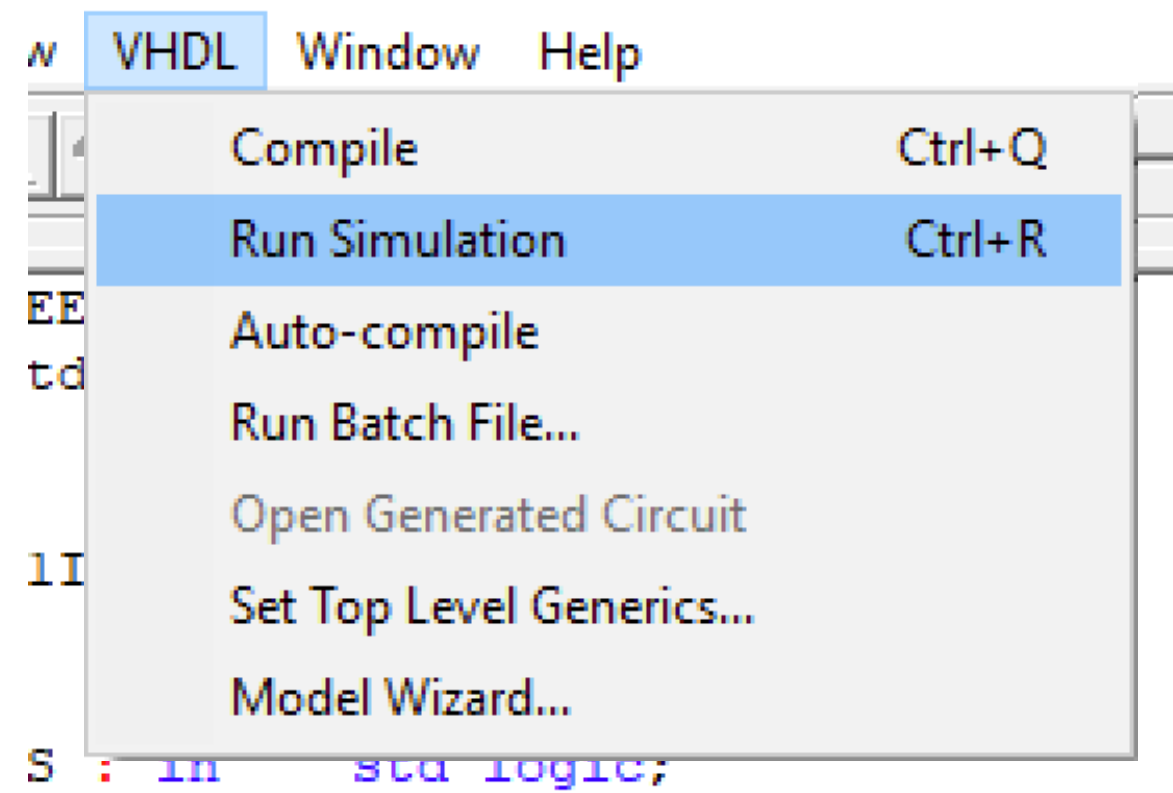 

I/O Page


Run

# Run Simulation

increase value (0 -> 1)      decrease value (1 -> 0)


pos	z	+	-	0
neg	z	+	-	0
out1	u	+	-	0

value fixing: 0

 





# Run Simulation

 

A screenshot of the I/O Panel in a simulation tool. The top part shows a code editor with the text `end arch1;`. Below it is a file browser showing `AND1INV.dvw`. The main area contains a table with columns for signal names and values.


pos	z	+	-	0
neg	z	+	-	0
out1	u	+	-	0

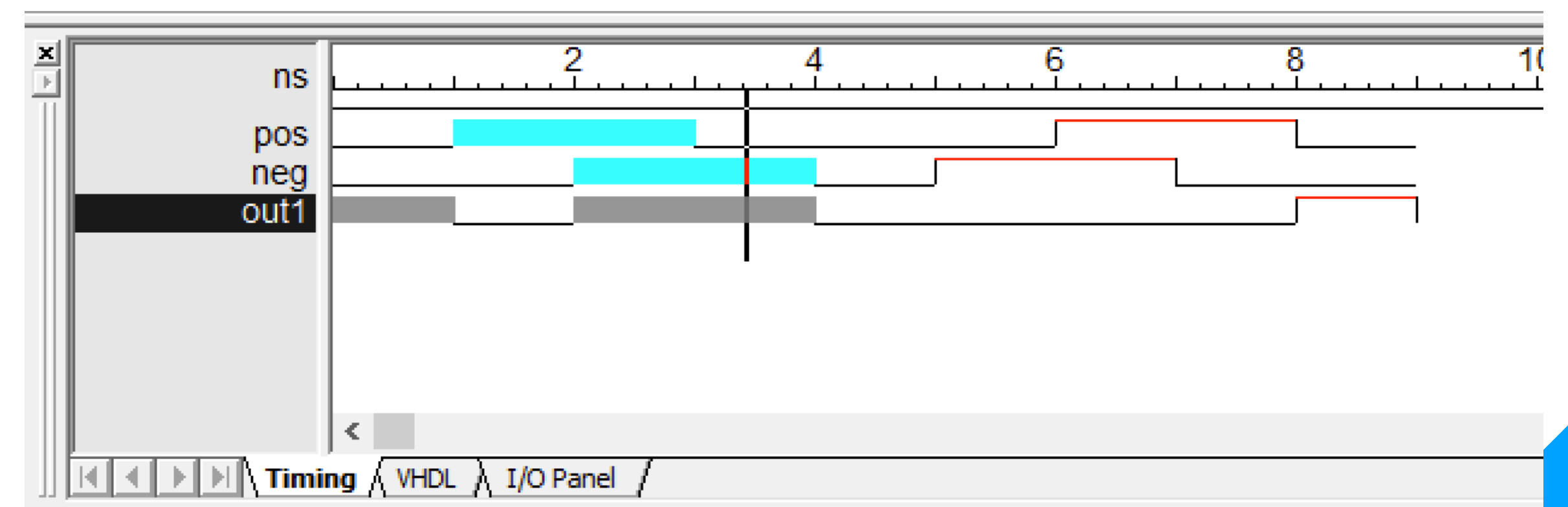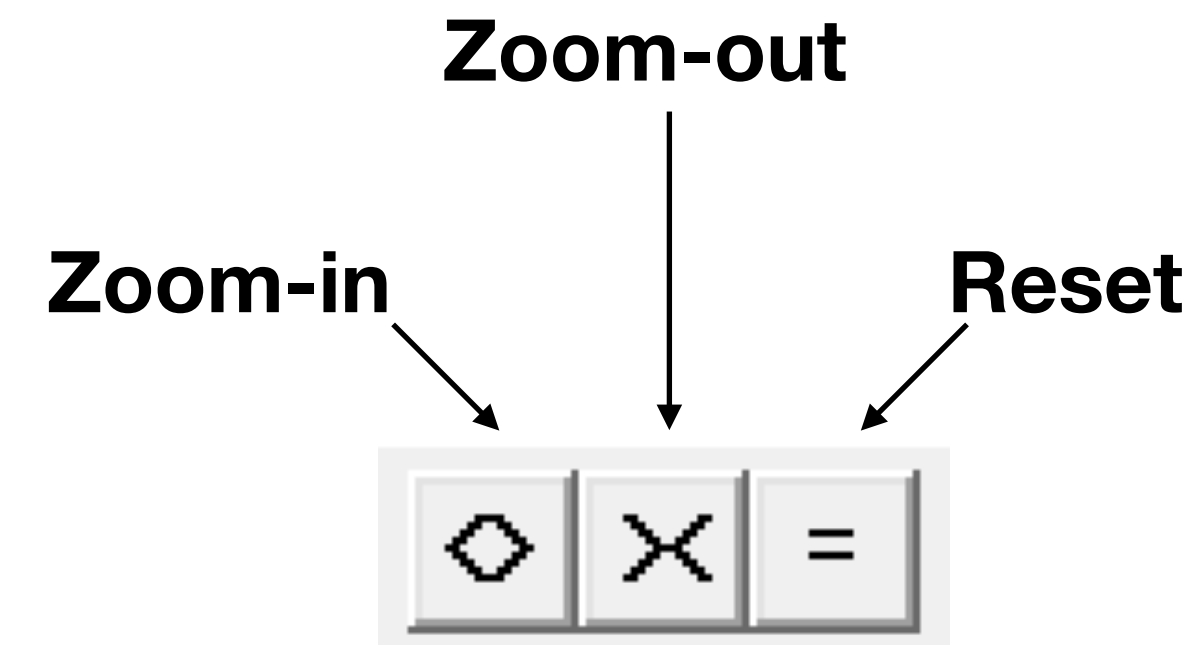At the bottom, there are navigation buttons and tabs labeled `Timing`, `VHDL`, and `I/O Panel`.


 
# Exe1: 1-bit Half Adder

- Create a new component in VHDL called `HalfAdder1`
- Input: X, Y
- Output: S, C
- Don't use `AFTER`



# Exe1: 1-bit Half Adder

architecture arch1 of HalfAdder is

begin

```
S <= X XOR Y;
```

```
C <= X AND Y;
```

end arch1;

