



04.02.20 14:27

# CSCI 150

## Introduction to Digital and Computer System Design

### Lecture 3: Combinational Logic Design I



Jetic Gū  
2020 Winter Semester (S1)

# Overview

- Focus: Methodology
- Architecture: Combinatory Logical Circuits
- Textbook v4: Ch3 3.1; v5: Ch3 3.1
- Core Ideas:
  1. Light Reading followed by My Lunch Break

# Lecture 1 & 2

- Lecture 1
  - What is digital (logic) circuit
  - How information is represented in digital (logic) circuit
- Lecture 2
  - Atomic components of digital (logic) circuit: Gates, I/O
  - Boolean Algebra

# Overview

- Focus: **Methodology**
- Architecture: Combinatory Logical Circuits
- Textbook v4: Ch3 3.1; v5: Ch3 3.1
- Core Ideas:
  1. How to **systematically use** what you've learned in Lecture 2
  2. **practice practice practice**

# Overview

- Focus: **Methodology**
- Architecture: Combinatory Logical Circuits
- Textbook v4: Ch3 3.1; v5: Ch3 3.1
- Core Ideas:
  1. How to **systematically use** what you've learned in Lecture 2
  2. **practice practice practice**

# Overview

- Focus: **Methodology**
- Architecture: Combinatory Logical Circuits
- Textbook v4: Ch3 3.1; v5: Ch3 3.1
- Core Ideas:
  1. How to **systematically use** what you've learned in Lecture 2
  2. **practice practice practice**

# Overview

- Focus: **Methodology**
- Architecture: Combinatory Logical Circuits
- Textbook v4: Ch3 3.1; v5: Ch3 3.1
- Core Ideas:
  1. How to **systematically use** what you've learned in Lecture 2
  2. **practice practice practice**

# Design Procedure

You, design this!



# Know the Problem

# Know the Problem

1. Specification of the Problem

# Know the Problem

1. Specification of the Problem
2. Basic Design, a functional Beta Implementation

# Know the Problem

1. Specification of the Problem
2. Basic Design, a functional Beta Implementation
3. Optimisation, Optimisation  
Harder, Better, Faster, Stronger

# Systematic Design Procedures

1. **Specification:** Write a specification for the circuit
2. **Formulation:** Derive relationship between inputs and outputs of the system e.g. using truth table or Boolean expressions
3. **Optimisation:** Apply optimisation, minimise the number of logic gates and literals required
4. **Technology Mapping:** Transform design to new diagram using available implementation technology
5. **Verification:** Verify the correctness of the final design in meeting the specifications

# Systematic Design Procedures (Universal)

1. **Specification:** Write a specification for the circuit
2. **Formulation:** Derive relationship between inputs and outputs of the system e.g. using truth table or Boolean expressions
3. **Optimisation:** Apply optimisation, minimise the number of logic gates and literals required
4. **Technology Mapping:** Transform design to new diagram using available implementation technology
5. **Verification:** Verify the correctness of the final design in meeting the specifications

# Systematic Design Procedures (Universal)

1. **Specification:** Write a specification for the circuit
2. **Formulation:** Derive relationship between inputs and outputs of the system  
e.g. using truth table or Boolean expressions
3. **Optimisation:** Apply optimisation, minimise the number of logic gates and literals required
4. **Technology Mapping:** Transform design to new diagram using available implementation technology
5. **Verification:** Verify the correctness of the final design in meeting the specifications

# Systematic Design Procedures

1. **Specification:** Write a specification for the circuit
2. **Formulation:** Derive relationship between inputs and outputs of the system e.g. using truth table or Boolean expressions
3. **Optimisation:** Apply optimisation, minimise the number of logic gates and literals required
4. **Technology Mapping:** Transform design to new diagram using available implementation technology
5. **Verification:** Verify the correctness of the final design in meeting the specifications



# Summary

# Summary

- Boolean Algebra III: K-Map

# Summary

- Boolean Algebra III: K-Map
  - Two Variable K-Map

# Summary

- Boolean Algebra III: K-Map
  - Two Variable K-Map
  - Three Variable K-Map

# Summary

- Boolean Algebra III: K-Map
  - Two Variable K-Map
  - Three Variable K-Map
  - Four Variable K-Map

# Summary

- Boolean Algebra III: K-Map
  - Two Variable K-Map
  - Three Variable K-Map
  - Four Variable K-Map
  - Don't care optimisation

# An Old Friend

Curtain Motors Revisited

# An Old Friend

- Curtain Motor Control
  - **Sensor1: 1 when curtain is fully closed**
  - **Sensor2: 1 when curtain is fully open**
  - Button1: 1 when user wants to open the curtain
  - Button2: 1 when user wants to close the curtain
  - Output1: 1 to make the motor open the window
  - Output2: 1 to make the motor close the window
  - Light: motor is active



- Stop the motor when the curtain is already fully opened/  
closed



# An Old Friend

## 1. Specification

- Curtain Motor Control
  - **Sensor1: 1 when curtain is fully closed**
  - **Sensor2: 1 when curtain is fully open**
  - Button1: 1 when user wants to open the curtain
  - Button2: 1 when user wants to close the curtain
  - Output1: 1 to make the motor open the window
  - Output2: 1 to make the motor close the window
  - Light: motor is active



- Stop the motor when the curtain is already fully opened/closed

# An Old Friend

## 1. Specification

- Curtain Motor Control

- Input • **Sensor1: 1 when curtain is fully closed**
- Input • **Sensor2: 1 when curtain is fully open**
- Input • Button1: 1 when user wants to open the curtain
- Input • Button2: 1 when user wants to close the curtain
- Output • Output1: 1 to make the motor open the window
- Output • Output2: 1 to make the motor close the window
- Output • Light: motor is active



- Stop the motor when the curtain is already fully opened/closed

# An Old Friend

## 1. Specification

- Curtain Motor Control

- Input** • **Sensor1: 1 when curtain is fully closed**
- Input** • **Sensor2: 1 when curtain is fully open**
- Input** • **Button1: 1 when user wants to open the curtain**
- Input** • **Button2: 1 when user wants to close the curtain**
- Output** • **Output1: 1 to make the motor open the window**
- Output** • **Output2: 1 to make the motor close the window**
- Output** • **Light: motor is active**



- Cond** Stop the motor when the curtain is already fully opened/closed

# An Old Friend

## 1. Specification

- Curtain Motor Control

- Switch • **Sensor1: 1 when curtain is fully closed**
- Switch • **Sensor2: 1 when curtain is fully open**
- Switch • **Button1: 1 when user wants to open the curtain**
- Switch • **Button2: 1 when user wants to close the curtain**
- Prob • **Output1: 1 to make the motor open the window**
- Prob • **Output2: 1 to make the motor close the window**
- Prob • **Light: motor is active**



- Cond Stop the motor when the curtain is already fully opened/closed

# An Old Friend

## 2. Formulation

- Curtain Motor Control

Switch • **Sensor1: 1 when curtain is fully closed**

Switch • **Sensor2: 1 when curtain is fully open**

Switch • Button1: 1 when user wants to **open** the curtain

Switch • Button2: 1 when user wants to **close** the curtain

Prob • Output1: 1 to make the motor **open** the window

Prob • Output2: 1 to make the motor **close** the window

Prob • Light: motor is active

Cond Stop the motor when the curtain is already fully opened/  
closed

# An Old Friend

## 2. Formulation

- Curtain Motor Control

Switch • Sensor1: 1 when curtain is fully closed

Switch • Sensor2: 1 when curtain is fully open

Switch • Button1: 1 when user wants to **open** the curtain

Switch • Button2: 1 when user wants to **close** the curtain

Prob • Output1: 1 to make the motor **open** the window

Prob • Output2: 1 to make the motor **close** the window

Prob • Light: motor is active

FullyClosed = Sensor1

FullyOpened = Sensor2

Cond Stop the motor when the curtain is already fully opened/  
closed



# An Old Friend

## 2. Formulation

- Curtain Motor Control

Switch • Sensor1: 1 when curtain is fully closed

Switch • Sensor2: 1 when curtain is fully open

Switch • Button1: 1 when user wants to **open** the curtain

Switch • Button2: 1 when user wants to **close** the curtain

Prob • Output1: 1 to make the motor **open** the window

Prob • Output2: 1 to make the motor **close** the window

Prob • Light: motor is active

FullyClosed = Sensor1

FullyOpened = Sensor2

Cond Stop the motor when the curtain is already fully opened/  
closed

# An Old Friend

## 2. Formulation

- Curtain Motor Control

Switch • **Sensor1: 1 when curtain is fully closed**

Switch • **Sensor2: 1 when curtain is fully open**

Switch • Button1: 1 when user wants to **open** the curtain

Switch • Button2: 1 when user wants to **close** the curtain

Prob • Output1: 1 to make the motor **open** the window

Prob • Output2: 1 to make the motor **close** the window

Prob • Light: motor is active

FullyClosed = Sensor1

FullyOpened = Sensor2

Light = Out1 + Out2

Cond Stop the motor when the curtain is already fully opened/closed



# An Old Friend

## 2. Formulation

- Curtain Motor Control

- Switch** • **Sensor1: 1 when curtain is fully closed**
- Switch** • **Sensor2: 1 when curtain is fully open**
- Switch** • Button1: 1 when user wants to **open** the curtain
- Switch** • Button2: 1 when user wants to **close** the curtain
- Prob** • Output1: 1 to make the motor **open** the window
- Prob** • Output2: 1 to make the motor **close** the window
- Prob** • Light: motor is active

FullyClosed = Sensor1  
FullyOpened = Sensor2  
Light = Out1 + Out2

**Cond** Stop the motor when the curtain is already fully opened/closed

# An Old Friend

## 2. Formulation

- Curtain Motor Control

- Switch • **Sensor1: 1 when curtain is fully closed**
- Switch • **Sensor2: 1 when curtain is fully open**
- Switch • Button1: 1 when user wants to **open** the curtain
- Switch • Button2: 1 when user wants to **close** the curtain
- Prob • Output1: 1 to make the motor **open** the window
- Prob • Output2: 1 to make the motor **close** the window
- Prob • Light: motor is active

$$\text{FullyClosed} = \text{Sensor1}$$
$$\text{FullyOpened} = \text{Sensor2}$$
$$\text{Light} = \text{Out1} + \text{Out2}$$

$$\text{Out1} = \text{Bu1} \cdot \overline{\text{FullyOpened}}$$

$$\text{Out2} = \text{Bu2} \cdot \overline{\text{FullyClosed}}$$

Cond Stop the motor when the curtain is already fully opened/closed

# An Old Friend

## 2. Formulation

- Curtain Motor Control

- Switch • **Sensor1: 1 when curtain is fully closed**
- Switch • **Sensor2: 1 when curtain is fully open**
- Switch • Button1: 1 when user wants to **open** the curtain
- Switch • Button2: 1 when user wants to **close** the curtain
- Prob • Output1: 1 to make the motor **open** the window
- Prob • Output2: 1 to make the motor **close** the window
- Prob • Light: motor is active

$$\text{FullyClosed} = \text{Sensor1}$$
$$\text{FullyOpened} = \text{Sensor2}$$
$$\text{Light} = \text{Out1} + \text{Out2}$$

$$\text{Out1} = \text{Bu1} \cdot \overline{\text{FullyOpened}}$$

$$\text{Out2} = \text{Bu2} \cdot \overline{\text{FullyClosed}}$$

Cond Stop the motor when the curtain is already fully opened/closed

# An Old Friend

## 2. Formulation

- Curtain Motor Control

- Switch** • **Sensor1: 1 when curtain is fully closed**
- Switch** • **Sensor2: 1 when curtain is fully open**
- Switch** • **Button1: 1 when user wants to **open** the curtain**
- Switch** • **Button2: 1 when user wants to **close** the curtain**
- Prob** • **Output1: 1 to make the motor **open** the window**
- Prob** • **Output2: 1 to make the motor **close** the window**
- Prob** • **Light: motor is active**

$$\text{FullyClosed} = \text{Sensor1}$$
$$\text{FullyOpened} = \text{Sensor2}$$
$$\text{Light} = \text{Out1} + \text{Out2}$$

$$\text{Out1} = \text{Bu1} \cdot \overline{\text{FullyOpened}} \cdot \overline{\text{BothPressed}}$$

$$\text{Out2} = \text{Bu2} \cdot \overline{\text{FullyClosed}} \cdot \overline{\text{BothPressed}}$$

$$\text{BothPressed} = \text{Bu1} \cdot \text{Bu2}$$

**Cond** Stop the motor when the curtain is already fully opened/  
closed

---

# An Old Friend

## 2. Formulation

- Curtain Motor Control

- Switch** • **Sensor1: 1 when curtain is fully closed**
- Switch** • **Sensor2: 1 when curtain is fully open**
- Switch** • **Button1: 1 when user wants to **open** the curtain**
- Switch** • **Button2: 1 when user wants to **close** the curtain**
- Prob** • **Output1: 1 to make the motor **open** the window**
- Prob** • **Output2: 1 to make the motor **close** the window**
- Prob** • **Light: motor is active**

$$\text{FullyClosed} = \text{Sensor1}$$
$$\text{FullyOpened} = \text{Sensor2}$$
$$\text{Light} = \text{Out1} + \text{Out2}$$

$$\text{Out1} = \text{Bu1} \cdot \overline{\text{FullyOpened}} \cdot \overline{\text{BothPressed}}$$

$$\text{Out2} = \text{Bu2} \cdot \overline{\text{FullyClosed}} \cdot \overline{\text{BothPressed}}$$

$$\text{BothPressed} = \text{Bu1} \cdot \text{Bu2}$$

**Cond** Stop the motor when the curtain is already fully opened/  
closed

---

# An Old Friend

## 3. Optimisation

$$\begin{aligned}\text{FullyClosed} &= \text{Sensor1} \\ \text{FullyOpened} &= \text{Sensor2} \\ \text{Light} &= \text{Out1} + \text{Out2} \\ \text{Out1} &= \text{Bu1} \cdot \overline{\text{FullyOpened}} \cdot \overline{\text{BothPressed}} \\ \text{Out2} &= \text{Bu2} \cdot \overline{\text{FullyClosed}} \cdot \overline{\text{BothPressed}} \\ \text{BothPressed} &= \text{Bu1} \cdot \text{Bu2}\end{aligned}$$

$$\begin{aligned}\text{Light} &= \text{Out1} + \text{Out2} \\ \text{Out1} &= \text{Bu1} \cdot \overline{\text{Sensor2}} \cdot \overline{\text{Bu1}} \cdot \overline{\text{Bu2}} \\ \text{Out2} &= \text{Bu2} \cdot \overline{\text{Sensor1}} \cdot \overline{\text{Bu1}} \cdot \overline{\text{Bu2}}\end{aligned}$$

# An Old Friend

## 4. Technology Mapping

$$\text{Light} = \text{Out1} + \text{Out2}$$

$$\text{Out1} = \text{Bu1} \cdot \overline{\text{Sensor2}} \cdot \overline{\text{Bu1}} \cdot \text{Bu2}$$

$$\text{Out2} = \text{Bu2} \cdot \overline{\text{Sensor1}} \cdot \overline{\text{Bu1}} \cdot \text{Bu2}$$

# An Old Friend

## 4. Technology Mapping

$$\text{Light} = \text{Out1} + \text{Out2}$$

$$\text{Out1} = \text{Bu1} \cdot \overline{\text{Sensor2}} \cdot \overline{\text{Bu1}} \cdot \text{Bu2}$$

$$\text{Out2} = \text{Bu2} \cdot \overline{\text{Sensor1}} \cdot \overline{\text{Bu1}} \cdot \text{Bu2}$$

- Available Components (Technology)



# An Old Friend

## 4. Technology Mapping

$$\text{Light} = \text{Out1} + \text{Out2}$$

$$\text{Out1} = \text{Bu1} \cdot \overline{\text{Sensor2}} \cdot \overline{\text{Bu1}} \cdot \overline{\text{Bu2}}$$

$$\text{Out2} = \text{Bu2} \cdot \overline{\text{Sensor1}} \cdot \overline{\text{Bu1}} \cdot \overline{\text{Bu2}}$$

- Available Components (Technology)
- AND, NAND, OR, NOT gate; Switch, Prob

# An Old Friend


## 4. Technology Mapping

$$\text{Light} = \text{Out1} + \text{Out2}$$

$$\text{Out1} = \text{Bu1} \cdot \overline{\text{Sensor2}} \cdot \overline{\text{Bu1}} \cdot \text{Bu2}$$

$$\text{Out2} = \text{Bu2} \cdot \overline{\text{Sensor1}} \cdot \overline{\text{Bu1}} \cdot \text{Bu2}$$

 - Available Components (Technology)
  - AND, NAND, OR, NOT gate; Switch, Prob



# An Old Friend

## 4. Technology Mapping


$$\text{Light} = \text{Out1} + \text{Out2}$$

$$\text{Out1} = \text{Bu1} \cdot \overline{\text{Sensor2}} \cdot \overline{\text{Bu1}} \cdot \text{Bu2}$$

$$\text{Out2} = \text{Bu2} \cdot \overline{\text{Sensor1}} \cdot \overline{\text{Bu1}} \cdot \text{Bu2}$$

- Available Components (Technology)
  - AND, NAND, OR gate; Switch, Prob

**NO NOT GATE!**

 

# An Old Friend

## 4. Technology Mapping


$$\text{Light} = \text{Out1} + \text{Out2}$$

$$\text{Out1} = \text{Bu1} \cdot \overline{\text{Sensor2}} \cdot \overline{\text{Bu1}} \cdot \text{Bu2}$$

$$\text{Out2} = \text{Bu2} \cdot \overline{\text{Sensor1}} \cdot \overline{\text{Bu1}} \cdot \text{Bu2}$$

- Available Components (Technology)
- AND, NAND, OR gate; Switch, Prob

**NO NOT GATE!**

 

# An Old Friend


## 4. Technology Mapping

$$\text{Light} = \text{Out1} + \text{Out2}$$

$$\text{Out1} = \text{Bu1} \cdot \overline{\text{Sensor2}} \cdot \overline{\text{Bu1}} \cdot \text{Bu2}$$


$$\text{Out2} = \text{Bu2} \cdot \overline{\text{Sensor1}} \cdot \overline{\text{Bu1}} \cdot \text{Bu2}$$

 - Available Components (Technology)
  - AND, NAND, OR, NOT gate; Switch, Prob



# An Old Friend

## 5. Verification

 

- Design test cases
  - Sensor2, Bu1 on
  - Sensor1, Bu2 on
  - Bu1, Bu2 on
  - Bu1 on
  - Bu2 on
  - etc...