



12.02.20 07:14

CSCI 150

Introduction to Digital and Computer System Design

Lecture 3: Combinational Logic Design IV



Jetic Gū
2020 Winter Semester (S1)

Overview


- Focus: Logic Functions
- Architecture: Combinatory Logical Circuits
- Textbook v4: Ch3 3.6, 3.7; v5: Ch3 3.6, 3.7
- Core Ideas:
 1. Encoder
 2. Multiplexer

Systematic Design Procedures

 1. **Specification:** Write a specification for the circuit
2. **Formulation:** Derive relationship between inputs and outputs of the system e.g. using truth table or Boolean expressions
3. **Optimisation:** Apply optimisation, minimise the number of logic gates and literals required
4. **Technology Mapping:** Transform design to new diagram using available implementation technology
5. **Verification:** Verify the correctness of the final design in meeting the specifications

Functional Components

- Value-Fixing, Transferring, Inverting, Enabler
- Decoder
 - Input: $A_0A_1 \dots A_{n-1}$
 - Output: $D_0D_1 \dots D_{2^n-1}$, $D_i = m_i$





Encoder

Wait, didn't we just covered this?
Oh, that's decoder

Encoder

  
- Inverse operation of a decoder
- 2^n inputs, only one is giving positive input¹
- n outputs



 1. In reality, could be less

Encoder


- Inverse operation of a decoder
- 2^n inputs, only one is giving positive input¹
- n outputs



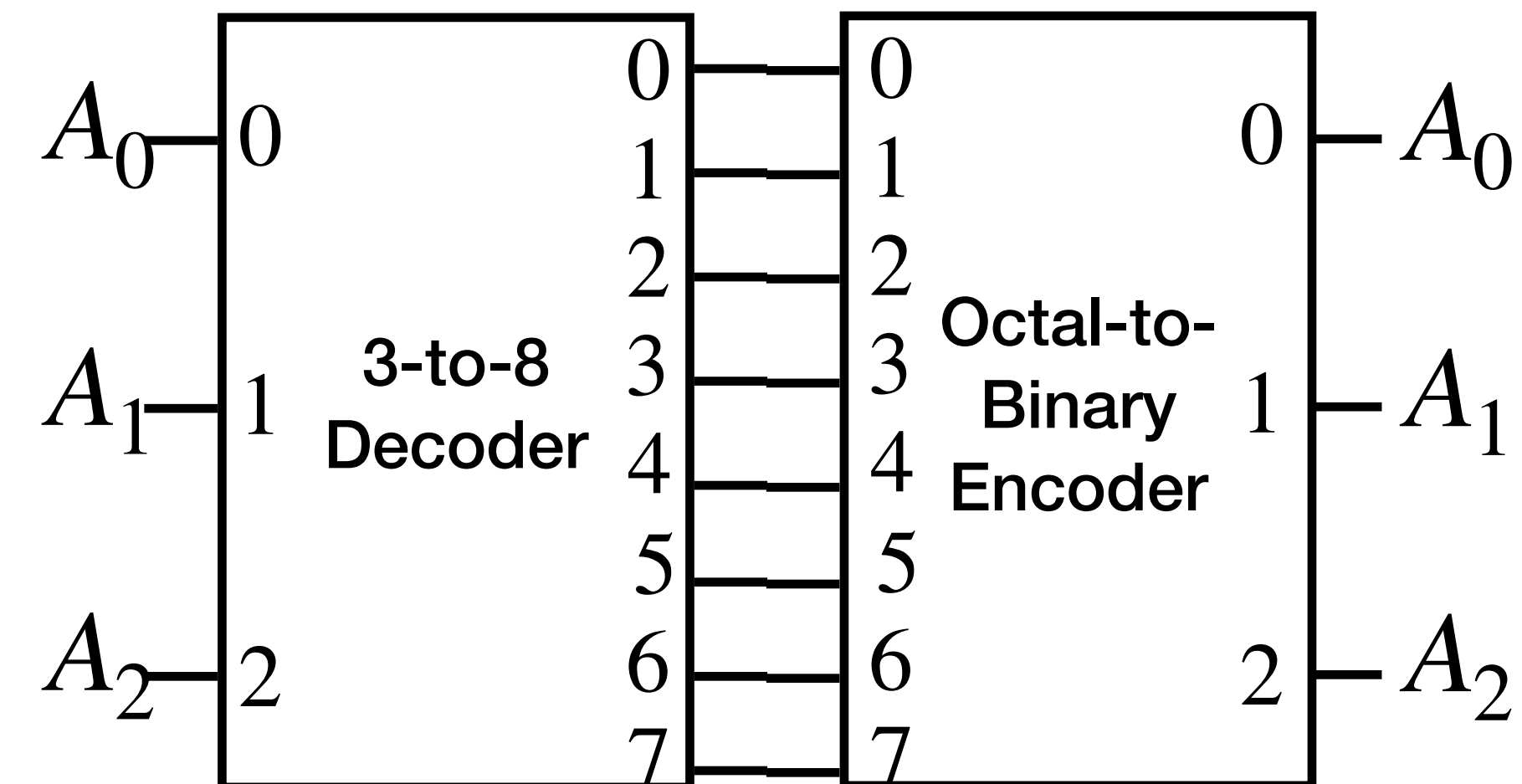1. In reality, could be less

Encoder


- Inverse operation of a decoder
- 2^n inputs, only one is giving positive input¹
- n outputs



1. In reality, could be less

Encoder

D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
							1	0	0	0
						1		0	0	1
					1			0	1	0
				1				0	1	1
			1					1	0	0
		1						1	0	1
	1							1	1	0
1								1	1	1

 

Concept


Encoder

D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
							1	0	0	0
						1		0	0	1
					1			0	1	0
				1				0	1	1
			1					1	0	0
		1						1	0	1
	1							1	1	0
1								1	1	1

$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

 


Encoder

$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$


$$A_2 = D_4 + D_5 + D_6 + D_7$$

 - What happens if the inputs are all 0s?
- What happens if the inputs include multiple 1s?




Priority Encoder

 - Additional Validity Output V
 - Indicating whether the input is valid (contains 1)
- Priority
 - Ignores $D_{<i}$ if $D_i = 1$




Priority Encoder

D ₃	D ₂	D ₁	D ₀	A ₁	A ₀	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

 


Priority Encoder

D ₃	D ₂	D ₁	D ₀	A ₁	A ₀	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

 


Priority Encoder

D ₃	D ₂	D ₁	D ₀	A ₁	A ₀	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

 

Priority Encoder

D ₃	D ₂	D ₁	D ₀	A ₁	A ₀	V
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

 

Concept

Priority Encoder


D_3	D_2	D_1	D_0	A_1	A_0	V
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

$$V = D_3 + D_2 + D_1 + D_0$$

$$A_1 = D_3 + \overline{D_3}D_2 = D_2 + D_3$$

$$A_0 = \overline{D_3}\overline{D_2}D_1 + D_3$$

$$= \overline{D_2}D_1 + D_3$$

 

Multiplexer


Switch Modes

Multiplexer

- Multiple n -variable input vectors
- Single n -variable output vector
- Switches: which input vectors to output


Multiplexer

 - Multiple n -variable input vectors
- Single n -variable output vector
- Switches: which input vectors to output




Multiplexer

 - Multiple n -variable input vectors
- Single n -variable output vector
- Switches: which input vectors to output




Multiplexer

 - Multiple n -variable input vectors
- Single n -variable output vector
- Switches: which input vectors to output




Multiplexer

 - Multiple n -variable input vectors
- Single n -variable output vector
- Switches: which input vectors to output




Multiplexer

 - Multiple n -variable input vectors
- Single n -variable output vector
- Switches: which input vectors to output




Single-Bit 2-to-1 Multiplexer

 - 2 single-bit inputs
- 1 single-bit output
- 1-bit switch




Single-Bit 2-to-1 Multiplexer

S	I ₀	I ₁	Y
0	0	X	0
0	1	X	1
1	X	0	0
1	X	0	1

 


Single-Bit 2-to-1 Multiplexer

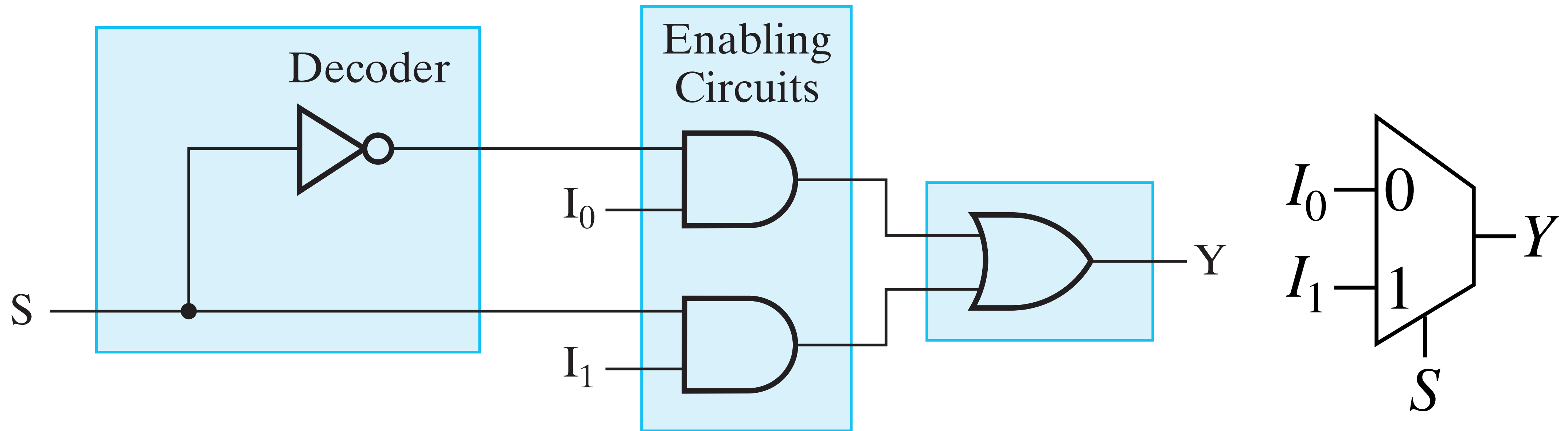- Technology
- 1 x 1-to-2 Decoder
 - 2 x 1-bit Enabler
 - 1 x 2-input OR Gate




Single-Bit 4-to-1 Multiplexer

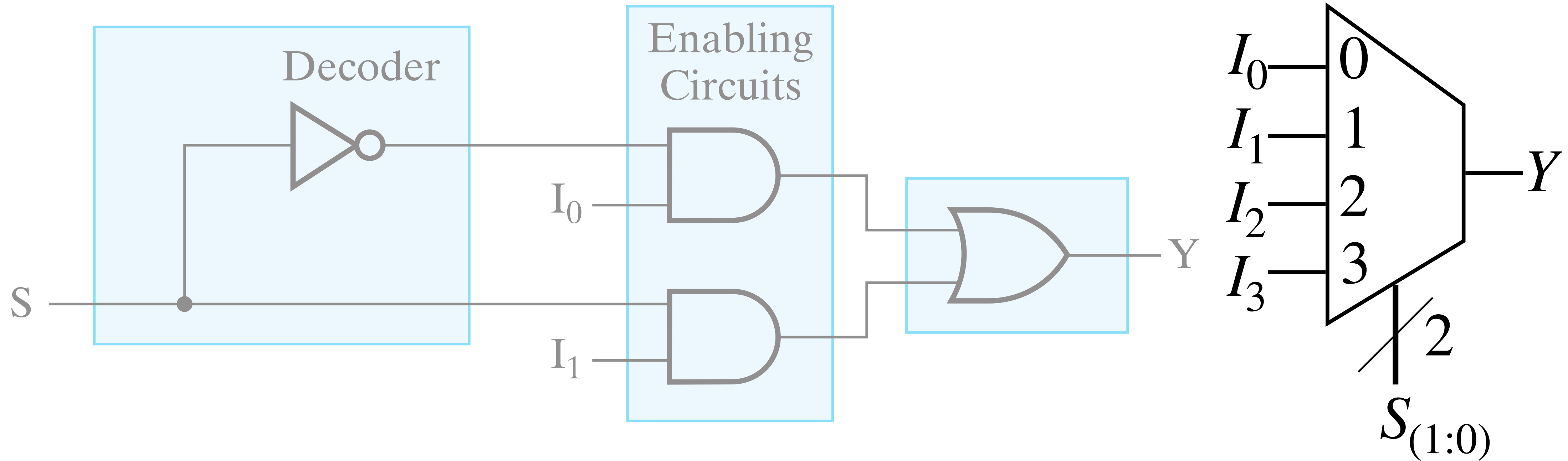
- Technology
- 1 x 2-to-4 Decoder
 - 4 x 1-bit Enabler
 - 1 x 4-input OR Gate



Single-Bit 4-to-1 Multiplexer

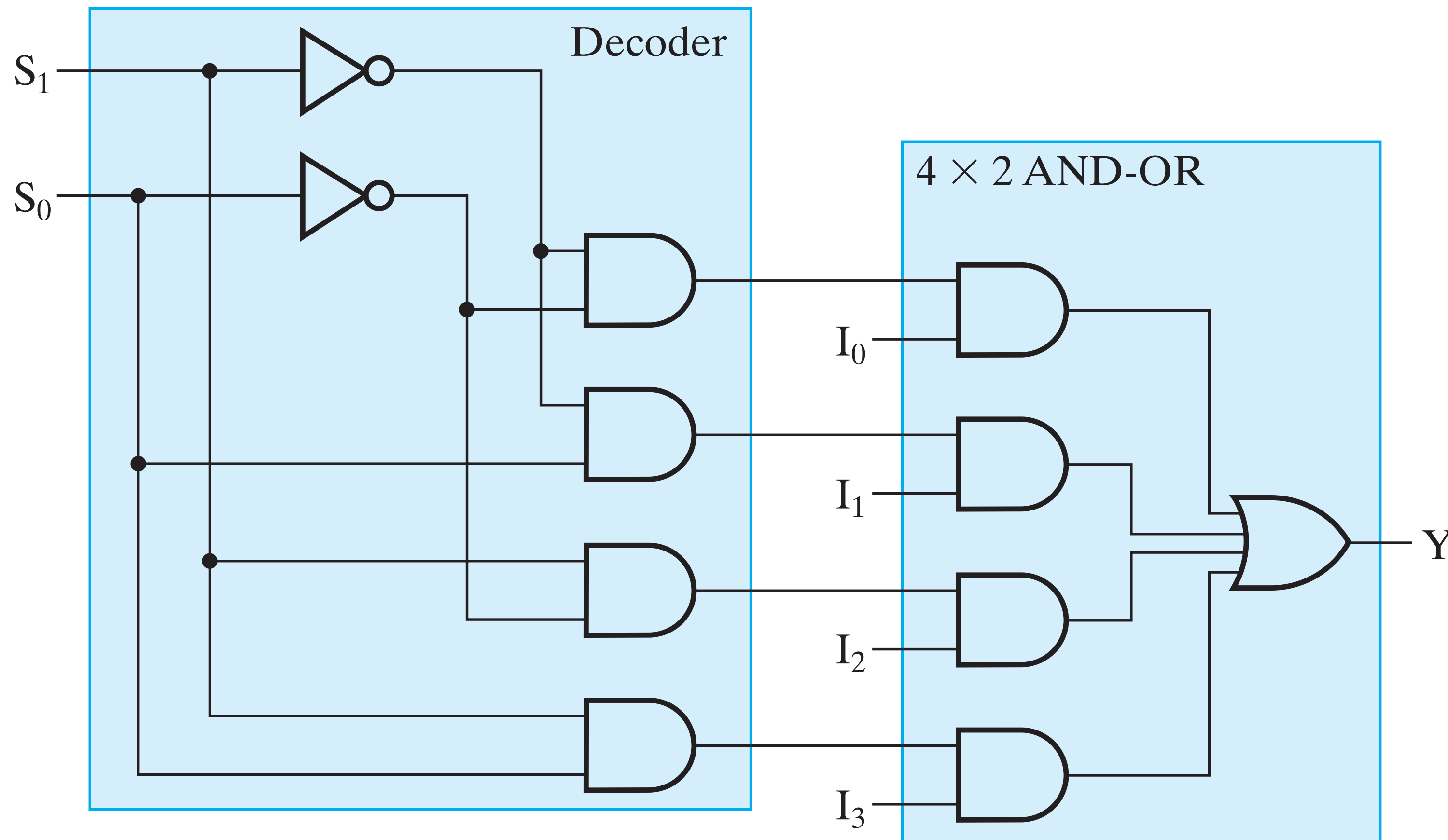

 - Technology
- 1 x 2-to-4 Decoder
 - 4 x 1-bit Enabler
 - 1 x 4-input OR Gate



Concept

Circuit Drawing Time!



It's OK, this is the last time...
Sorta...

Last Circuit Drawing Practice



1. Sub-circuit
2. Implementing 2-to-4 Decoder using drawing tools
3. Implementing 3-to-8 Decoder using 2-to-4 Decoders
4. Implementing Octal-to-Binary Priority Encoder using drawing tools¹
5. Implementing Multiplexer using drawing tools¹

1. You will be reusing these designs in later lectures and assignments

Sub-circuit

 
 


Sub-circuit

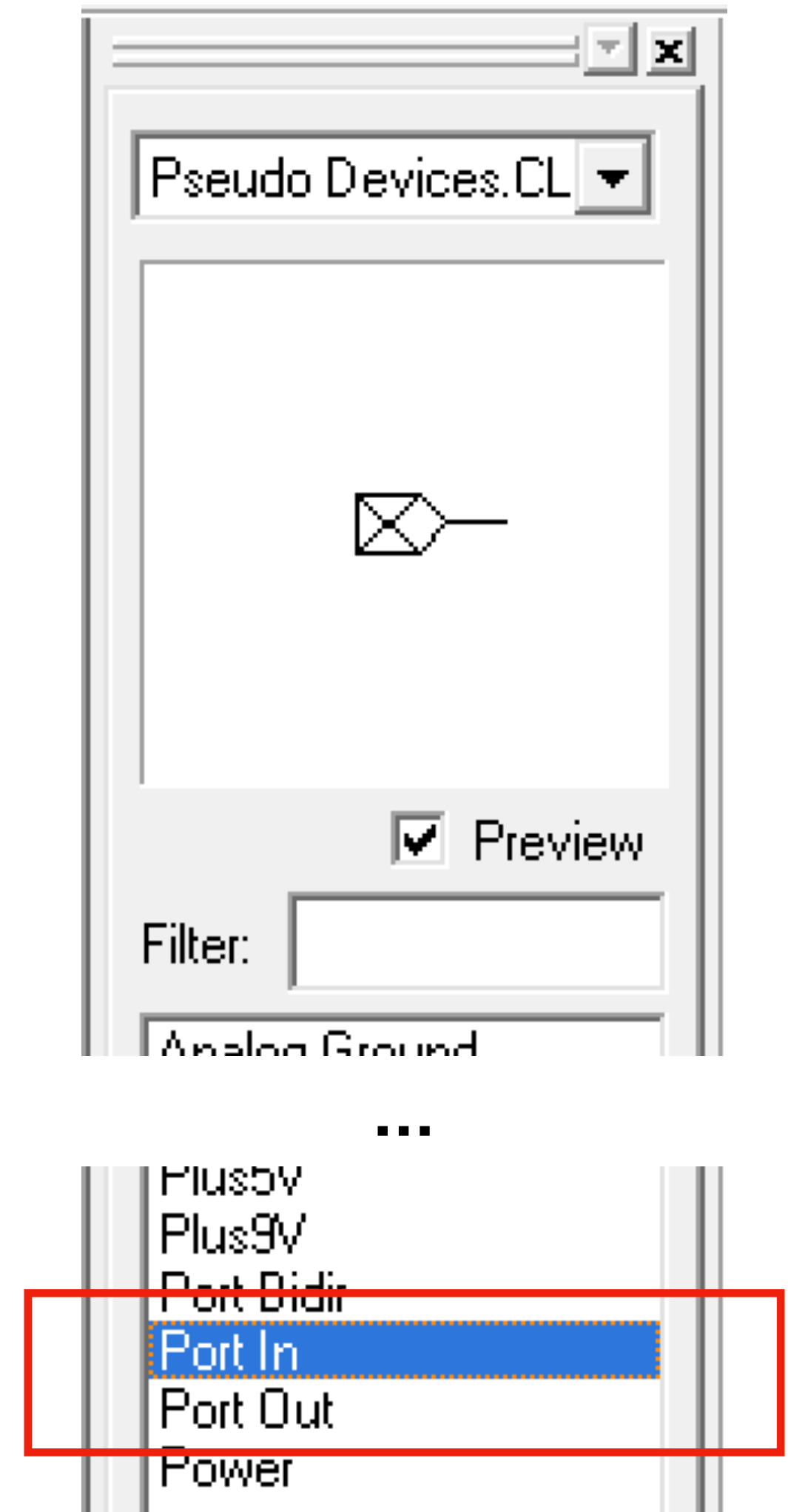 


2. Replace the switch with Port In, replace the probs with Port Out


Sub-circuit

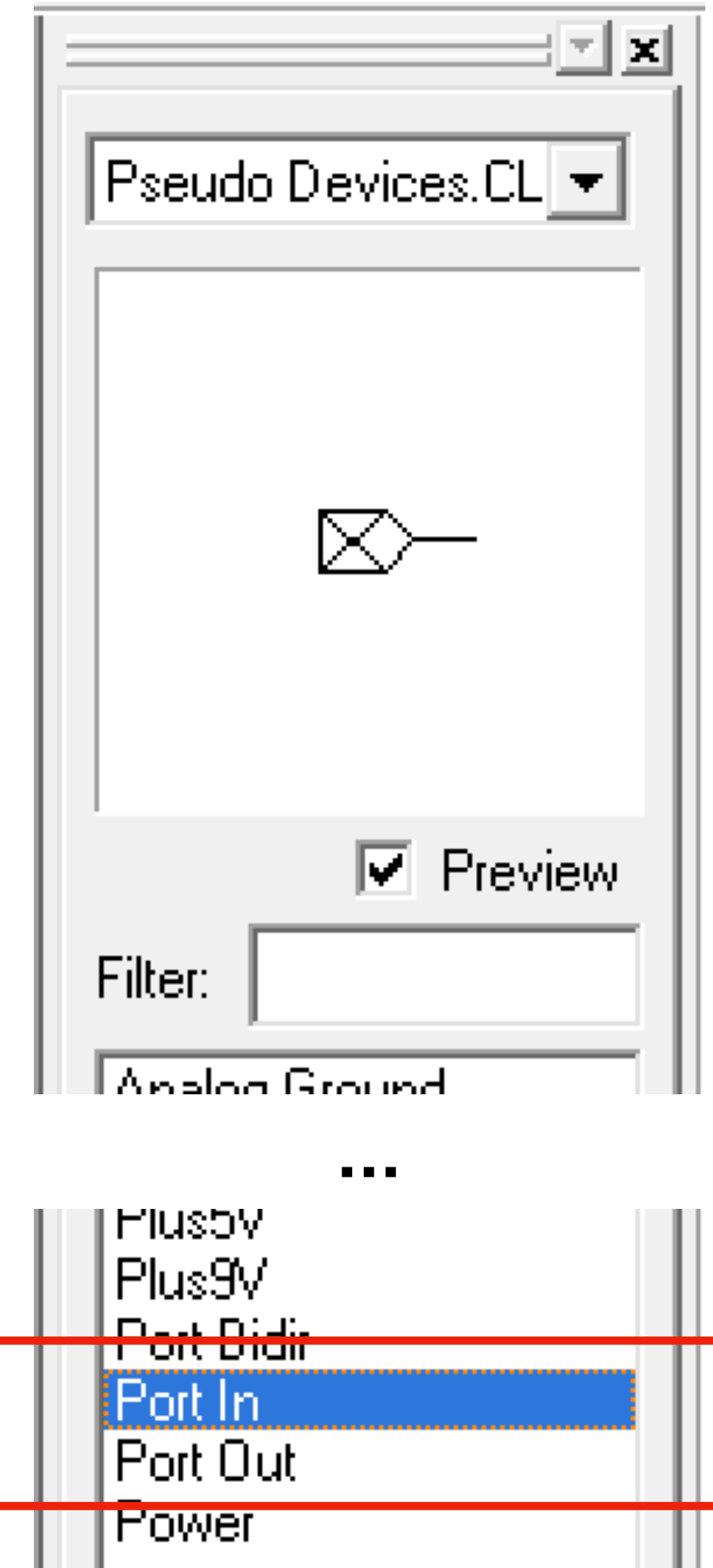 


Sub-circuit

 


Sub-circuit

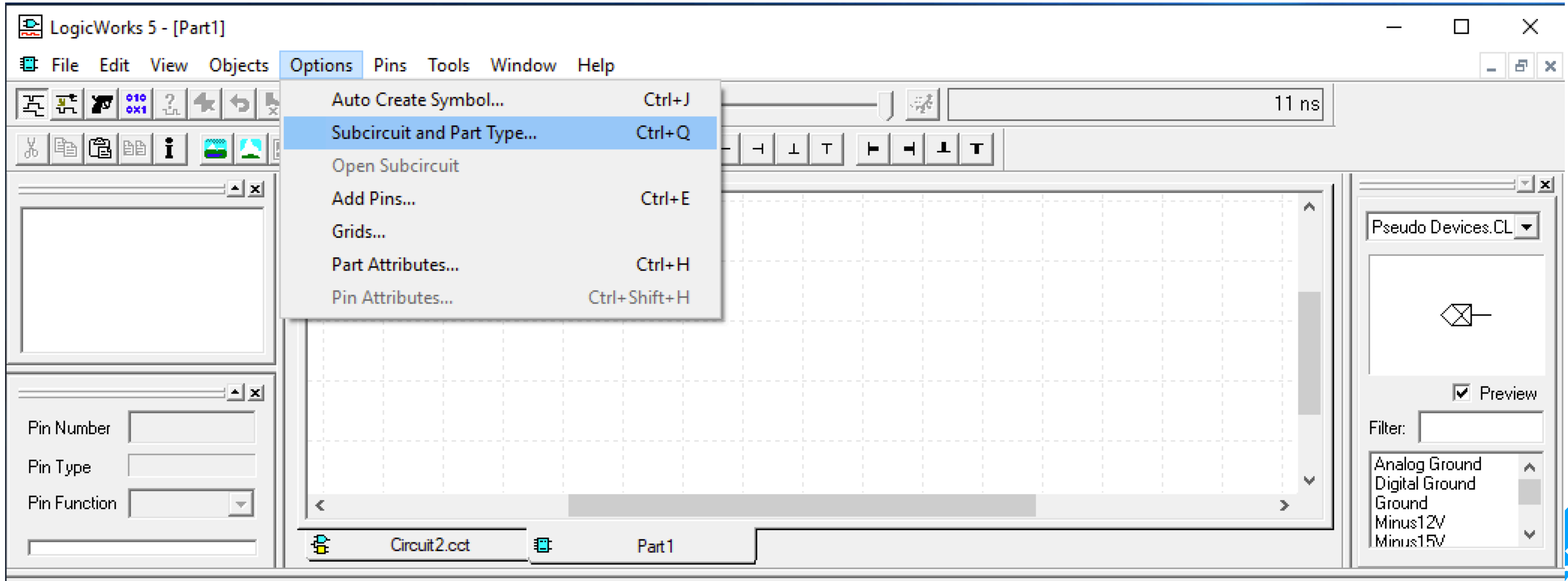


Sub-circuit

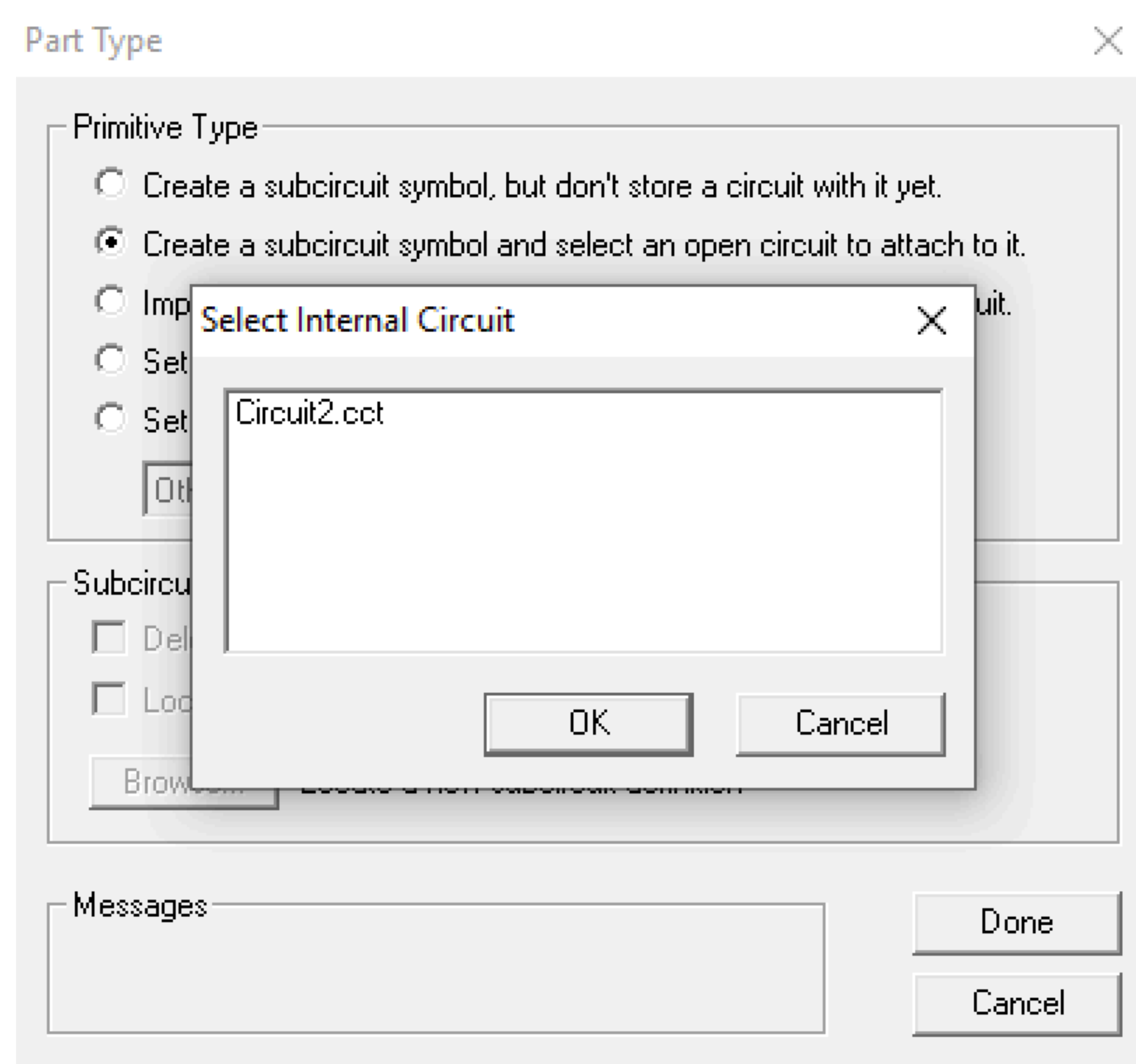


Sub-circuit

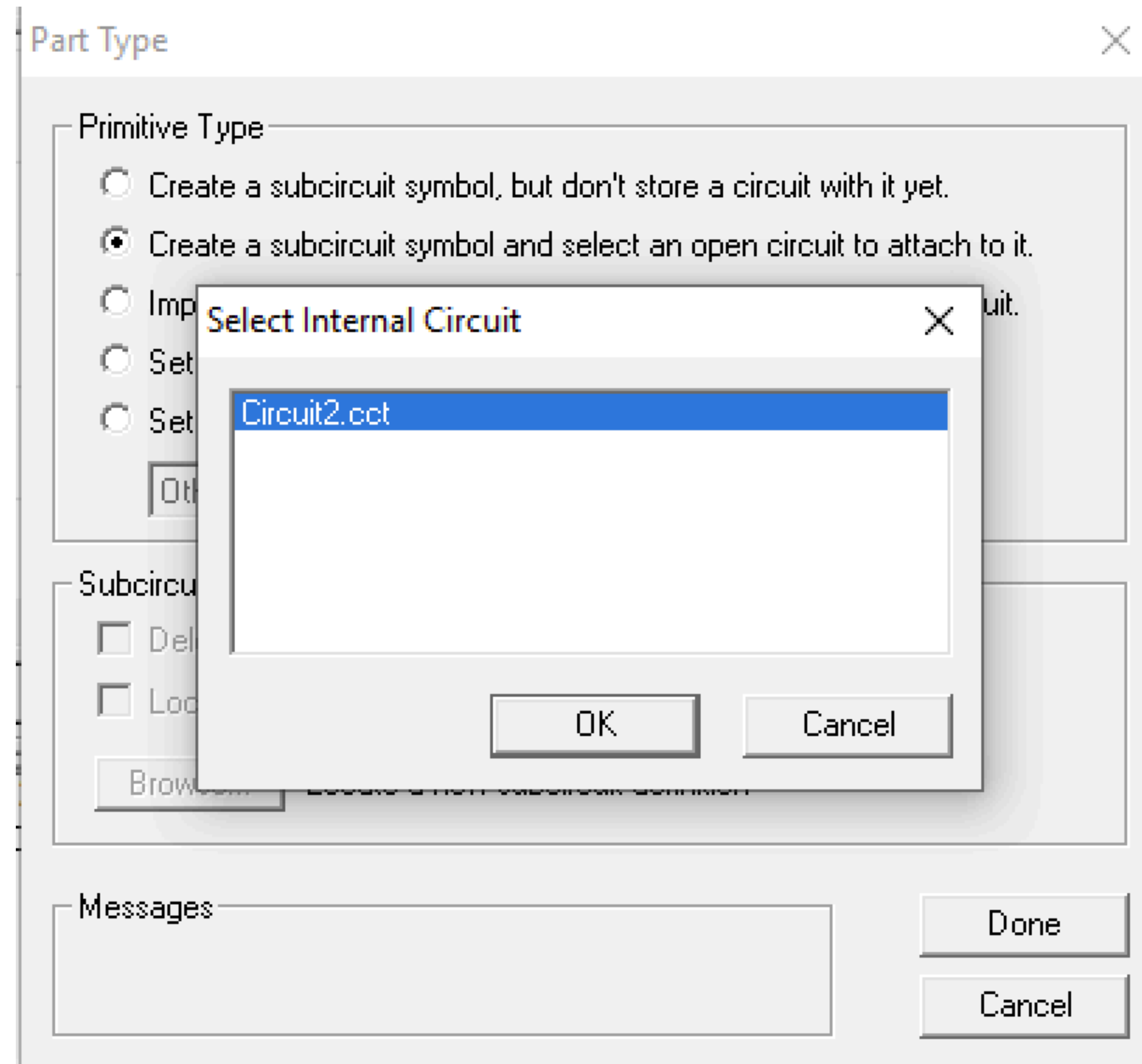


Sub-circuit

 

Use these pins only!

 


Add a text description

 



Technical

Sub-circuit

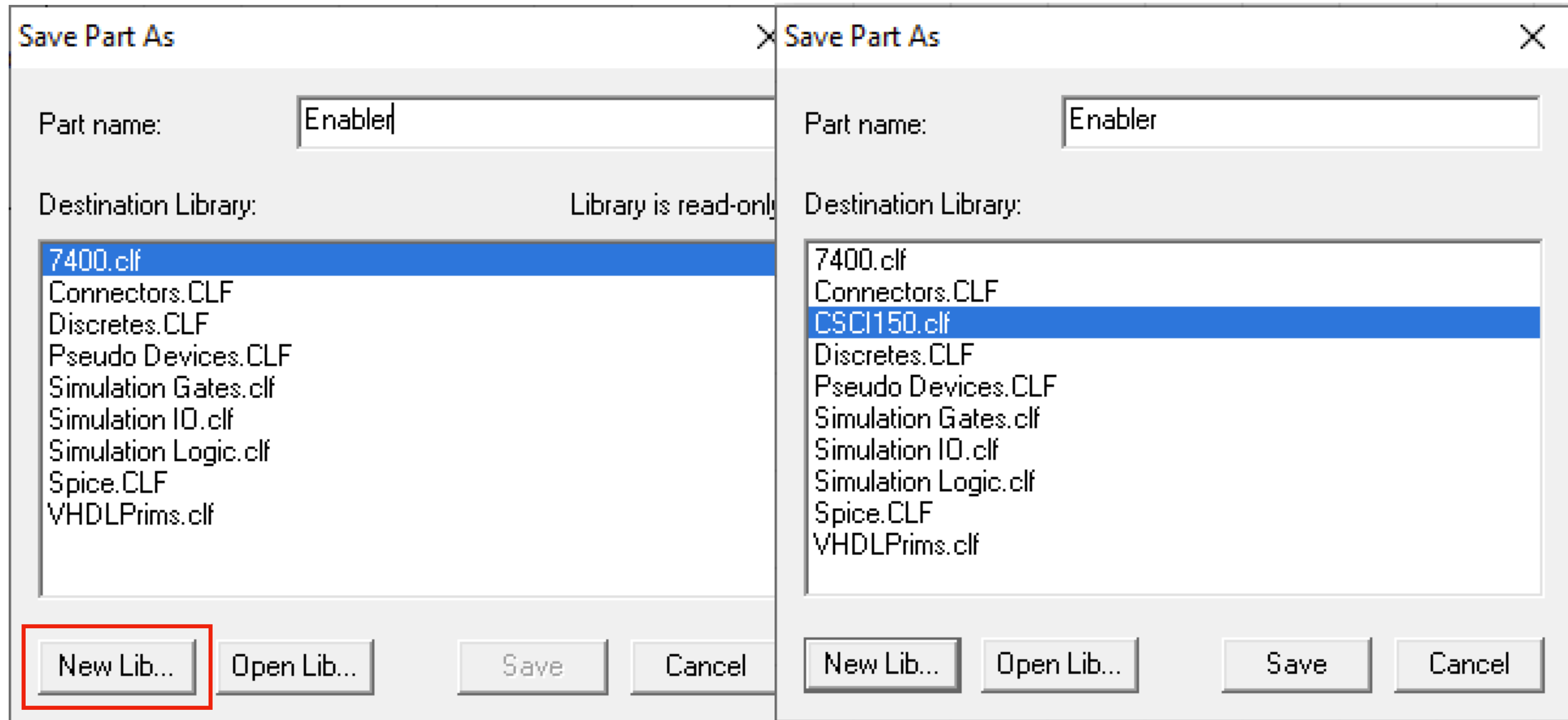

Technical

Sub-circuit

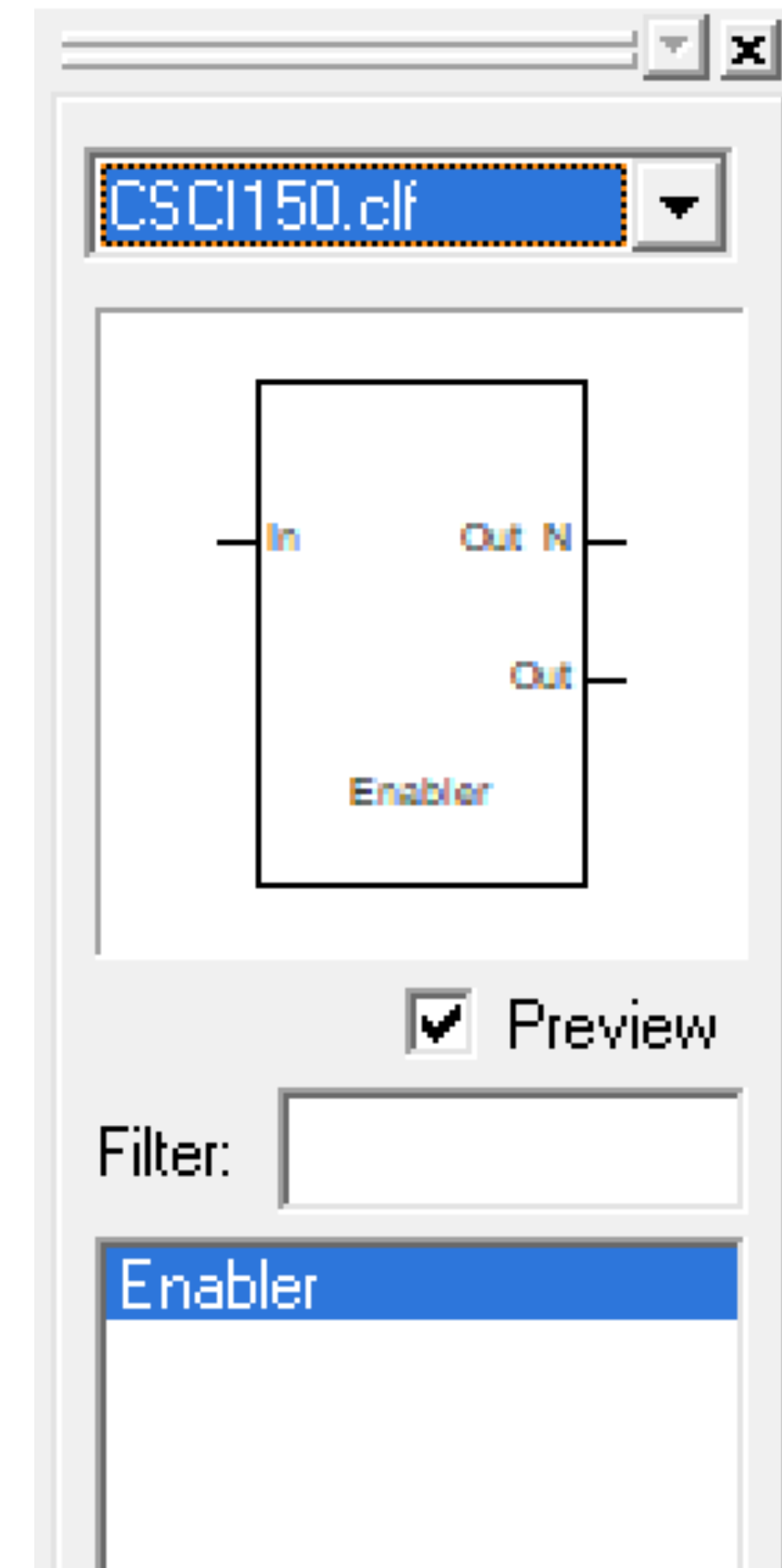 

Technical

Last Circuit Drawing Practice

1. Sub-circuit
2. Implementing 2-to-4 Decoder using drawing tools
3. Implementing 3-to-8 Decoder using 2-to-4 Decoders
4. Implementing Octal-to-Binary Priority Encoder using drawing tools¹
5. Implementing Multiplexer using drawing tools¹

1. You will be reusing these designs in later lectures and assignments