



CSCI 150

Introduction to Digital and Computer System Design

Lecture 3: Combinational Logic Design II



Jetic Gū
2020 Summer Semester (S2)

Overview

- Focus: Methodology
- Architecture: Combinatory Logical Circuits
- Textbook v4: Ch3 3.1, 3.2, 3.3; v5: Ch3 3.1, 3.2
- Core Ideas:
 1. BCD-to-Seven-Segment Decoder
 2. 4-bit Equity Comparator
 3. Technology Mapping

Systematic Design Procedures


1. **Specification:** Write a specification for the circuit
2. **Formulation:** Derive relationship between inputs and outputs of the system
e.g. using truth table or Boolean expressions
3. **Optimisation:** Apply optimisation, minimise the number of logic gates and literals required
4. **Technology Mapping:** Transform design to new diagram using available implementation technology
5. **Verification:** Verify the correctness of the final design in meeting the specifications

BCD-to-Seven-Segment Decoder

Ah, not again


LED Seven Segment Display

 - LED: Light-Emitting Diodes
- A single digit display takes 7bit inputs (and an optional one for decimal point)



BCD to 7 Segment Display(s)

 - BCD: Each digit is represented using 4bit binary int
- BCD-to-7-segment decoder
A Combinational circuit that
 - takes a decimal digit in BCD (4bit int A, B, C, D); and
 - generates the appropriate control signals for the display unit (a, b, c, d, e, f, g)




1. Specification

- BCD: Each digit is represented using 4bit binary int
- BCD-to-7-segment decoder
A Combinational circuit that

Input • takes a decimal digit in BCD (4bit int A, B, C, D); and


Output • generates the appropriate control signals for the display unit (a, b, c, d, e, f, g)

Output

 

2. Formulation


Decimal	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	
1											
2											
3											
4											
5											
6											
7											
8											
9											

 

Example

2. Formulation


Decimal	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	
1	0	0	0	1		1	1				
2											
3											
4											
5											
6											
7											
8											
9											

 

Example

2. Formulation


Decimal	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	
1	0	0	0	1		1	1				
2	0	0	1	0	1	1		1	1		1
3											
4											
5											
6											
7											
8											
9											

 

Example

2. Formulation


Decimal	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	
1	0	0	0	1		1	1				
2	0	0	1	0	1	1		1	1		1
3	0	0	1	1	1	1	1	1			1
4											
5											
6											
7											
8											
9											

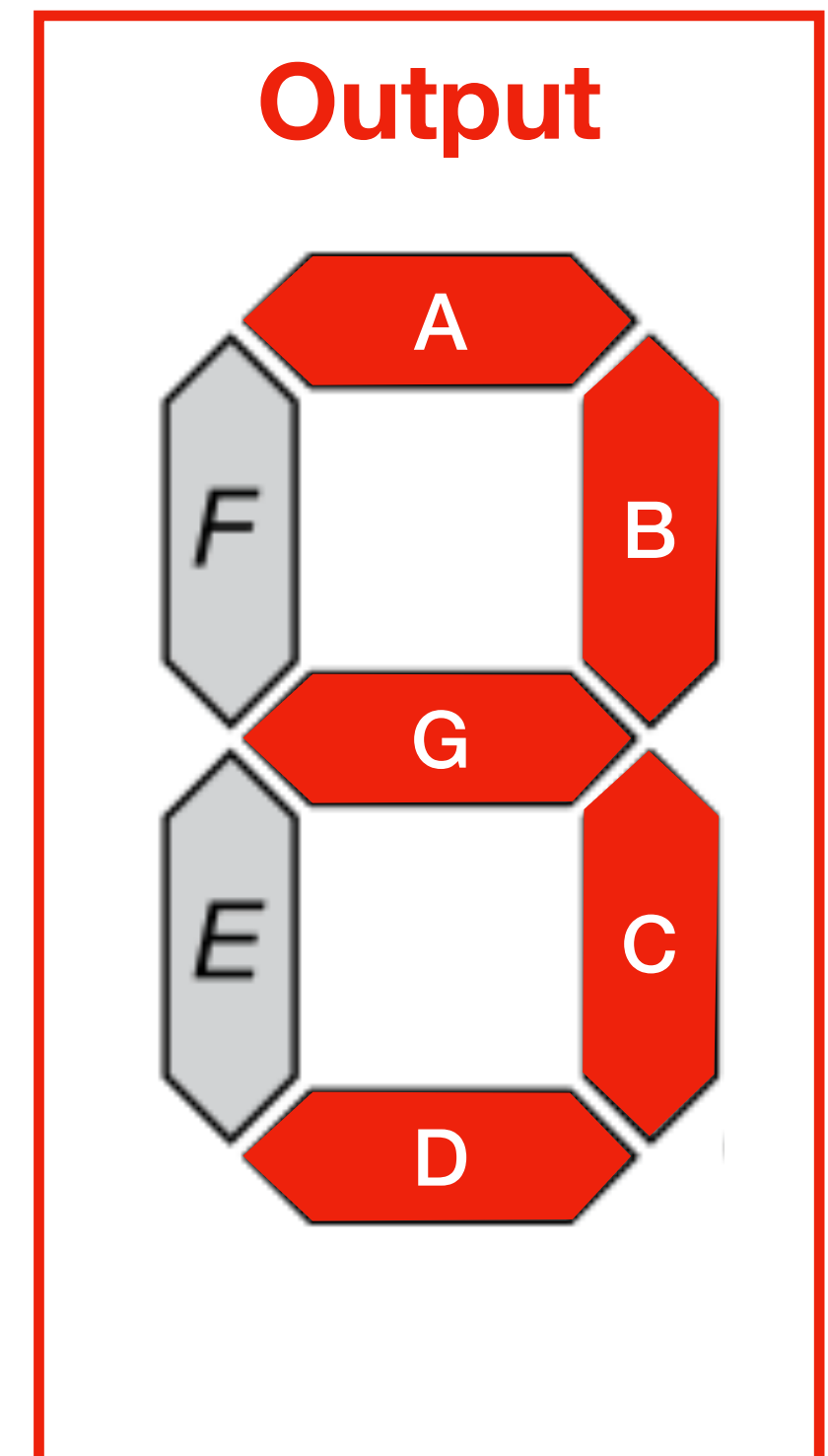

Example

2. Formulation


Decimal	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	
1	0	0	0	1		1	1				
2	0	0	1	0	1	1		1	1		1
3	0	0	1	1	1	1	1	1			1
4	0	1	0	0		1	1			1	1
5											
6											
7											
8											
9											

 

Example

2. Formulation


Decimal	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	
1	0	0	0	1		1	1				
2	0	0	1	0	1	1		1	1		1
3	0	0	1	1	1	1	1	1			1
4	0	1	0	0		1	1			1	1
5	0	1	0	1	1		1	1		1	1
6											
7											
8											
9											

 

Example

2. Formulation


Decimal	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	
1	0	0	0	1		1	1				
2	0	0	1	0	1	1		1	1		1
3	0	0	1	1	1	1	1	1			1
4	0	1	0	0		1	1			1	1
5	0	1	0	1	1		1	1		1	1
6	0	1	1	0	1		1	1	1	1	1
7											
8											
9											

 

Example

2. Formulation


Decimal	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	
1	0	0	0	1		1	1				
2	0	0	1	0	1	1		1	1		1
3	0	0	1	1	1	1	1	1			1
4	0	1	0	0		1	1			1	1
5	0	1	0	1	1		1	1		1	1
6	0	1	1	0	1		1	1	1	1	1
7	0	1	1	1	1	1	1				
8											
9											

 

Example

2. Formulation


Decimal	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	
1	0	0	0	1		1	1				
2	0	0	1	0	1	1		1	1		1
3	0	0	1	1	1	1	1	1			1
4	0	1	0	0		1	1			1	1
5	0	1	0	1	1		1	1		1	1
6	0	1	1	0	1		1	1	1	1	1
7	0	1	1	1	1	1	1				
8	1	0	0	0	1	1	1	1	1	1	1
9											

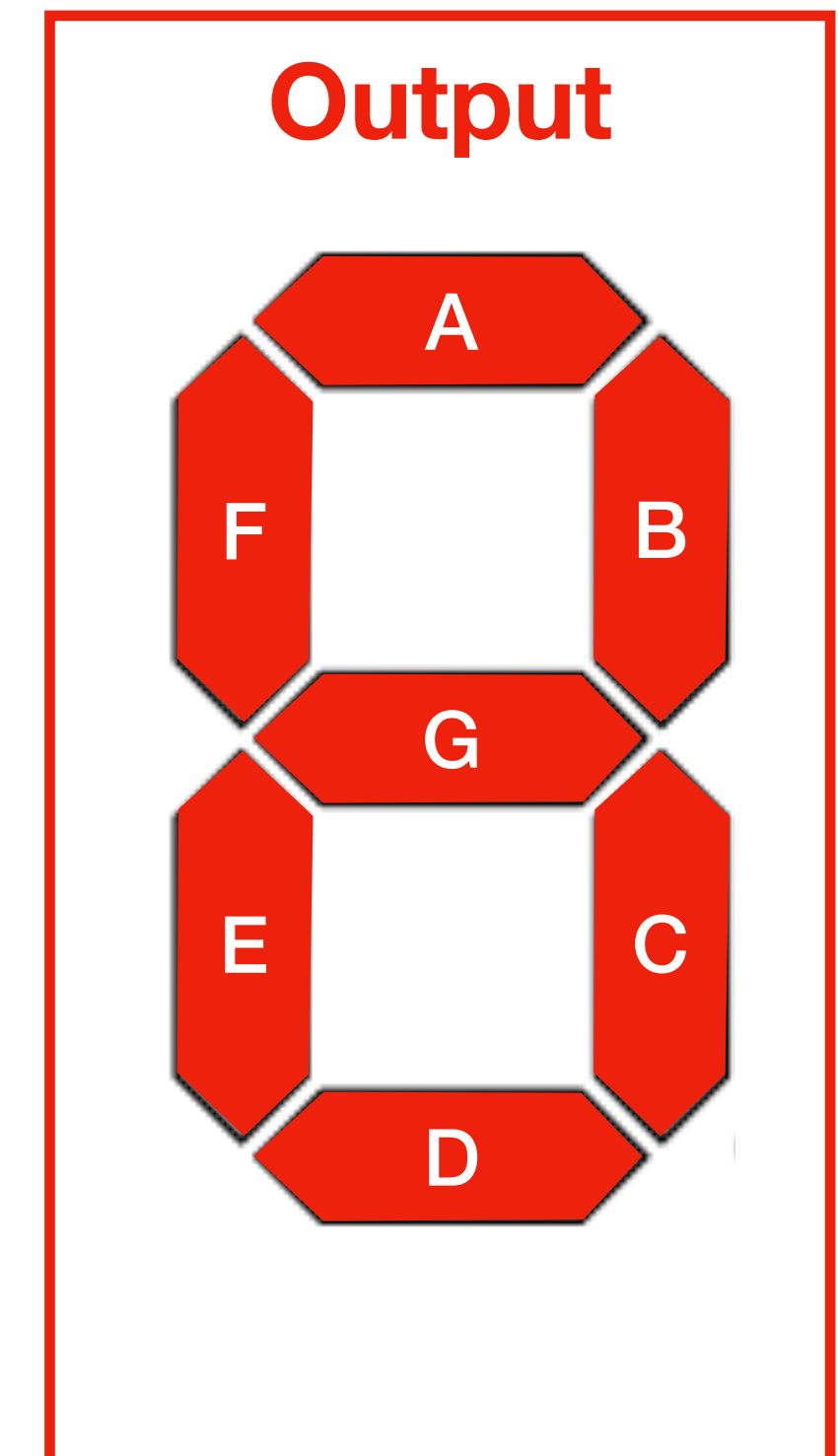

Example

2. Formulation

Decimal	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	
1	0	0	0	1		1	1				
2	0	0	1	0	1	1		1	1		1
3	0	0	1	1	1	1	1	1			1
4	0	1	0	0		1	1			1	1
5	0	1	0	1	1		1	1		1	1
6	0	1	1	0	1		1	1	1	1	1
7	0	1	1	1	1	1	1				
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1		1	1

 

Example

3. Optimisation

- Convert to Boolean expression

Decimal	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1

3. Optimisation

- Convert to Boolean expression

$$a = \bar{A}C + \bar{A}BD + \bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}$$

$$b = \bar{A}\bar{B} + \bar{A}\bar{C}\bar{D} + \bar{A}CD + A\bar{B}\bar{C}$$

$$c = \bar{A}B + \bar{A}D + \bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}$$

$$d = \bar{A}C\bar{D} + \bar{A}\bar{B}C + \bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C} + \bar{A}B\bar{C}D$$

$$e = \bar{A}C\bar{D} + \bar{B}\bar{C}\bar{D}$$

$$f = \bar{A}B\bar{C} + \bar{A}\bar{C}\bar{D} + \bar{A}B\bar{D} + A\bar{B}\bar{C}$$

$$g = \bar{A}C\bar{D} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C}$$

4. Technology Mapping

- Convert to Boolean expression
- Indie: 27 AND
7 OR gates

$$a = \bar{A}C + \bar{A}BD + \boxed{\bar{B}\bar{C}\bar{D}} + \boxed{A\bar{B}\bar{C}}$$

$$b = \bar{A}\bar{B} + \boxed{\bar{A}\bar{C}\bar{D}} + \bar{A}CD + \boxed{A\bar{B}\bar{C}}$$

$$c = \bar{A}B + \bar{A}D + \boxed{\bar{B}\bar{C}\bar{D}} + \boxed{A\bar{B}\bar{C}}$$

$$d = \boxed{\bar{A}C\bar{D}} + \boxed{\bar{A}\bar{B}C} + \boxed{\bar{B}\bar{C}\bar{D}} + \boxed{A\bar{B}\bar{C}} + \bar{A}B\bar{C}D$$

$$e = \boxed{\bar{A}C\bar{D}} + \boxed{\bar{B}\bar{C}\bar{D}}$$

$$f = \boxed{\bar{A}B\bar{C}} + \boxed{\bar{A}\bar{C}\bar{D}} + \bar{A}B\bar{D} + \boxed{A\bar{B}\bar{C}}$$

$$g = \boxed{\bar{A}C\bar{D}} + \boxed{\bar{A}\bar{B}C} + \boxed{\bar{A}B\bar{C}} + \boxed{A\bar{B}\bar{C}}$$

5. Verification (Skipped here)

- Convert to Boolean expression
- Indie: 27 AND
7 OR gates

$$a = \bar{A}C + \bar{A}BD + \boxed{\bar{B}\bar{C}\bar{D}} + \boxed{A\bar{B}\bar{C}}$$

$$b = \bar{A}\bar{B} + \boxed{\bar{A}\bar{C}\bar{D}} + \bar{A}CD + \boxed{A\bar{B}\bar{C}}$$

$$c = \bar{A}B + \bar{A}D + \boxed{\bar{B}\bar{C}\bar{D}} + \boxed{A\bar{B}\bar{C}}$$

$$d = \boxed{\bar{A}C\bar{D}} + \boxed{\bar{A}\bar{B}C} + \boxed{\bar{B}\bar{C}\bar{D}} + \boxed{A\bar{B}\bar{C}} + \bar{A}B\bar{C}D$$


$$e = \boxed{\bar{A}C\bar{D}} + \boxed{\bar{B}\bar{C}\bar{D}}$$

$$f = \boxed{\bar{A}B\bar{C}} + \boxed{\bar{A}\bar{C}\bar{D}} + \bar{A}B\bar{D} + \boxed{A\bar{B}\bar{C}}$$

$$g = \boxed{\bar{A}C\bar{D}} + \boxed{\bar{A}\bar{B}C} + \boxed{\bar{A}B\bar{C}} + \boxed{A\bar{B}\bar{C}}$$

BCD to 7 Segment Display

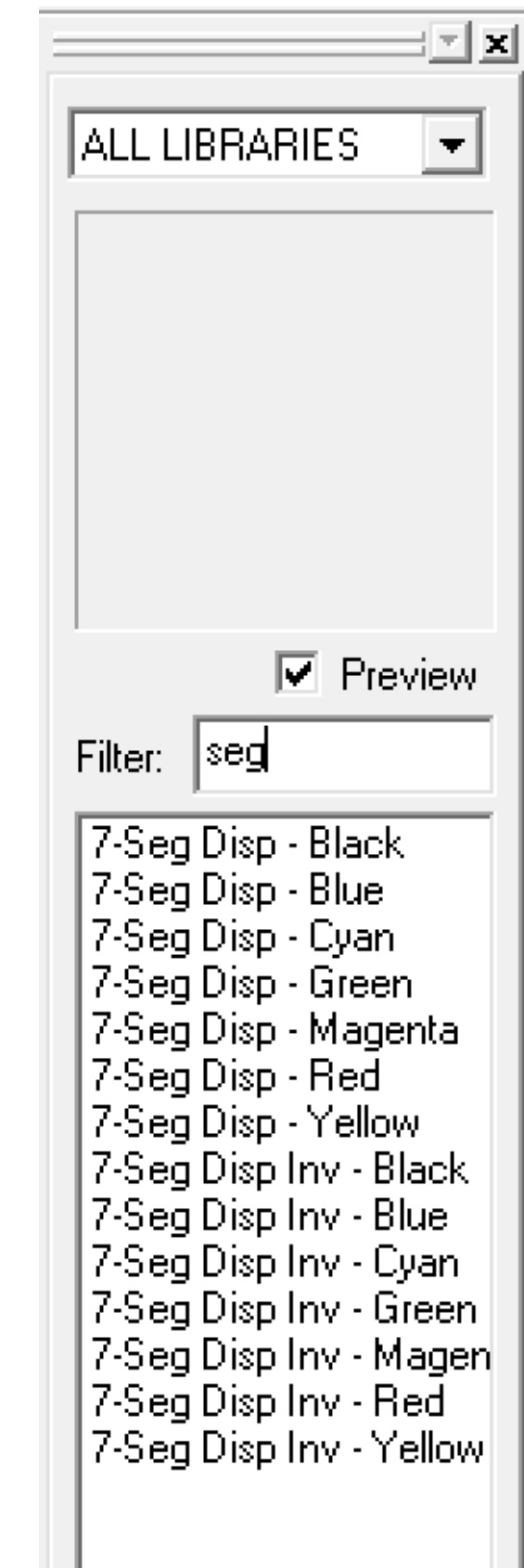- 'BCD-to-seven-segment *decoder*'
- '*decodes*' binary code for decimal digit
- usually decoders mean something different, which we'll discuss later



4-bit Equity Comparator

Ah, not again


4-bit Equity Comparator

- Compare two numbers
- Equal or not

1. Specification

- Input: $A_3A_2A_1A_0, B_3B_2B_1B_0$
- Output: $E = 1$ for equal, 0 for not

2. Formulation

 


- 2 things are happening
 - We need to compare pairs of binary values and see if they are equal
 - We need to combine the comparison of all these different bits to make up E

Hierarchical Design


- "divide-and-conquer"
- Circuit is broken up into individual functional pieces (blocks)
 - Each block has explicitly defined **Interface** (I/O) and **Behaviour**
 - A single block can be **reused** multiple times to simplify design process
 - If a single block is too complex, it can be **further divided into smaller blocks**, to allow for easier designs

3. Optimisation

 


- 2 things are happening
 - We need to compare pairs of binary values and see if they are equal MX
 - We need to combine the comparison of all these different bits to make up E ME



3. Optimisation

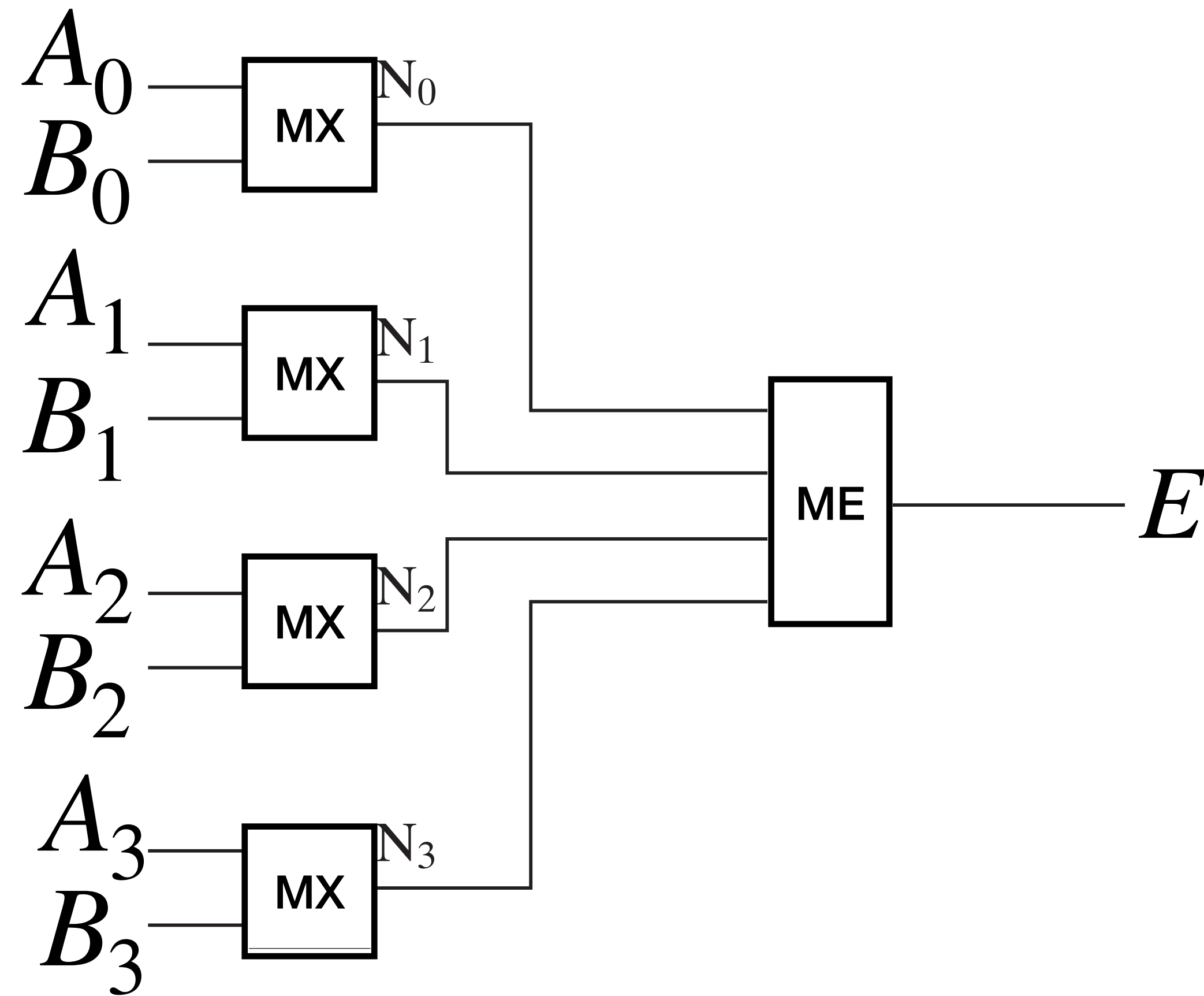

3. Optimisation

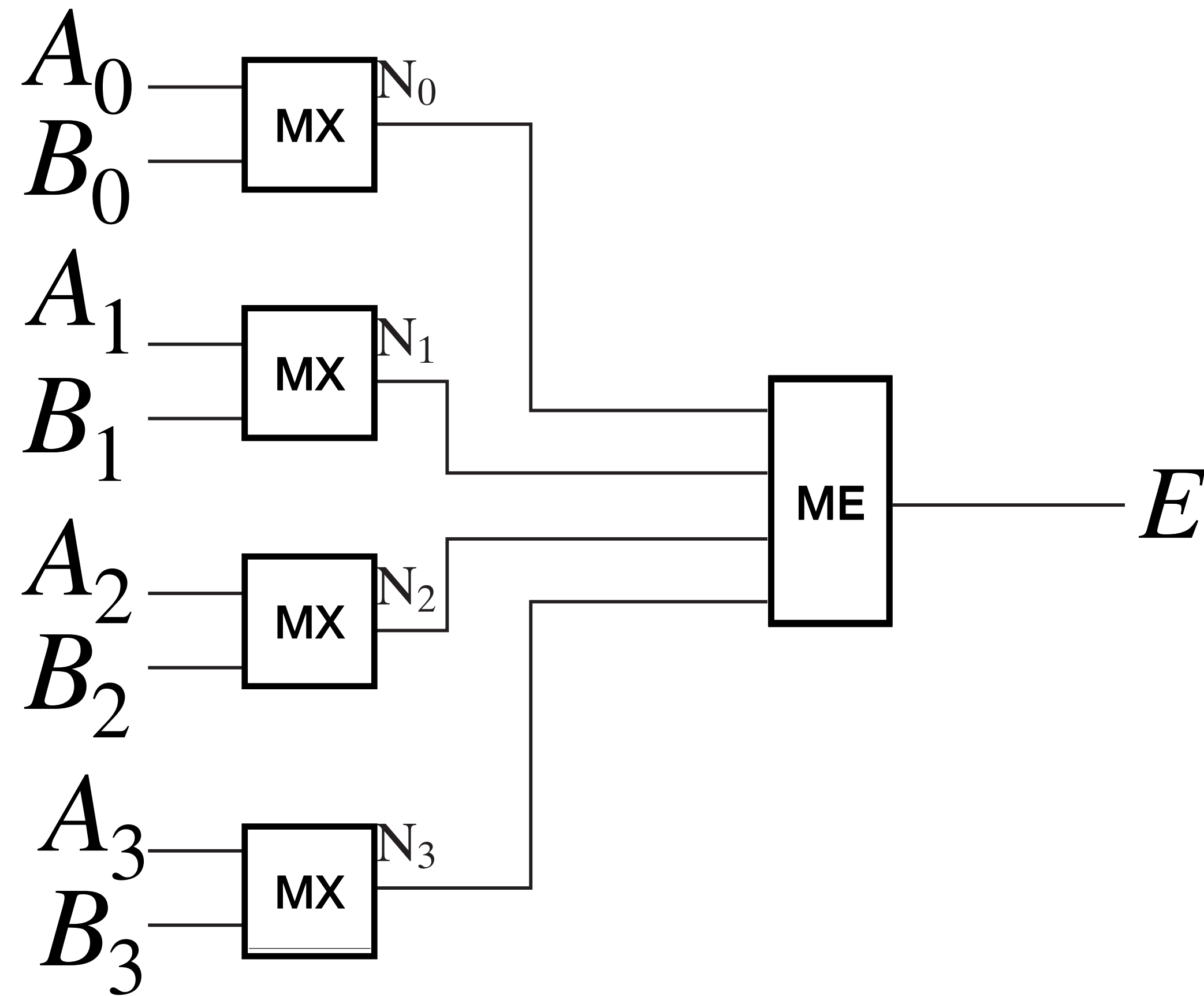




3. Optimisation

 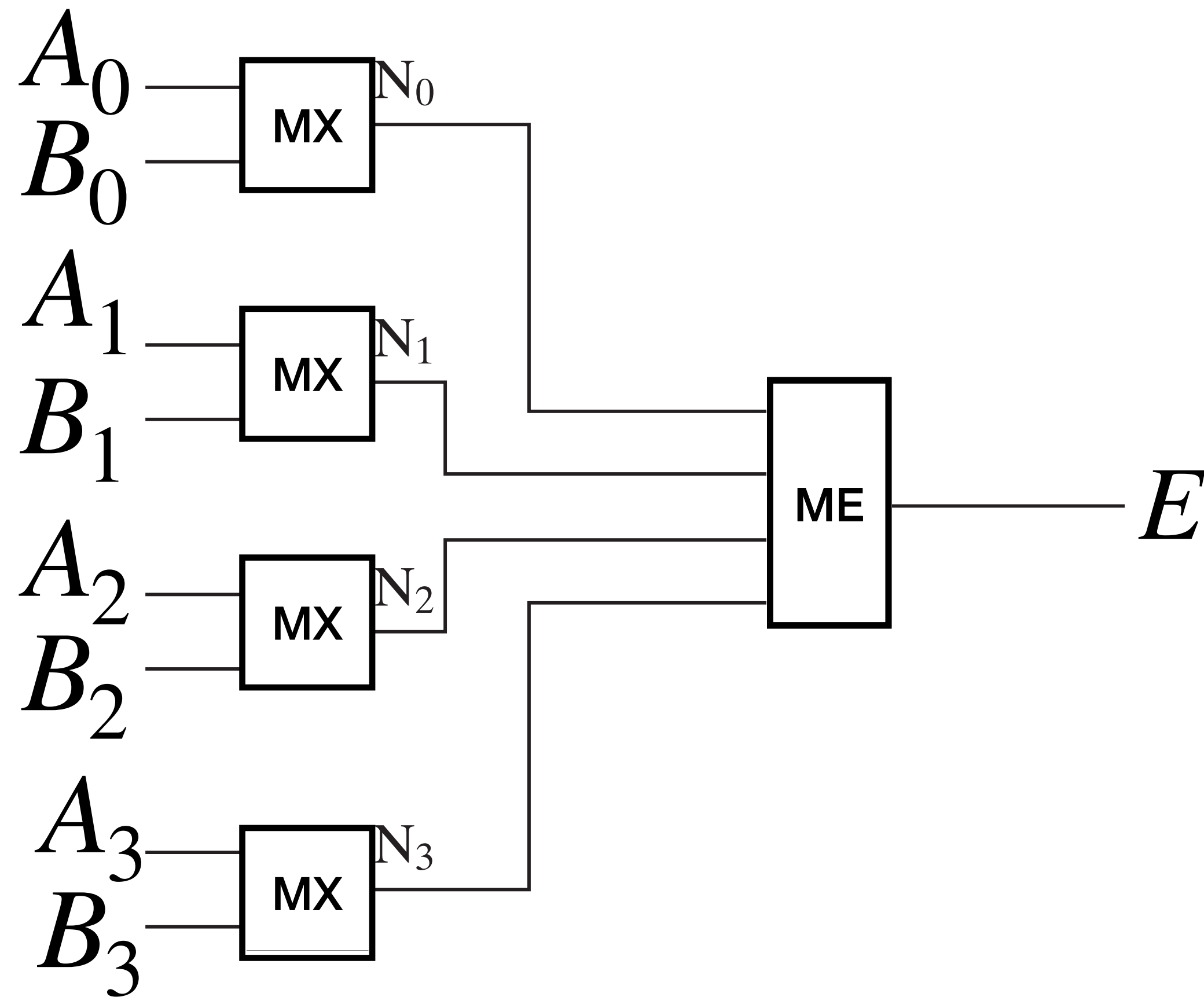

$$MX(A_i, B_i) = N_i = 0 \text{ if } A_i = B_i$$

$$MX(A_i, B_i) = N_i = \bar{A}_i B_i + A_i \bar{B}_i$$

3. Optimisation

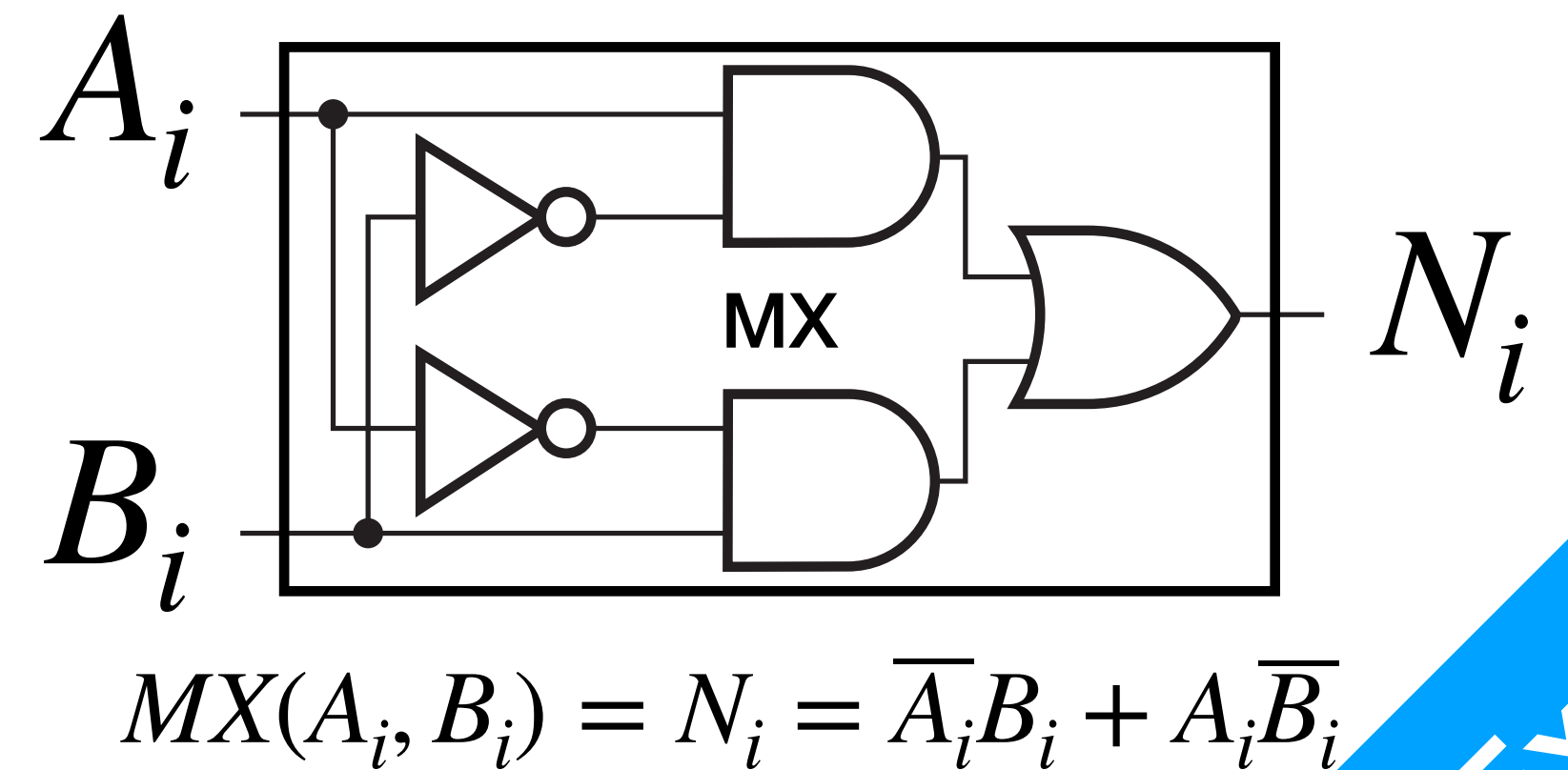 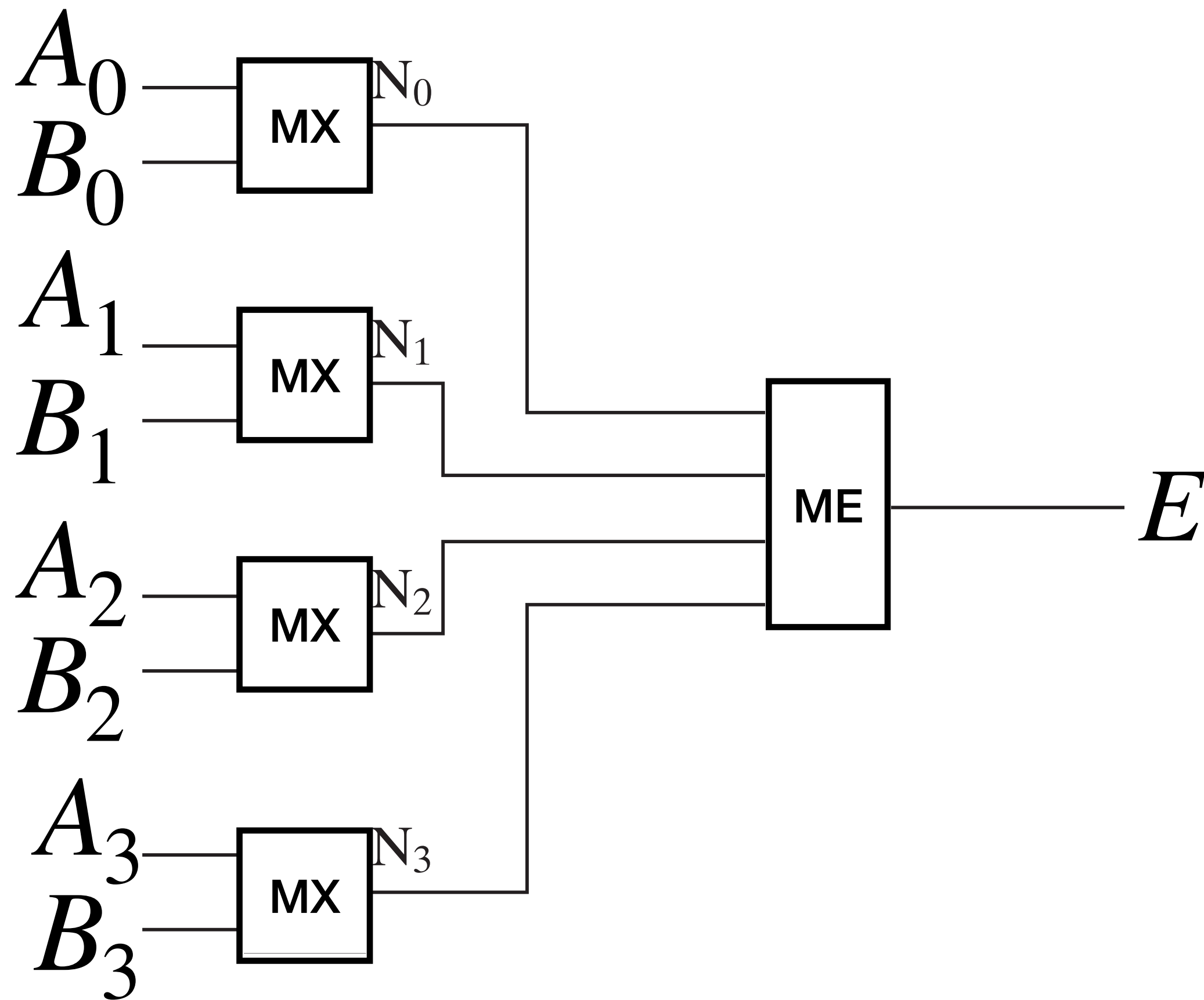

Technology Mapping


Mostly Old Tech, no new iPhones

Technology Mapping


- Technology
 - Available physical components
 - Programmable implementation technology e.g. Field-Programmable Gate Array (FPGA)
 - VHDL; Verilog Language

Technology Mapping

 - $\text{NAND} == \text{AND} + \text{Inverter};$
- $\text{AND} == \text{NAND} + \text{Inverter};$
- $\text{NOR} == \text{OR} + \text{Inverter};$
- $\text{OR} == \text{NOR} + \text{Inverter};$
- DeMorgan's Rule




(a) Mapping to NAND gates

 

 (b) Mapping to NOR gates

Technology Mapping


- Implement the circuit diagram with NAND gates and Inverters only



Technology Mapping


- Implement the circuit diagram with NAND gates and Inverters only

1. Replacement

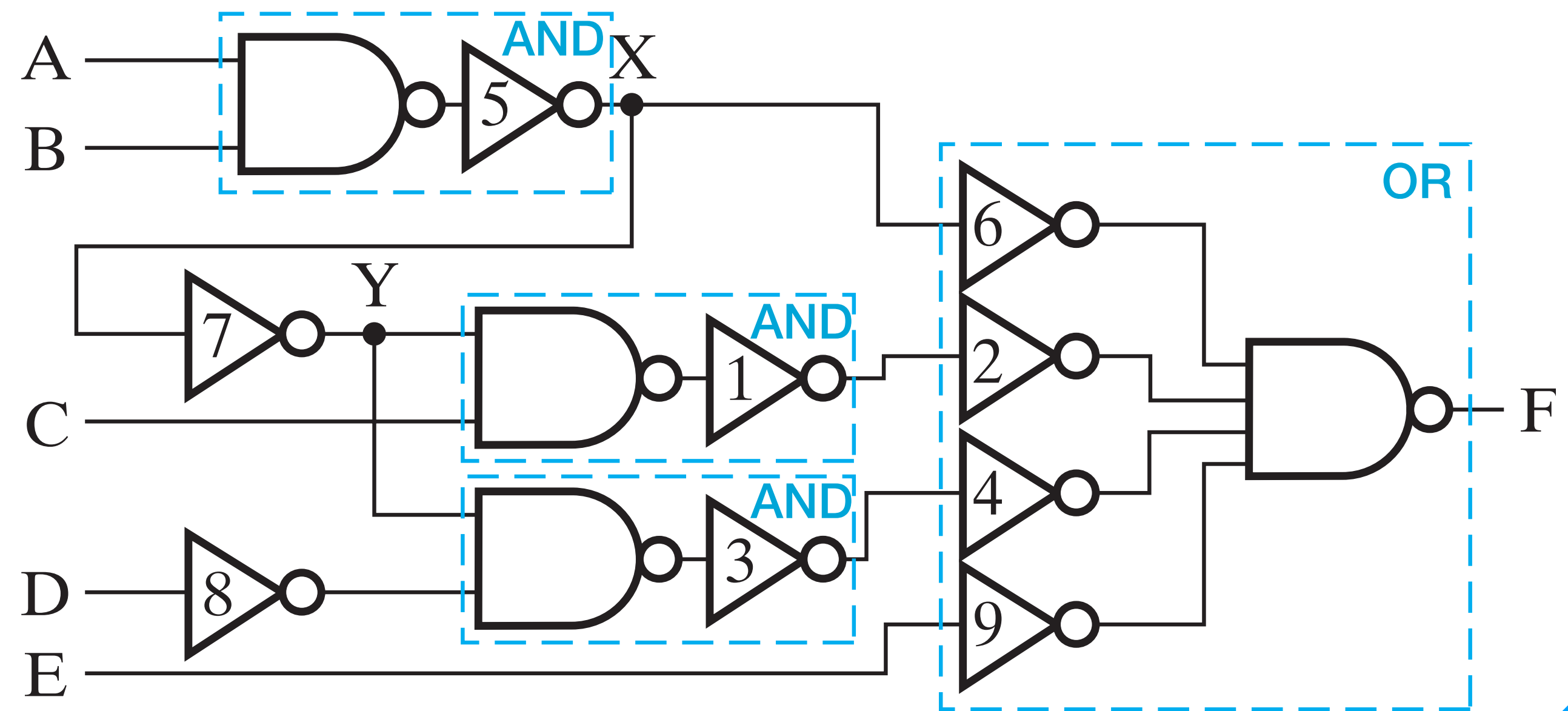

Technology Mapping

 - Implement the circuit diagram with NAND gates and Inverters only
 1. Replacement
 2. Simplification



Verification

Manual vs Auto

Verification

- Manual
 - Use the truth table, row by row
- Auto
 - Use computer simulation to go through the truth table