



22.06.20 14:51

CSCI 150

Introduction to Digital and Computer System Design

Lecture 3: Combinational Logic Design VII



Jetic Gū
2020 Summer Semester (S2)

Overview


- Focus: Arithmetic Functional Blocks
- Architecture: Combinatory Logical Circuits
- Textbook v4: Ch4 4.3, 4.4, 4.7; v5: Ch2 2.9, Ch3 3.10, 3.11
- Core Ideas:
 1. Subtraction II
 2. Subtraction III
 3. VHDL

Unsigned Binary Subtraction I

Review

Unsigned 1-bit Binary Subtraction

 
- Implementation using 3-to-8 Decoder
 - $B = \Sigma m(1,2,3,7)$
 - $D = \Sigma m(1,2,4,7)$



Unsigned Binary Subtraction

Technology

- 1 bit Unsigned Subtractor

 

	<i>B</i>		<i>Z</i>
Borrows	0	0	0
Minuend $X_{0:n-1}$	1	0	1
Subtrahend $Y_{0:n-1}$	-	1	0
Difference $D_{0:n-1}$	0	0	1

Input
Output

Unsigned Binary Subtraction II

$X - Y$ when $Y > X$

What we have so far

- Binary Adder
- Binary Subtractor ($X - Y, X \geq Y$)

Unsigned Binary Subtraction

$$X > Y, F = X - Y$$

- We learned to perform subtraction, by subtracting the smaller number from the greater number
- What if it's the opposite? i.e. $X < Y, F = X - Y$?

Unsigned Binary Subtraction

Borrows	
Minuend	10011
Subtrahend	— 00110
Difference	

Borrows	
Minuend	00110
Subtrahend	— 10011
Difference	

Unsigned Binary Subtraction

Borrows	011000
Minuend	10011
Subtrahend	—00110
	—————
Difference	01101

This is correct

Borrows	100110
Minuend	00110
Subtrahend	—10011
	—————
Difference	10011

This is incorrect

Unsigned Binary Subtraction

- Standard subtraction module works if the Minuend is bigger than the Subtrahend

Borrows	011000
Minuend	10011
Subtrahend	-00110
	01101
Difference	

This is correct

Borrows	100110
Minuend	00110
Subtrahend	-10011
	10011
Difference	

This is incorrect

Unsigned Binary Subtraction

- Standard subtraction module works if the Minuend is bigger than the Subtrahend

- Incorrect output D
 $= 2^n + X - Y$

- Correct output D'
 $= -(Y - X)$
 $= -(2^n - D)$
 $= -(\bar{D} + 1)$ (2's compliment)

Borrows	100110
Minuend X	00110
Subtrahend Y	- 10011
Difference D	10011
Corrected D'	- 01101

This is incorrect

2s compliment

- Given binary unsigned integer of n bits D , its 2s compliment $2^n - D = \bar{D} + 1$
- Proof
 - Biggest number represented in n bit: $(11\dots1)_2 = 2^n - 1$
 - $2^n - D = [(11\dots1)_2 + 1] - D = (11\dots1)_2 - D + 1 = \bar{D} + 1$
- Implementation
 - Inversion and plus 1, easily doable as complementer

Subtraction

1. Compute $20-15=5$ using 6-bit binary
 - $20 = (010100)_2$, $15 = (001111)_2$
2. Compute $15-20=-5$ using 6-bit binary and 2s complement

Borrows	0	0	1	1	1	1	0
	0	1	0	1	0	0	
	-	0	0	1	1	1	1
<hr/>							
	0	0	0	1	0	1	

Subtraction

1. Compute $20-15=5$ using 6-bit binary
 - $20 = (010100)_2$, $15 = (001111)_2$
2. Compute $15-20=-5$ using 6-bit binary and 2s complement
 - Correction: $(111011)_2$ 2s complement: $(000101)_2$

Borrows

$$\begin{array}{r} 1\ 100000 \\ 001111 \\ -010100 \\ \hline 111011 \\ 000101 \end{array}$$

Example

Subtraction

1. Compute $20-15=5$ using 6-bit binary
 - $20 = (010100)_2$, $15 = (001111)_2$
2. Compute $15-20=-5$ using 6-bit binary and 2s complement
 -

Borrows

$$\begin{array}{r} 1\ 100000 \\ 001111 \\ -010100 \\ \hline 111011 \end{array}$$


Subtraction

1. Compute $7-15=-8$ using 6-bit binary and 2s complement


Full Unsigned Subtraction

- Solution 1
 - Compare the Minuend and Subtrahend, switch places if the Subtrahend is greater, then add negative sign
- Solution 2
 - Use 2s compliment


Full Unsigned Subtraction

 

Full Unsigned Subtraction

 

Adder-Subtractor

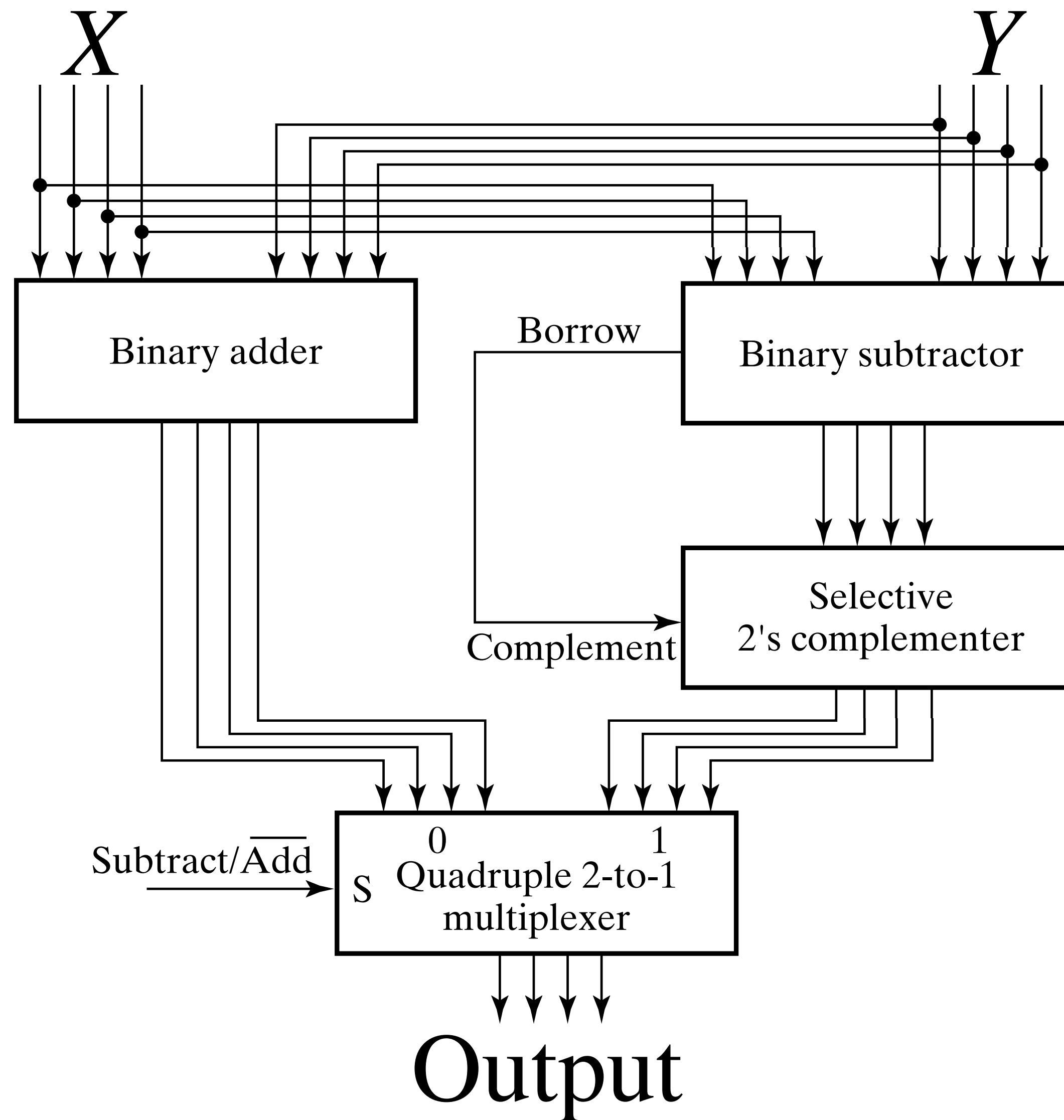

Unsigned Binary Subtraction III

What do you mean we can do subtraction using an adder?

2s compliment

$$2^n - D = \bar{D} + 1$$

Subtraction using 2s Complement

- Input: X and Y
- Y : 2s complement $Y' = \bar{Y} + 1$ ($\bar{Y} + 1 = 2^n - Y$)
- $X - Y = X + (2^n - Y) - 2^n = X + Y' - 2^n$
- Since $2^n = (10\dots0)_2$, and we only output n -bits, it can be discarded

Subtraction using 2s Complement

- 84 - 67 (10bit)

$$X = 0001010100$$

$$Y = 0001000011$$

2s complement

$$Y' = 1110111101$$

$$X + Y' = 10000010001$$

discard carry

$$X + Y' - 2^{10} = 0000010001$$


correct!

verify


$$(84 - 67)_{10} = 17_{10} = 10001 = 0000010001$$

Adder-Subtractor Unit

 1. Adder
 2. Complementer (Inverting and add 1)
 - Or just inverting, and then plus one
- Addition: $X + Y$
 - Subtraction: $X - Y = X + \bar{Y} + 1 - 2^n$
 - We are using n -bit adder, 2^n can be disregarded
 - The plus 1 here can be Z input to the adder



Adder-Subtractor Unit

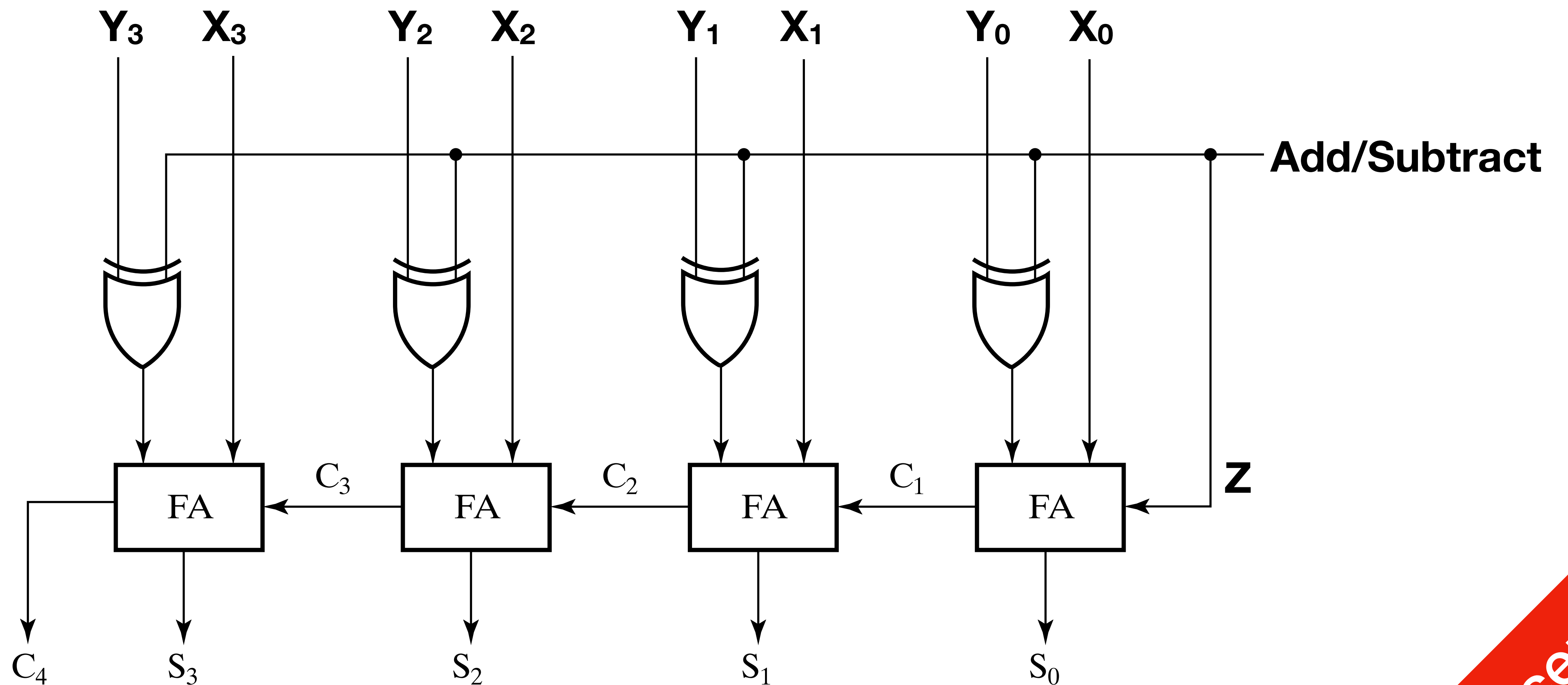

Adder Subtractor Units (Unsigned)

- Binary Adder
- Binary Subtractor
- Binary Adder-Subtractor Unit, using Adder, Subtractor, Complementer and Multiplexer
- Binary Adder-Subtractor Unit using Adder and XOR

Excercises

2s Complement
Subtraction using 2s Complement

Subtraction

- Compute $10-7$ using 4-bit binary using Adder and 2s complement

Subtraction


- Compute $24-17$ using 8-bit binary using Adder and 2s complement

Hardware Description Language

VHDL (VHSIC-HDL): Very High Speed Integrated
Circuit Hardware Description Language

Previous: 1-bit Half Adder

 - Create a new component in VHDL called `HalfAdder1`
- Input: X, Y
- Output: S, C
- Don't use `AFTER`



Previous: 1-bit Half Adder


architecture arch1 of HalfAdder is

begin

```
S <= X XOR Y;
```

```
C <= X AND Y;
```

end arch1;

 

Today's Tasks

- 1-bit Half Adder
- 1-bit Full Adder using Schema Diagram (Logic Circuit Diagram)
- 4-bit Full Adder using Schema Diagram (Logic Circuit Diagram)
- 4-bit Adder-Subtractor using Schema Diagram (Logic Circuit Diagram)