



02.07.20 11:22

CSCI 150

Introduction to Digital and Computer System Design

Midterm Review II



Jetic Gū
2020 Summer Semester (S2)

Overview

- Focus: Review
- Architecture: Combinational Logic Circuit
- Textbook v4: Ch1-4; v5: Ch1-3
- Core Ideas:
 1. Digital Information Representation (Lecture 1)
 2. Combinational Logic Circuits (Lecture 2)
 3. Combinational Functional Blocks, Arithmetic Blocks (Lecture 3)

Lecture 3: Combinational Logic Design

5 Steps Systematic Design Procedures; Functional
Blocks; Decoder, Enabler, Multiplexer; Arithmetic Blocks

Systematic Design Procedures

1. **Specification:** Write a specification for the circuit
2. **Formulation:** Derive relationship between inputs and outputs of the system
e.g. using truth table or Boolean expressions
3. **Optimisation:** Apply optimisation, minimise the number of logic gates and literals required
4. **Technology Mapping:** Transform design to new diagram using available implementation technology
5. **Verification:** Verify the correctness of the final design in meeting the specifications

Hierarchical Design

- "divide-and-conquer"
- Circuit is broken up into individual functional pieces (blocks)
 - Each block has explicitly defined **Interface** (I/O) and **Behaviour**
 - A single block can be **reused** multiple times to simplify design process
 - If a single block is too complex, it can be **further divided into smaller blocks**, to allow for easier designs

Value-Fixing, Transferring, and Inverting


- ① **Value-Fixing:** giving a constant value to a wire
 - $F = 0; F = 1;$
- ② **Transferring:** giving a variable (wire) value from another variable (wire)
 - $F = X;$
- ③ **Inverting:** inverting the value of a variable
 - $F = \bar{X}$

Vector Denotation


④ Multiple-bit Function

- Functions we've seen so far has only one-bit output: 0/1
- Certain functions may have n -bit output
- $F(n - 1 : 0) = (F_{n-1}, F_{n-2}, \dots, F_0)$, each F_i is a one-bit function
- Curtain Motor Control Circuit: $F = (F_{\text{Motor}_1}, F_{\text{Motor}_2}, F_{\text{Light}})$

Taking part of the Vector

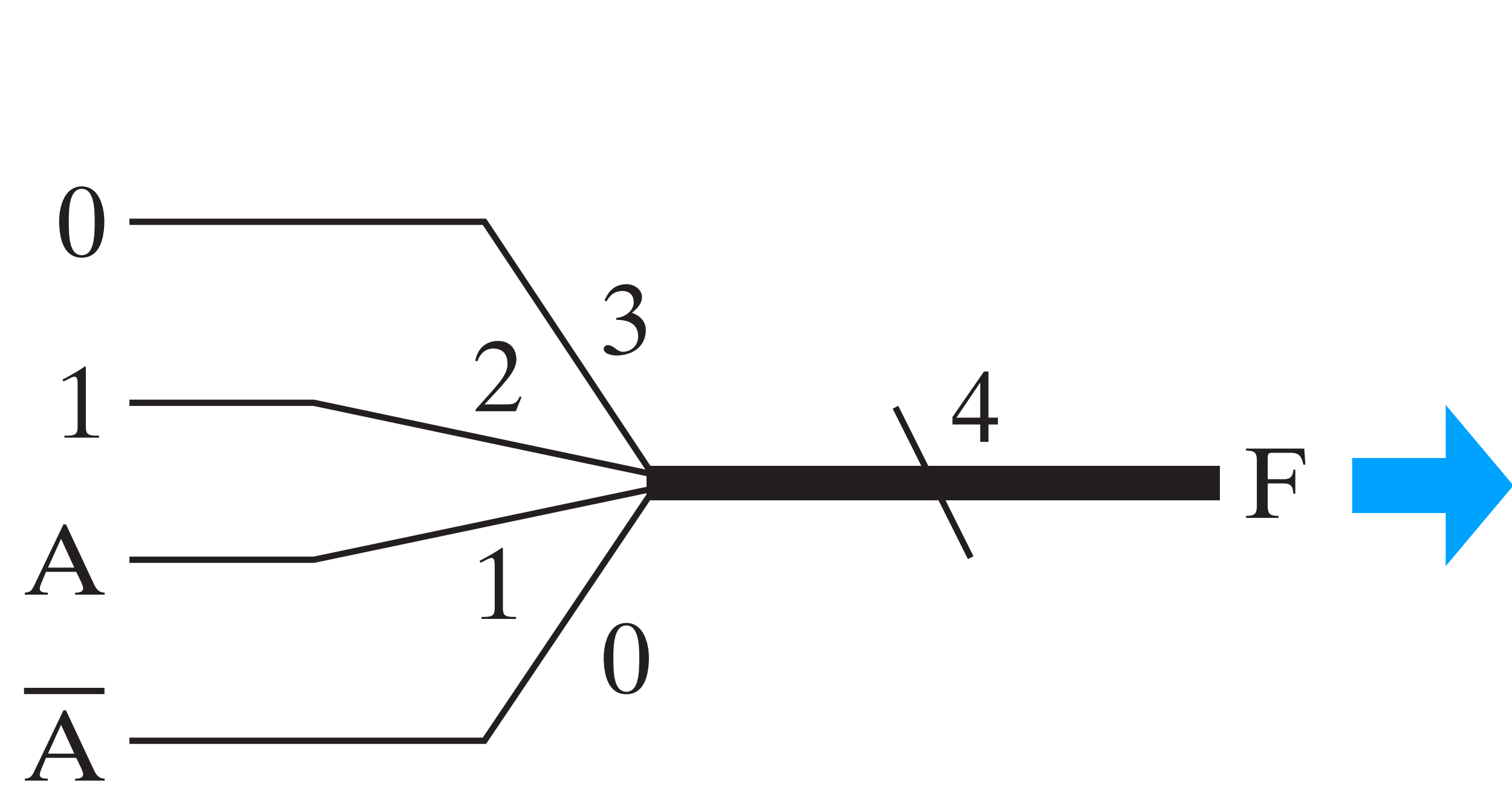

④ Multiple-bit Function

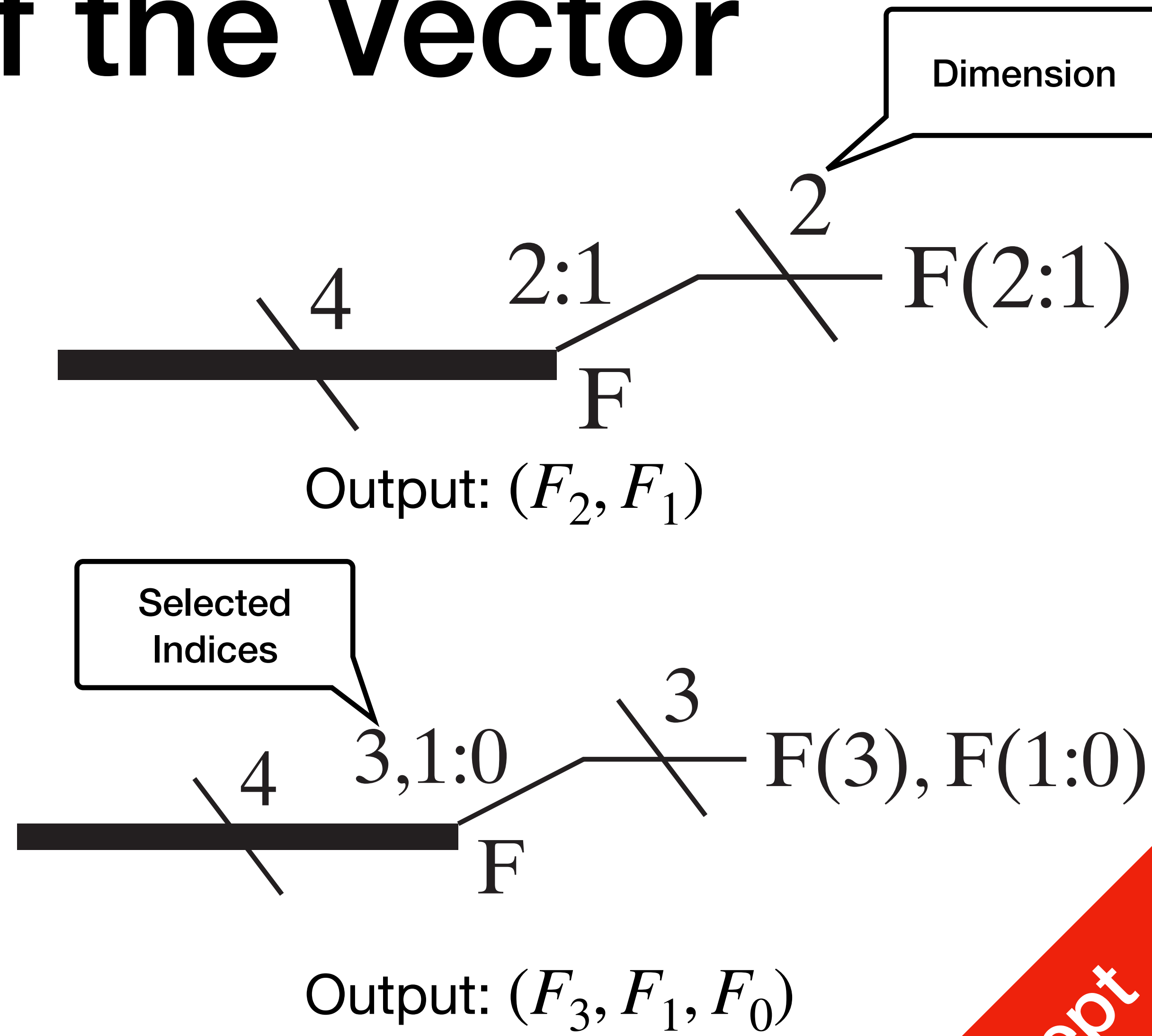

Concept

Enabler

⑤ Enabler



- Transferring function, but with an additional *EN* signal acting as switch

EN	X	F
0	X	0
1	0	0
1	1	1

Enabler

⑤ Enabler

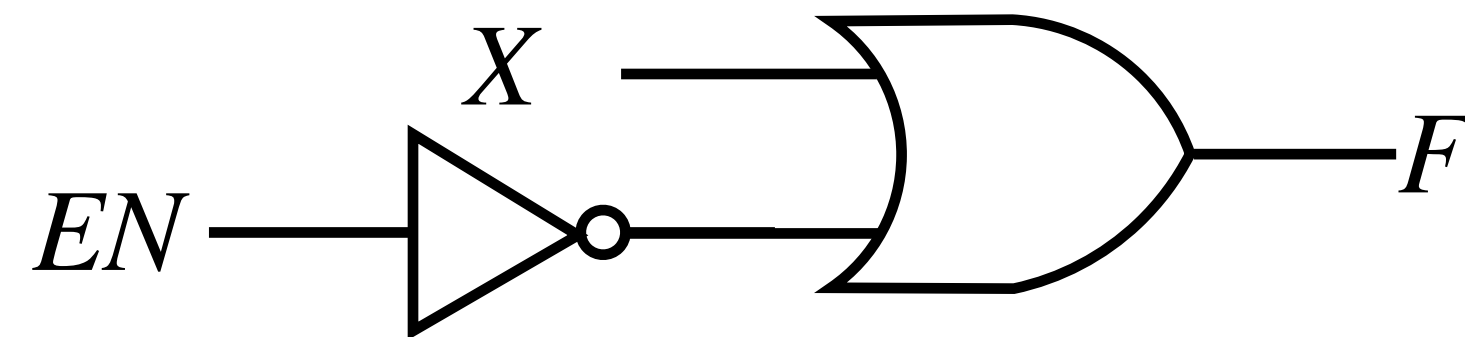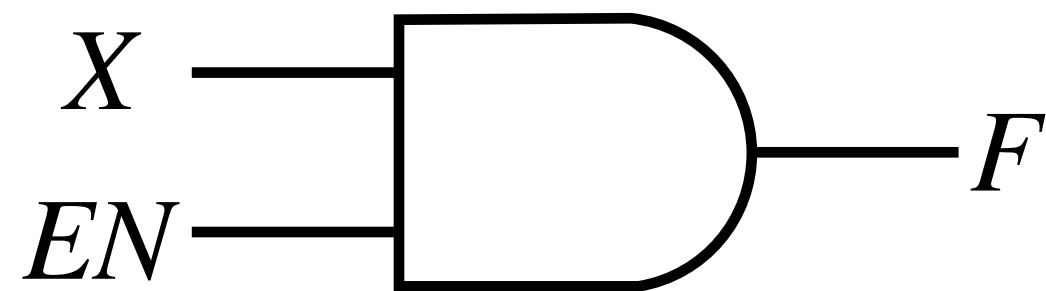- Transferring function, but with an additional EN signal acting as switch




Decoder

- n -bit input, 2^n bits output
- $D_i = m_i$

- Design: use hierarchical designs!


A_1	A_0	D_0	D_1	D_2	D_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

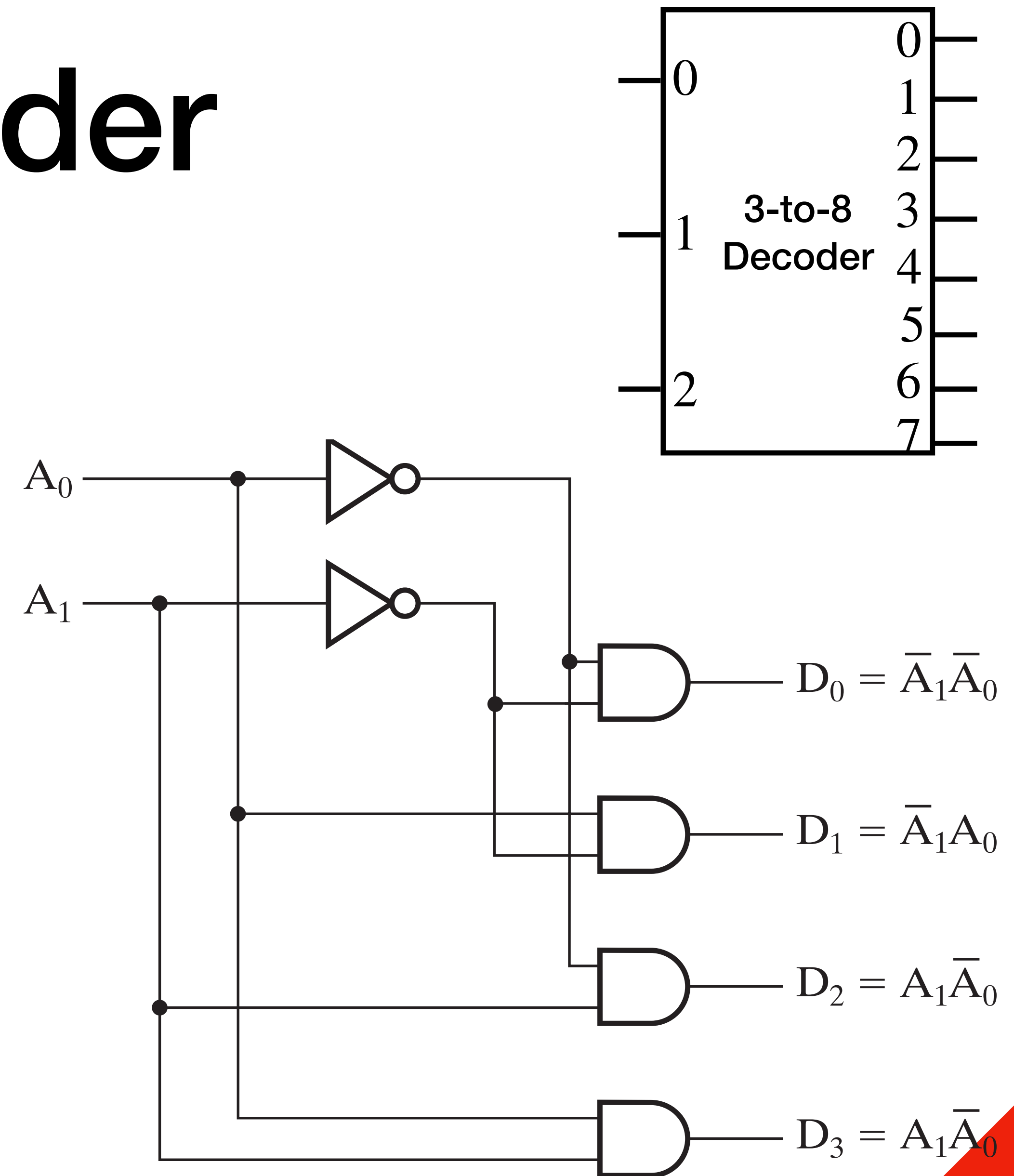

Concept

Encoder

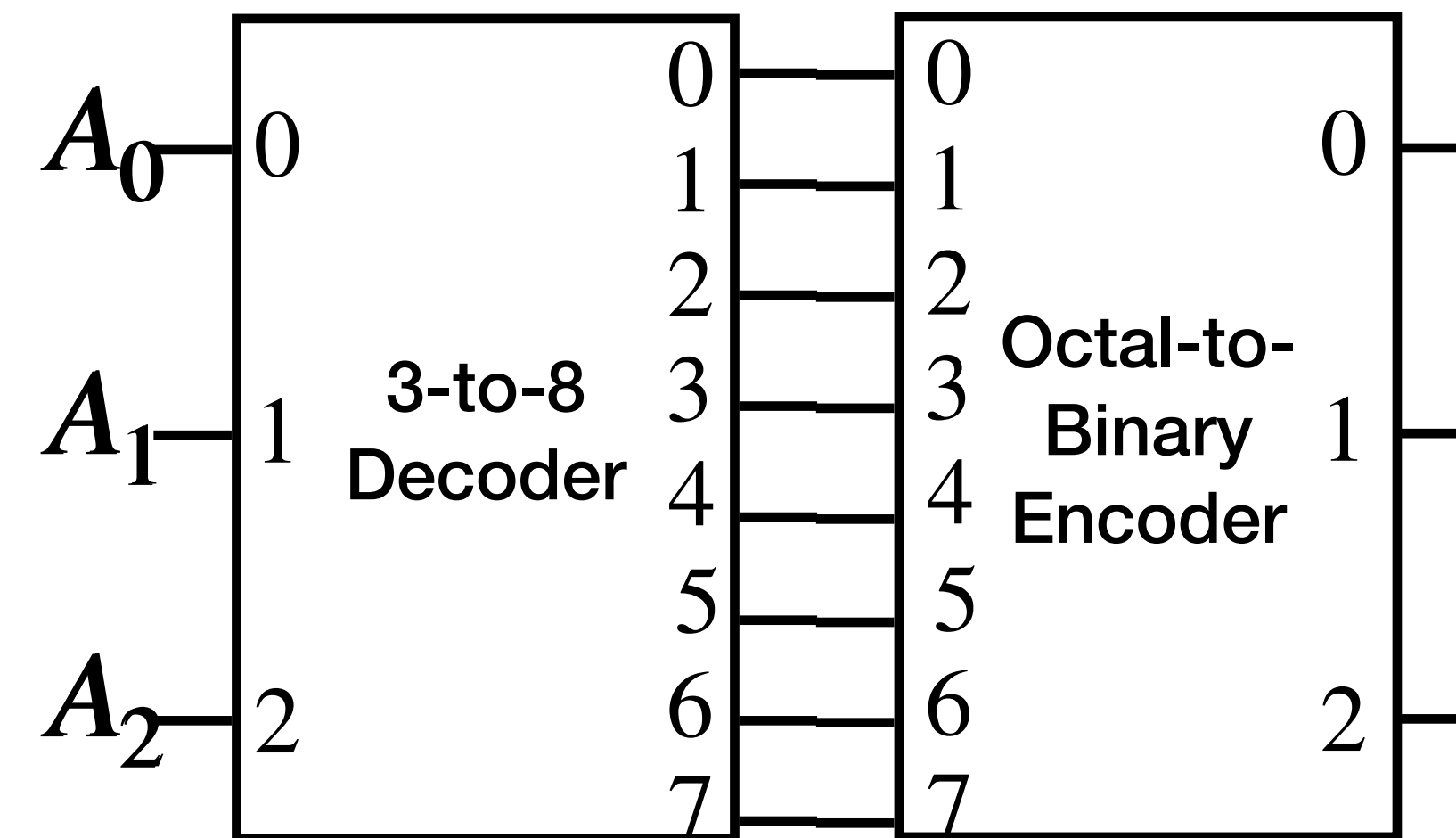- Inverse operation of a decoder
- 2^n inputs, only one is giving positive input¹
- n outputs



1. In reality, could be less


Encoder

D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
							1	0	0	0
						1		0	0	1
					1			0	1	0
				1				0	1	1
			1					1	0	0
		1						1	0	1
	1							1	1	0
1								1	1	1

$A_0 = D_1 + D_3 + D_5 + D_7$

$A_1 = D_2 + D_3 + D_6 + D_7$


$A_2 = D_4 + D_5 + D_6 + D_7$

 

Concept

Priority Encoder

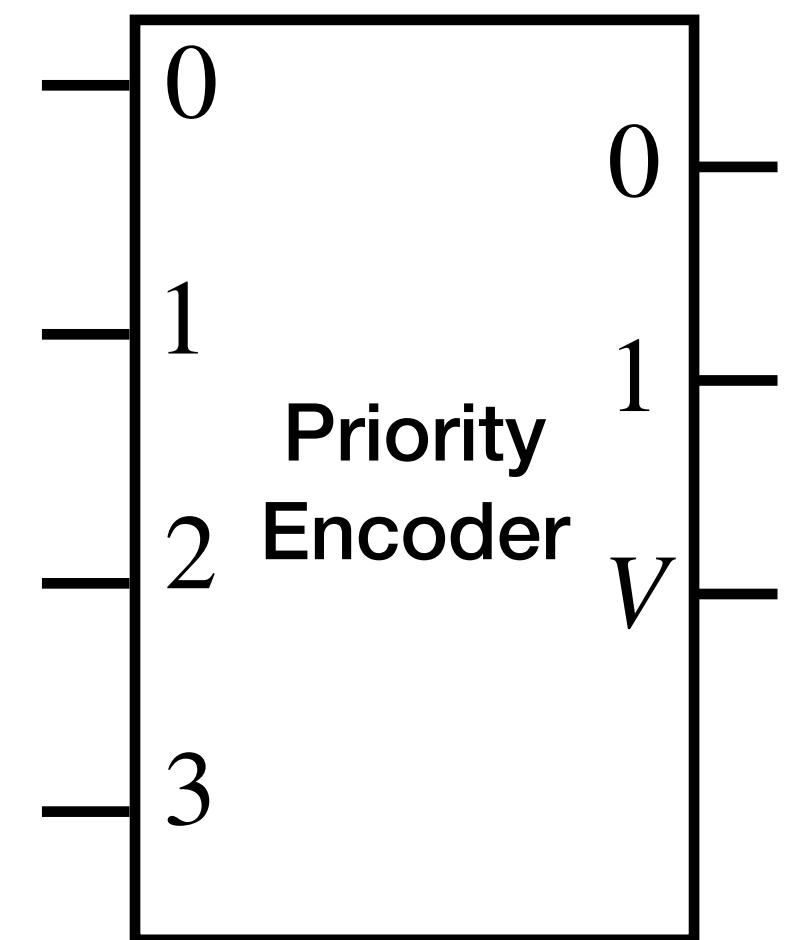
- Additional Validity Output V
 - Indicating whether the input is valid (contains 1)
- Priority
 - Ignores $D_{<i}$ if $D_i = 1$



Priority Encoder

D ₃	D ₂	D ₁	D ₀	A ₁	A ₀	V
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

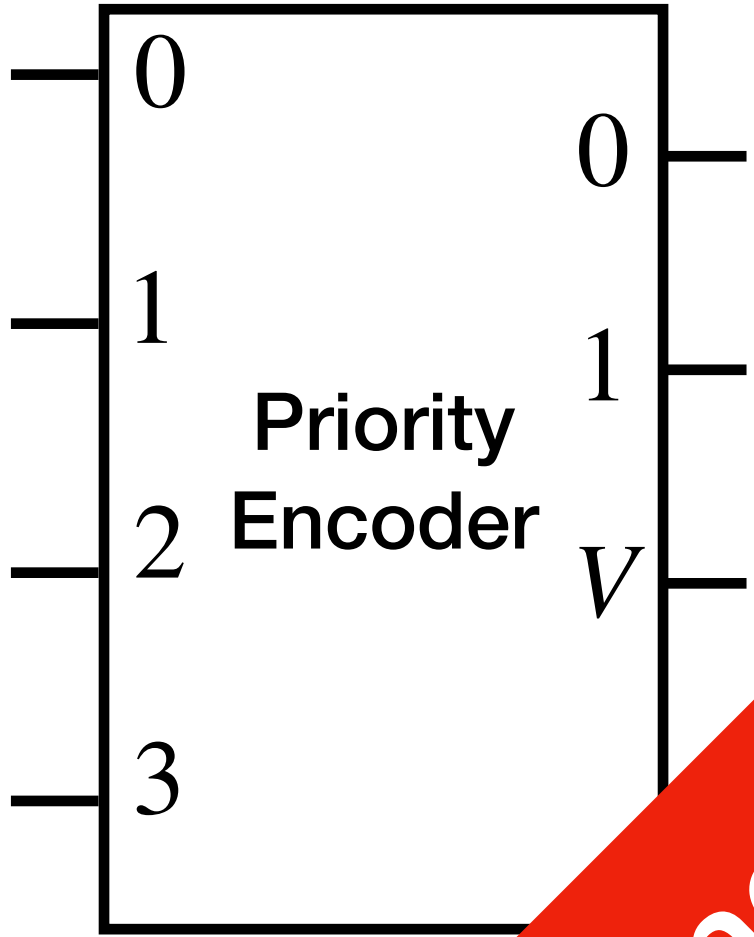
$$V = D_3 + D_2 + D_1 + D_0$$
$$A_1 = D_3 + \overline{D_3}D_2 = D_2 + D_3$$
$$A_0 = \overline{D_3}\overline{D_2}D_1 + D_3$$
$$= \overline{D_2}D_1 + D_3$$



Concept

Multiplexer

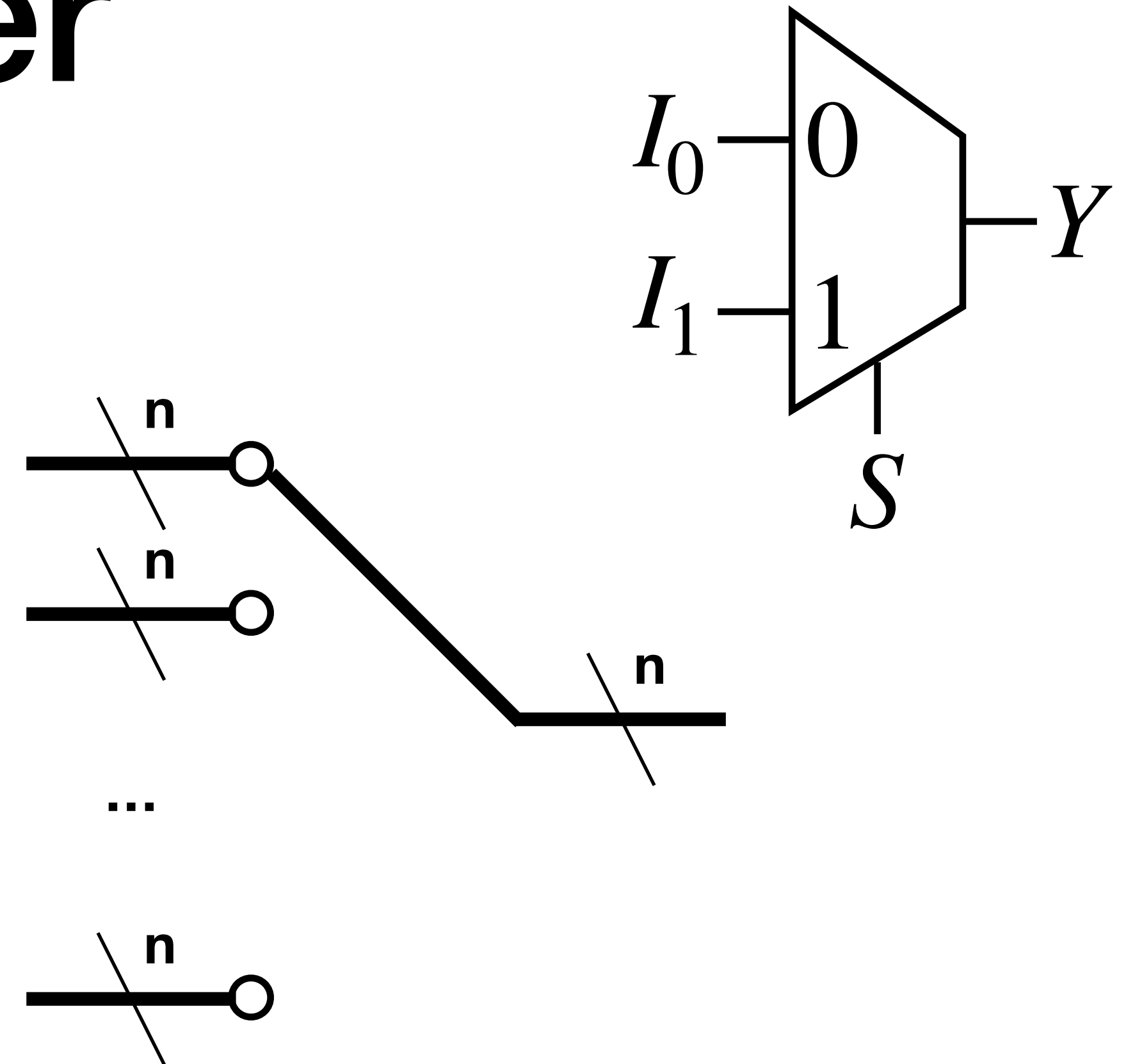- Multiple n -variable input vectors
- Single n -variable output vector
- Switches: which input vectors to output




Common Techniques

- Implementing Multiplexer using Decoders
- Implementing Multiplexer using smaller Multiplexers
- Implementing Sum-of-Minterm using Decoder
(use OR gate)
- Implementing Sum-of-Minterm using Multiplexer
(use value fixing)


Arithmetic Blocks

- 1-bit Half Adder and Full Adder
- n-bit Adder
- 1-bit subtractor and n-bit subtractor
- 2s complement and binary adder-subtractor

1-bit Adder

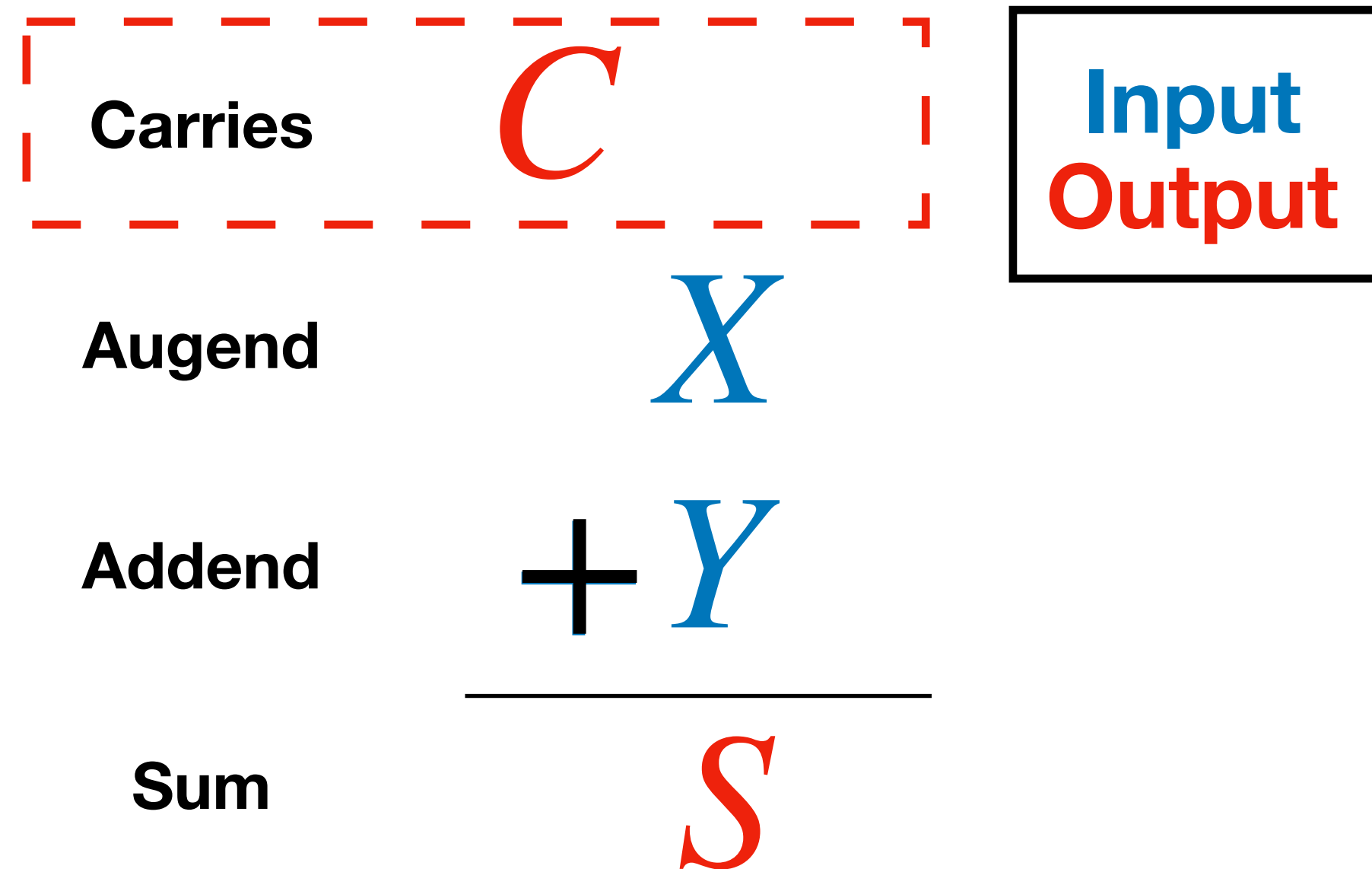

- Half adder
input X, Y
output S, C

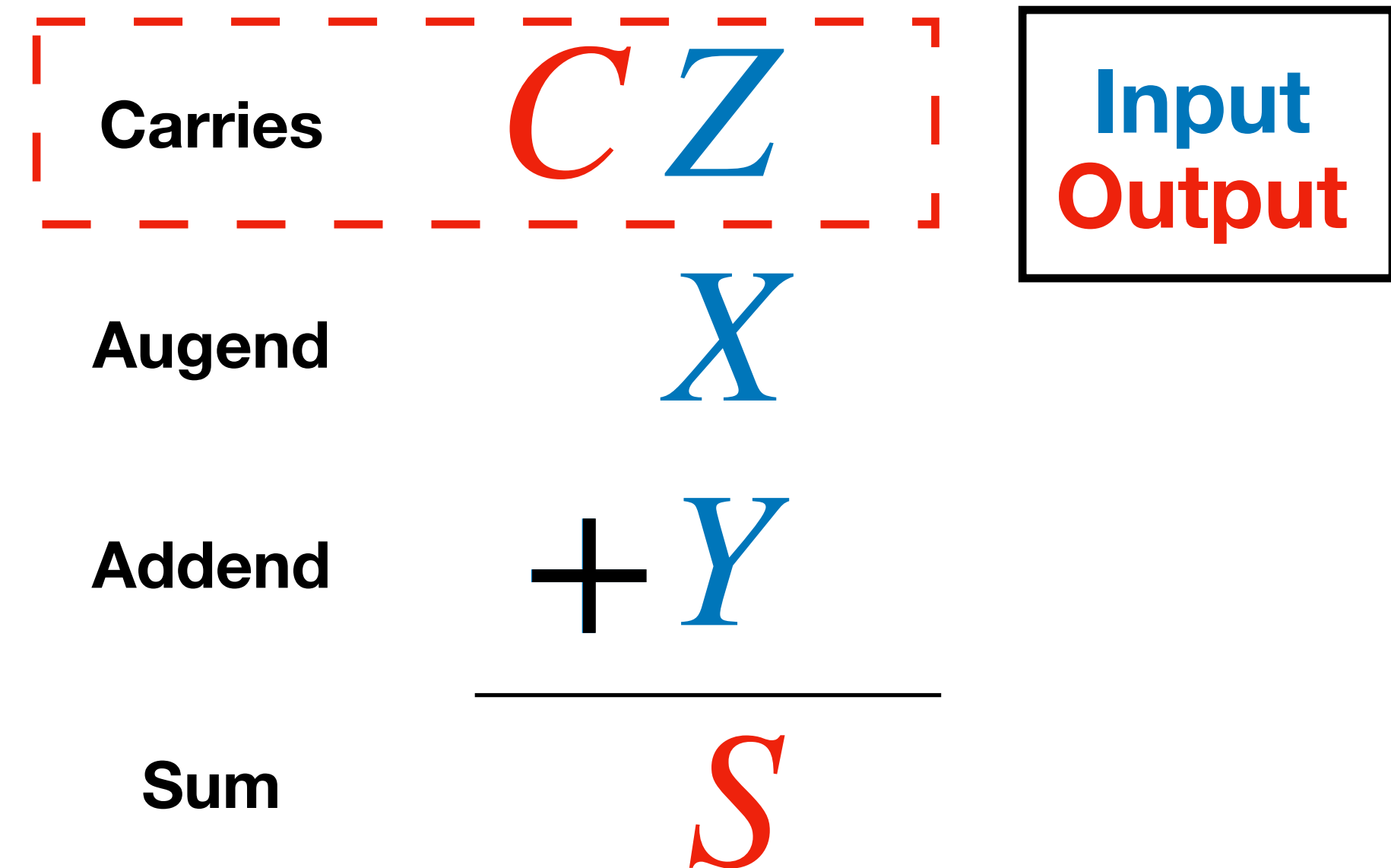


- Full adder
input X, Y, Z ;
output S, C

Unsigned Binary Subtraction

Technology


- 1 bit Unsigned Subtractor

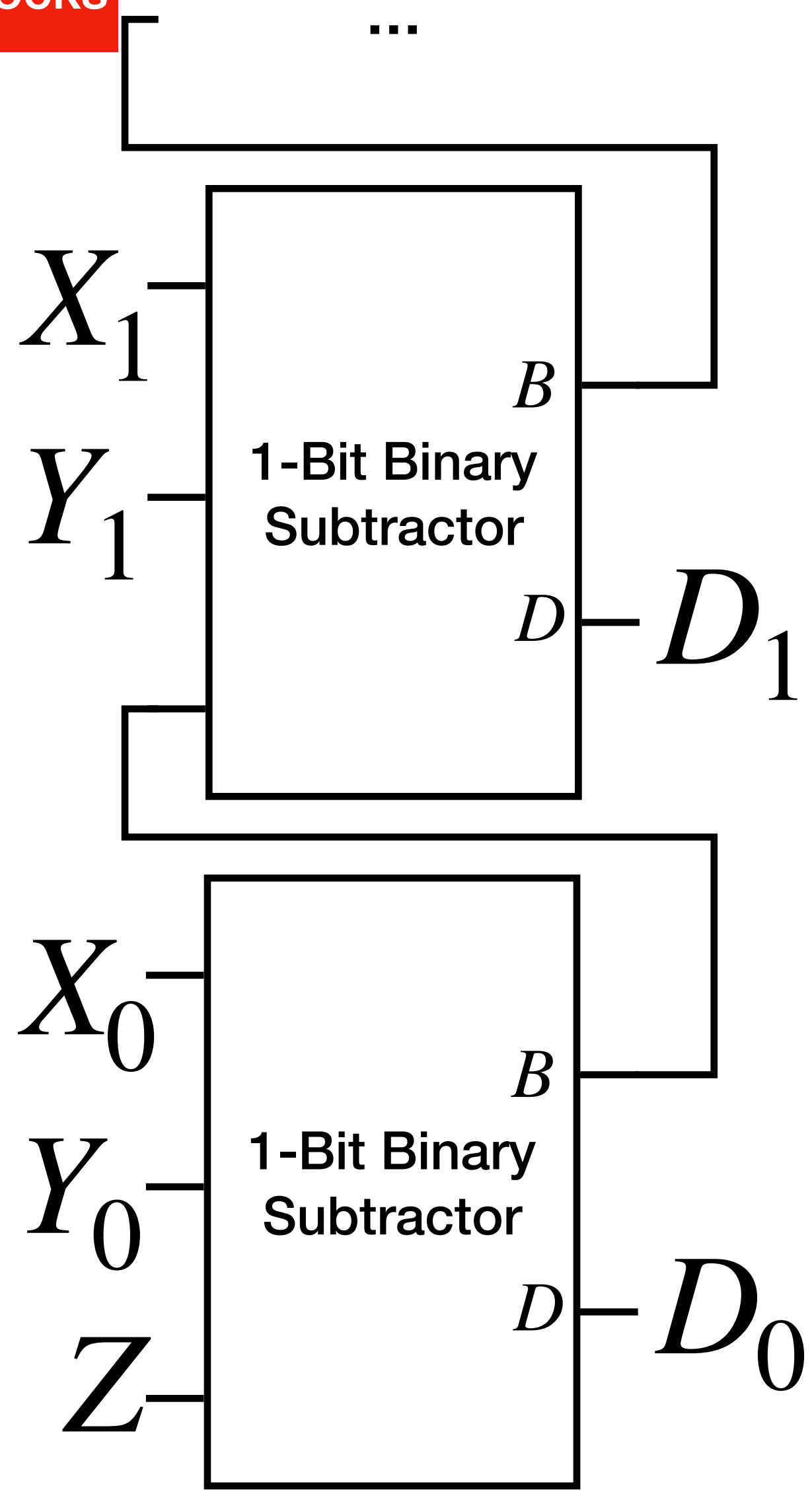


	<i>B</i>		<i>Z</i>			
Borrows	0	0	0	1	1	0
Minuend $X_{0:n-1}$	1	0	1	1	0	
Subtrahend $Y_{0:n-1}$			1	0	0	1
Difference $D_{0:n-1}$	0	0	0	1	1	

Input
Output

Full Unsigned Subtraction

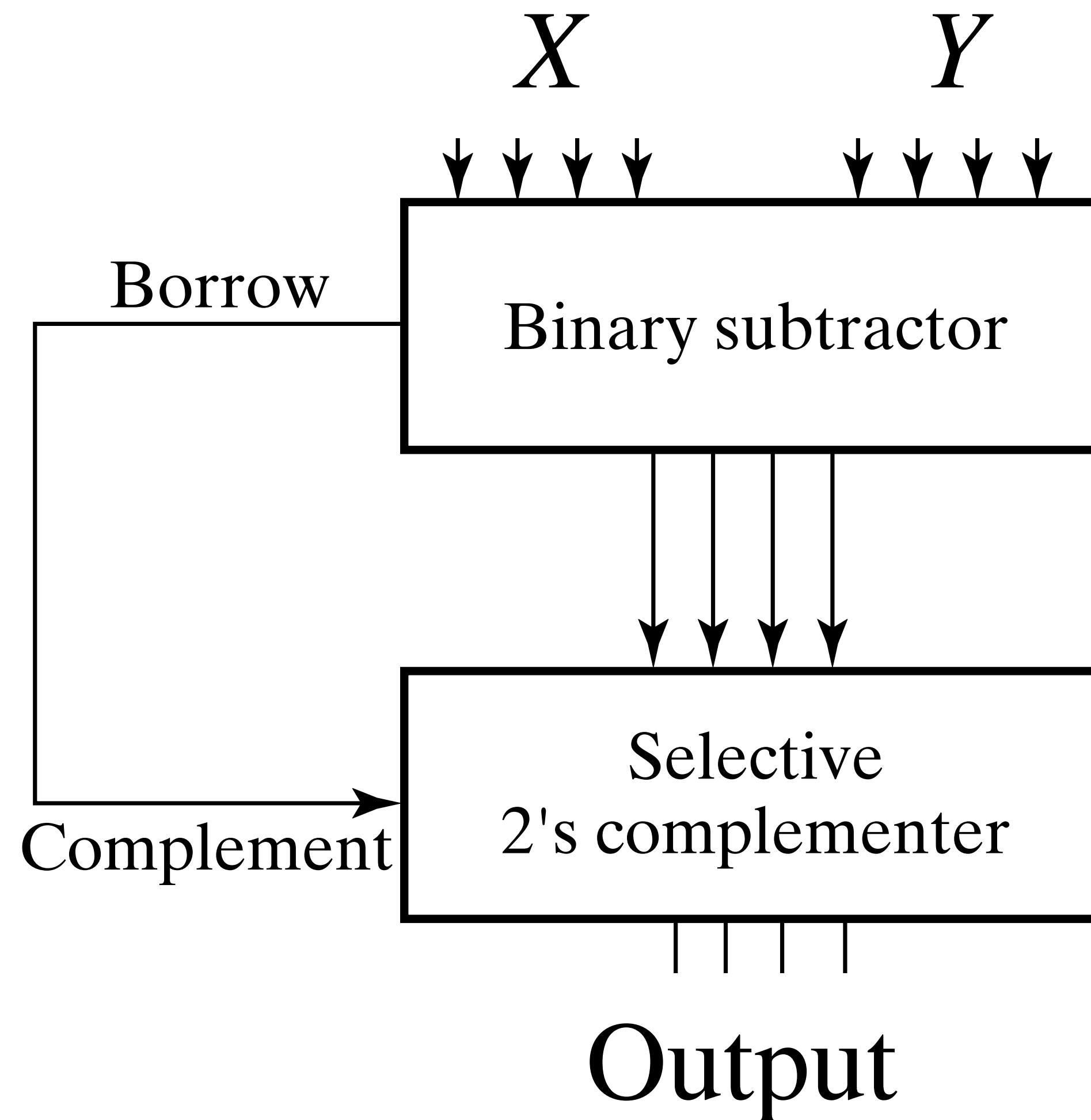

Adder Subtractor I

 

Adder-Subtractor II

