



08.07.20 12:33

# CSCI 150

## Introduction to Digital and Computer System Design

### Lecture 4: Sequential Circuit I




Jetic Gū  
2020 Summer Semester (S2)

# Overview

- Focus: Basic Information Retaining Blocks
- Architecture: Sequential Circuit
- Textbook v4: Ch5 5.1, 5.2; v5: Ch4 4.1 4.2
- Core Ideas:
  1. Introduction
  2.  $SR$  and  $\overline{SR}$  Latches,  $D$  Latch

 
# Combinational Logic Circuit Design

- Design Principles
  - Knows: fixed-Length input and output
  - Knows: input/output mapping relations
  - Optimisation: Minimise overall delay



 
# Combinational Logic Circuit Design

- Features
  - Fixed-Length input and output
  - The same input will always give the same output
  - Operations are simultaneous with minimum delay


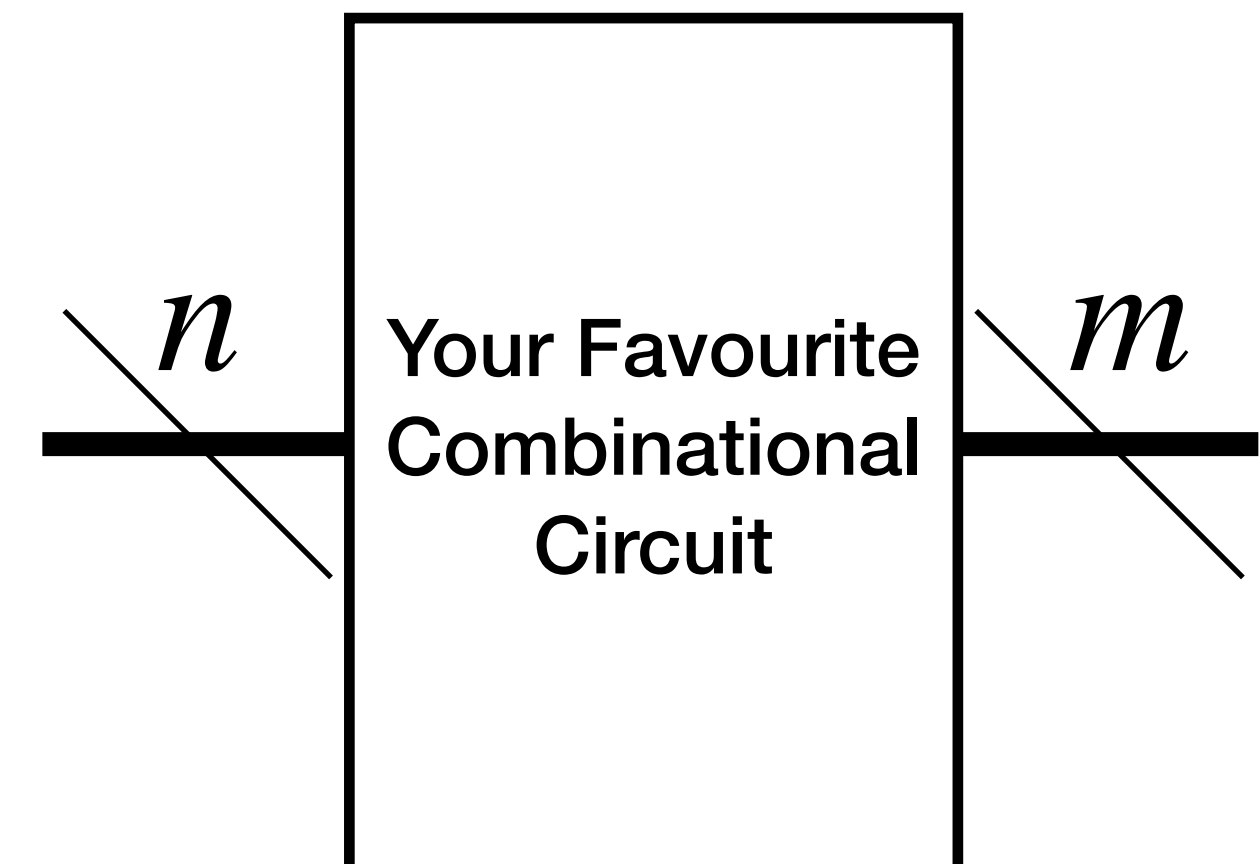
# Combinational Logic Circuit Design


- Cannot handle variable length input
- Cannot store information
- Cannot perform multi-step tasks



# Introduction to Sequential Circuit

 
# Solution

- Cannot handle variable length input
- Cannot store information
- Cannot perform multi-step tasks



 
# Solution: Storage!

- Cannot handle variable length input
- Cannot store information
- Cannot perform multi-step tasks






# Solution: Storage!

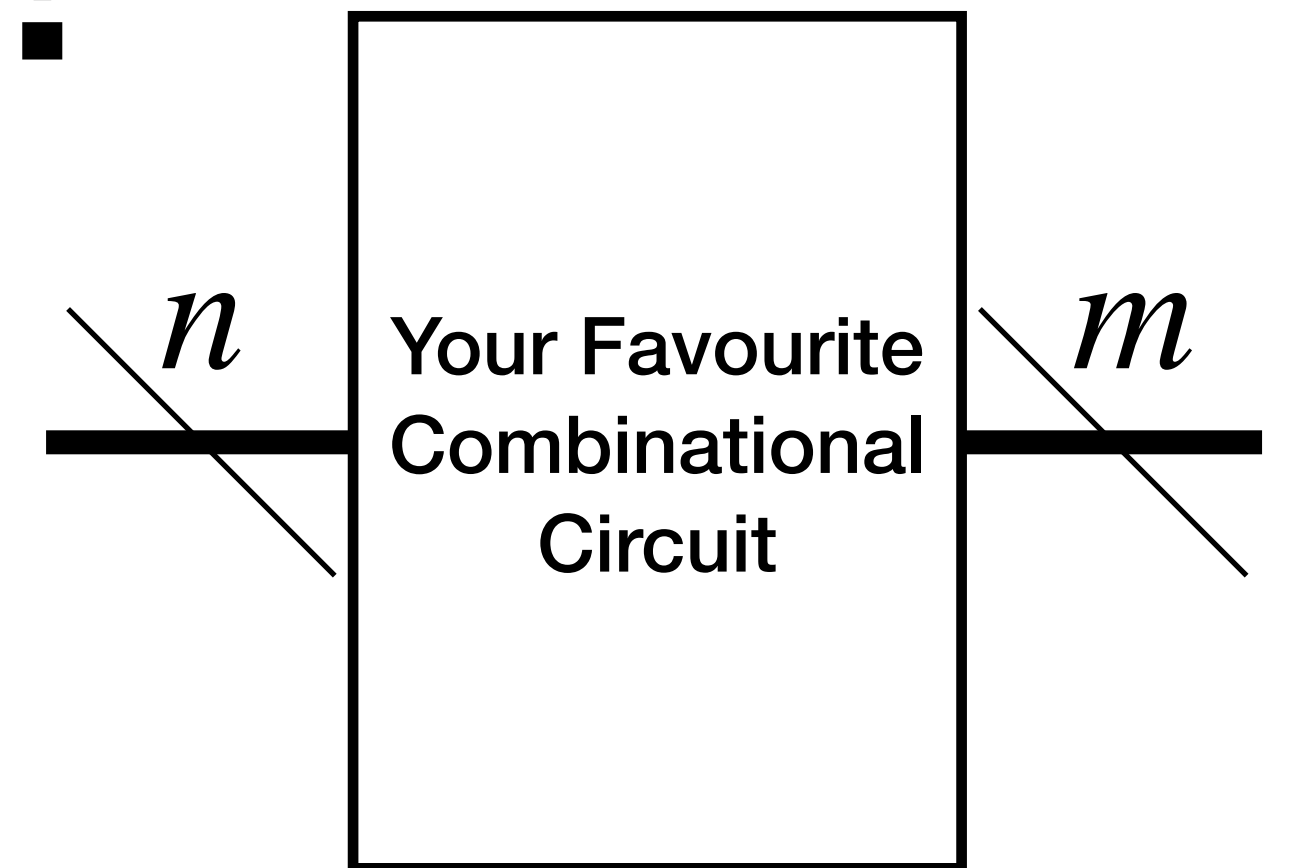

- Cannot handle variable length input
- Cannot store information
- Cannot perform multi-step tasks
- Storage of partial input
- Storage of partial results and states
- Storage of instructions

 
# Sequential Circuits

- Handle variable-length input
- Store information
- Multi-step tasks
- **State Transition** from time  $t$  to  $t + 1$



# Definitions

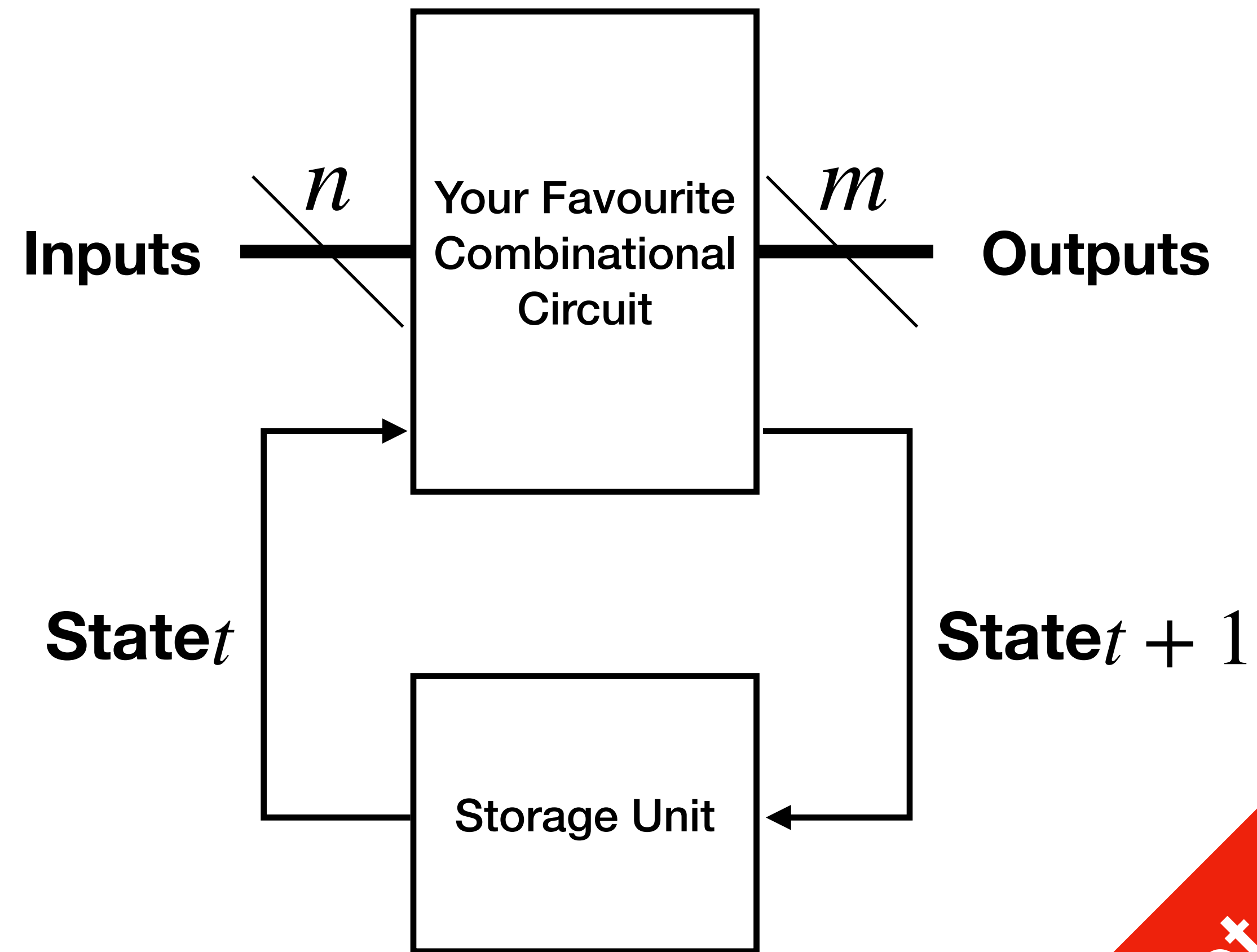1. **Storage Elements**  
circuits that can store binary information
2. **State**  
partial results, instructions, etc.
3. **Synchronous Sequential Circuit**  
Signals arrive at discrete instants of time,  
outputs at next time step
4. **Asynchronous Sequential Circuit**  
Signals arrive at any instant of time,  
outputs when ready



# Definitions

### 3. Synchronous Sequential Circuit


Signals arrive at discrete instants of time, outputs at next time step

- Has Clock

### 4. Asynchronous Sequential Circuit

Signals arrive at any instant of time, outputs when ready

- May not have Clock

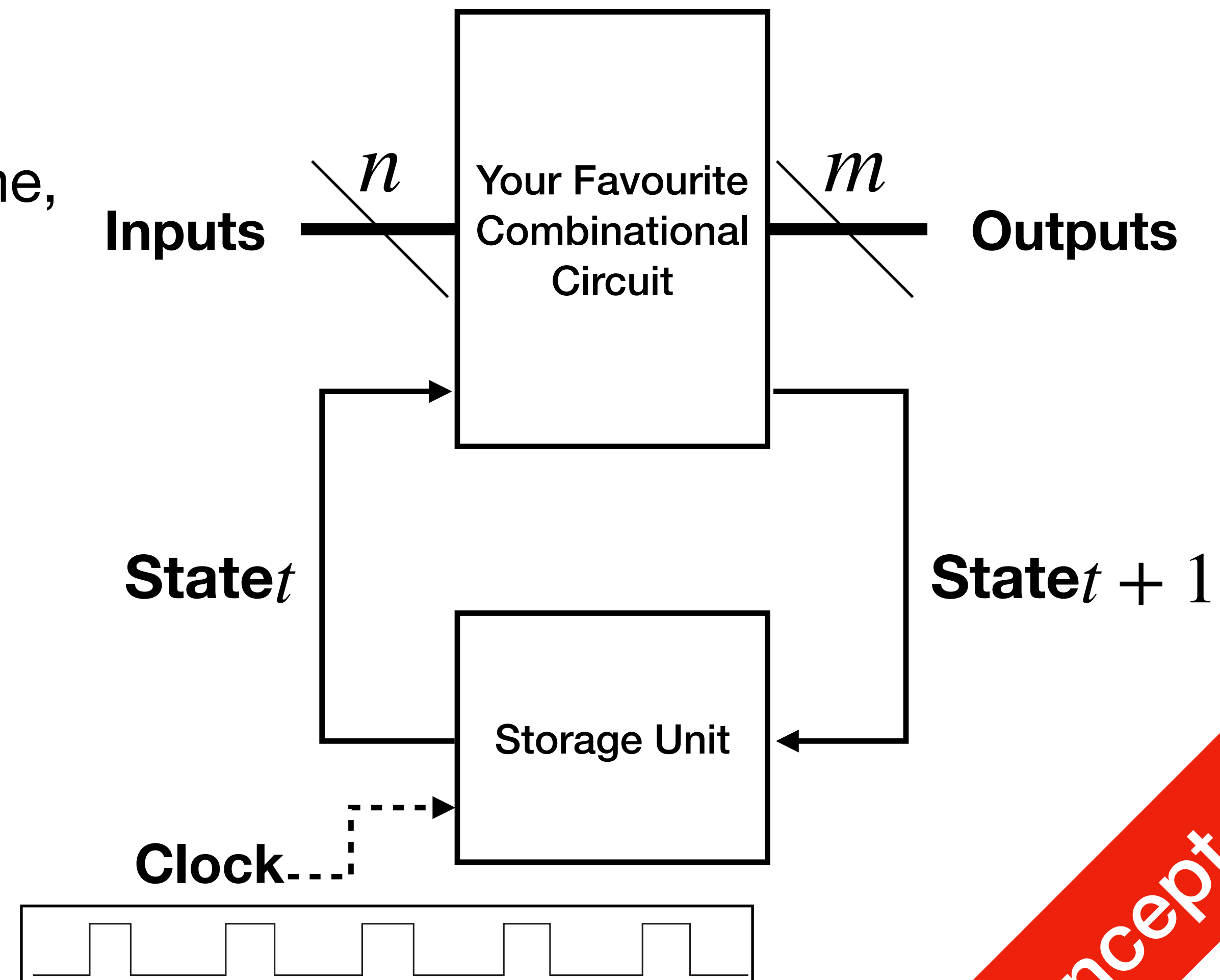

# Question

1. Are calculators designed using **Combinational Circuits** or **Sequential Circuits**?
  - What about your microwave and toaster?
  - What about your digital watch (not smart)?
  - What about computers/smartphones?

# Question



# Question

2. Is this calculator using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?





# Question

2. Is this calculator using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?
  - What are the states for this calculator?






# Question



2. Is this calculator using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?
  - What are the states for this calculator?
  - What kind of information is stored?


# Question

 




# Question

 3. Is this calculator using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?



# Question

 

3. Is this calculator using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?
- What are the states for this calculator?




# Question




3. Is this calculator using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?
- What are the states for this calculator?
  - What kind of information is stored?

# Question

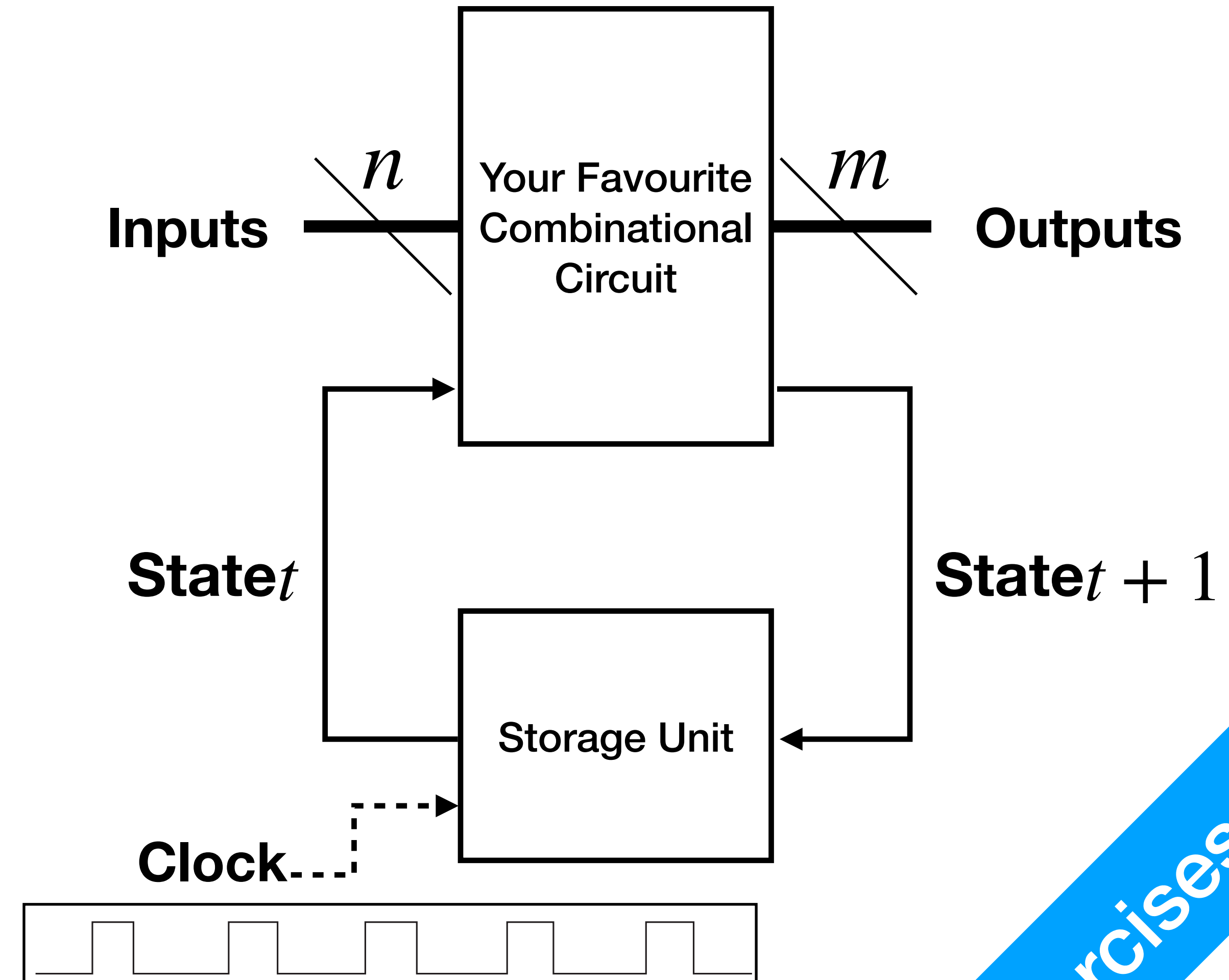


# Question

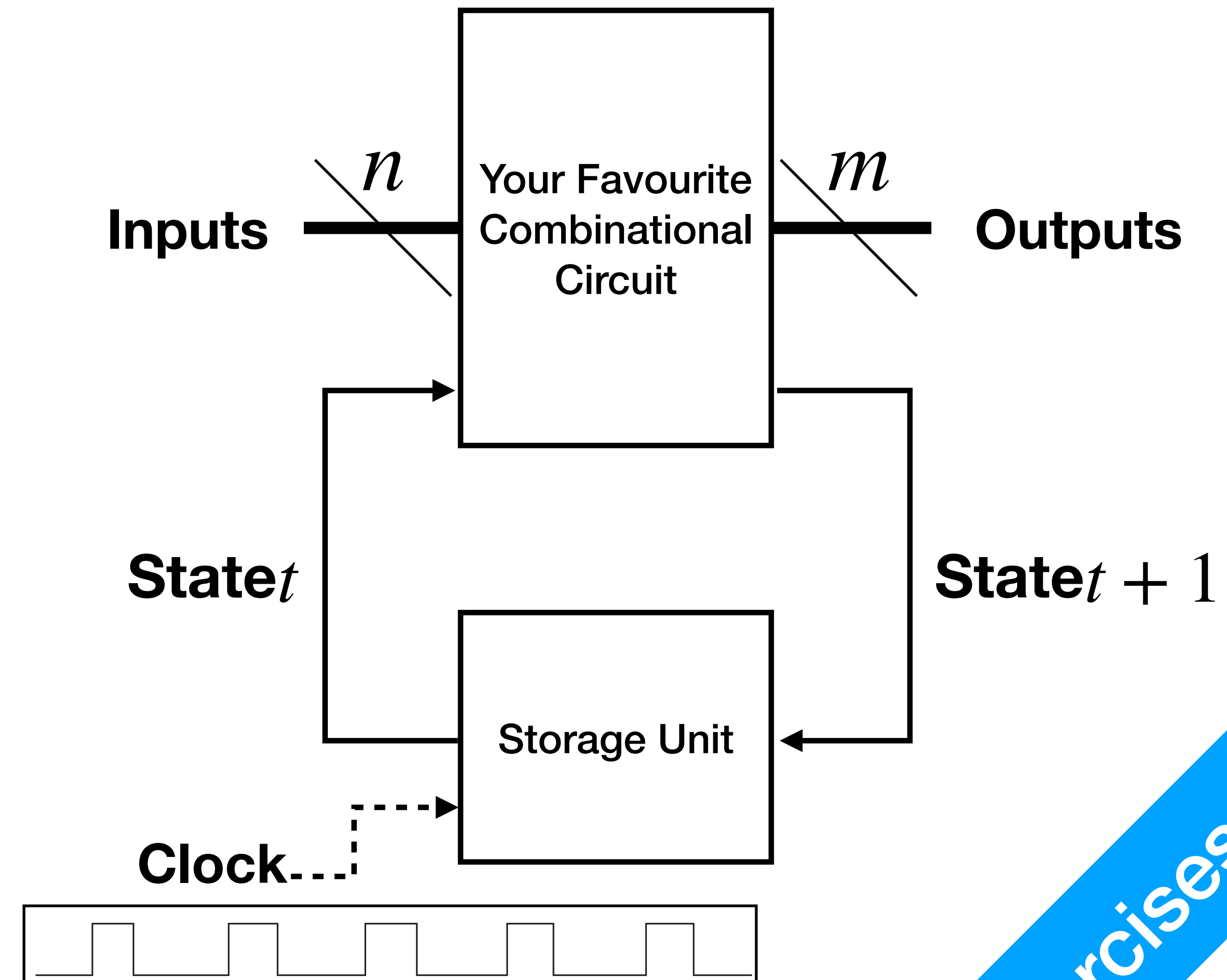4. Is your laptop/PC/smartphone using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?



# Question

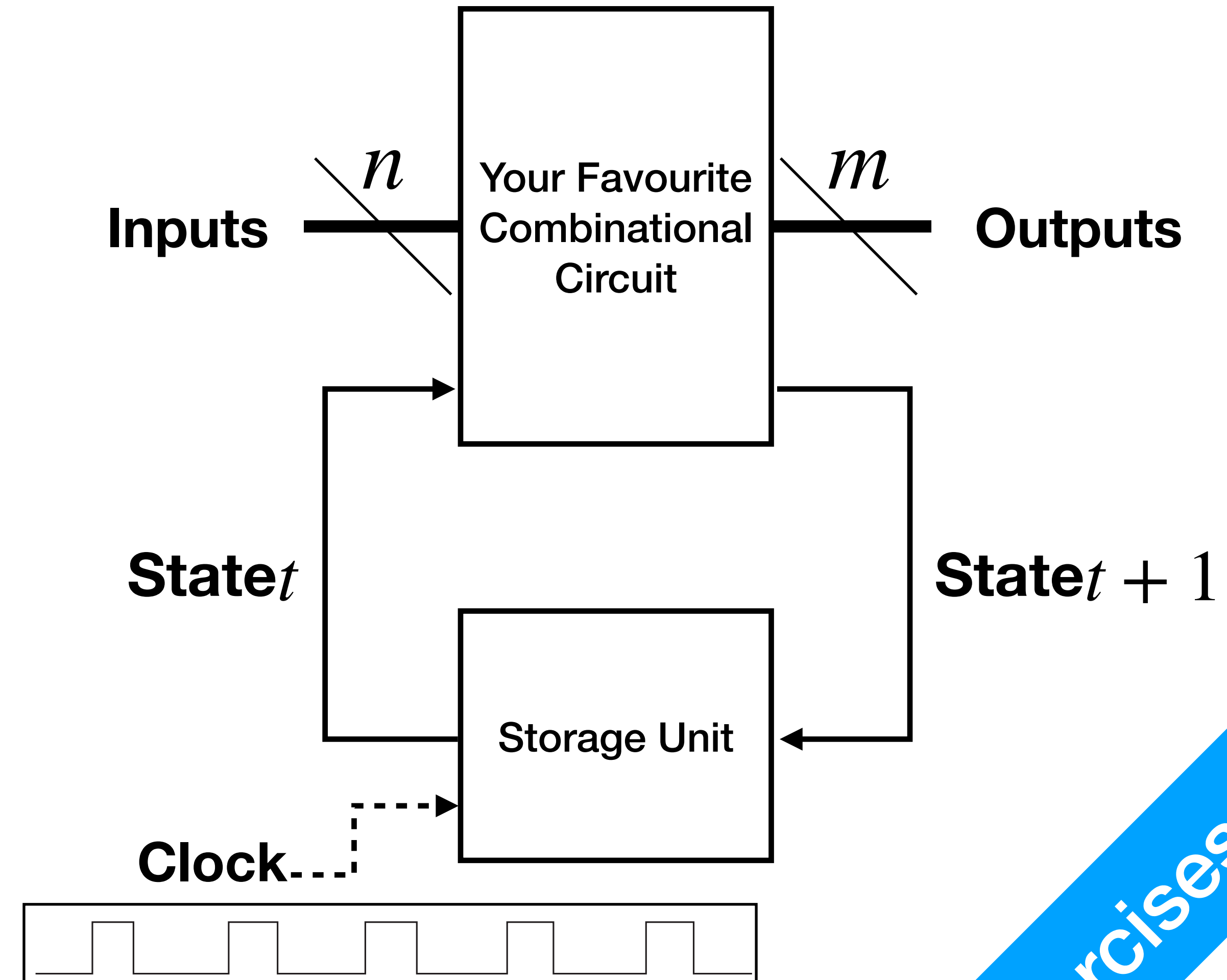
4. Is your laptop/PC/smartphone using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?
- What are the Input/Output devices of these computers?






# Question

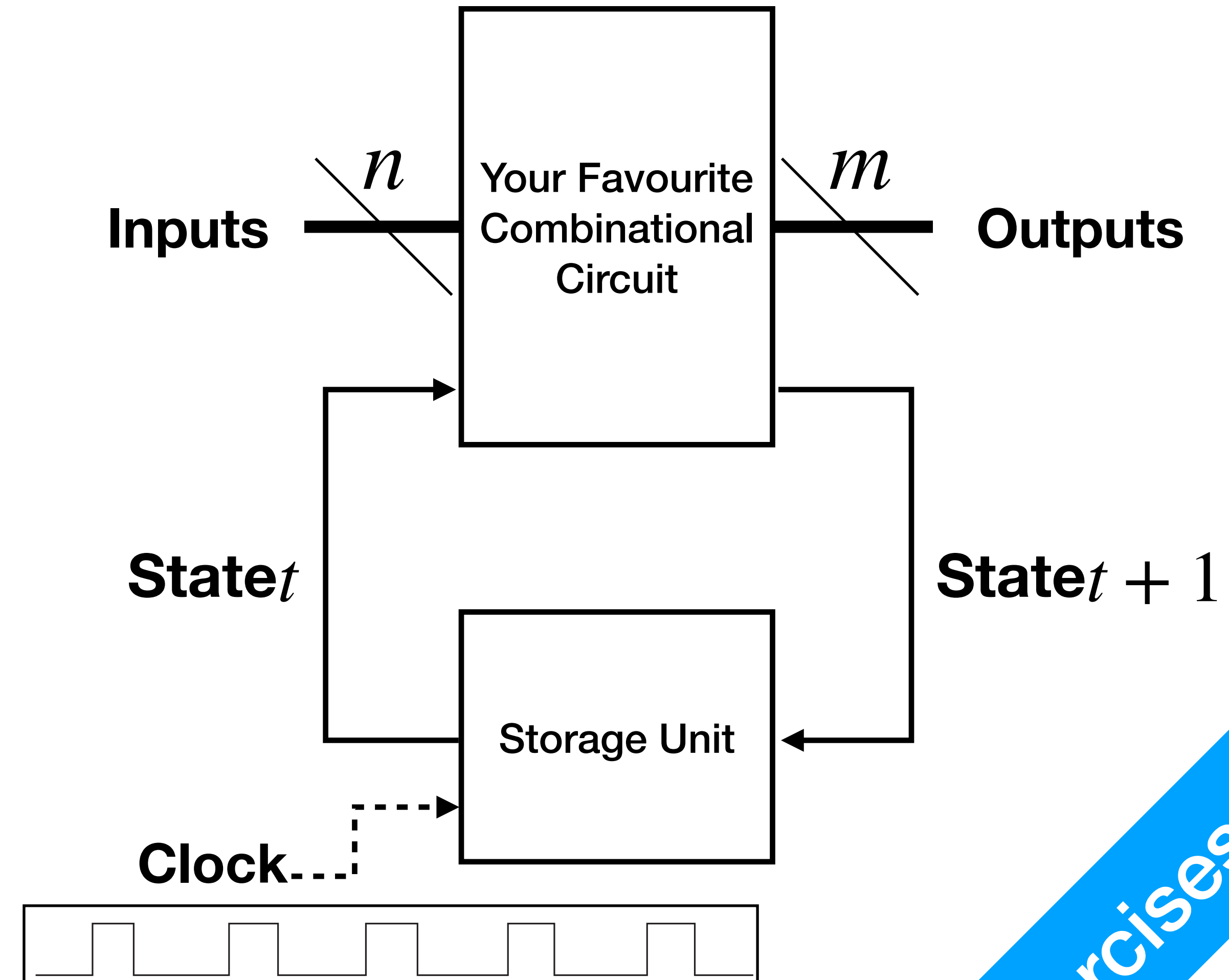4. Is your laptop/PC/smartphone using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?
- What are the Input/Output devices of these computers?
  - What are the storage devices?



# Question

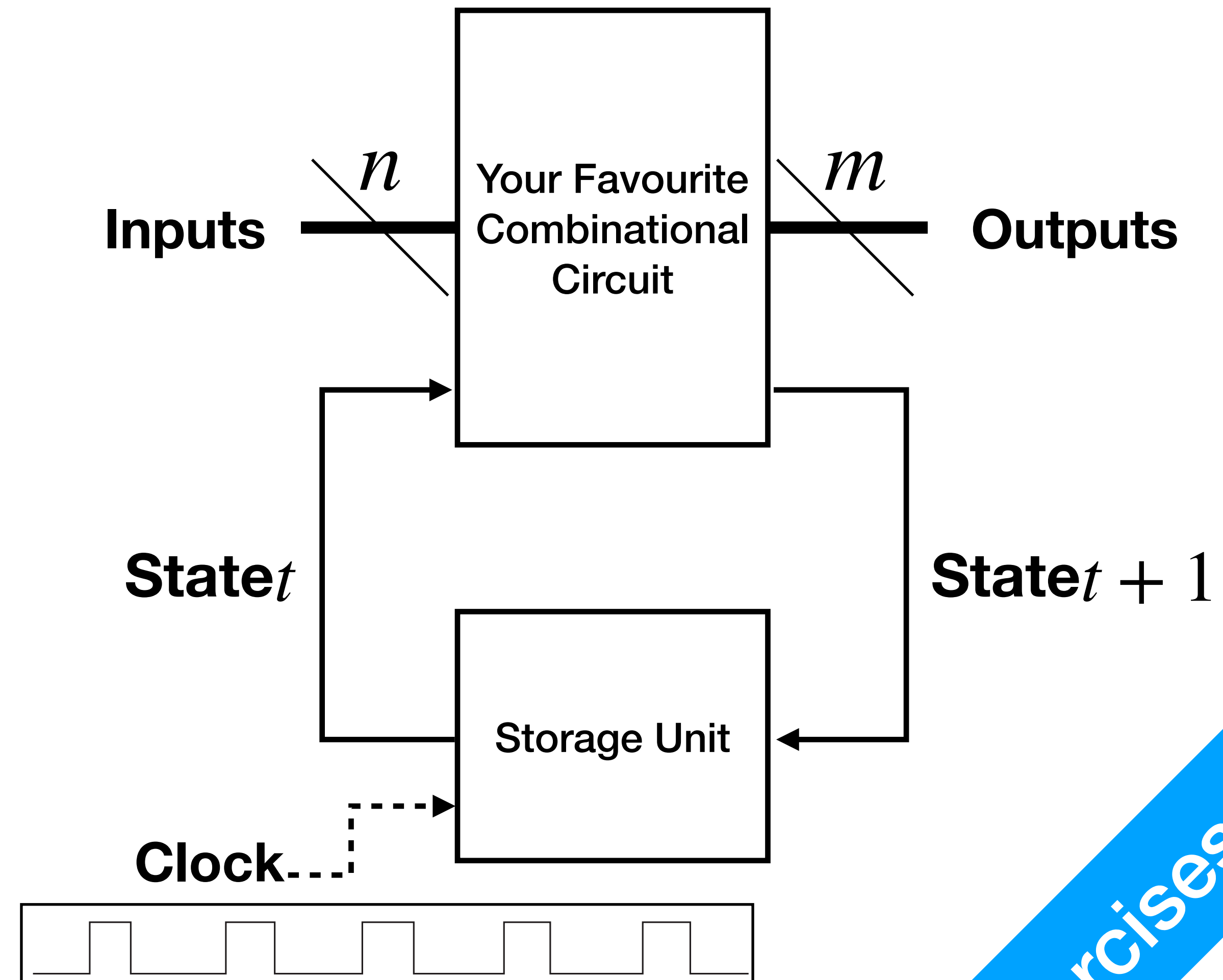4. Is your laptop/PC/smartphone using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?
- What are the Input/Output devices of these computers?
  - What are the storage devices?
  - What about CPU?




# Latches

$SR$  and  $\overline{SR}$  Latches,  $D$  Latch

 
# Stability

- Stable State: the values in a circuit after brief changing due to delay in passing information, reaches a state where it doesn't change anymore -



 
# Stability

- Stable State: the values in a circuit after brief changing due to delay in passing information, reaches a state where it doesn't change anymore -



 
# Stability

- Stable State: the values in a circuit after brief changing due to delay in passing information, reaches a state where it doesn't change anymore -



 
# Stability

- Stable State: all values in a circuit after some changes due to delay in passing signals, reach a state where they don't anymore


 
# Stability


- Stable State: all values in a circuit after some changes due to delay in passing signals, reach a state where they don't anymore





 
# Stability

- Stable State: all values in a circuit after some changes due to delay in passing signals, reach a state where they don't anymore


 
# Stability

- Stable State: all values in a circuit after some changes due to delay in passing signals, reach a state where they don't anymore



- What other scenarios might bring about these instabilities?

# Latches


- Basic Storage Elements
  - Maintain a binary state indefinitely, as long as there's power
  - The binary state inside can be changed




# Summary

- $SR$  Latches and  $\overline{SR}$  Latches
- $D$  Latches


# SR Latch: Stored value = 0

 


# SR Latch: Stored value = 0

 

# SR Latch: Stored value = 0

 


# SR Latch: Stored value = 0

 





# SR Latch: Stored value = 0

 


# SR Latch: Stored value = 0

 


# SR Latch: Stored value = 0

 


# SR Latch: Stored value = 0

 


# SR Latch: Stored value = 0

 

# SR Latch: Stored value = 0

 


# SR Latch: Stored value = 0

 





# SR Latch: Stored value = 0

 


# SR Latch: Stored value = 0

 


# SR Latch: Stored value = 0

 


# SR Latch: Stored value = 0

 


# SR Latch: Stored value = 0

 

# SR Latch: Stored value = 0

 


# SR Latch: Stored value = 0

 





# SR Latch: Stored value = 0

 


# SR Latch: Stored value = 0

 


# SR Latch: Stored value = 0

 


# SR Latch: Stored value = 1

 


# SR Latch: Stored value = 1

 

# SR Latch: Stored value = 1

 


# SR Latch: Stored value = 1

 





# SR Latch: Stored value = 1

 


# SR Latch: Stored value = 1

 


# SR Latch: Stored value = 1

 


# SR Latch: Stored value = 1

 


# SR Latch: Stored value = 1

 

# SR Latch: Stored value = 1

 


# SR Latch: Stored value = 1

 





# SR Latch: Stored value = 1

 


# SR Latch: Stored value = 1

 


# SR Latch: Stored value = 1

 


# SR Latch: Stored value = 1

 


# SR Latch: Stored value = 1

 

# SR Latch: Stored value = 1

 


# SR Latch: Stored value = 1

 

 
# Exercise

- Draw the  $SR$  Latch in LogicWorks as below, make sure it works as intended






# $\overline{SR}$ Latch

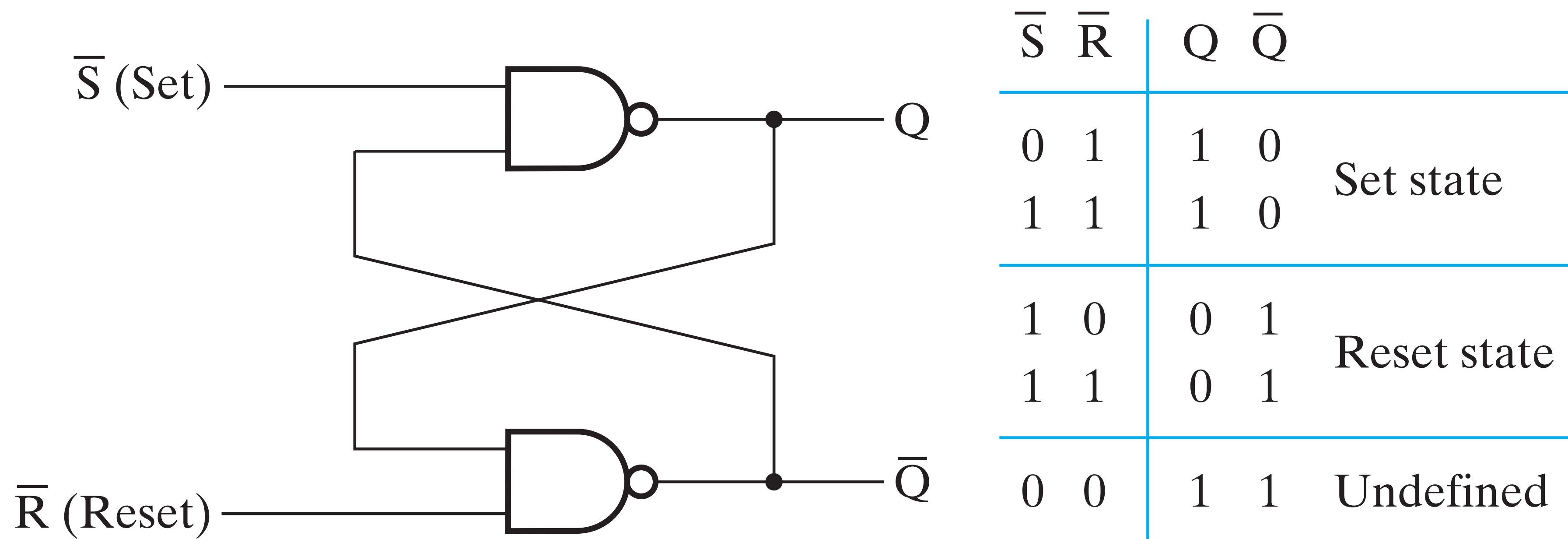

- Design similar to  $SR$  latches, but with NANDS
- Functions equivalent to  $SR$  latches with  $S$  and  $R$  inverted

# D Latch

 

C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

- Implemented using  $\overline{SR}$  latches
- $C$ : Signals changes to the stored states;  $D$  the value to change to

# Latches

- Implement  $\overline{SR}$  latch, save as a component in your library
- Implement  $D$  latch, save as a component in your library

