



13.07.20 15:20

CSCI 150

Introduction to Digital and Computer System Design

Lecture 4: Sequential Circuit II



Jetic Gū
2020 Summer Semester (S2)

Announcements


- Assignment 1-3 and Lab 1-2 marks are out
- If you get a zero due to **formatting** issues, you can send me an email ASAP with the correct version and I'll regrade them for you. Don't worry.
- Quiz 2-3 marks will be released today.
- Late submissions will not be graded. 20mins of extra time was given for uploads, if you missed it, it's your own fault
- Midterm is tomorrow, submission before **15:10**
- Be prepared, submit **ON TIME**. Late submissions will **NOT** be graded.




Overview

- Focus: Basic Information Retaining Blocks
- Architecture: Sequential Circuit
- Textbook v4: Ch5 5.2, 5.3; v5: Ch4 4.2, 5.3
- Core Ideas:
 1. Flip-Flops

SR Latch

 


\overline{SR} Latch

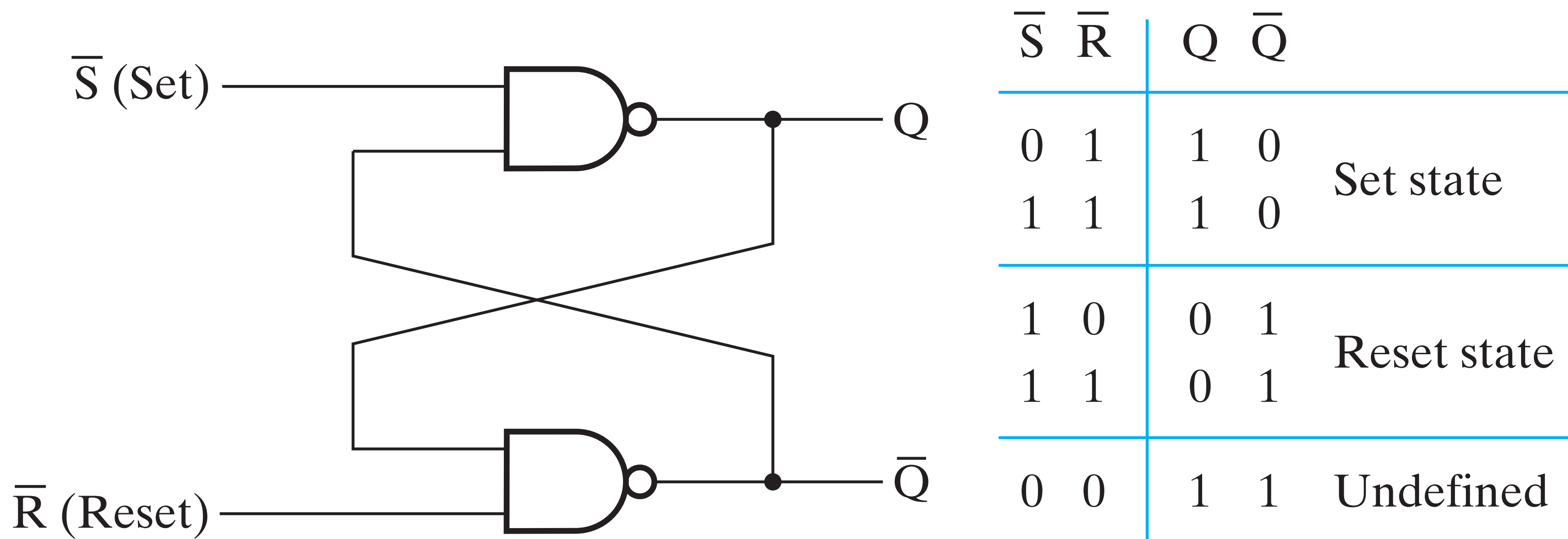

- Design similar to SR latches, but with NANDS
- Functions equivalent to SR latches with S and R inverted


D Latch

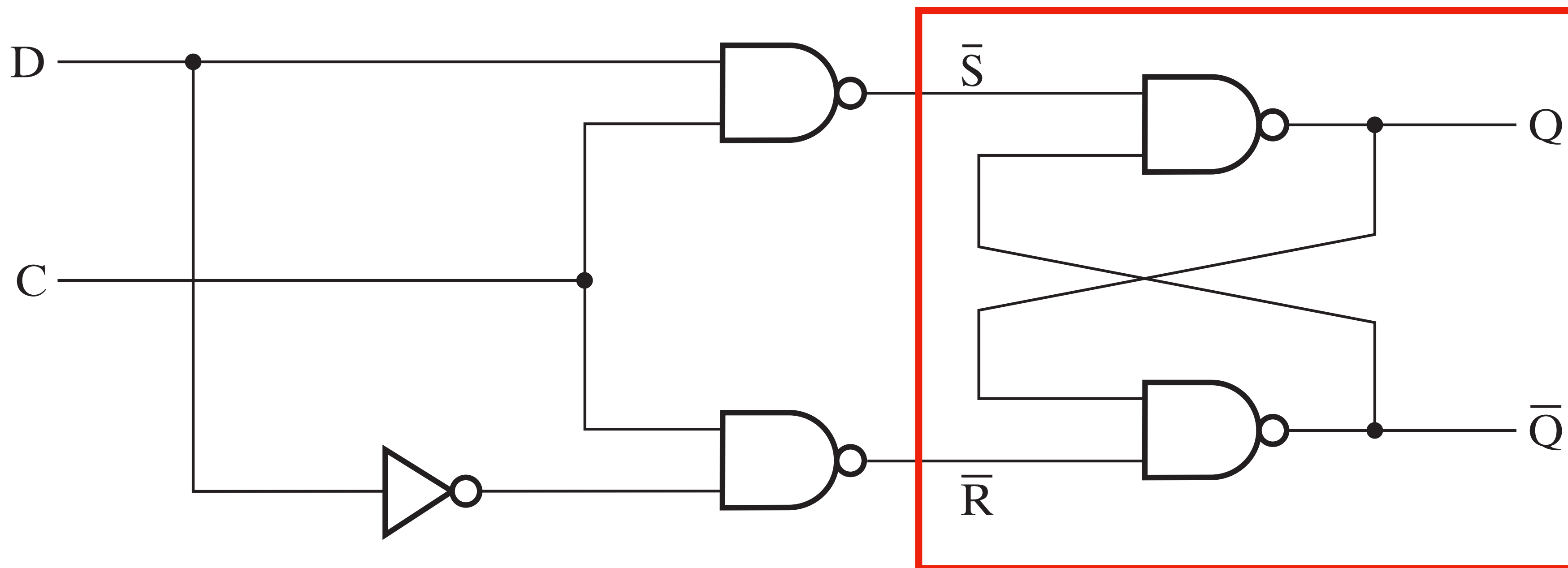


C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

- Implemented using \overline{SR} latches
- C : Signals changes to the stored states; D the value to change to


Latches

 


SR

 

$\bar{S}\bar{R}$

 

D with 1 Control

 


D with 0 Control

Flip-Flops

No, flip-flops are not proper shoes, nor shoes


SR Latch with Control Input

 

C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	Q = 0; Reset state
1	1	0	Q = 1; Set state
1	1	1	Undefined

- Implemented using \overline{SR} latches
- C acts as an enabler; otherwise the entire circuit functions as an SR latch

SR Latch with Control Input

 

C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	Q = 0; Reset state
1	1	0	Q = 1; Set state
1	1	1	Undefined


- Implemented using \overline{SR} latches
- C acts as an enabler; otherwise the entire circuit functions as an SR latch

Latches

- What happens if the control pulse remains active?
 - any changes in the data input will change the state of the latch immediately!
- latches are **transparent**
input can be seen from outputs while control pulse is 1

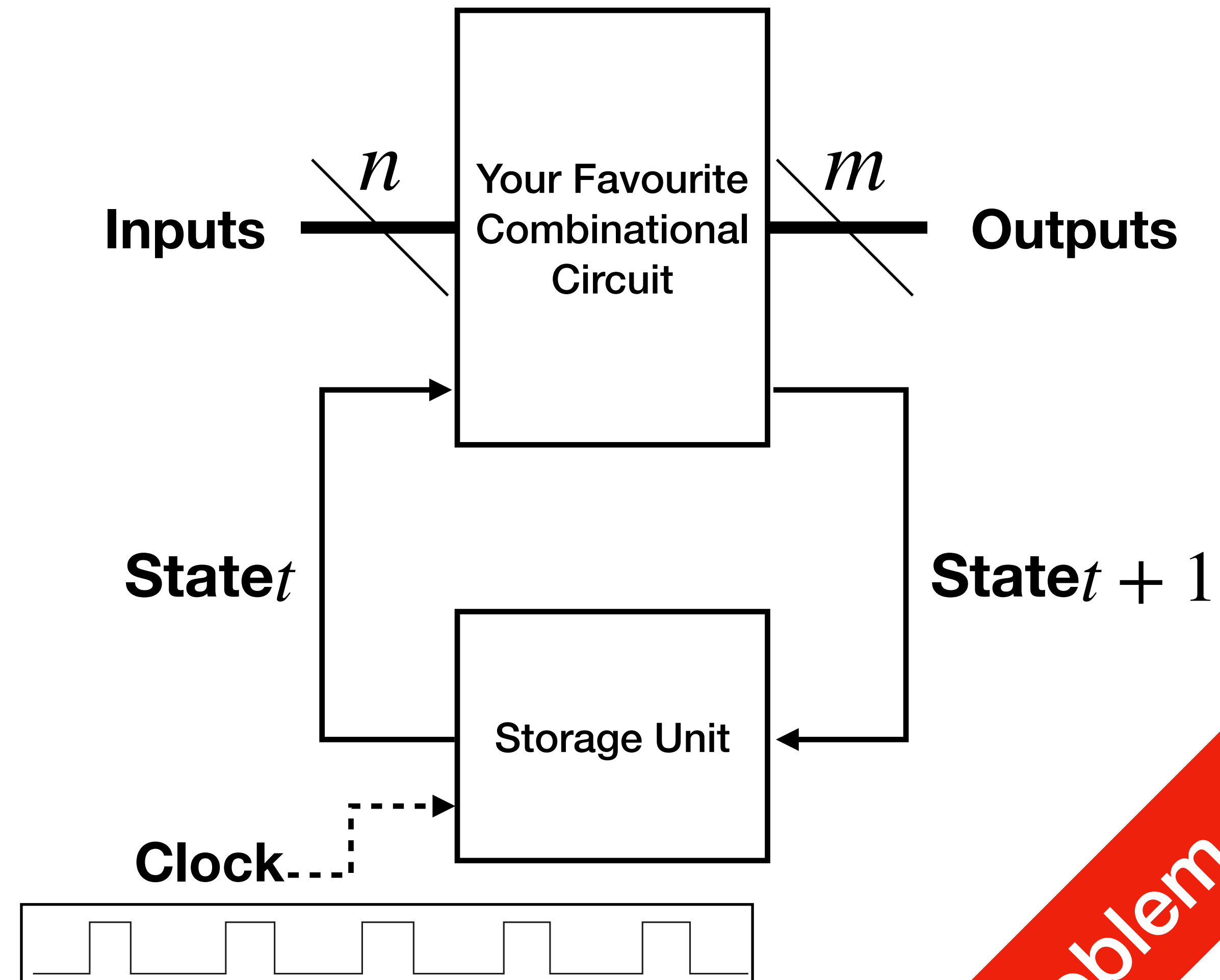Problems with Latches

- Transparent: changes happen instantly
- Time t , input changes
- Time $(t, t + 1)$, output stabilises
- Time $t + 1$, output stored in Storage Unit




Problem

Problems with Latches

- Transparent: changes happen
- Time t , input changes
- Time $(t, t + 1)$, output stabilises
- Time $t + 1$, output stored in Storage Unit

During this period, storage unit must keep outputting $State_t$, otherwise output may not stabilise

Latches cannot accomplish this!

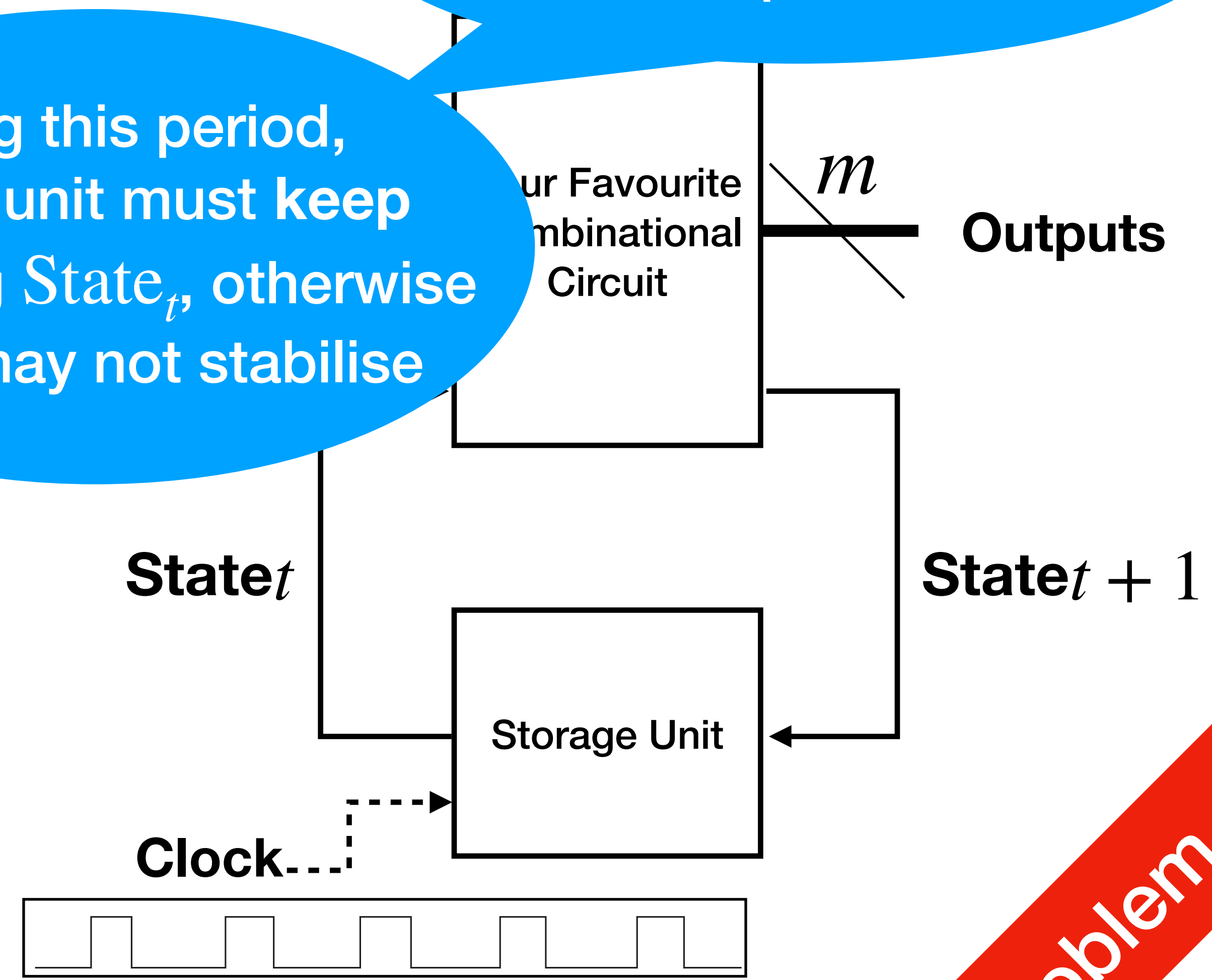


Problem

Flip-Flops


- Time t , clock flips, new input arrives
- Time $(t, t + 1)$: output State_t
 - meanwhile, new inputs arrives;
 State_{t+1} stabilises
- Time $t + 1$, clock flips, storage rewritten as State_{t+1} , new input arrives
- Time $(t + 1, t + 2)$: output State_{t+1}
 - ...

Flip-Flops

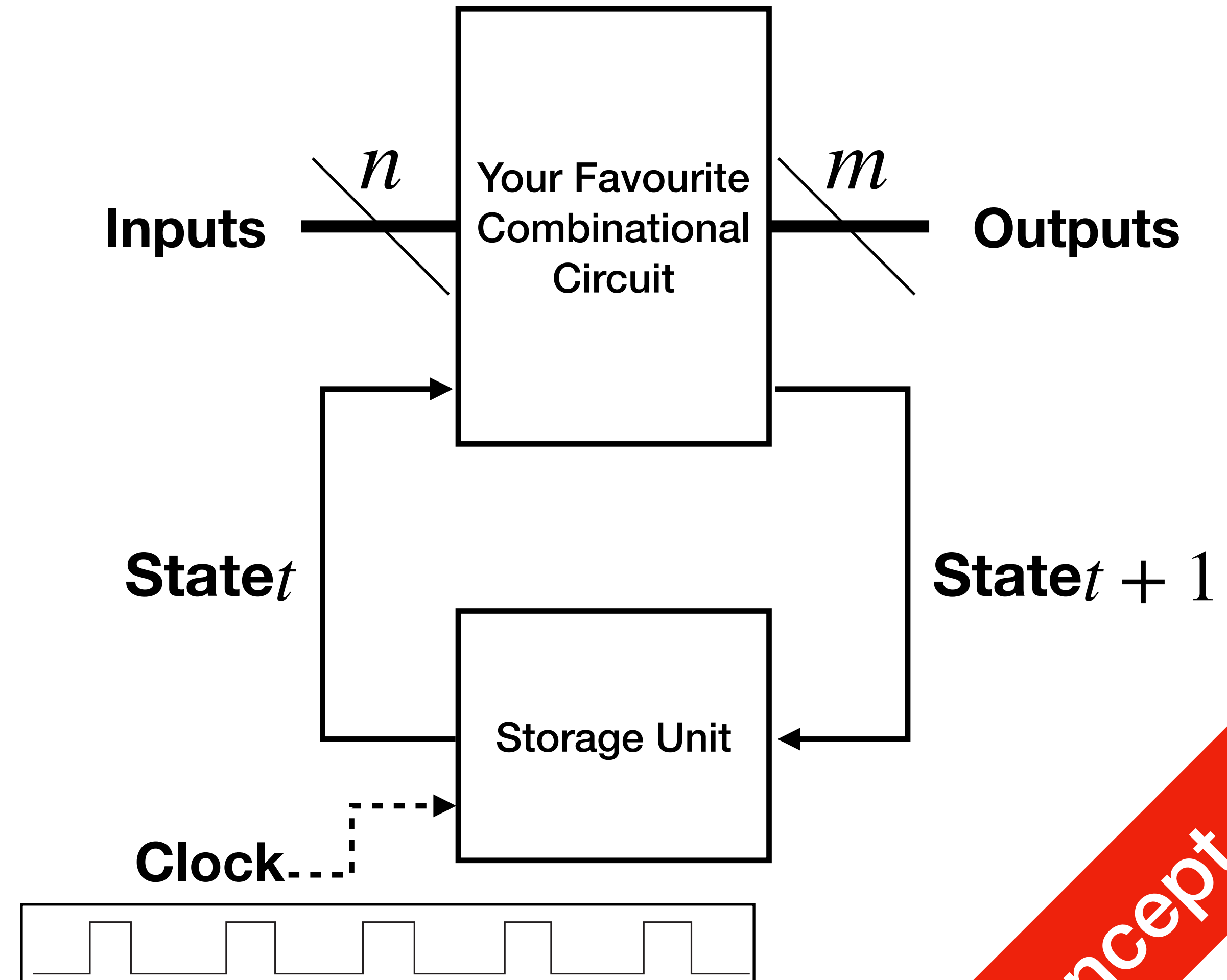- Time t , clock flips, new input arrives
- Time $(t, t + 1)$: output State_t
 - meanwhile, new inputs arrives;
 State_{t+1} stabilises
- Time $t + 1$, clock flips, storage rewritten as State_{t+1} , new input arrives
- Time $(t + 1, t + 2)$: output State_{t+1}
- ...




SR Master-Slave Flip-Flop

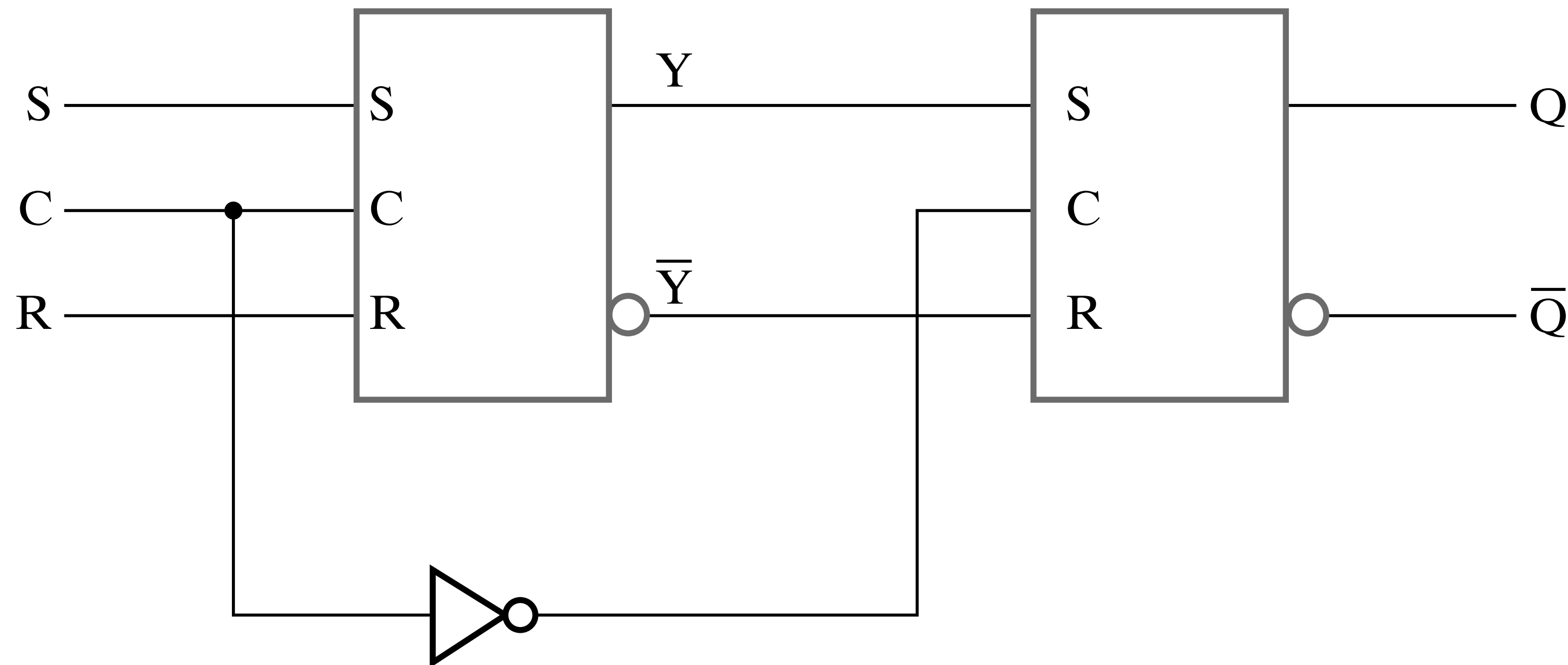


- Constructed using *SR* latches, left Master, right Slave
- Output state changes require $C = 0 \rightarrow C = 1 \rightarrow C = 0$ (Positive Pulse)

SR Master-Slave Flip-Flop

 


- Constructed using *SR* latches, left Master, right Slave
- Output state changes require $C = 0 \rightarrow C = 1 \rightarrow C = 0$ (Positive Pulse)

SR Master-Slave Flip-Flop

 


- Constructed using *SR* latches, left Master, right Slave
- Output state changes require $C = 0 \rightarrow C = 1 \rightarrow C = 0$ (Positive Pulse)

SR Master-Slave Flip-Flop

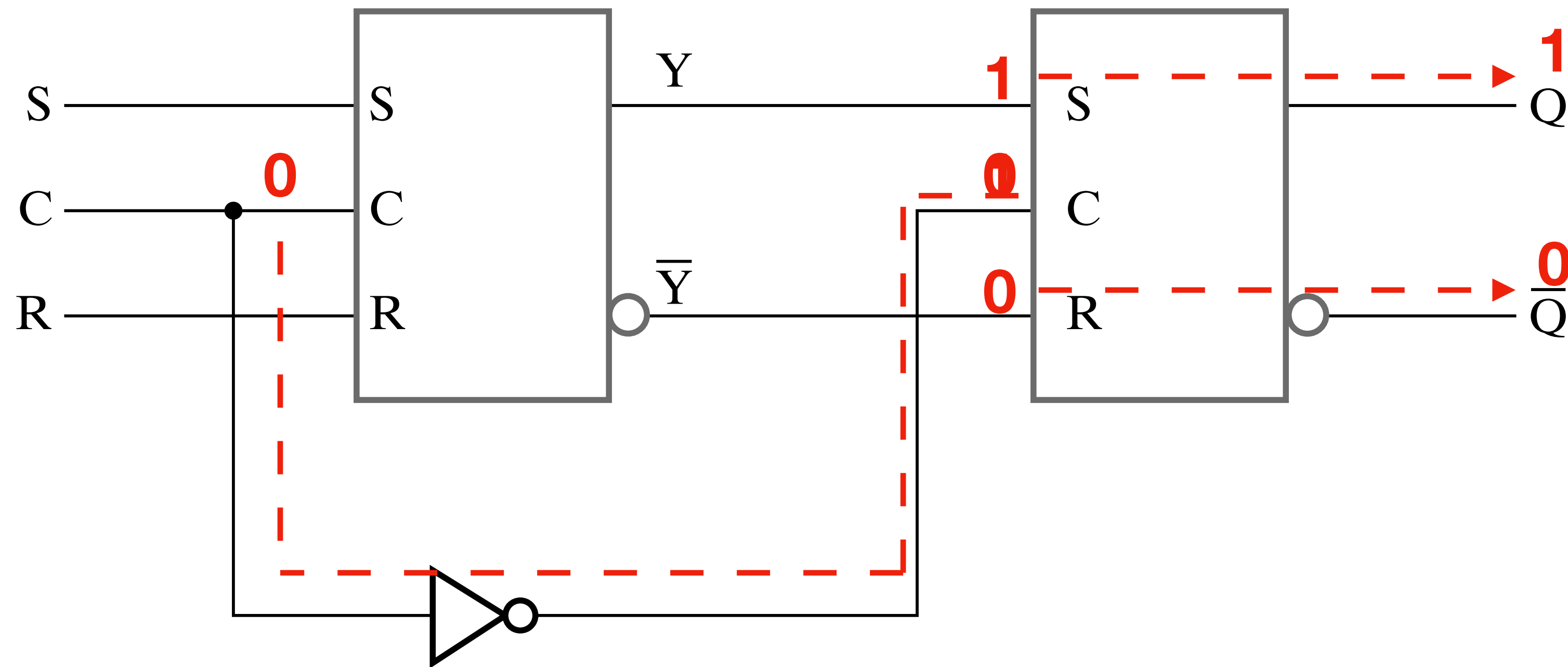


- Constructed using *SR* latches, left Master, right Slave
- Output state changes require $C = 0 \rightarrow C = 1 \rightarrow C = 0$ (Positive Pulse)

SR Master-Slave Flip-Flop

 

- Constructed using *SR* latches, left Master, right Slave
- Output state changes require $C = 0 \rightarrow C = 1 \rightarrow C = 0$ (Positive Pulse)
- Also called: **Positive Pulse Triggered SR** (Flip-Flop)



SR Master-Slave Flip-Flop

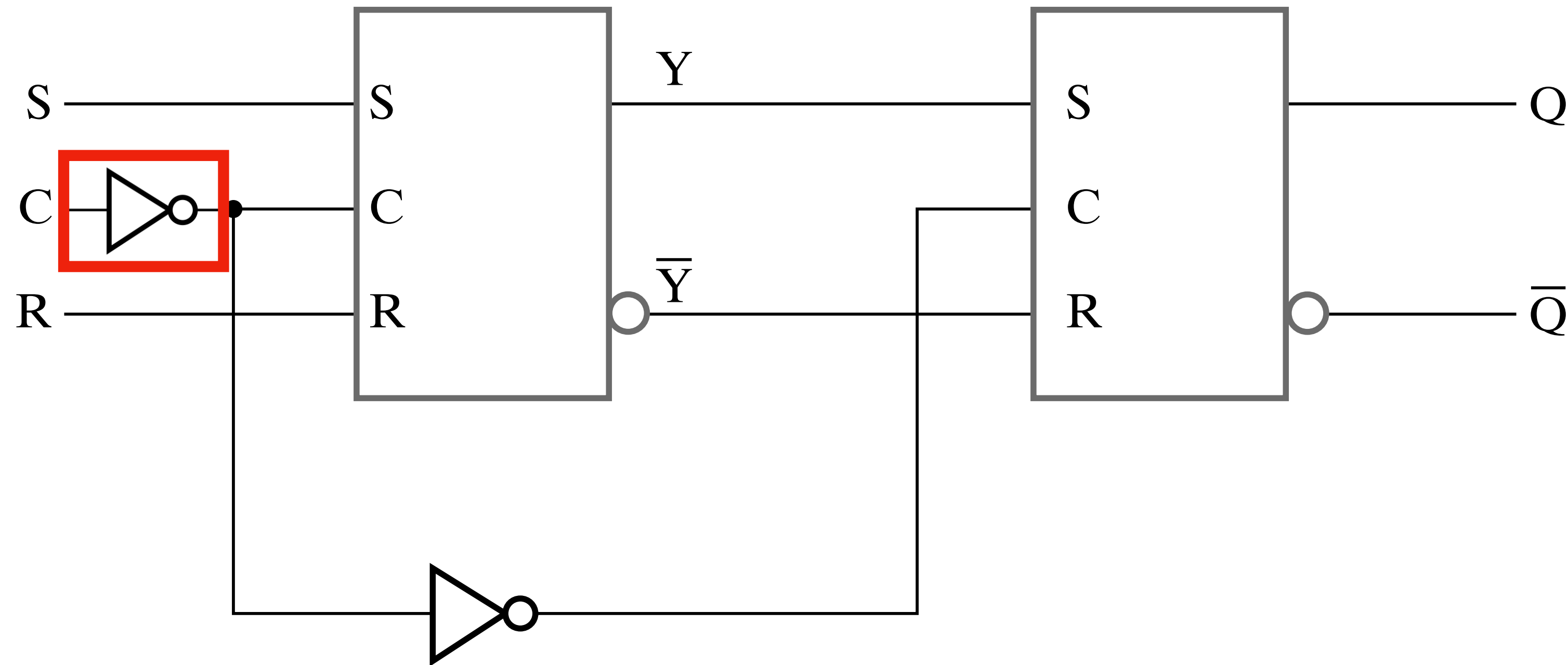


- Output state changes require $C = 1 \rightarrow C = 0 \rightarrow C = 1$ (Negative Pulse)
- **Negative Pulse Triggered SR** (Flip-Flop)

Implement Positive Pulse Triggered SR

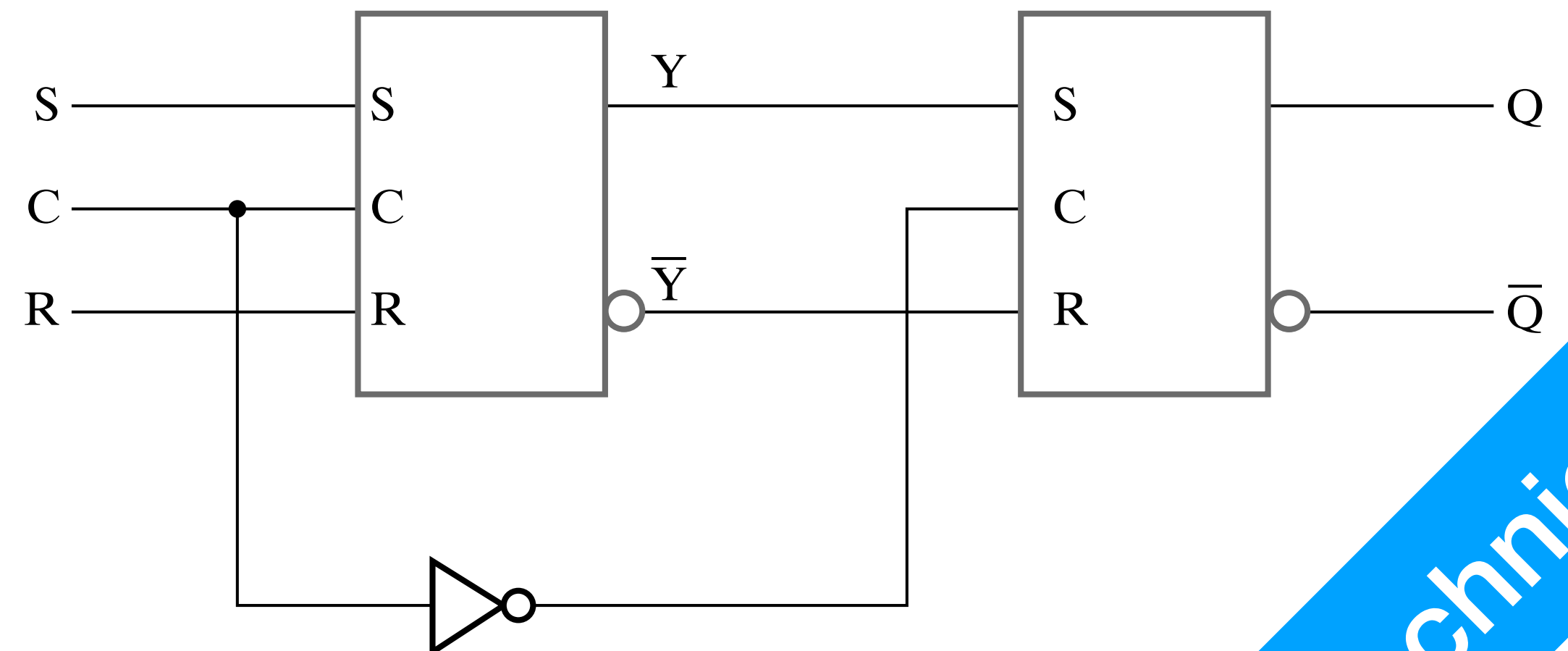 - Implement SR Latch with Control Input using $\overline{S}\overline{R}$ Latch
- Implement Positive Pulse Triggered SR using SR latch with Control Input




D Flip-Flop

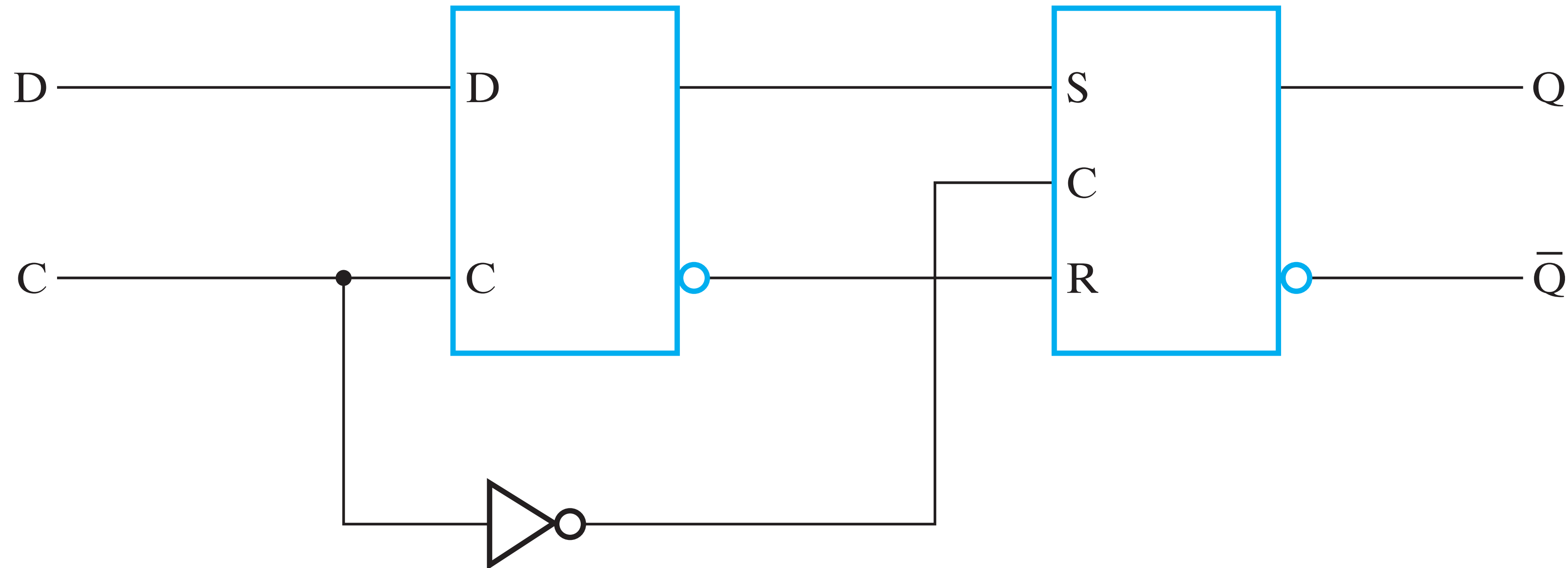


- Replaces *SR* master in *SR* Master-Slave with *D* master Latch
- **Negative Edge Triggered *D*** (Flip-Flop): $C = 1 \rightarrow C = 0$

D Flip-Flop

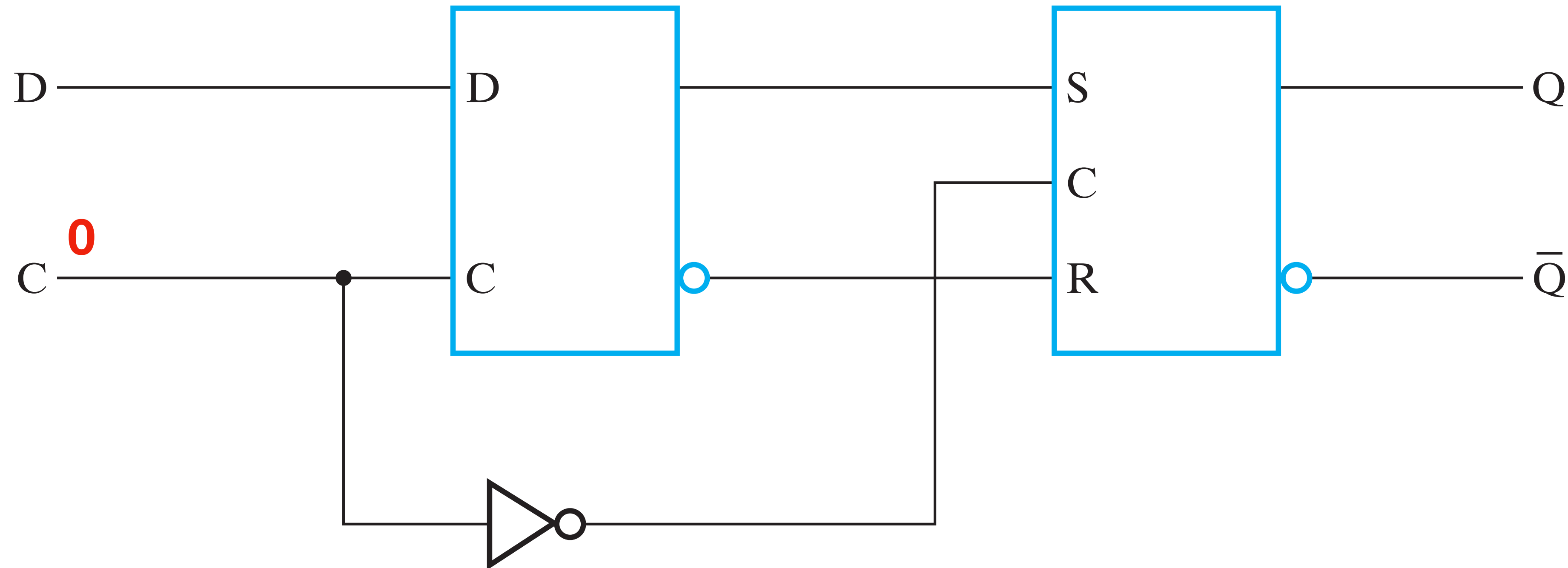


- Replaces *SR* master in *SR* Master-Slave with *D* master Latch
- **Negative Edge Triggered *D*** (Flip-Flop): $C = 1 \rightarrow C = 0$

D Flip-Flop

 


- Replaces *SR* master in *SR* Master-Slave with *D* master Latch
- **Negative Edge Triggered *D*** (Flip-Flop): $C = 1 \rightarrow C = 0$

D Flip-Flop

 


- Replaces *SR* master in *SR* Master-Slave with *D* master Latch
- **Negative Edge Triggered *D*** (Flip-Flop): $C = 1 \rightarrow C = 0$


Flip Flops

 


Triggered SR

 

Triggered SR

 


Triggered D

 


Triggered D


Flip Flops

 


Triggered SR

 

Triggered SR

 

Triggered D
Triggered D

 

Triggered D
Triggered D

Summary

