



13.07.20 15:21

# CSCI 150

## Introduction to Digital and Computer System Design

### Lecture 4: Sequential Circuit III




Jetic Gū  
2020 Summer Semester (S2)

# Overview

- Focus: Basic Information Retaining Blocks
- Architecture: Sequential Circuit
- Textbook v4: Ch5 5.3, 5.4; v5: Ch4 4.2 4.3
- Core Ideas:
  1. Latches and Flip-Flops (with Direct Input)
  2. Sequential Circuit Analysis

 
# Combinational Logic Circuit Design

- Design Principles
  - Knows: fixed-Length input and output
  - Knows: input/output mapping relations
  - Optimisation: Minimise overall delay



 
# Combinational Logic Circuit Design

- Cannot handle variable length input
- Cannot store information
- Cannot perform multi-step tasks



# Definitions

 1. **Storage Elements**  
circuits that can store binary information
2. **State**  
partial results, instructions, etc.
3. **Synchronous Sequential Circuit**  
Signals arrive at discrete instants of time,  
outputs at next time step
4. **Asynchronous Sequential Circuit**  
Signals arrive at any instant of time,  
outputs when ready



# Definitions

## 3. Synchronous Sequential Circuit


Signals arrive at discrete instants of time, outputs at next time step

- Has Clock

## 4. Asynchronous Sequential Circuit

Signals arrive at any instant of time, outputs when ready

- May not have Clock

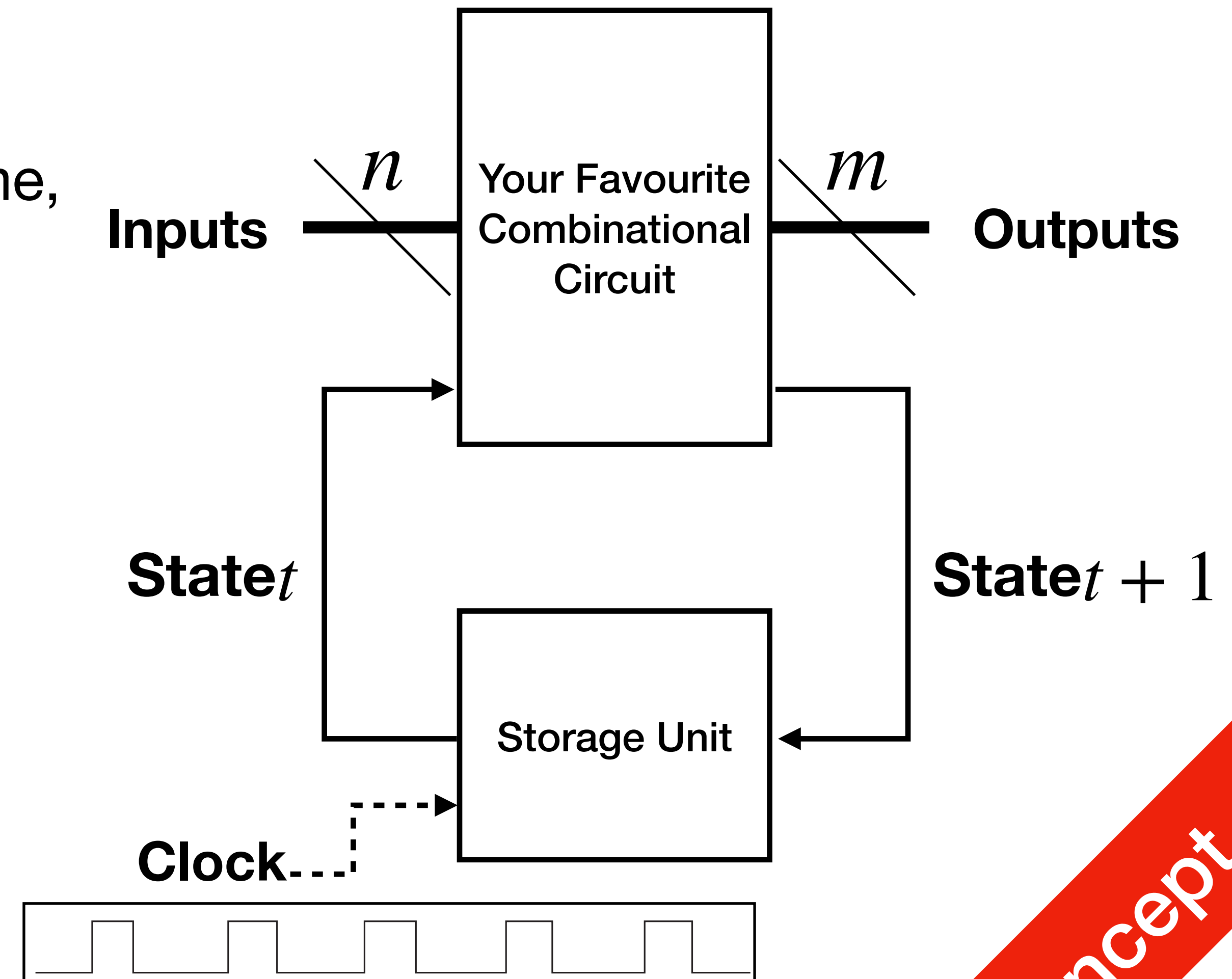


# Review:

# Latches and Flip-Flops

*SR* Latches, D Latches, D Flip-Flops

# $SR$ Latch with Control Input

 


C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	Q = 0; Reset state
1	1	0	Q = 1; Set state
1	1	1	Undefined

- Implemented using  $\overline{SR}$  latches
- $C$  acts as an enabler; otherwise the entire circuit functions as an  $SR$  latch



# *D* Latch

 


C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

- Implemented using  $\overline{S}\overline{R}$  latches
- *C*: Signals changes to the stored states; *D* the value to change to

# Flip-Flops


- Latches are **Transparent**  
input can be seen from outputs while control pulse is 1
- Flip-Flops are not **Transparent**  
Output state changes require changes of control signal

# *SR* Master-Slave Flip-Flop

 


- Constructed using *SR* latches, left Master, right Slave
- Output state changes require  $C = 0 \rightarrow C = 1 \rightarrow C = 0$  (Positive Pulse)

# *SR* Master-Slave Flip-Flop

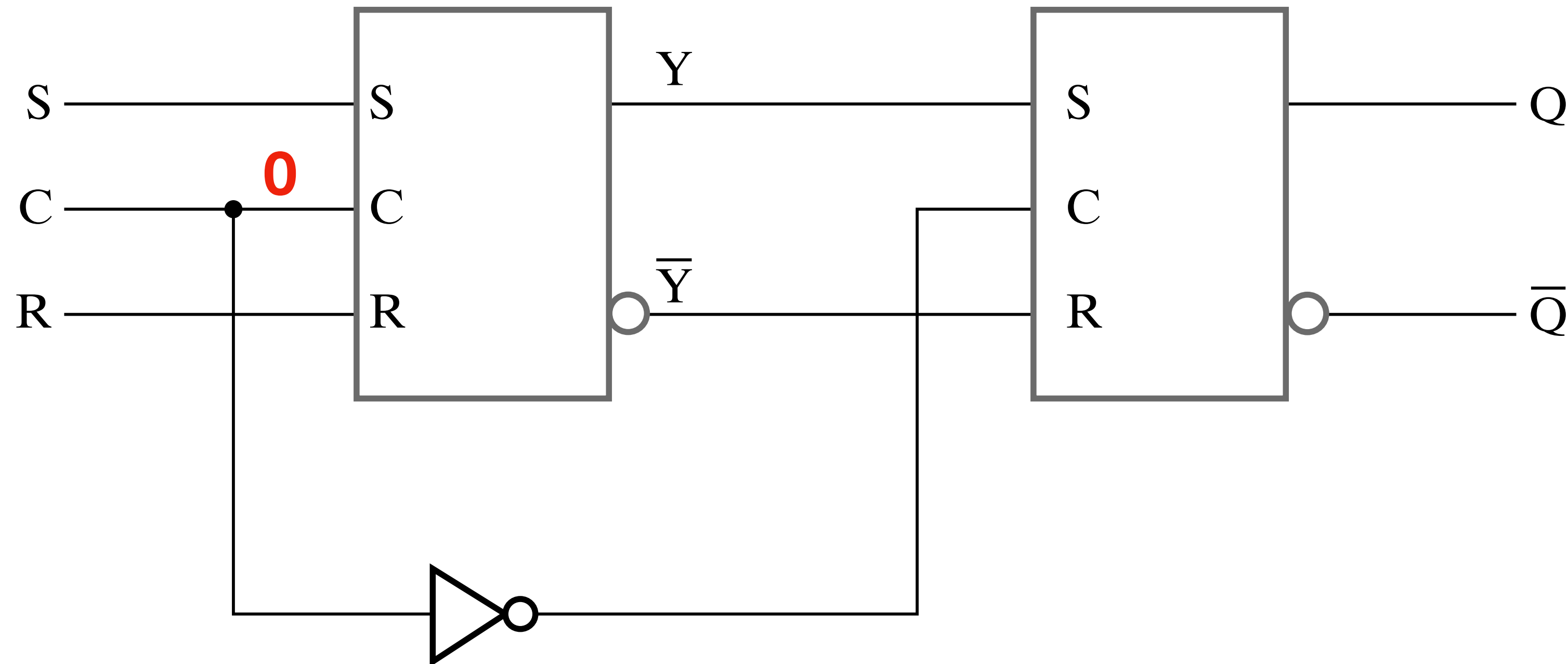


- Constructed using *SR* latches, left Master, right Slave
- Output state changes require  $C = 0 \rightarrow C = 1 \rightarrow C = 0$  (Positive Pulse)

# *SR* Master-Slave Flip-Flop

 


- Constructed using *SR* latches, left Master, right Slave
- Output state changes require  $C = 0 \rightarrow C = 1 \rightarrow C = 0$  (Positive Pulse)

# *SR* Master-Slave Flip-Flop

 


- Constructed using *SR* latches, left Master, right Slave
- Output state changes require  $C = 0 \rightarrow C = 1 \rightarrow C = 0$  (Positive Pulse)

# *D* Flip-Flop

 

- Replaces *SR* master in *SR* Master-Slave with *D* master Latch
- **Negative Edge Triggered *D*** (Flip-Flop):  $C = 1 \rightarrow C = 0$


# *D* Flip-Flop

 

- Replaces  $SR$  master in  $SR$  Master-Slave with  $D$  master Latch
- **Negative Edge Triggered  $D$  (Flip-Flop):**  $C = 1 \rightarrow C = 0$




# $D$ Flip-Flop

 

- Replaces  $SR$  master in  $SR$  Master-Slave with  $D$  master Latch
- **Negative Edge Triggered  $D$**  (Flip-Flop):  $C = 1 \rightarrow C = 0$


# $D$ Flip-Flop

 


- Replaces  $SR$  master in  $SR$  Master-Slave with  $D$  master Latch
- **Negative Edge Triggered  $D$**  (Flip-Flop):  $C = 1 \rightarrow C = 0$

# Summary

## Latches

 


SR

 

D with 1 Control

## Flip-Flops

 

Triggered D

# Sequential Circuit Analysis

State Table; State Diagram

Summary


# State Table

- Similar to truth table
  - Input, and Current states
  - Output and Next states

# State Table

Truth Table


X	Y	Z	F
0	0	0	0
0	1	0	1
1	0	0	0
1	1	0	0
0	0	1	0
0	1	1	1
1	0	1	1
1	1	1	1

 

# State Table

State Table

Present State	X	Y	Next State	F
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

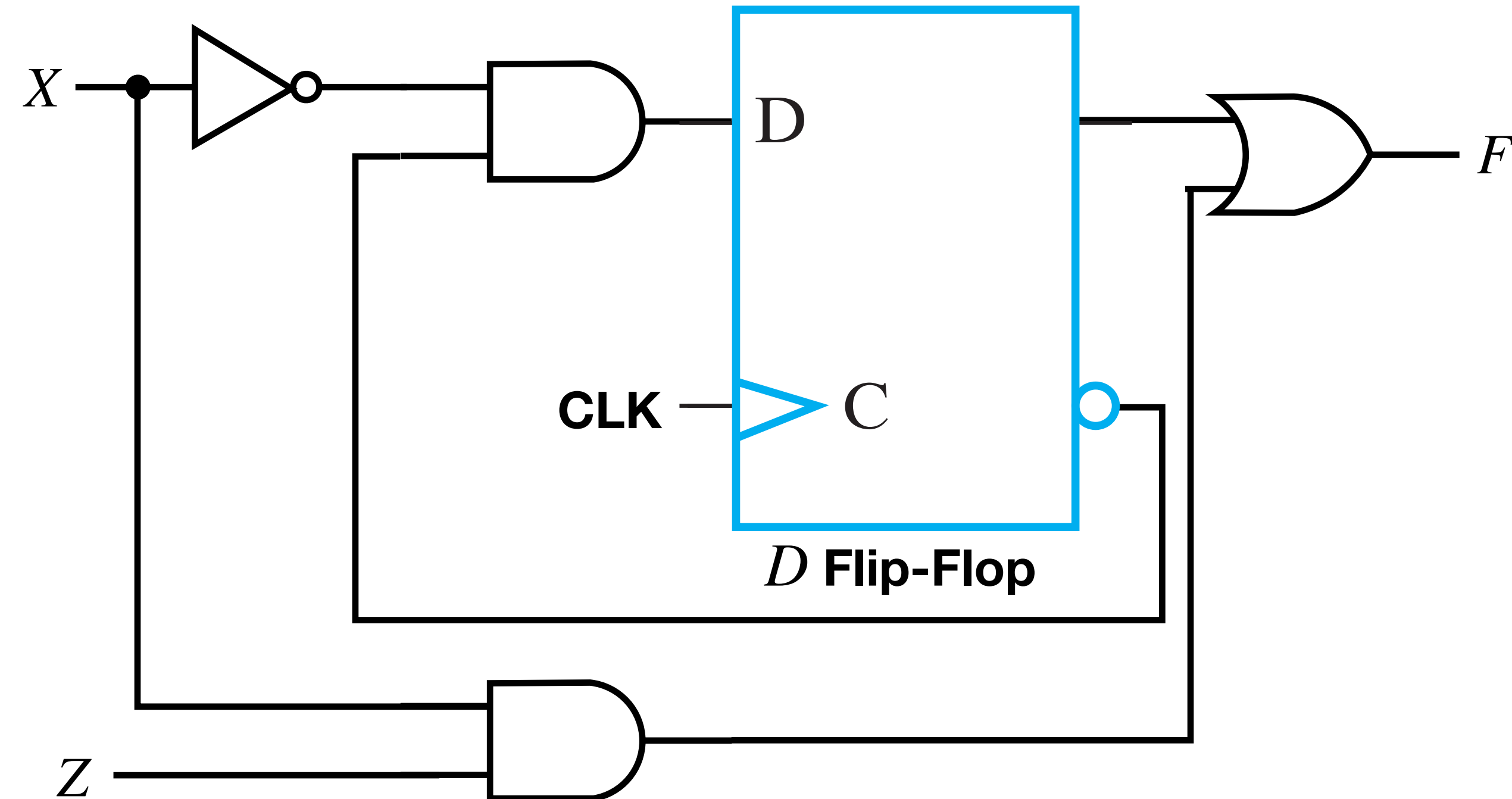


- When filling the state table, consider CLK = 0
- When CLK = 1, next state becomes current state

# State Table

State Table

Present State	X	Y	Next State	F
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

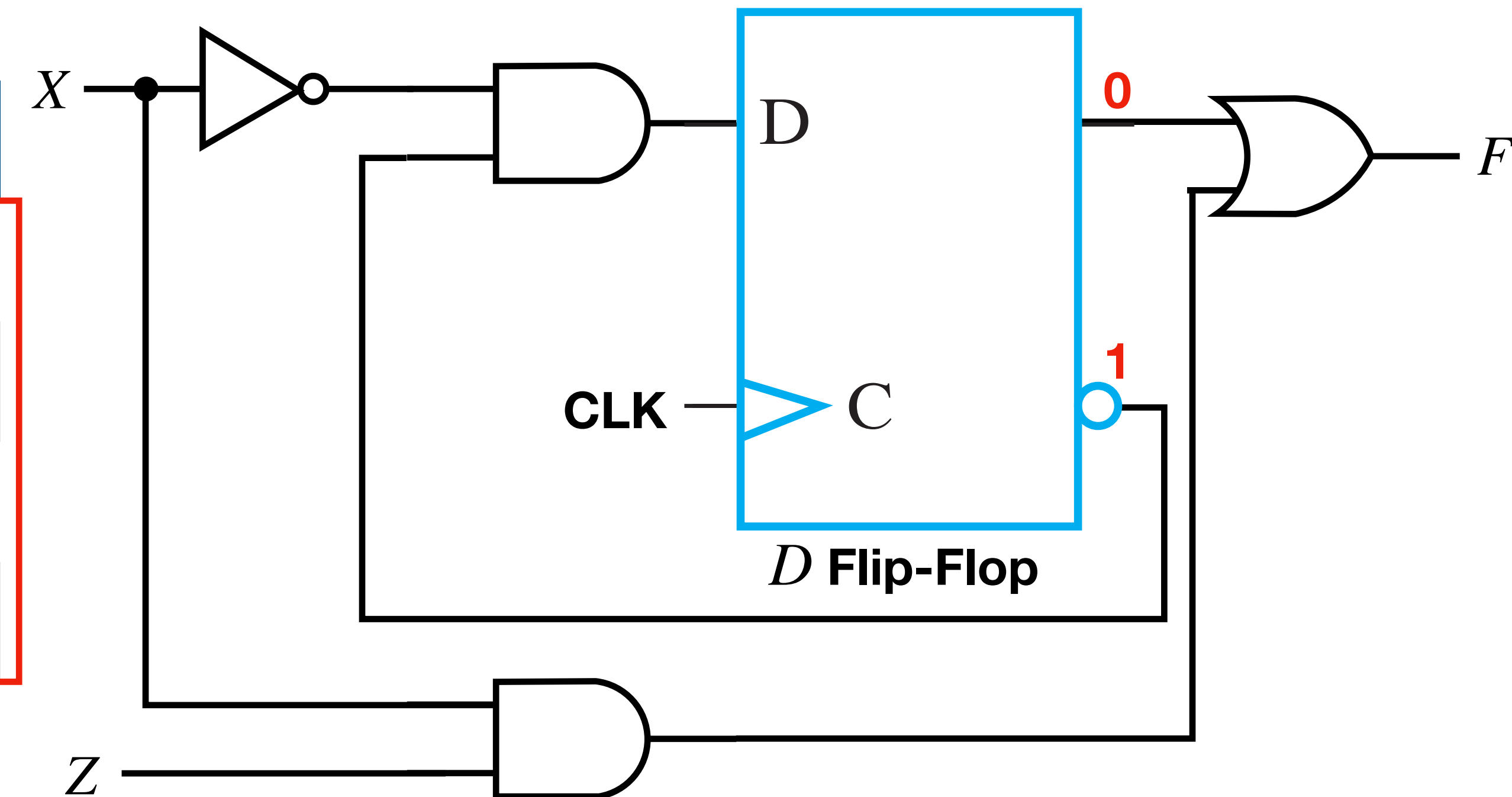


- When filling the state table, consider CLK = 0
- When CLK = 1, next state becomes current state



# State Table

State Table

Present State	X	Y	Next State	F
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

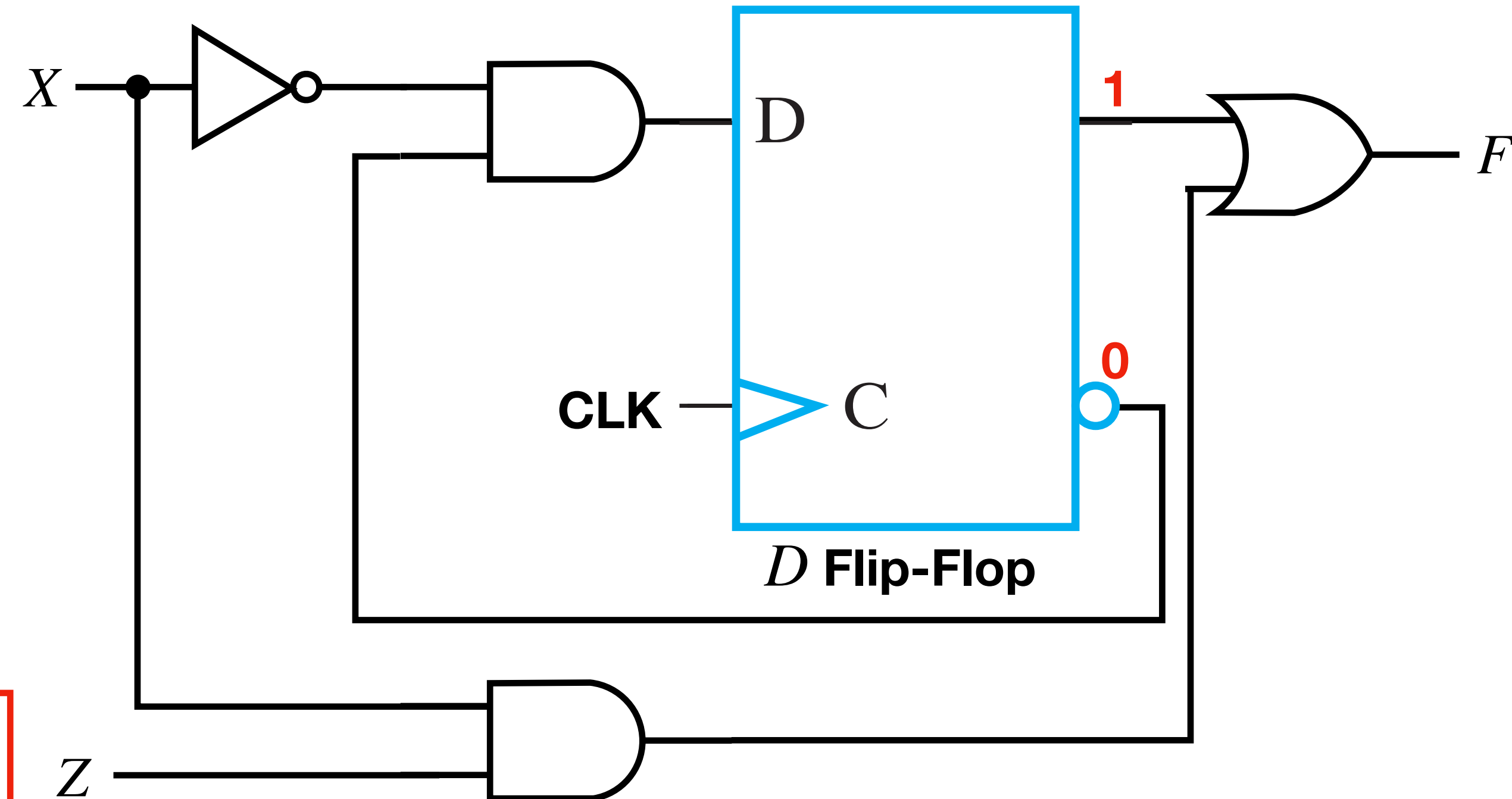


- When filling the state table, consider CLK = 0
- When CLK = 1, next state becomes current state

Example

# State Table

State Table

Present State	X	Y	Next State	F
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

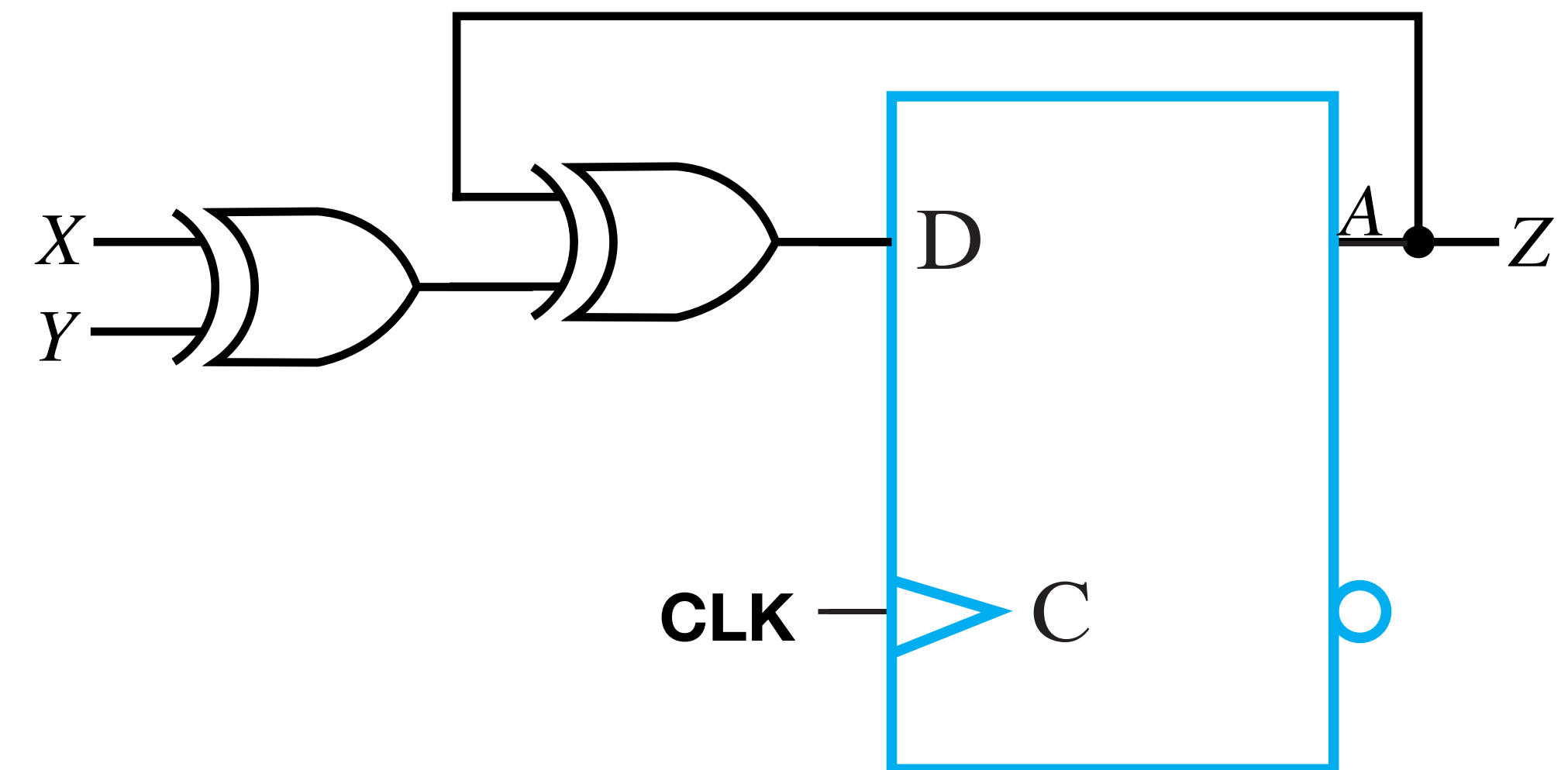


$$D_A = X \oplus Y \oplus A$$

- When filling the state table, consider CLK = 0
- When CLK = 1, next state becomes current state

# State Table

State Table

Present State	X	Y	Next State	F
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0		
1	0	1		
1	1	0		
1	1	1		

 


- When filling the state table, consider CLK = 0
- When CLK = 1, next state becomes current state

# State Table

State Table

Present State	X	Y	Next State	F
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0		
1	0	1		
1	1	0		
1	1	1		

 


- When filling the state table, consider CLK = 0
- When CLK = 1, next state becomes current state

# State Table

State Table

Present State	X	Y	Next State	F
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

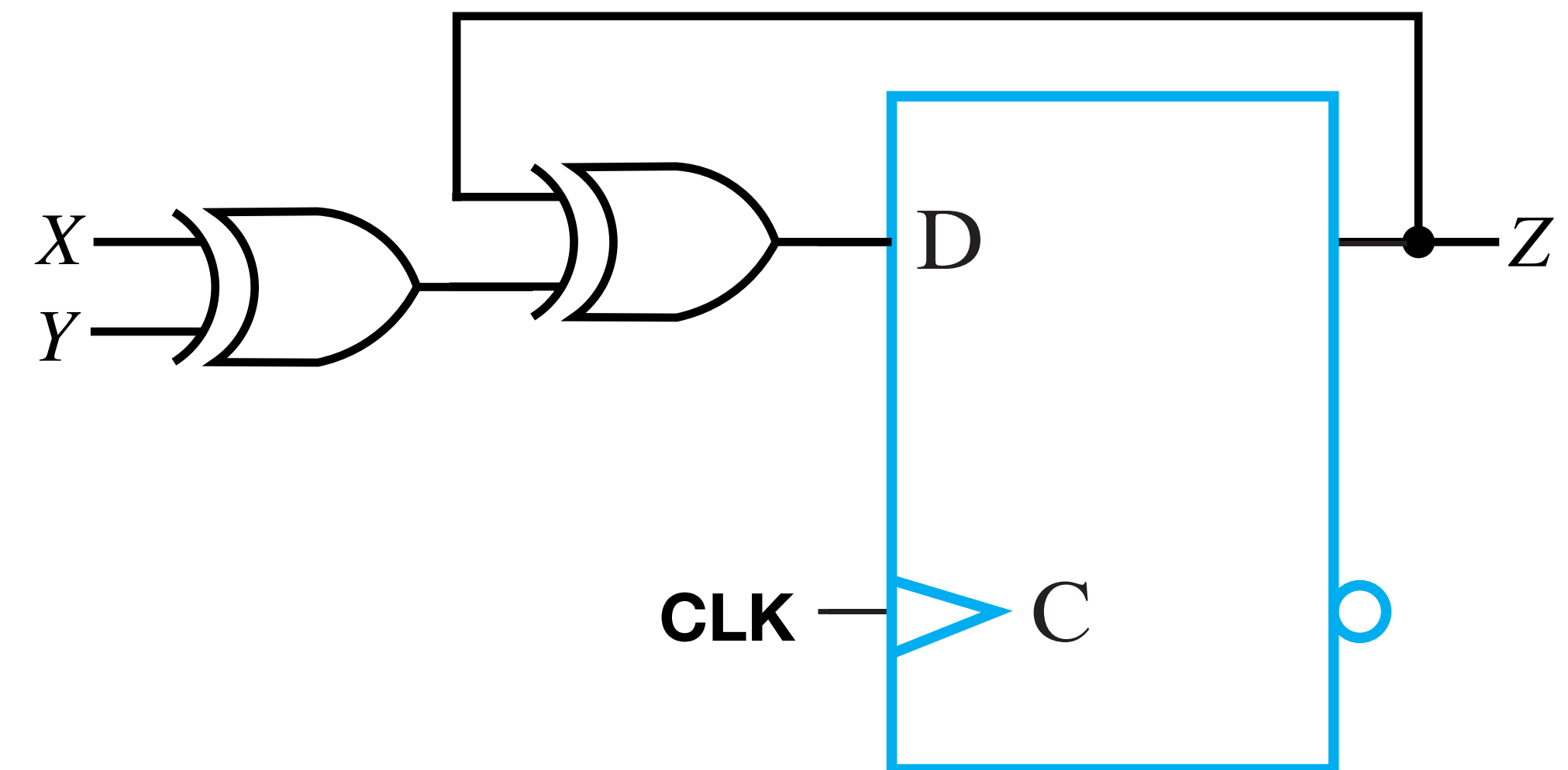

- When filling the state table, consider CLK = 0
- When CLK = 1, next state becomes current state

# State Table

State Table

Present State		X	Y	Next State		Z
A	B			A	B	
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			

...

$$D_A = \bar{X}A + XY$$

$$D_B = \bar{X}B + XA$$

$$Z = XB$$

- Draw circuit diagram
- Fill the 8 rows

Exercise

# State Table

- What happens when there are multiple flip-flops?
- Does it work with Latches?

# In Class Exercise 1

- A circuit with one  $D$  flip-flop:  $D_A = A \oplus X$
- Draw the circuit diagram
- Do the state table

State Table

Present State	$X$	Next State
0	0	
0	1	
1	1	
1	0	



# In Class Exercise 2

- A circuit with 2  $D$  flip-flops:  $D_A = A \oplus B$ ,  $D_B = \bar{B} \cdot X$ ,  $F = \bar{A}B$


State Table

- Do the state table

Present State		X	Next State		F
A	B		A	B	
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

 
# State Diagram

- Similar to state table
- Models state transitions
- A state is represented in a bubble



- Directed links between bubbles: the input used to perform transition  
Source: **present** state, Target: **next** state (next **CLK**); (optional output  $F$ )



 
- State bubble with state as  $S$  (optional output  $F$ )



# State Diagram

State Table

Present State	X	Y	Next State	F
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

  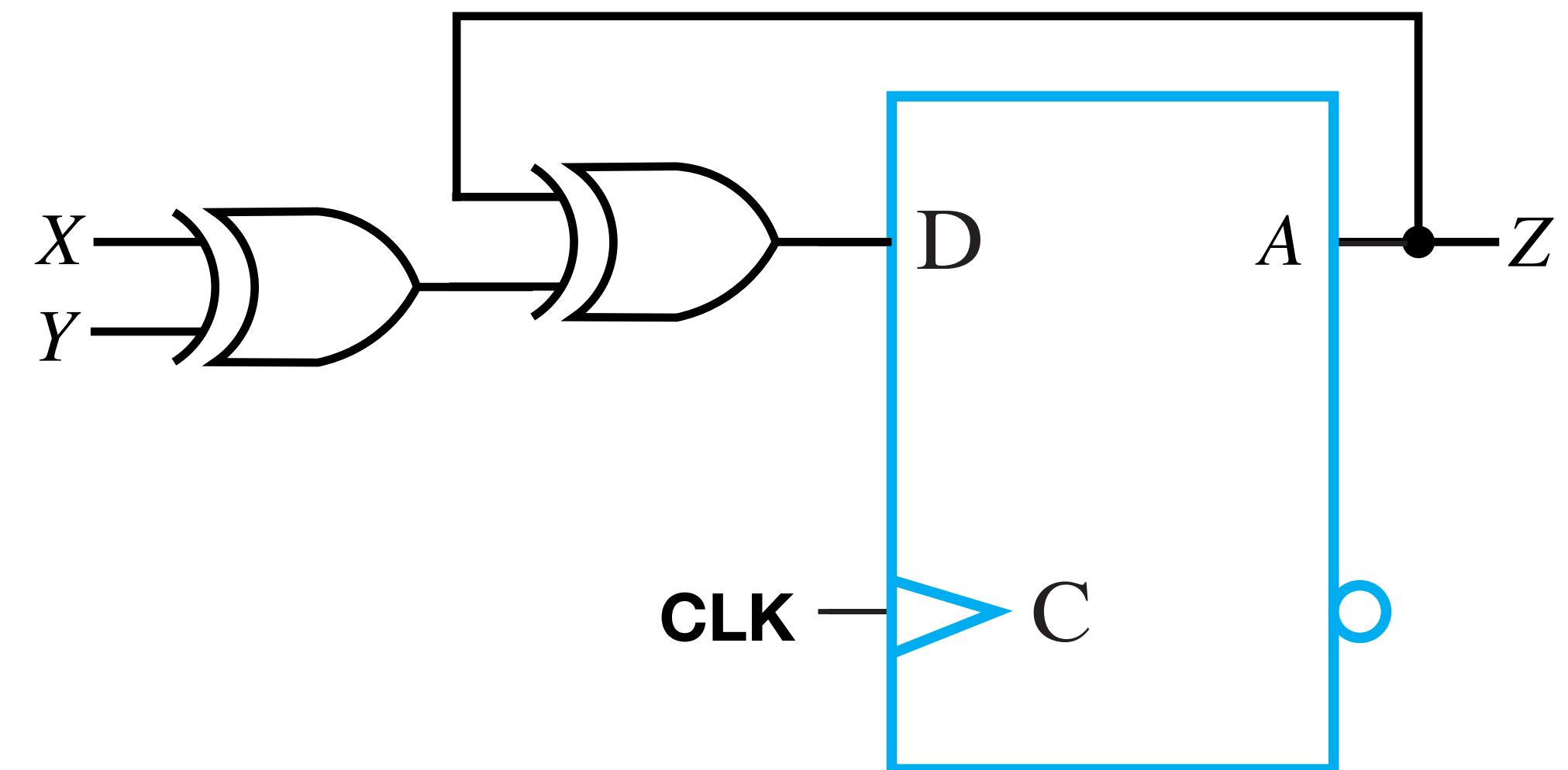

A single state bubble






A single link

Concept

# State Diagram

State Table

Present State	X	Y	Next State	F
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

  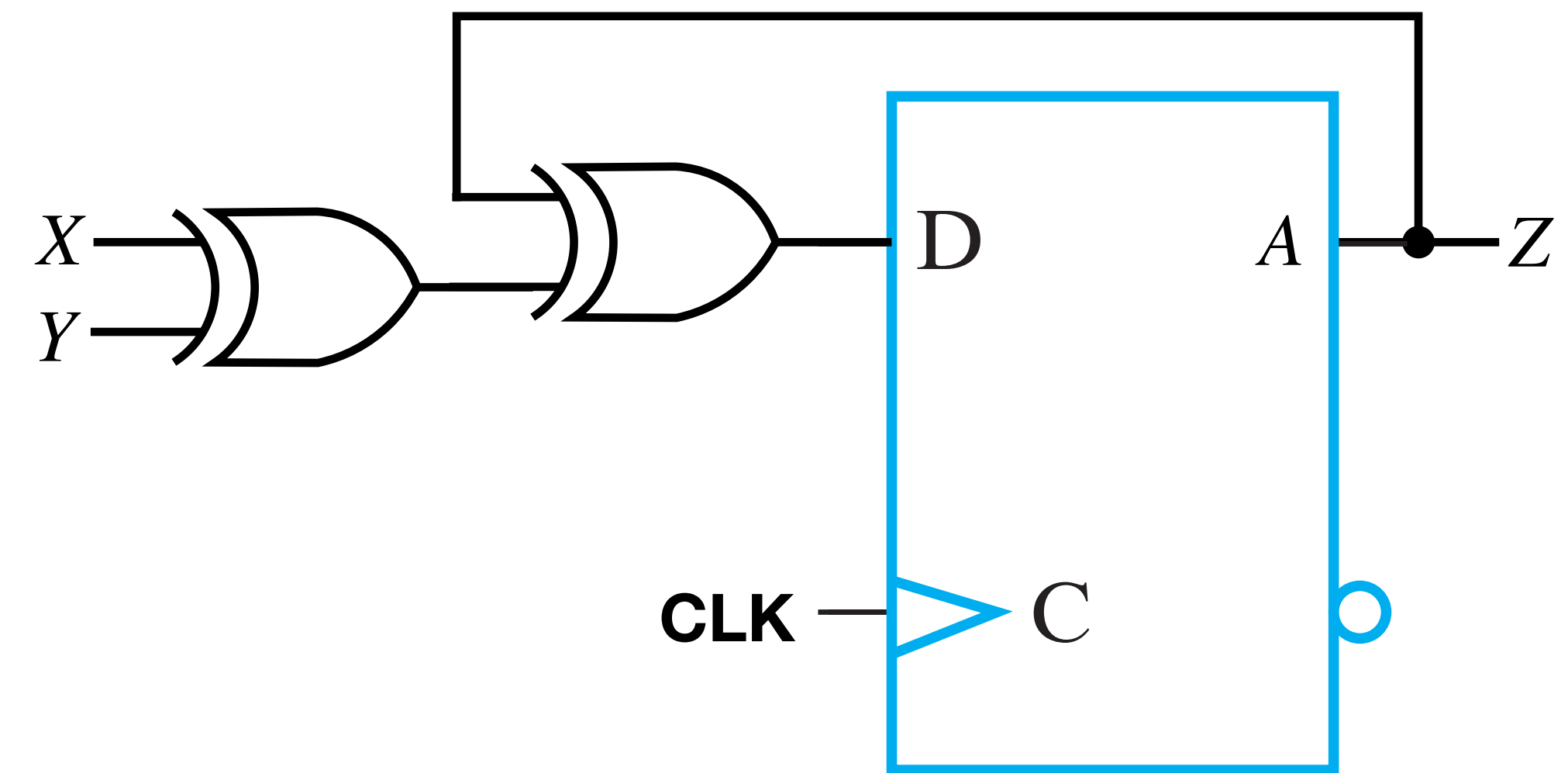

A single state bubble






A single link

# State Diagram

State Table

Present State	X	Y	Next State	Z
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

   


A single state bubble



A single link

Concept

# State Diagram

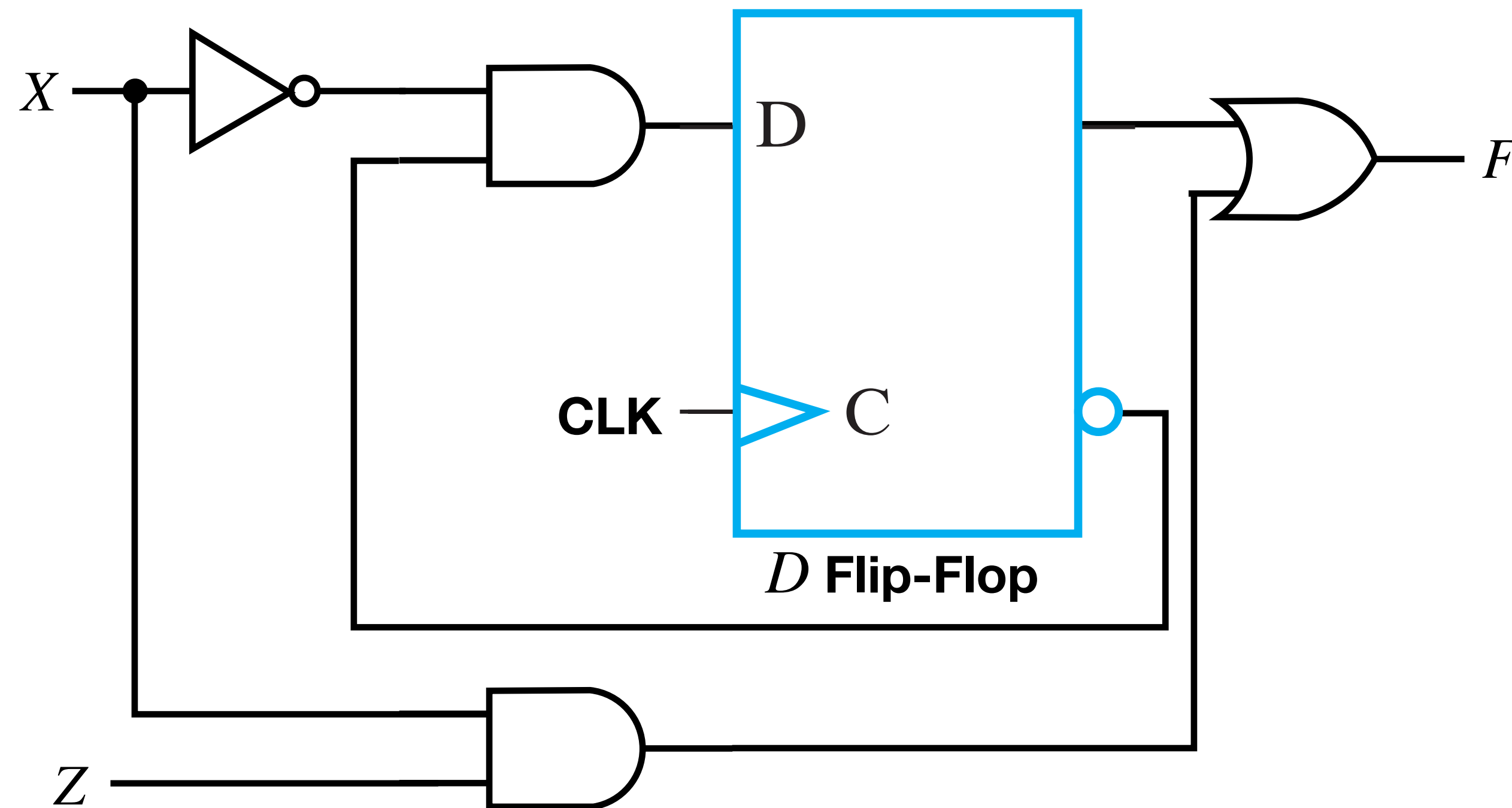

# State Diagram

- Draw the state diagram for:  $D_A = \bar{X}A + XY$ ,  $D_B = \bar{X}B + XA$ ,  $Z = XB$

# In Class Exercise 1

- A circuit with one  $D$  flip-flop:  $D_A = A \oplus X$
- Draw the state diagram

State Table

Present State	$X$	Next State
0	0	0
0	1	1
1	0	1
1	1	0



# In Class Exercise 2

- A circuit with 2  $D$  flip-flops:  $D_A = A \oplus B$ ,  $D_B = \bar{B} \cdot X$ ,  $F = \bar{A}B$

State Table

- Do the state diagram

Present State		X	Next State		F
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	1
0	1	1	1	0	1
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	0	0	0

# LogicWorks Exercise

- Implement  $D$  flip flop using  $D$  latch and  $SR$  latch  
Save it as a component in your library
- Implement circuit  $D_S = X \oplus Y \oplus S$ , where  $D_S$  is a  $D$  flip flop
- Implement  $D_A = \bar{X}A + XY$ ,  $D_B = \bar{X}B + XA$ ,  $Z = XB$
- Draw the state table and diagram, and verify your table with LogicWorks

