



27.07.20 12:40

CSCI 150

Introduction to Digital and Computer System Design

Lecture 5: Registers II



Jetic Gū
2020 Summer Semester (S2)

Overview

- Focus: Fundamentals of Complex Digital Circuit Design
- Architecture: von Neumann
- Textbook v4: Ch7 7.6; v5: Ch6 6.6
- Core Ideas:
 1. Implementation of Register Microoperations

Register Transfer Operations

	Operator	Example
Assignment	<code><=</code>	<code>ax <= 12h</code>
Reg. Transfer	<code><=</code>	<code>ax <= bx</code>
Addition	<code>+</code>	<code>ax + bx</code>
Subtraction	<code>-</code>	<code>ax - bx</code>
Shift Left	<code>sll</code>	<code>ax sll 2</code>
Shift Right	<code>srl</code>	<code>ax srl 2</code>

	Operator	Example
Bitwise AND	<code>and</code>	<code>ax and bx</code>
Bitwise OR	<code>or</code>	<code>ax or bx</code>
Bitwise NOT	<code>not</code>	<code>not ax</code>
Bitwise XOR	<code>xor</code>	<code>ax xor bx</code>
Vectors		<code>ax(3 down to 0)</code> <code>ax(3 down to 0)</code>
Concatenate	<code>&</code>	<code>ax(7 down to 4)</code> <code>&ax(3 down to 0)</code>


Implementation of Datapath I

Architecture

Datapath and Control Unit

1. ALU connected to Reg for 1st input
2. ALU connected to Reg for 2nd input
3. ALU connected to Reg to store result
4. CU tells ALU which register to take as 1st input
5. CU tells ALU which register to take as 2nd input
6. CU tells ALU which operation to do
7. CU tells which Reg to store result in
Using decoder and EN on each Register

Red: Address
Green: Mode

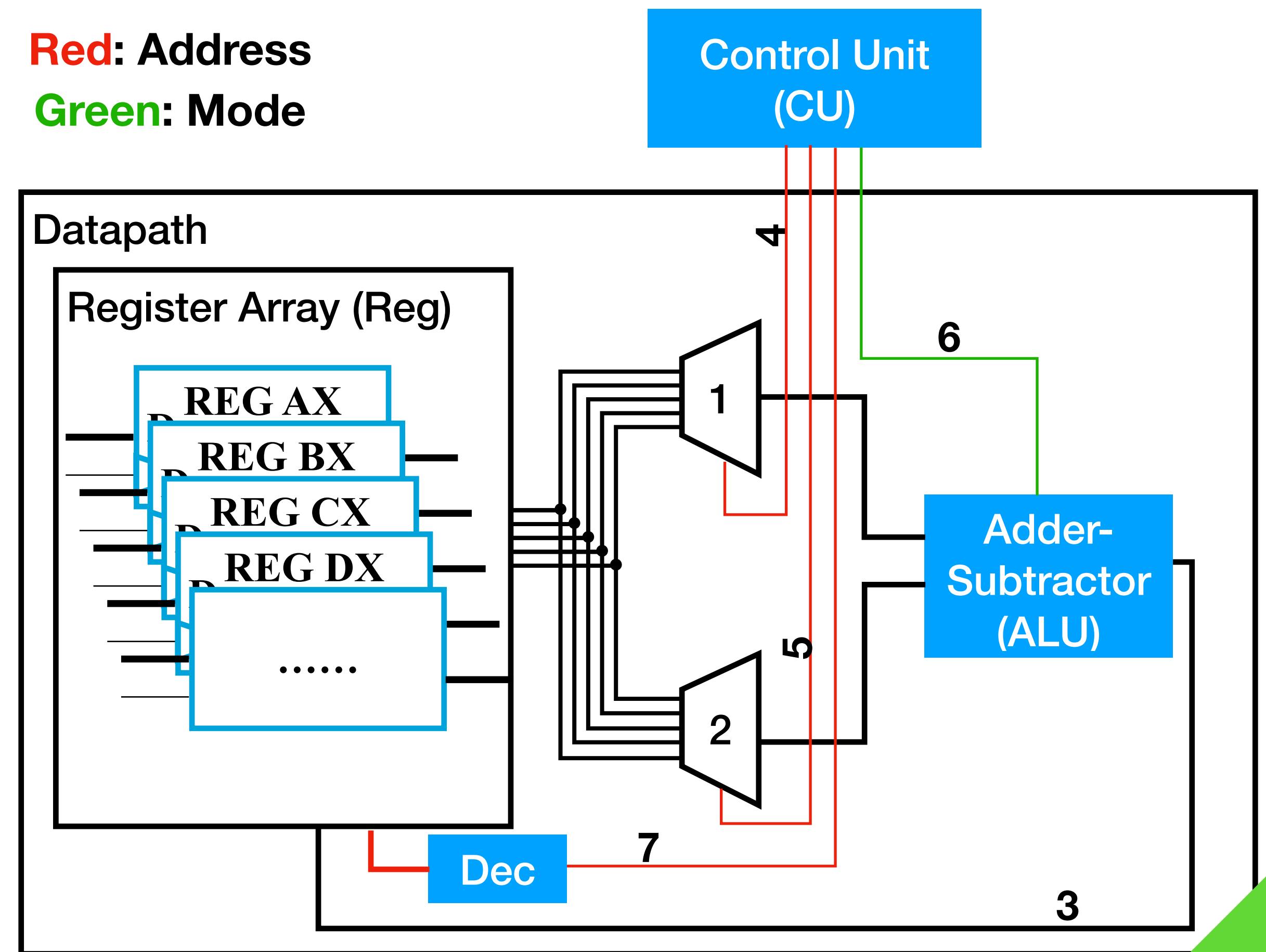

Single Register Microoperations

- In reality, a single circuit is designed to do multiple stuff
 - a CPU can perform thousands/millions of different types of instructions
- How to design it?
- Let's start with single register Microoperations
 - Input: one of the registers; Output: another one of the registers;


Single Register Microoperations

	Operator	Example		Operator	Example
Assignment	<code><=</code>	<code>ax <= 12h</code>	Bitwise AND	<code>and</code>	<code>ax and bx</code>
Reg. Transfer	<code><=</code>	<code>ax <= bx</code>	Bitwise OR	<code>or</code>	<code>ax or bx</code>
Addition	<code>+</code>	<code>ax + bx</code>	Bitwise NOT	<code>not</code>	<code>not ax</code>
Subtraction	<code>-</code>	<code>ax - bx</code>	Bitwise XOR	<code>xor</code>	<code>ax xor bx</code>
Shift Left	<code>sll</code>	<code>ax sll 2</code>	Vectors		<code>ax(3 down to 0) ax(3 down to 0)</code>
Shift Right	<code>srl</code>	<code>ax srl 2</code>	Concatenate	<code>&</code>	<code>ax(7 down to 4) &ax(3 down to 0)</code>

Select Registers for Input

- Suppose we have 4 registers, we want to select one to provide input to a functional block

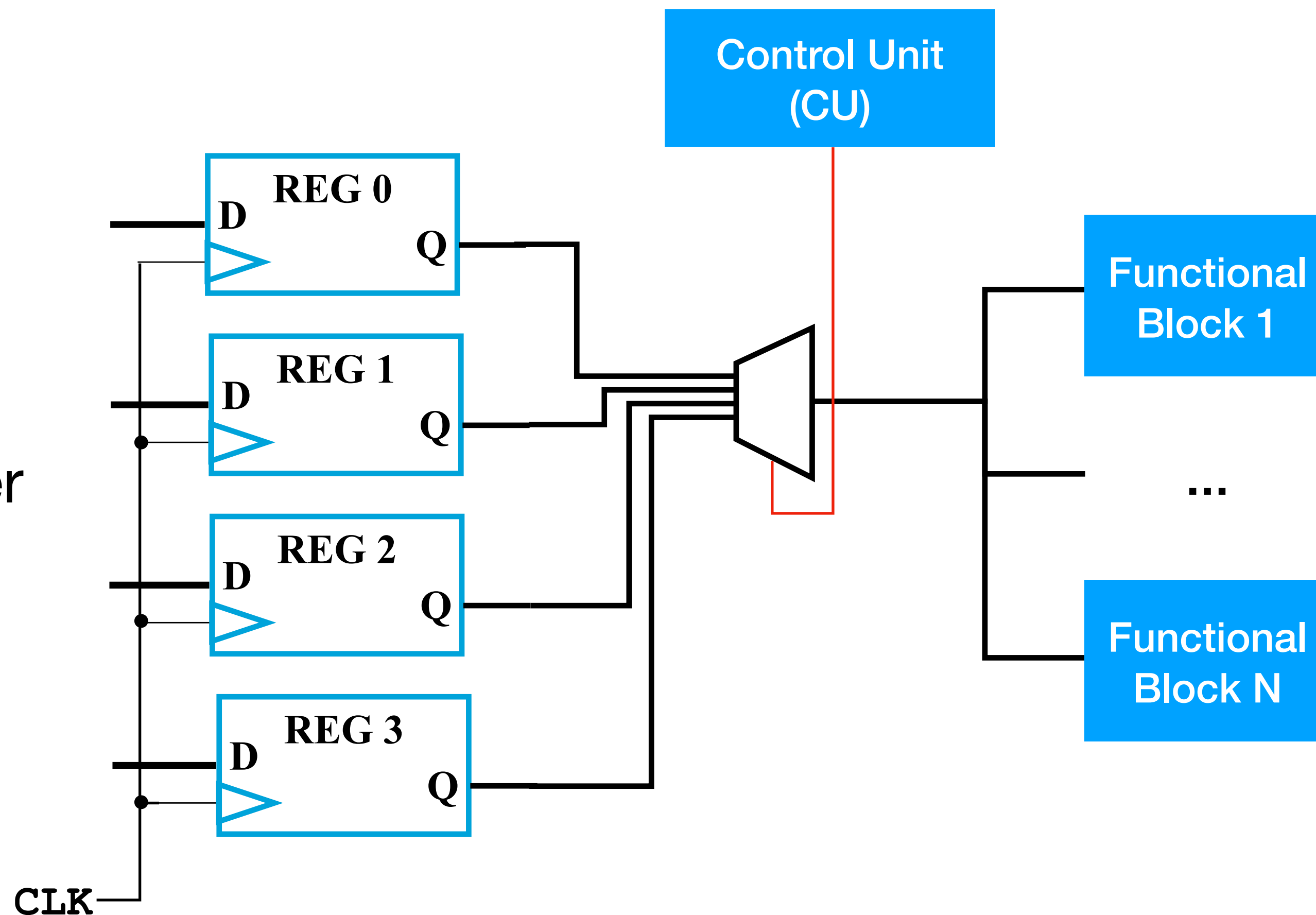
- Suppose 2^n registers, each 8-bit
- What kind of multiplexer should be used?
- How many bits on the red wire?



Select Registers to Output

- Suppose we have 4 registers, we want to select one to store our output

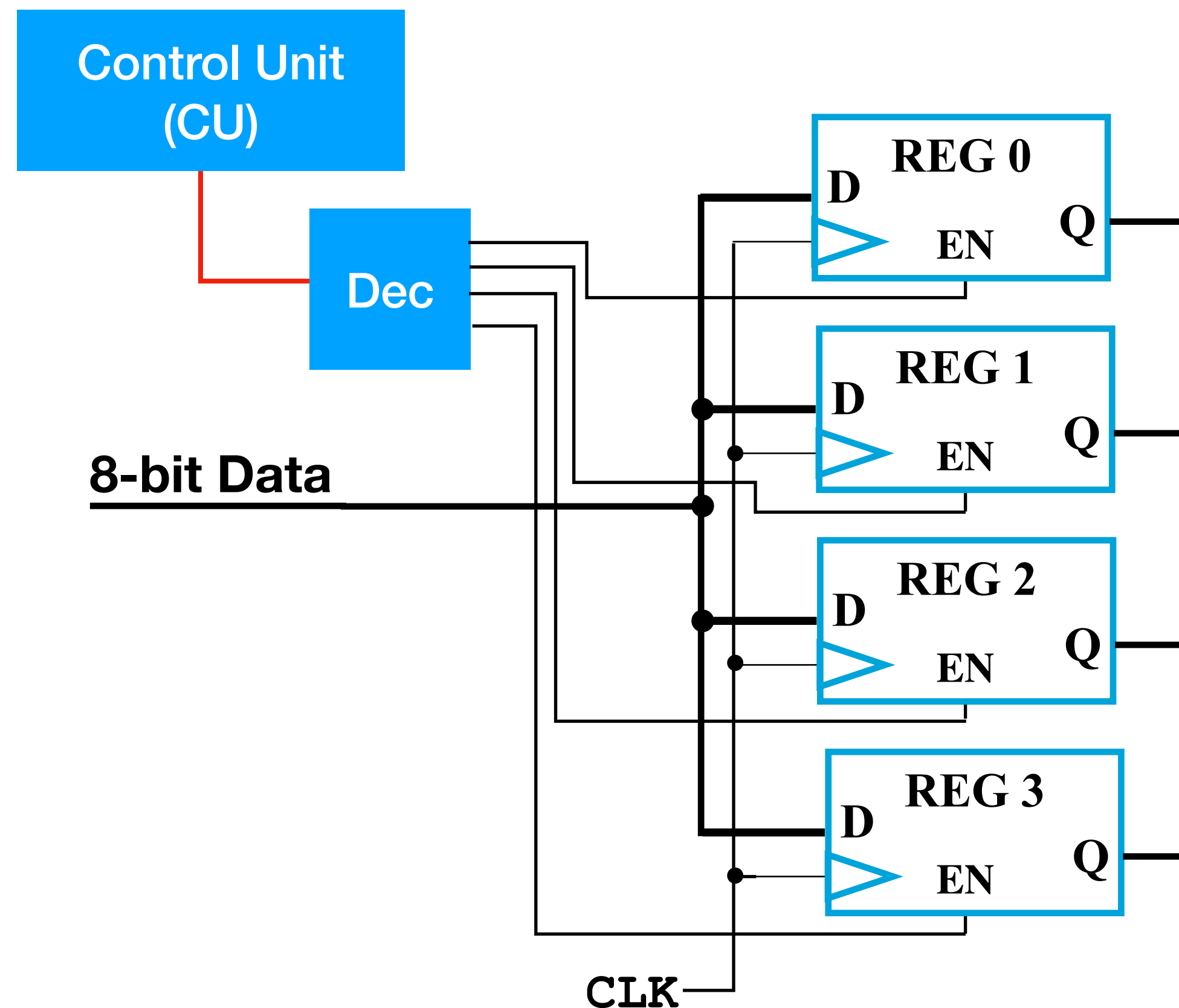- Suppose 2^n registers, each 8-bit
- What kind of decoder should be used?
- How many bits on the red wire?



Single Register Microoperations

- Assignment
e.g. `ax <= 12h`
- Register Transfer
e.g. `ax <= bx`
- Shift left by $X < 8$
e.g. `ax sll X`
- Shift right by $X < 8$
e.g. `ax srl X`
- Bitwise NOT
e.g. `not ax`
- Vector by
 $0 \leq X \leq Y < 8$
e.g. `ax (Y down to X)`
- Rotate left by $X < 8$
e.g. `ax rll X`
- Rotate right by $X < 8$
e.g. `ax rrl X`

Functional
Block 1

...

Functional
Block N

Single Register Microoperations

0. Assignment

e.g. `ax <= 12h`

1. Register Transfer

e.g. `ax <= bx`

2. Shift left by $X < 8$

e.g. `ax sll X`

2. Shift right by $X < 8$

e.g. `ax srl X`

3. Bitwise NOT

e.g. `not ax`

4. Vector by

$0 \leq X \leq Y < 8$

e.g. `ax (Y down to X)`

5. Rotate left by $X < 8$

e.g. `ax rll X`

5. Rotate right by $X < 8$

e.g. `ax rrl X`

Functional
Block 1

...

Functional
Block N

Example

Single Register Microoperations

0. Assignment

e.g. `ax <= 12h`

1. Register Transfer

e.g. `ax <= bx`

2. Shift left by $X < 8$

e.g. `ax sll X`

2. Shift right by $X < 8$

e.g. `ax srl X`

3. Bitwise NOT

e.g. `not ax`

4. Vector by

$0 \leq X \leq Y < 8$

e.g. `ax (Y down to X)`

5. Rotate left by $X < 8$

e.g. `ax rll X`

5. Rotate right by $X < 8$

e.g. `ax rrl X`

0. Assign.

1. Transfer

2. Shift L/R

3. NOT

4. Vector

5. Rotate L/R


Example

Single Register Microoperations

Red: Address

Green: Mode

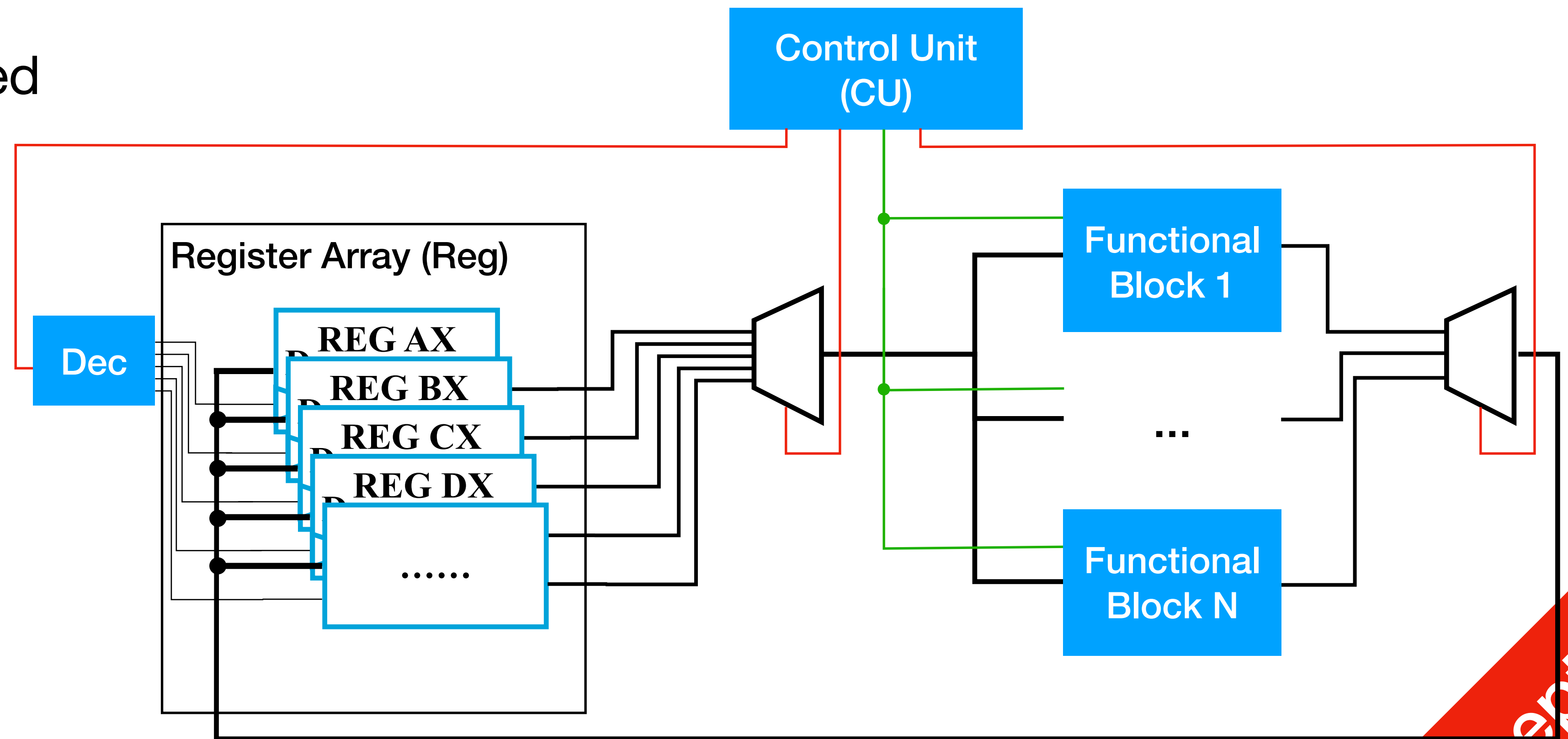- **Select** Input REG to be fed into Processing Blocks
- Select **mode** for Processing Blocks
- **Select** Processing Block for output to REG
- **Select** Receiving REG




Multiple Register Microoperations

	Operator	Example		Operator	Example
Assignment	<code><=</code>	<code>ax <= 12h</code>	Bitwise AND	<code>and</code>	<code>ax and bx</code>
Reg. Transfer	<code><=</code>	<code>ax <= bx</code>	Bitwise OR	<code>or</code>	<code>ax or bx</code>
Addition	<code>+</code>	<code>ax + bx</code>	Bitwise NOT	<code>not</code>	<code>not ax</code>
Subtraction	<code>-</code>	<code>ax - bx</code>	Bitwise XOR	<code>xor</code>	<code>ax xor bx</code>
Shift Left	<code>sll</code>	<code>ax sll 2</code>	Vectors		<code>ax(3 down to 0)</code> <code>ax(3 down to 0)</code>
Shift Right	<code>srl</code>	<code>ax srl 2</code>	Concatenate	<code>&</code>	<code>ax(7 down to 4)</code> <code>&ax(3 down to 0)</code>

Concept

Multiple Register Microoperations

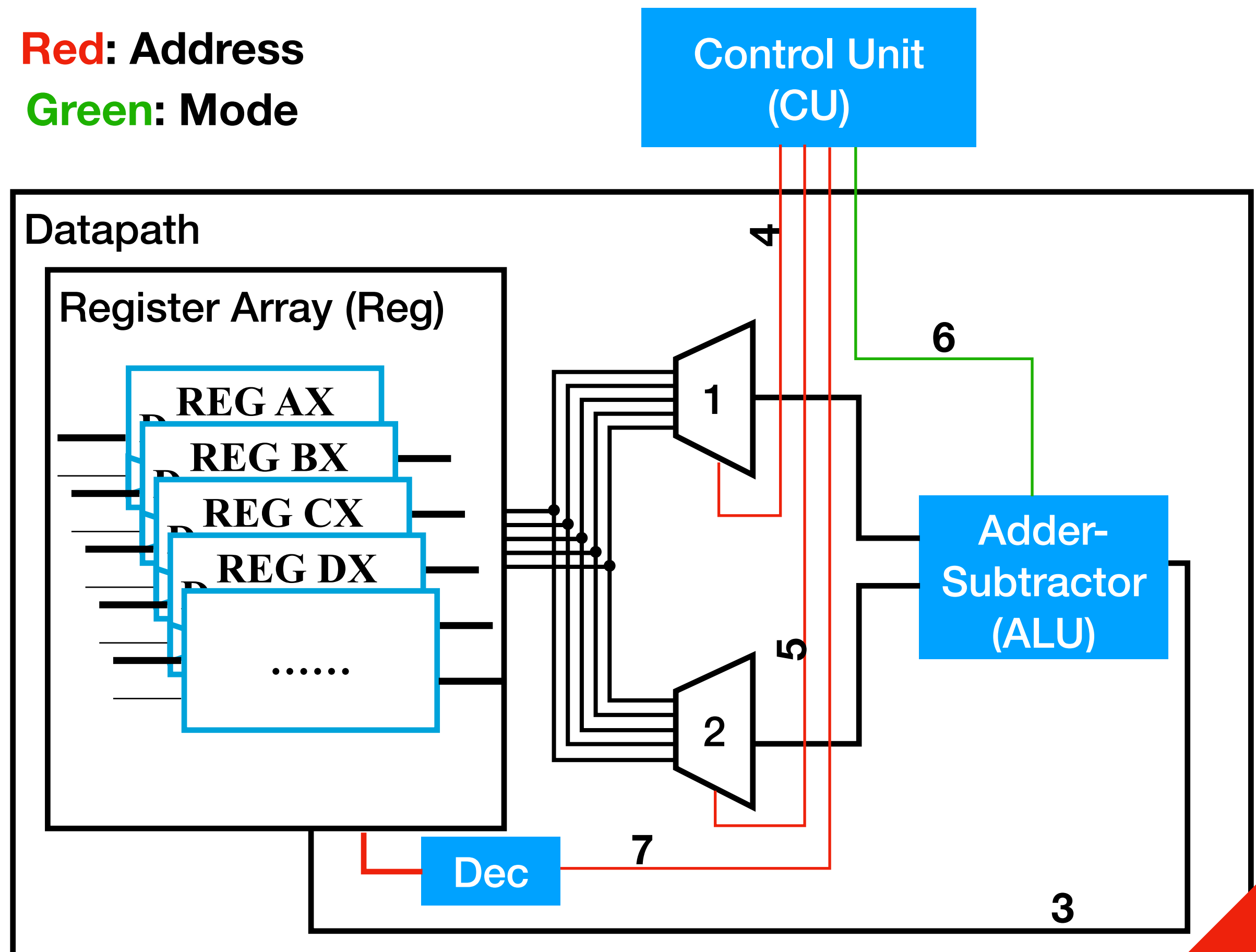
- Extension: how to incorporate more multiple register functional blocks?
- Extension: how to incorporate more single register functional blocks?



Example Datapath Question 1

- The control unit selects between 4 operations A, B, C, D.
- A, B, C, D each takes 1/1/2/2 register(s) as input and outputs to 1 register
- A, B, C, D doesn't have additional mode selections
- Specify the control unit interface to the datapath
- Draw the circuit diagram of such datapath with a register array

Example Datapath Question 1

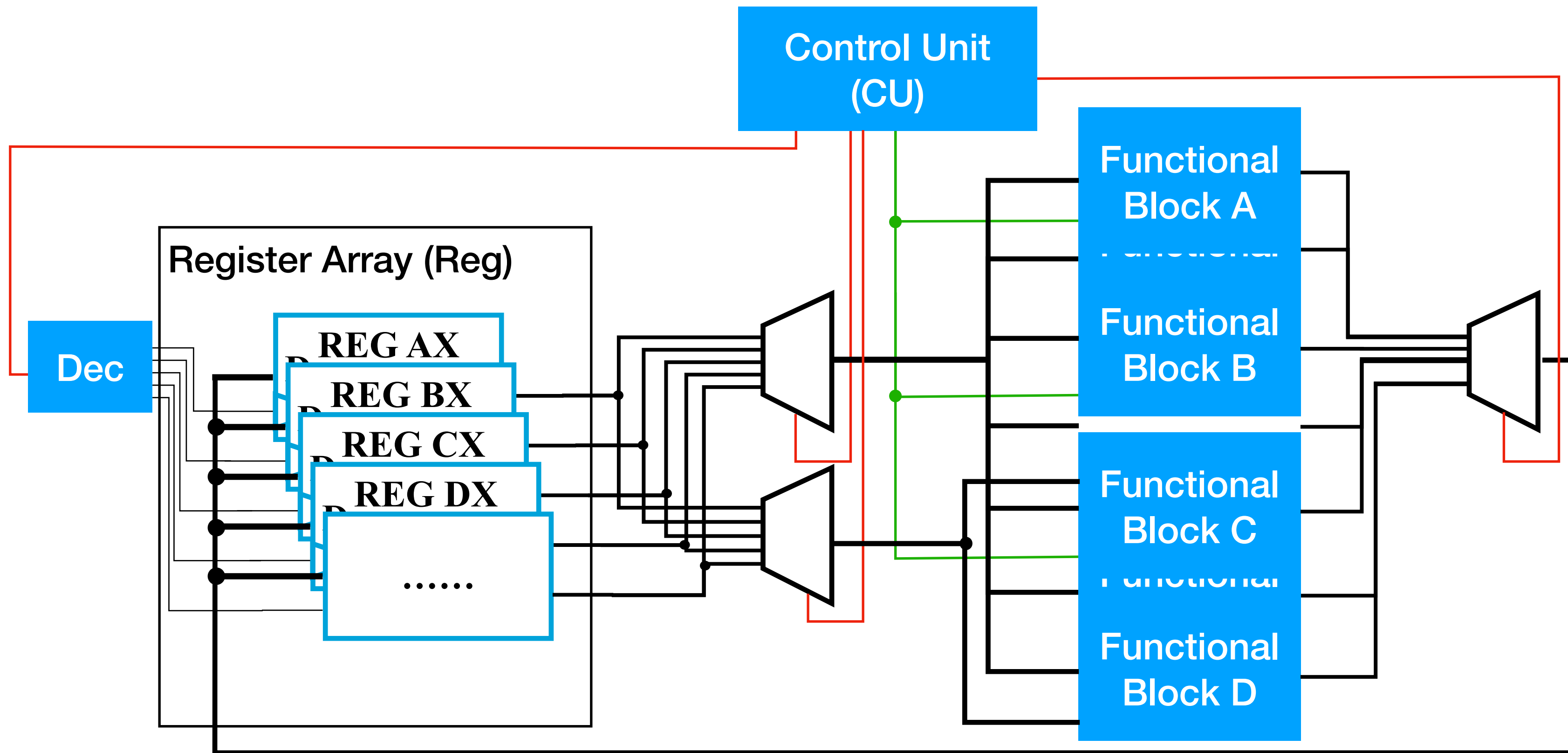

Exercise