



05.08.20 12:34

CSCI 150

Introduction to Digital and Computer System Design

Lecture 4: Sequential Circuit Flashback



Jetic Gū
2020 Summer Semester (S2)

Overview

- Focus: Sequential Circuit Exercises
- Architecture: von Neumann
- Textbook v4: Ch5; v5: Ch4
- Core Ideas:
 1. Latches and Flip-Flips
 2. State Diagram and State Table
 3. Exercise


How to study for CSCI 150

- You have to study
 - Attend lectures and pay attention
 - Do you OWN Homework and Labs
 - ASK if you have questions


Concept

Latches and Flip-Flops

Latches

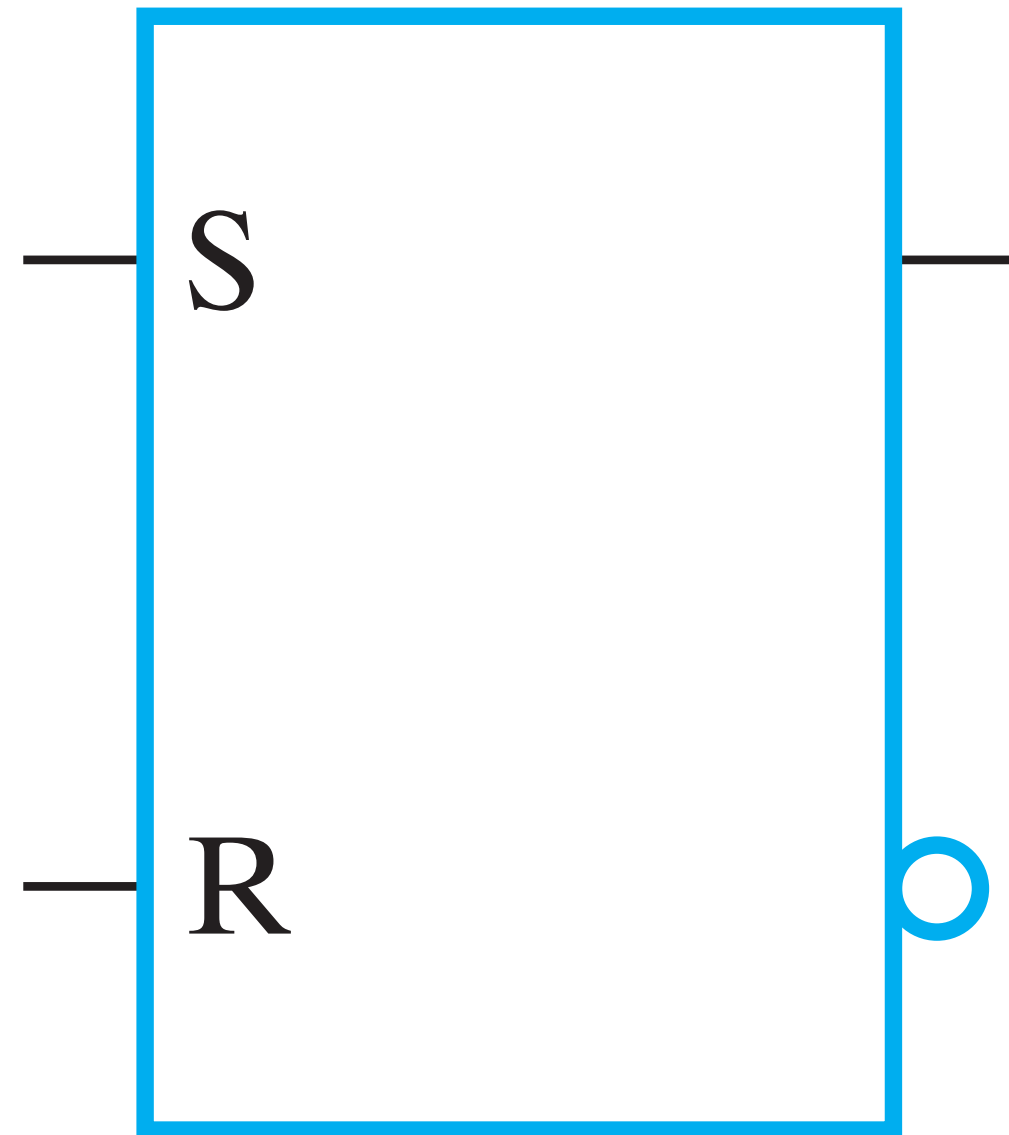


SR

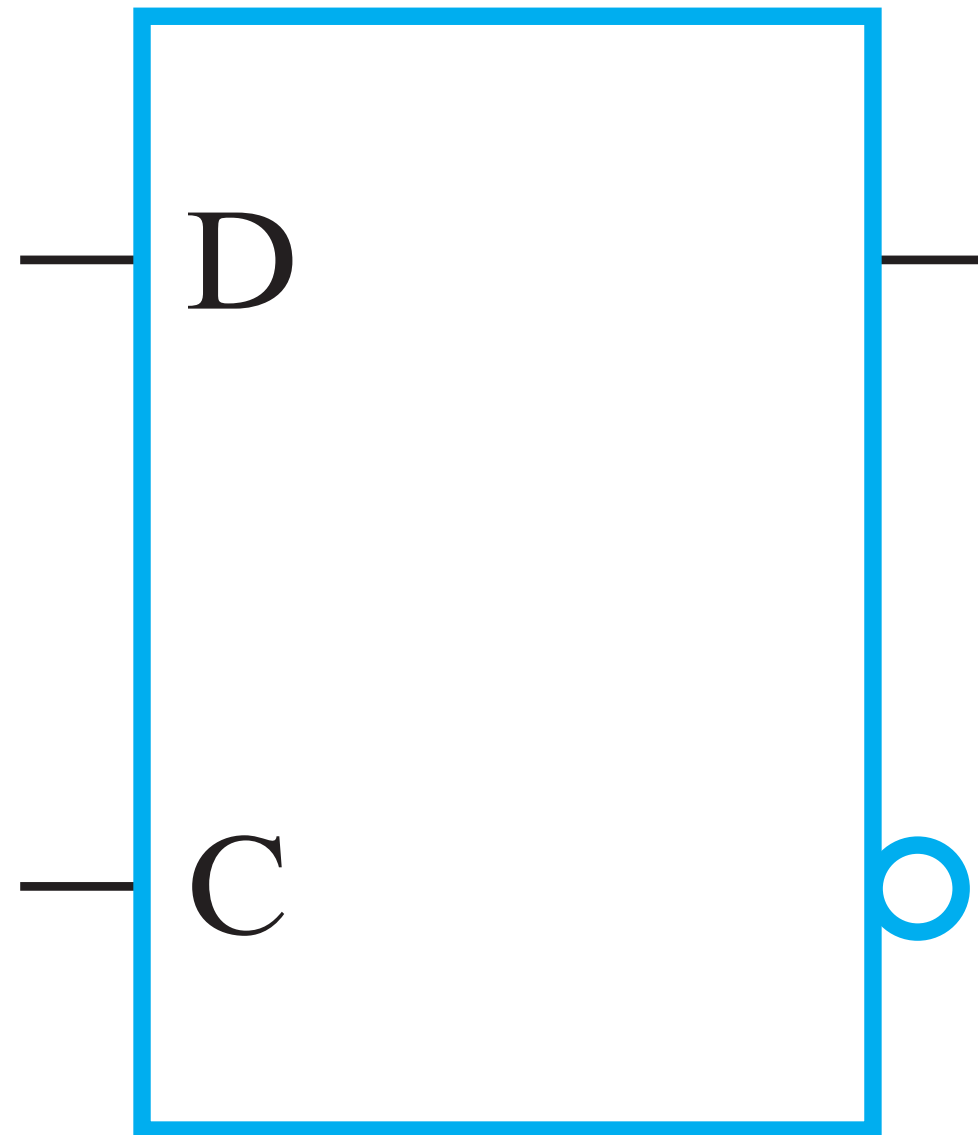

D with 1 Control



Flip-Flops

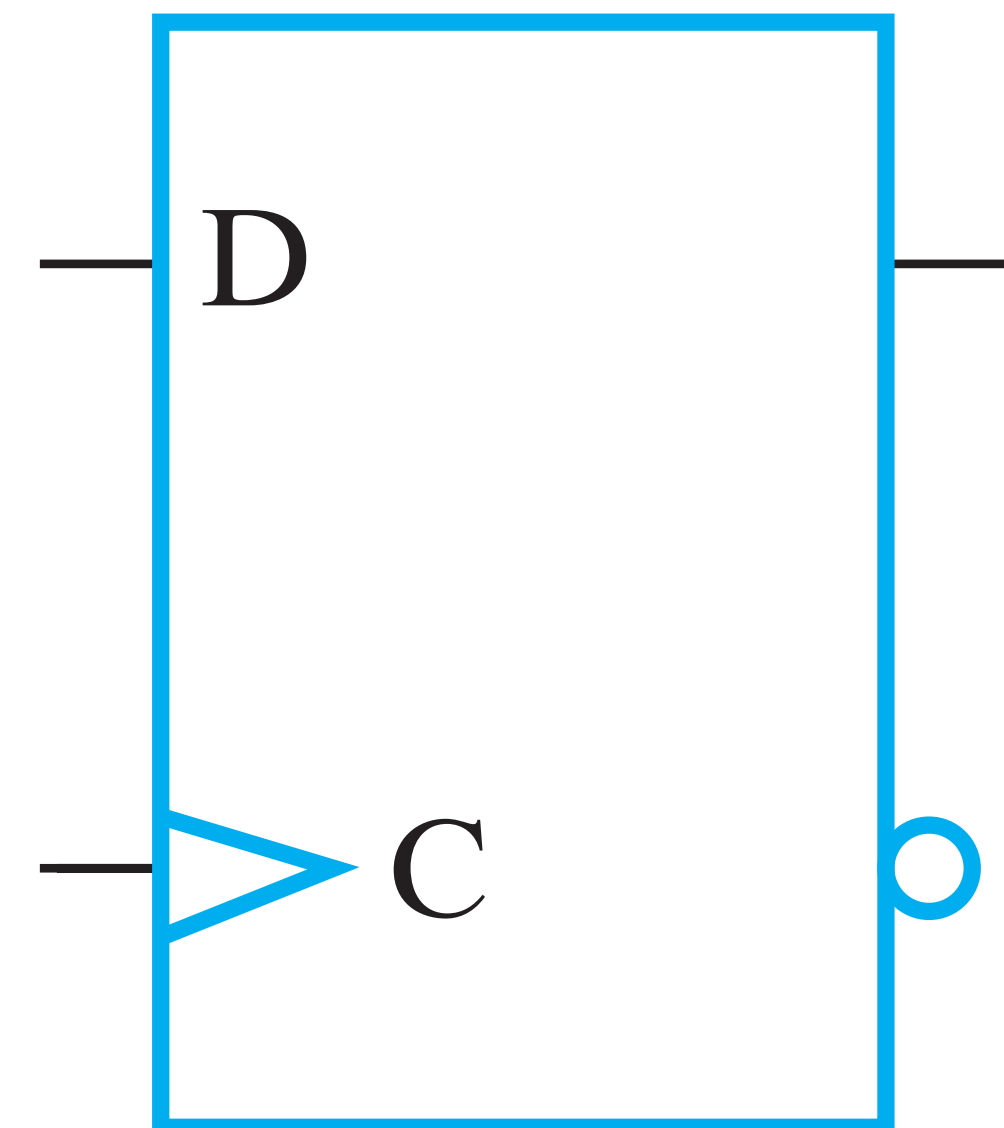


Triggered D

Latches and Flip-Flops

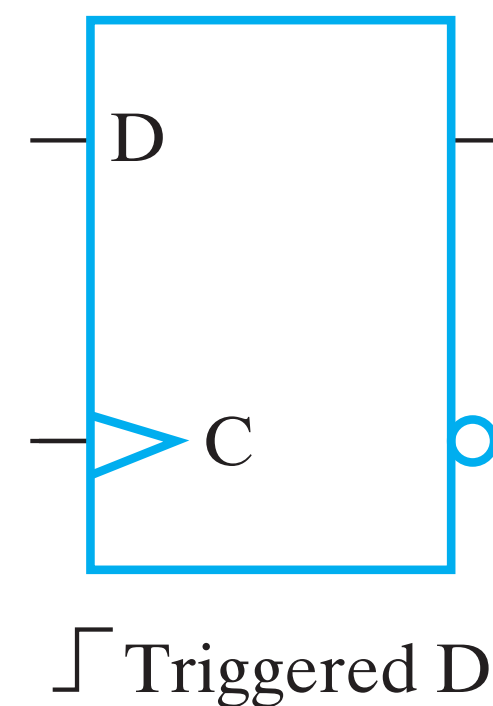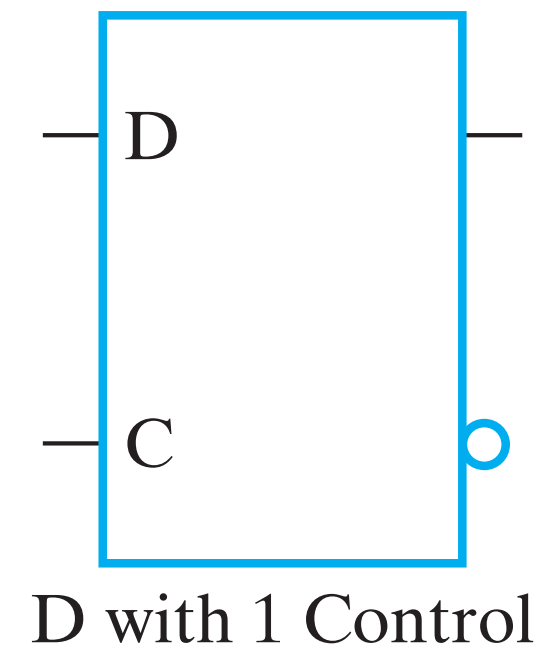- Latches are Transparent
 - Internal values change immediately after C pin receives positive signal
- Flip-Flops
 - Two latches: one changes immediately, the other changes at the next step




D Flip-Flop

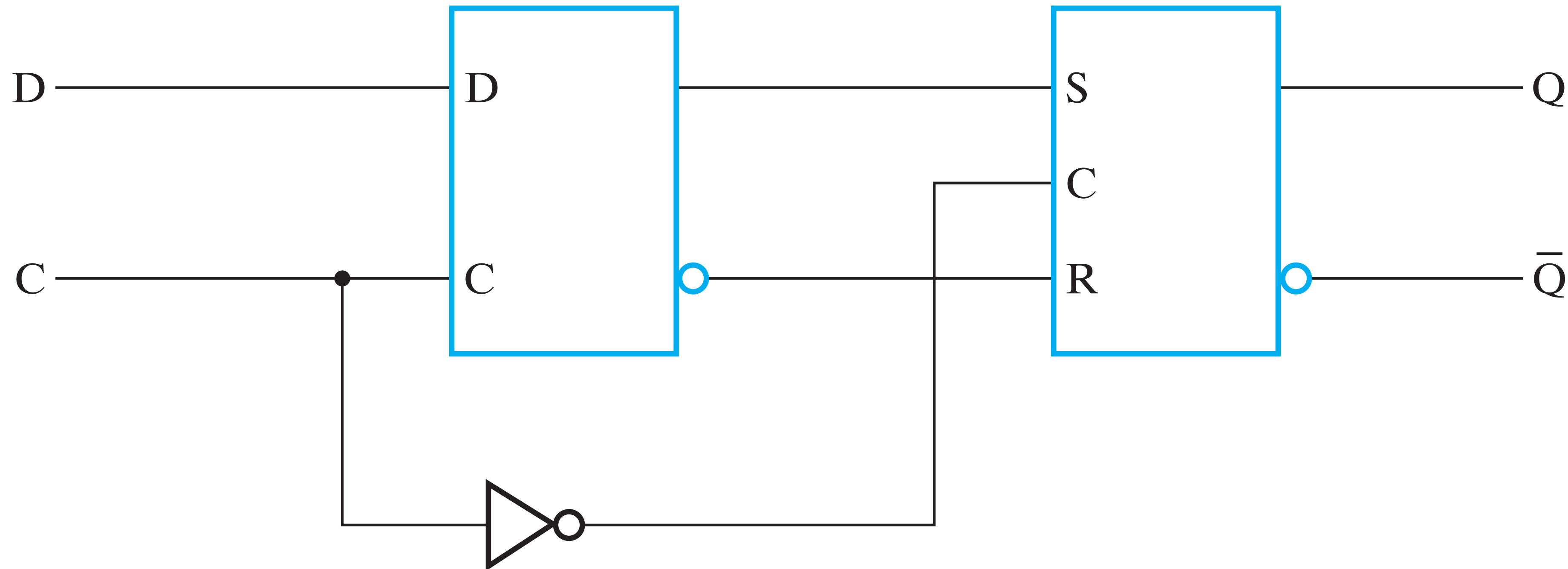


- Replaces *SR* master in *SR* Master-Slave with *D* master Latch
- **Negative Edge Triggered *D*** (Flip-Flop): $C = 1 \rightarrow C = 0$

D Flip-Flop

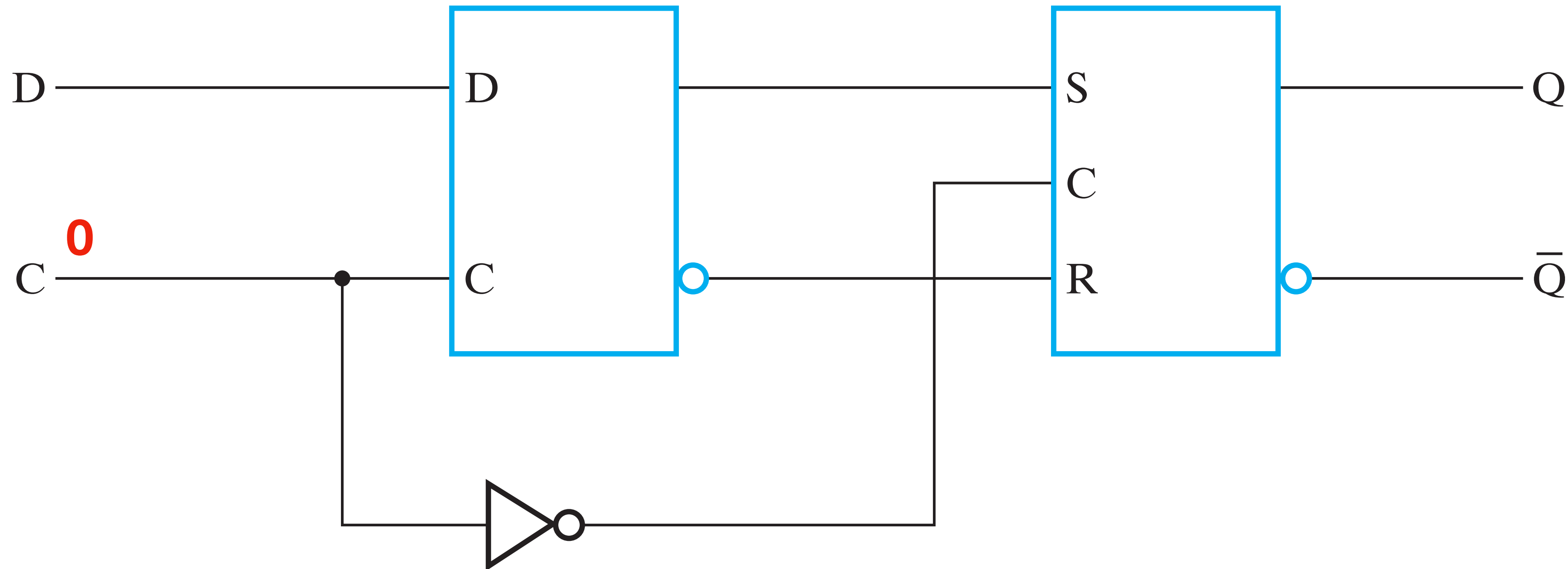


- Replaces *SR* master in *SR* Master-Slave with *D* master Latch
- **Negative Edge Triggered *D*** (Flip-Flop): $C = 1 \rightarrow C = 0$

D Flip-Flop

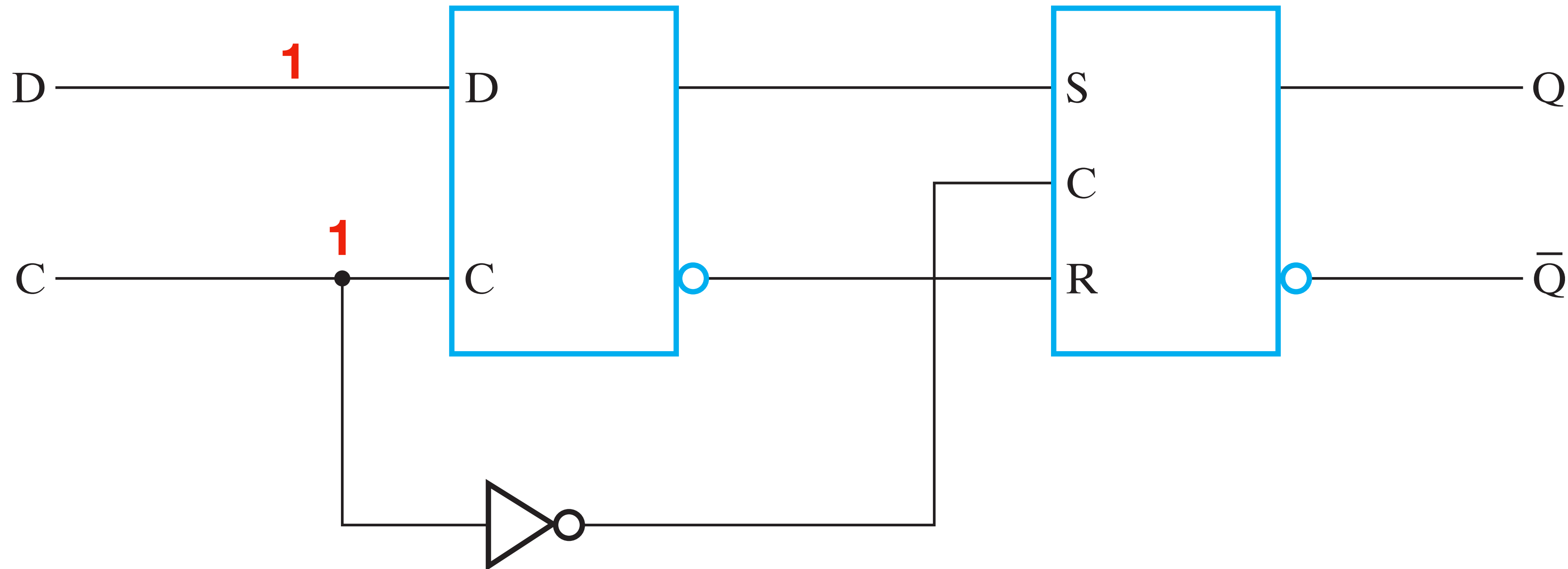


- Replaces *SR* master in *SR* Master-Slave with *D* master Latch
- **Negative Edge Triggered *D*** (Flip-Flop): $C = 1 \rightarrow C = 0$

D Flip-Flop

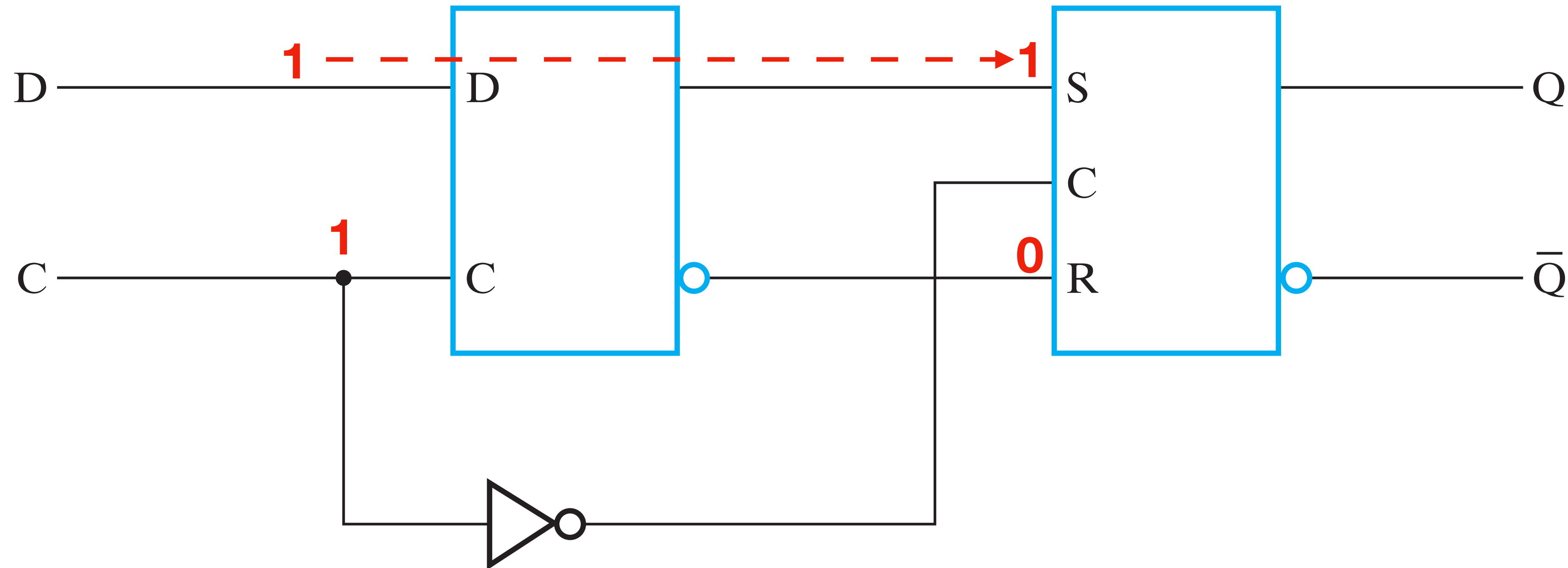


- Replaces SR master in SR Master-Slave with D master Latch
- **Negative Edge Triggered D** (Flip-Flop): $C = 1 \rightarrow C = 0$

D Flip-Flop

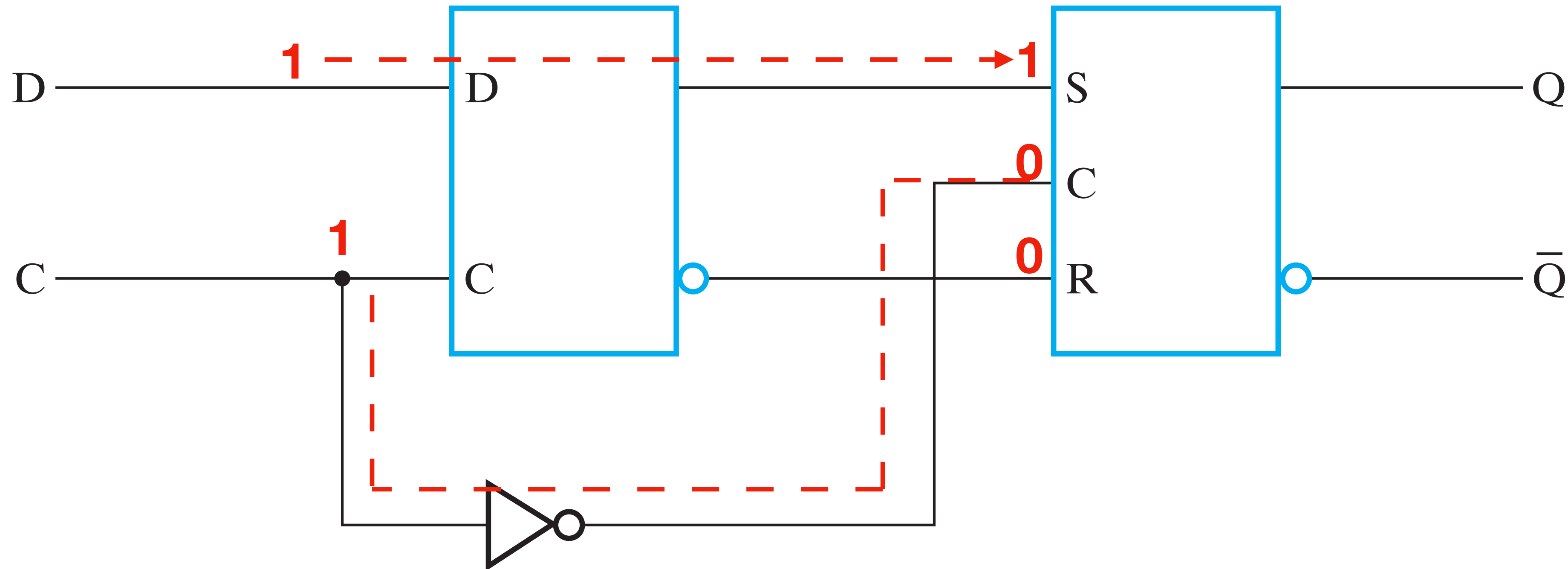


- Replaces SR master in SR Master-Slave with D master Latch
- **Negative Edge Triggered D (Flip-Flop):** $C = 1 \rightarrow C = 0$

D Flip-Flop

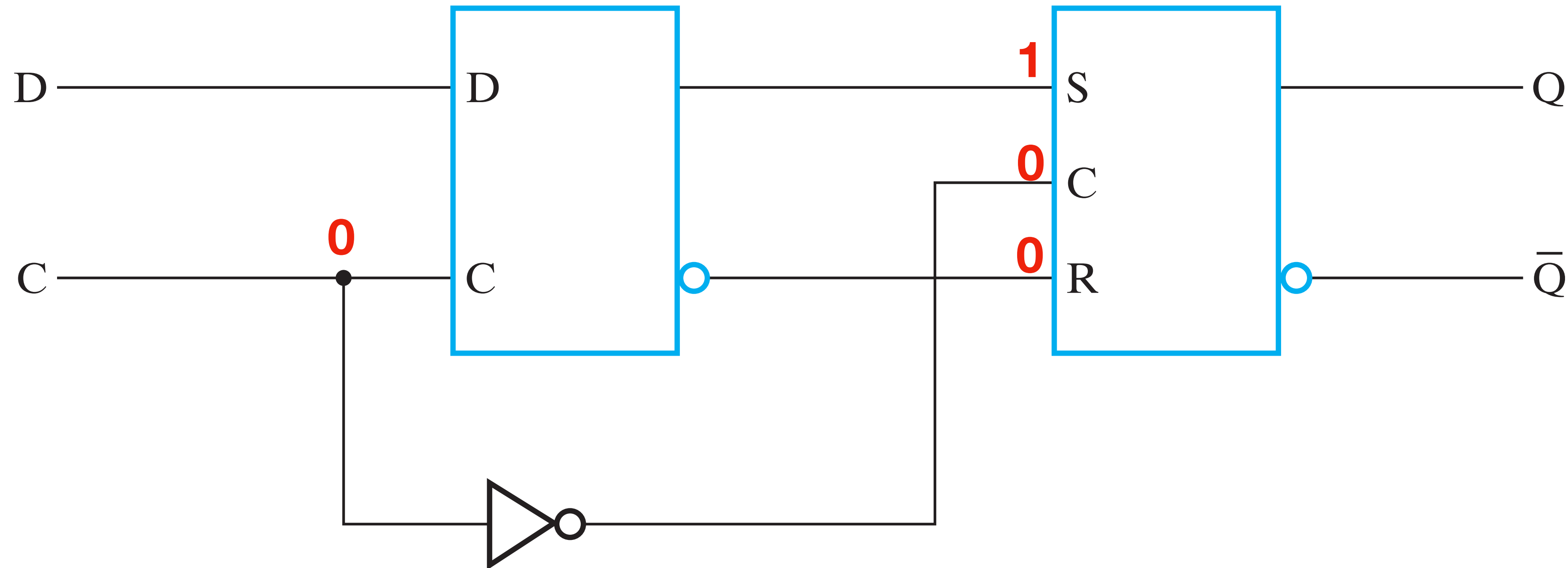


- Replaces SR master in SR Master-Slave with D master Latch
- **Negative Edge Triggered D** (Flip-Flop): $C = 1 \rightarrow C = 0$

D Flip-Flop

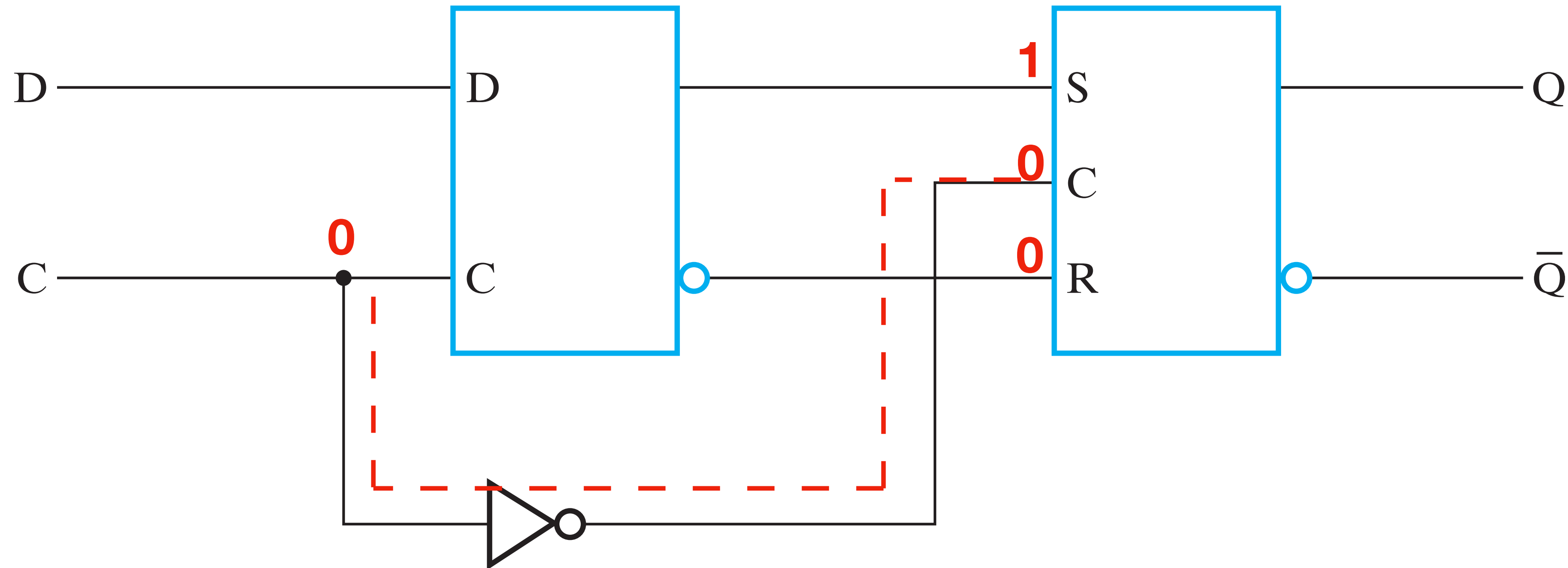


- Replaces *SR* master in *SR* Master-Slave with *D* master Latch
- **Negative Edge Triggered *D*** (Flip-Flop): $C = 1 \rightarrow C = 0$

D Flip-Flop

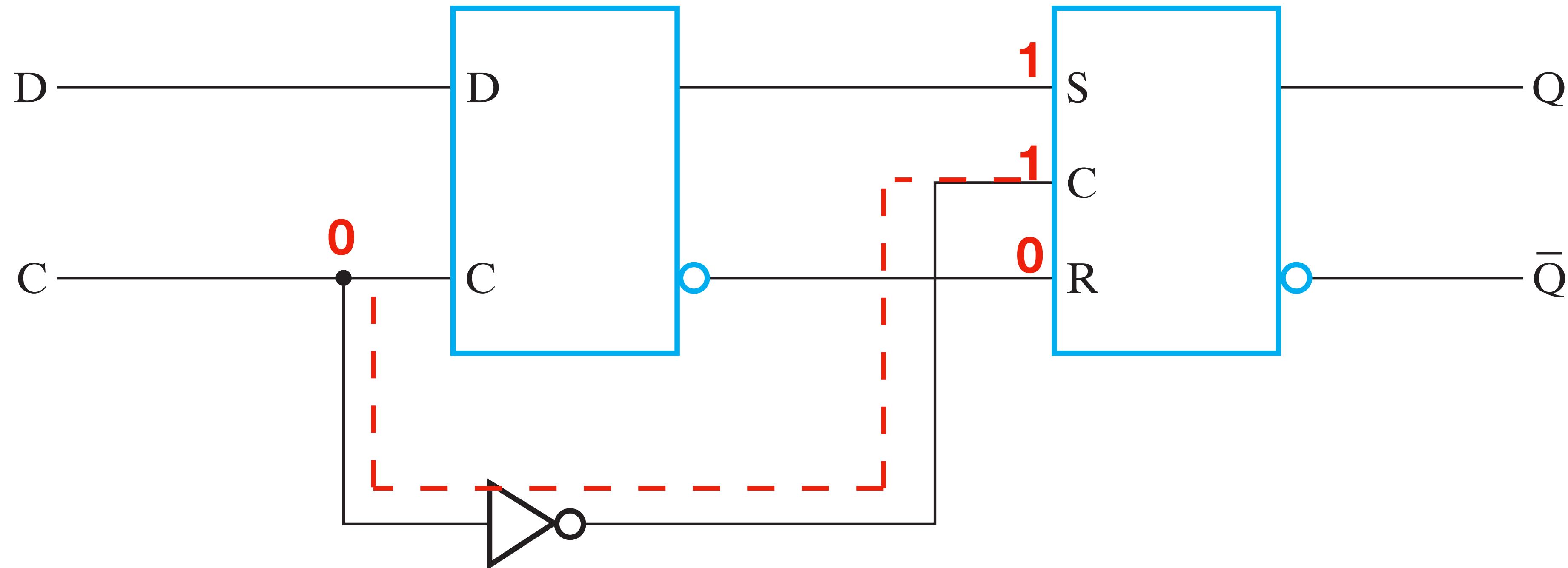

- Replaces *SR* master in *SR* Master-Slave with *D* master Latch
- **Negative Edge Triggered *D*** (Flip-Flop): $C = 1 \rightarrow C = 0$


D Flip-Flop

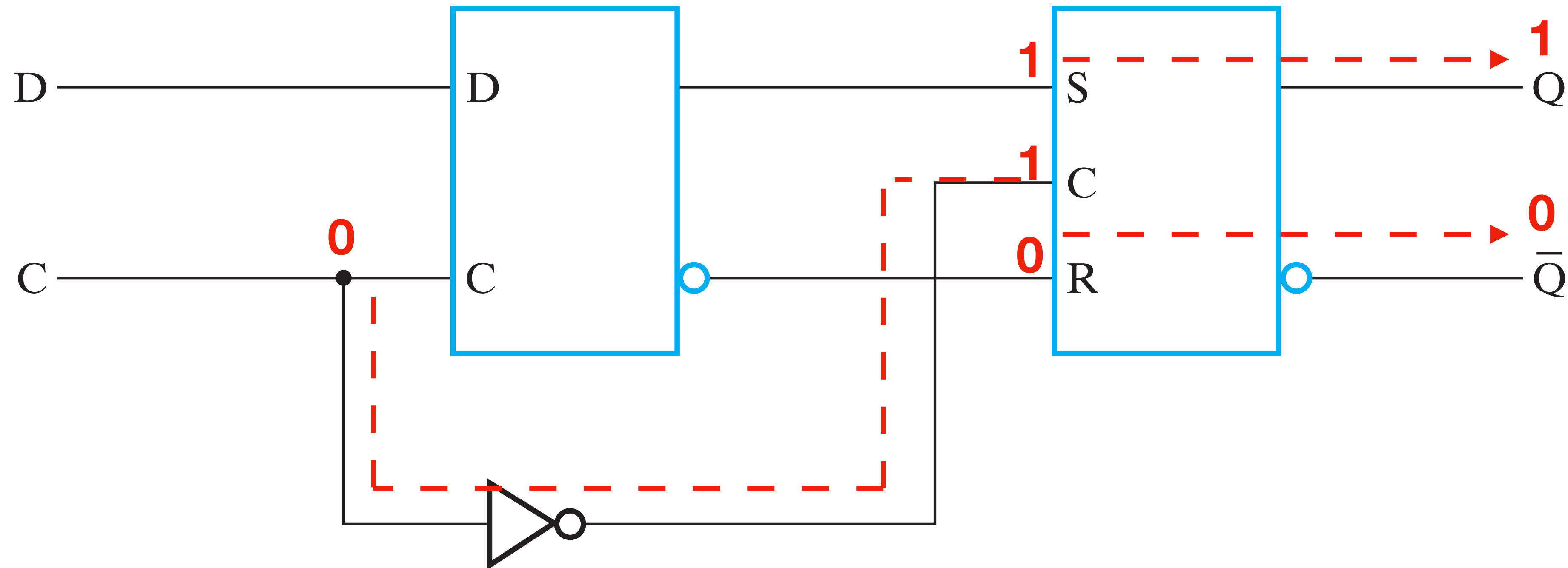

- Replaces *SR* master in *SR* Master-Slave with *D* master Latch
- **Negative Edge Triggered *D*** (Flip-Flop): $C = 1 \rightarrow C = 0$


Sequential Circuit Analysis

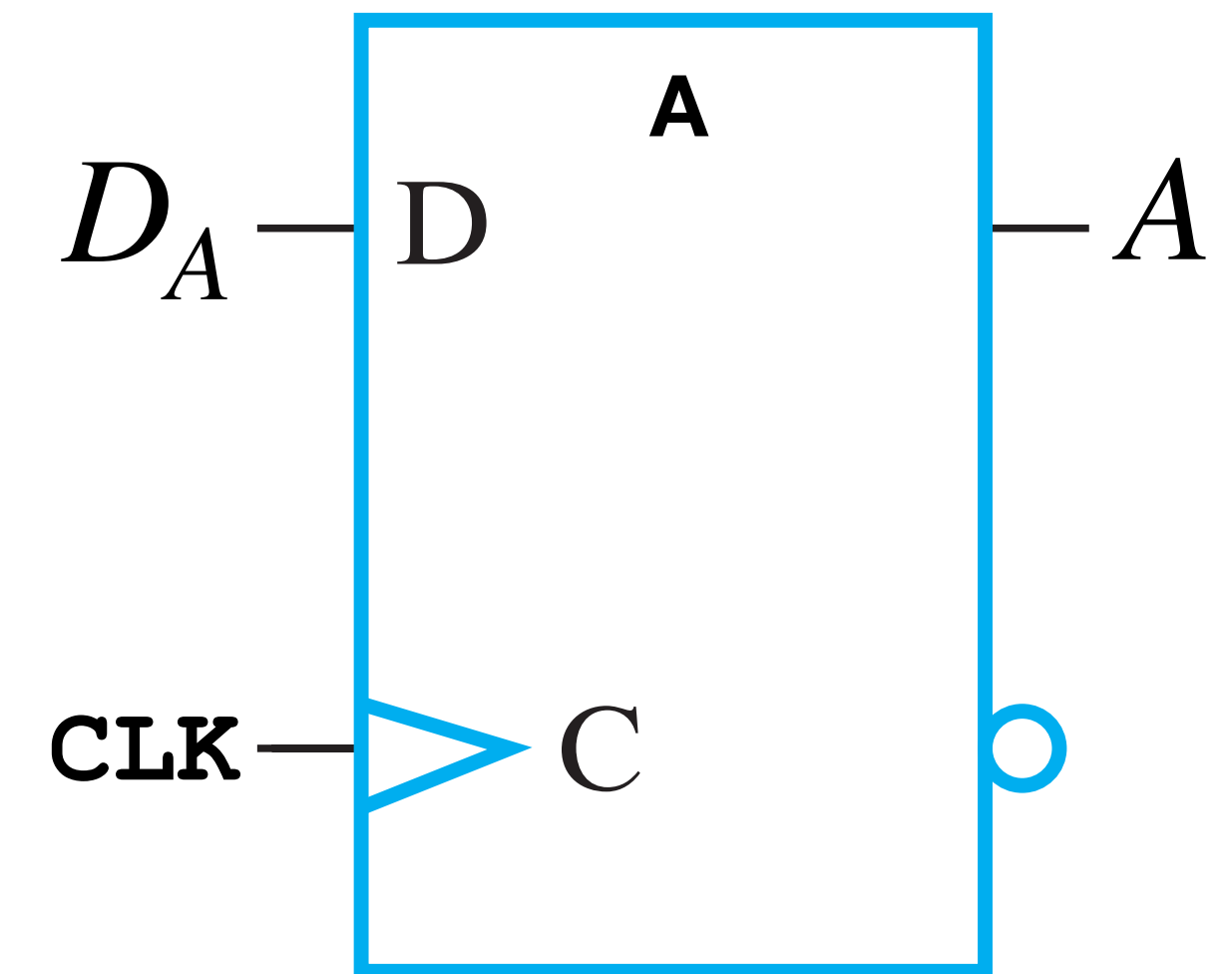- Any D flip-flop named A in a sequential circuit at anytime
 - Is giving out A (present state)
 - Is receiving D_A (next state)
 - State Table: treat A as input, D_A as output in Truth Table



Sequential Circuit Analysis

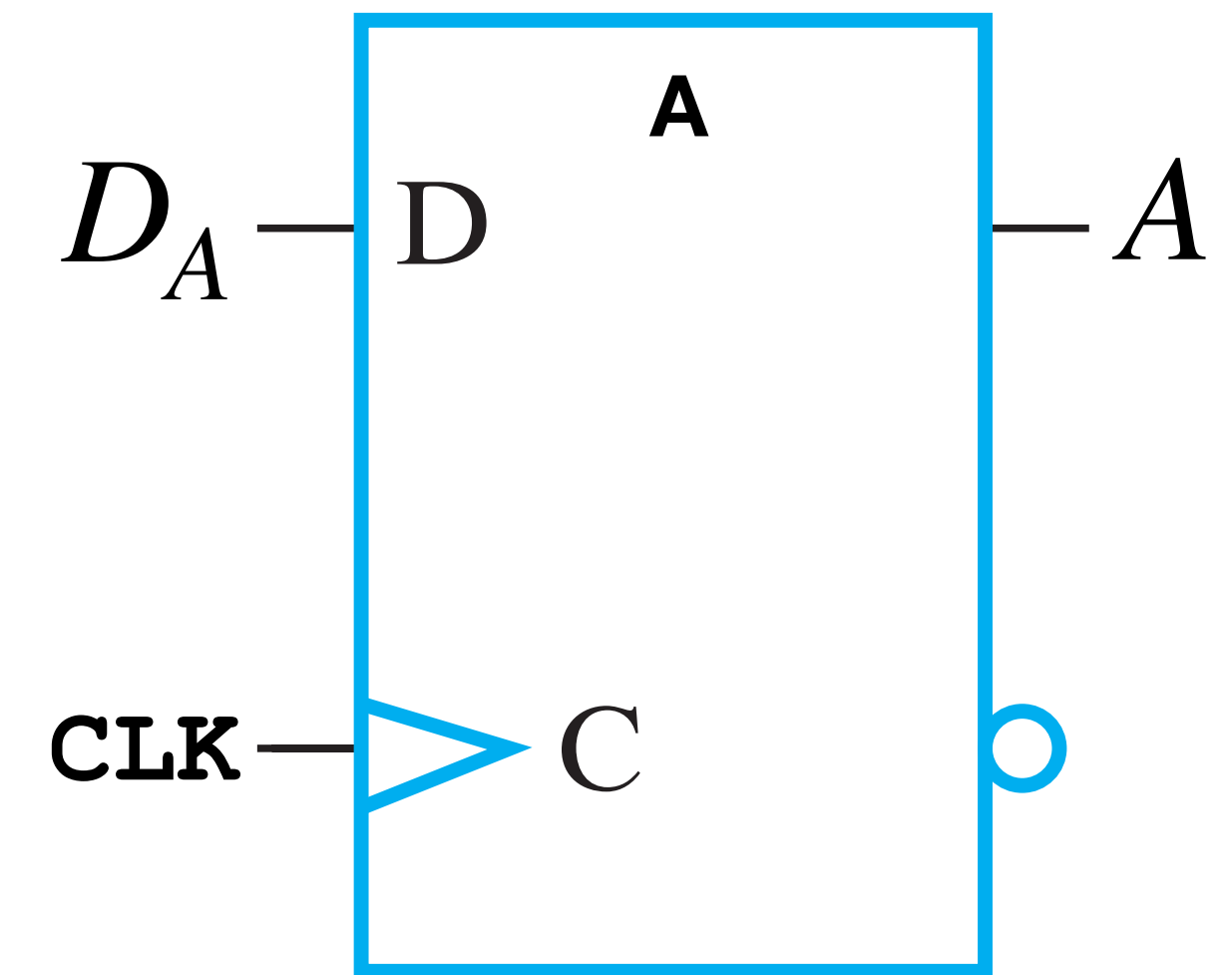- When multiple Flip-Flops $0, 1, \dots, n-1$ are in a circuit
 - the combined internal value $A_{n-1:0}$ is called the present state
 - the combined receiving value $D_{A_{n-1:0}}$ is called the next state



State Table

The diagram illustrates a truth table structure. It features a large blue rectangle on the left, representing the input space, and a large white rectangle on the right, representing the output space. The blue rectangle is labeled "Input Pins" at the top and "W, X, Y, Z, ..." below it. The white rectangle is labeled "Output Pins" at the top and "I, J, K, L, ..." below it. A vertical line separates the two rectangles. The text "Truth Table" is centered between the two rectangles. The diagram is divided into four horizontal sections by three horizontal lines. The top section is white, the second section is light gray, the third section is white, and the bottom section is light gray.


State Table

Present State	Input Pins	Output Pins	Next State
A, B, C, D, ...	W, X, Y, Z, ...	I, J, K, L, ...	D _A , D _B , D _C , D _D , ...

State Table


State Diagram

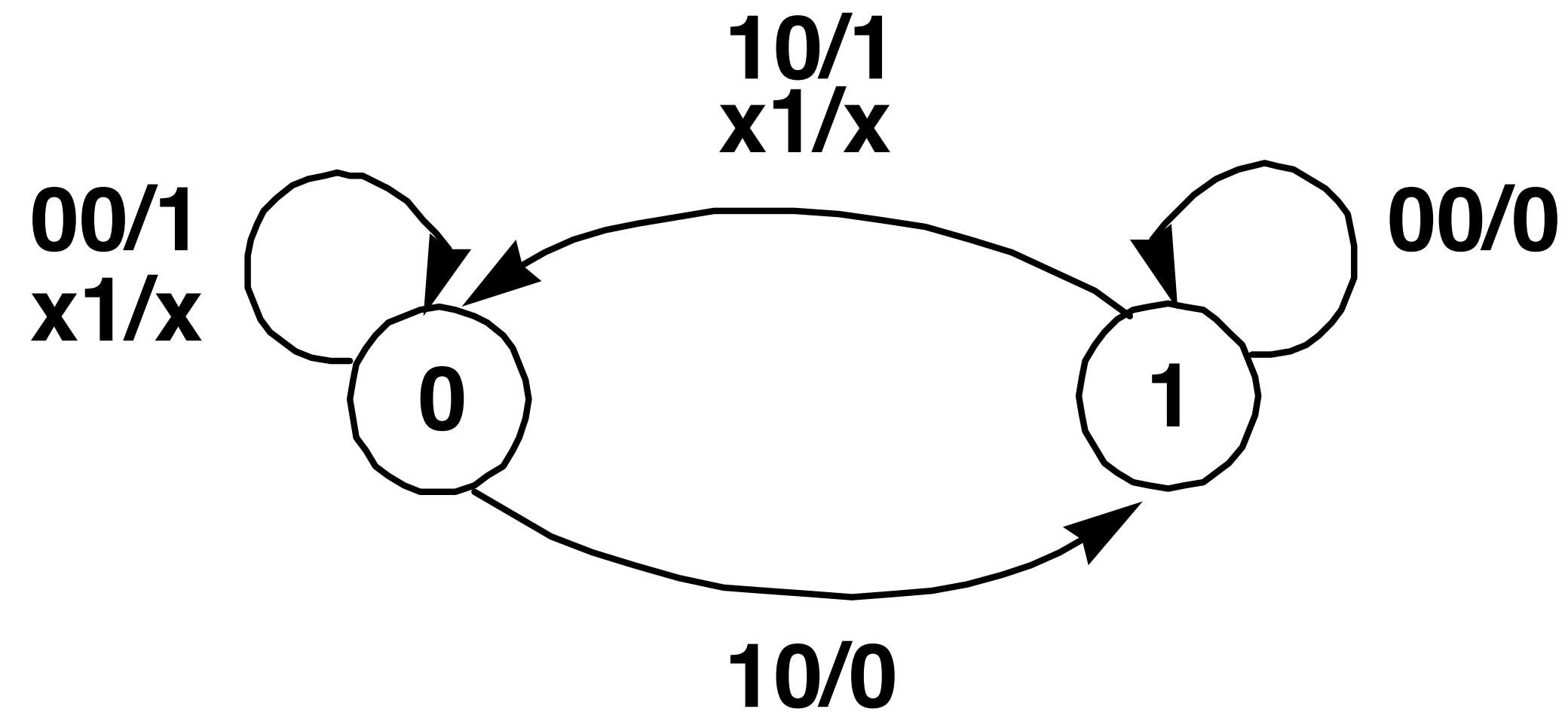- State transitions
- Transition Conditions and Output Conditions



State Diagram

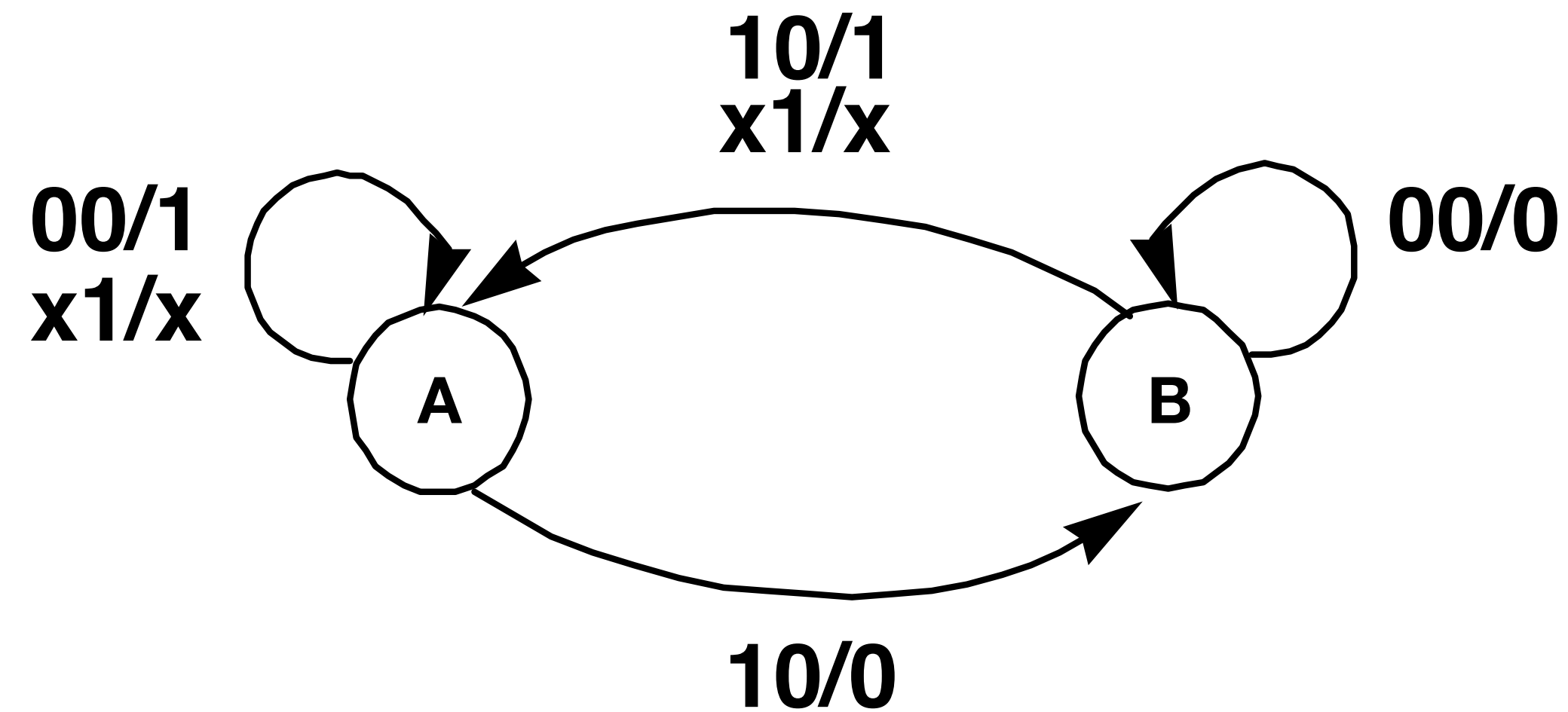- State transitions
- Transition Conditions and Output Conditions



State Assignments

- Given states written in variables $A, B, C, D, E...$
- Sequential assignment, n states, $\log n$ bits
 - $A = 000, B = 001, C = 010, D = 011, E = 100, ...$
- One-hot assignment, n states, n bits
 - $A = 00000001, B = 00000010, C = 00000100, D = 00001000, E = 00010000, ...$

Equation Determination

- Input equation for $D_{A_{n-1:0}}$, using $A_{n-1:0}$ as input
- Output equation for actual outputs

Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$

1. Identify flip-flops (present states and next states), inputs, and outputs
 - Present State: AB ; Next State: D_AD_B ; Input: Y ; Output: Z ;
2. Draw State Table / State Diagram

Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$

Present state		Input	Next state		Output
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	1	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	1	0
1	1	1	1	0	0

Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$

Present state		Input	Next state		Output
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	1	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	1	0
1	1	1	1	0	0

Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$


Present state		Input	Next state		Output
A	B		A	B	
0	0	0	0	1	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	1	0
1	1	1	1	0	0

00

Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$


Present state		Input	Next state		Output
A	B		A	B	
0	0	0	0	1	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	1	0
1	1	1	1	0	0

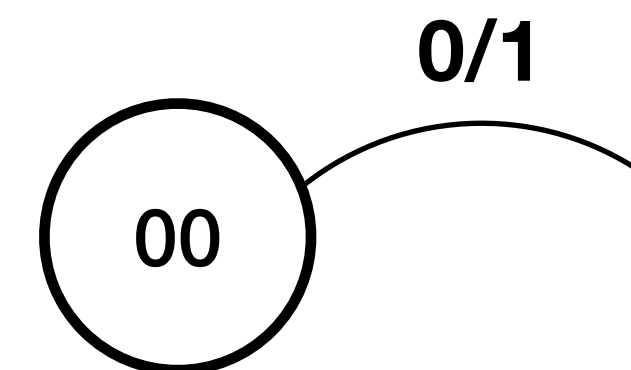

Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$


Present state		Input	Next state		Output
A	B		A	B	
0	0	0	0	1	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	1	0
1	1	1	1	0	0

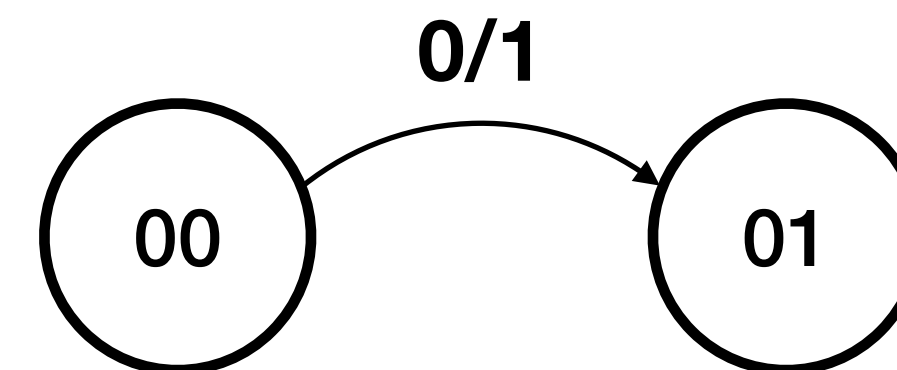

Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$


Present state		Input	Next state		Output
A	B		A	B	
0	0	0	0	1	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	1	0
1	1	1	1	0	0

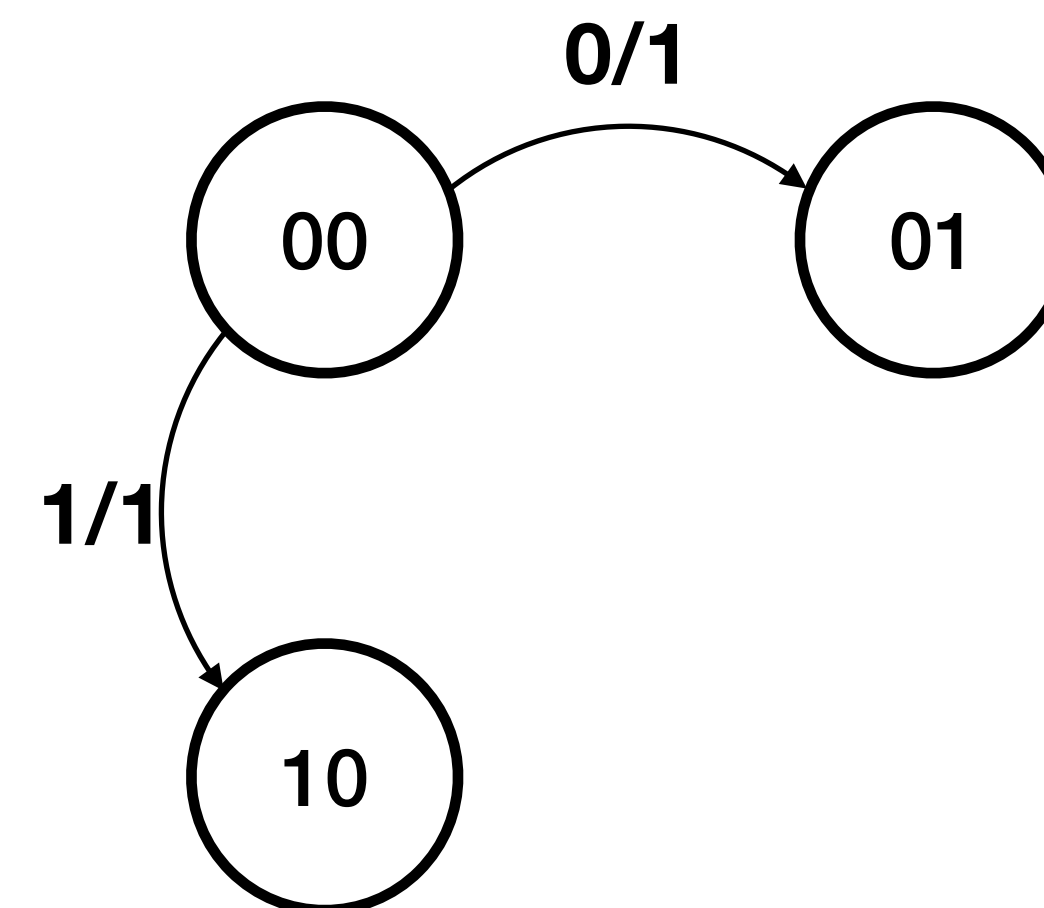

Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$


Present state		Input	Next state		Output
A	B		A	B	
0	0	0	0	1	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	1	0
1	1	1	1	0	0

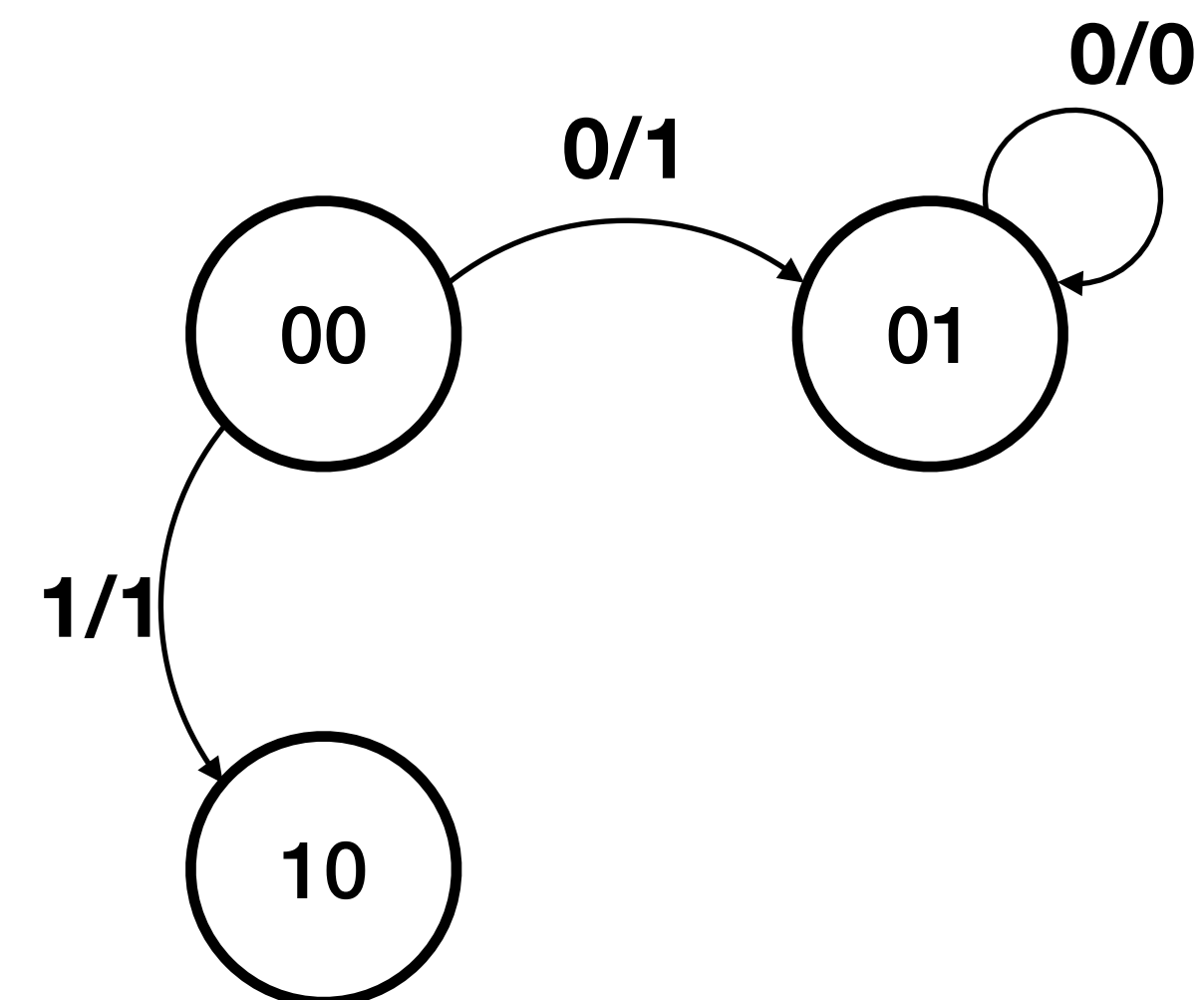

Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$


Present state		Input	Next state		Output
A	B		A	B	
0	0	0	0	1	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	1	0
1	1	1	1	0	0

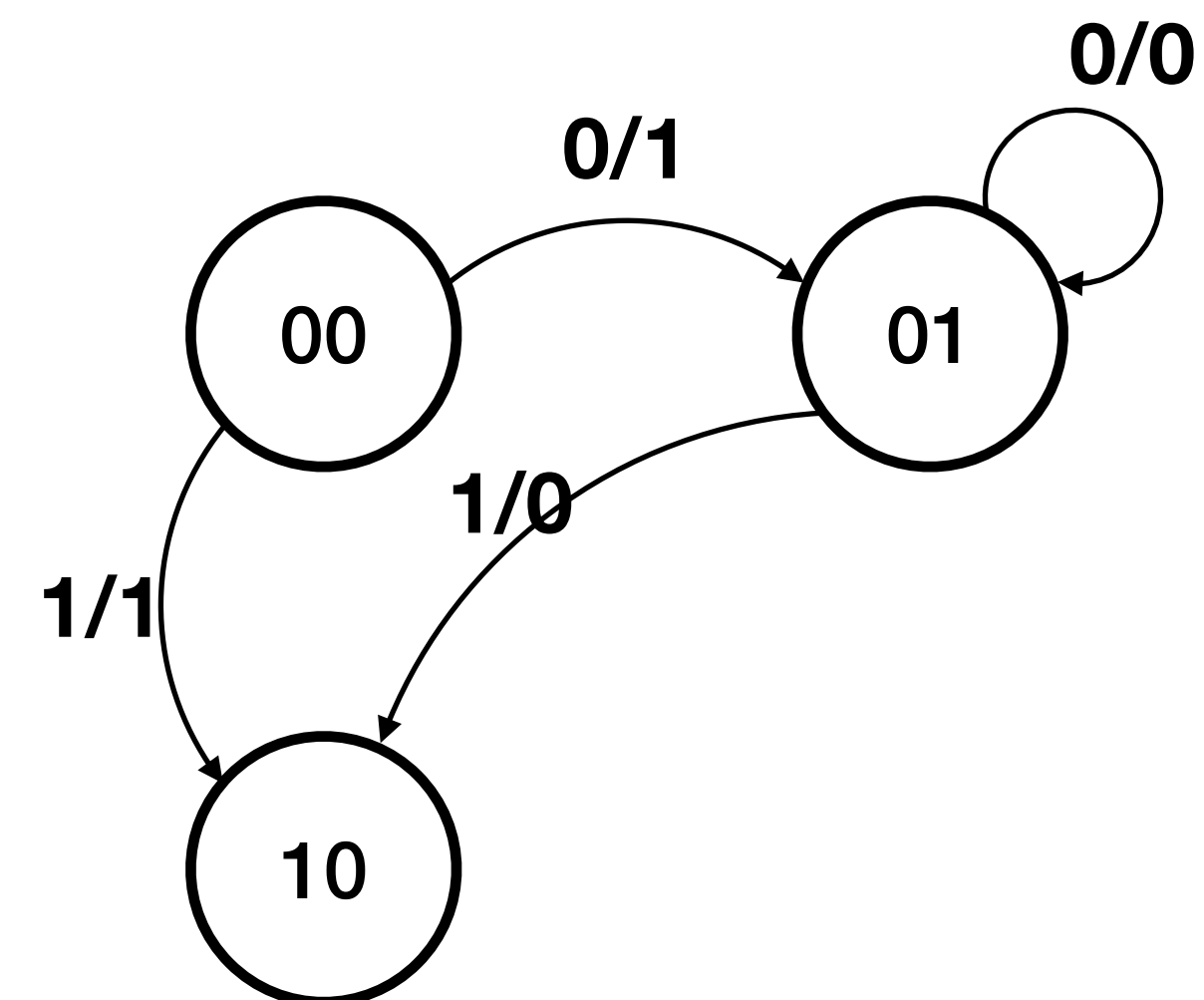

Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$


Present state		Input	Next state		Output
A	B		A	B	
0	0	0	0	1	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	1	0
1	1	1	1	0	0

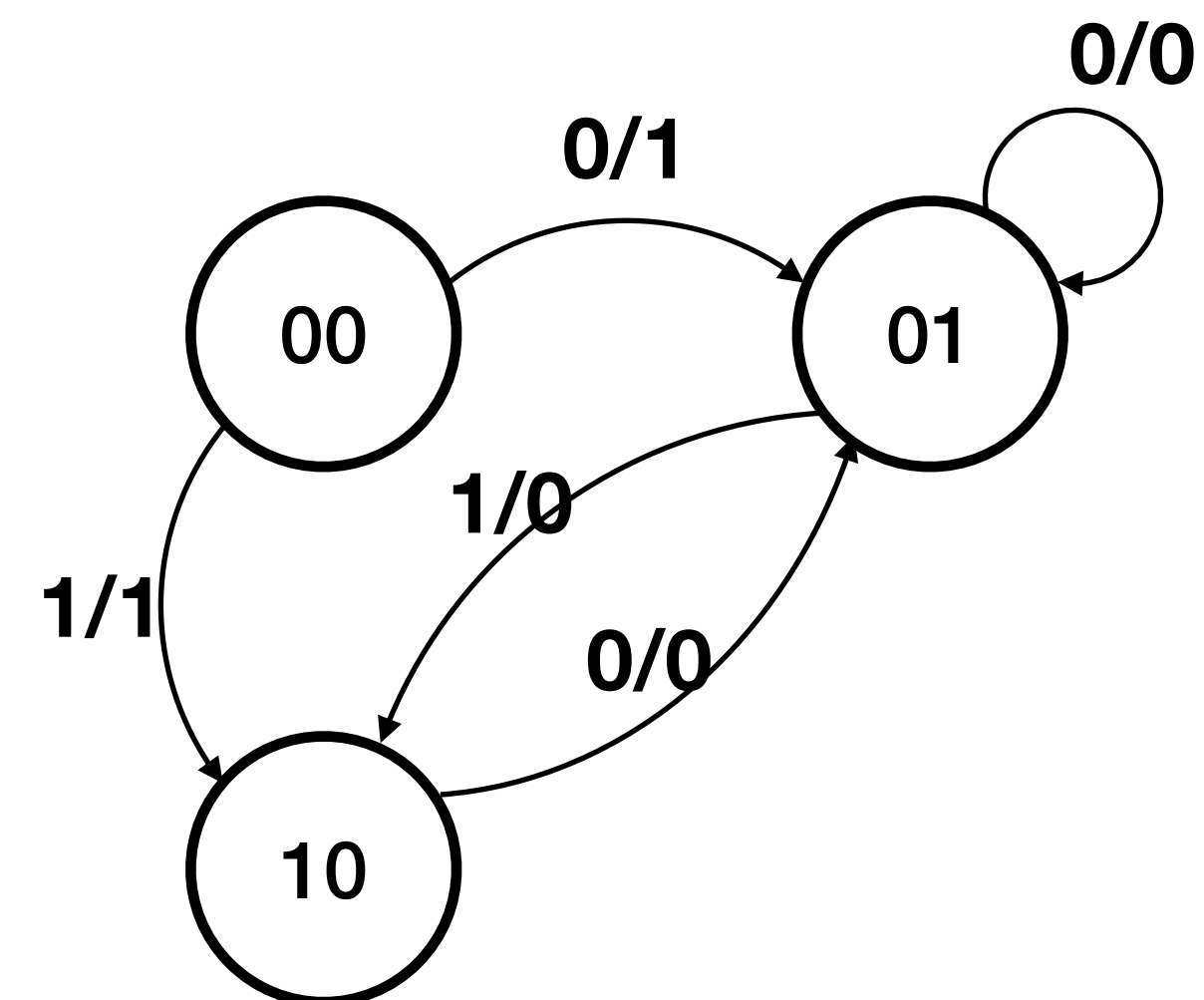

Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$


Present state		Input	Next state		Output
A	B		A	B	
0	0	0	0	1	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	1	0
1	1	1	1	0	0

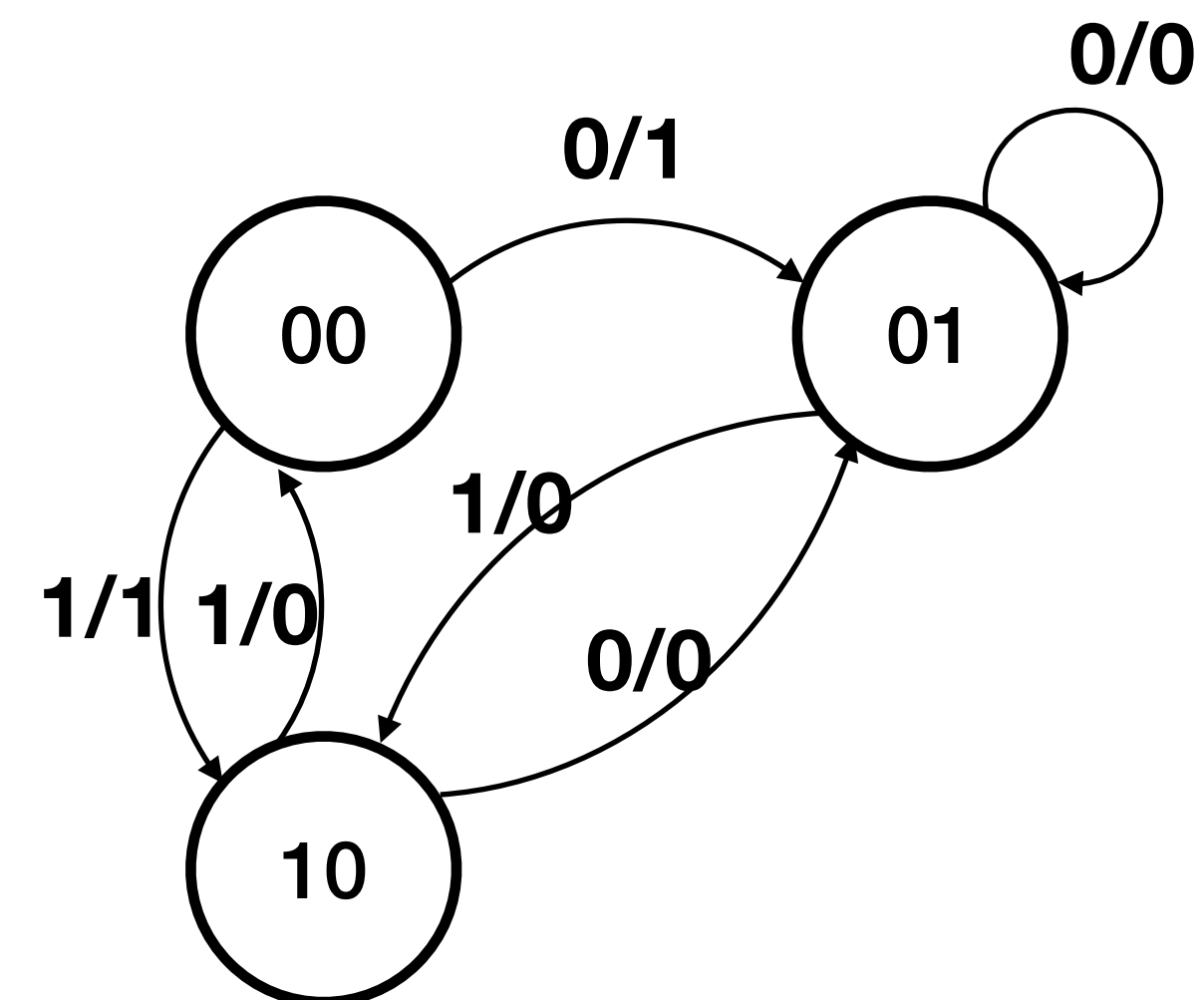

Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$


Present state		Input	Next state		Output
A	B		A	B	
0	0	0	0	1	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	1	0
1	1	1	1	0	0

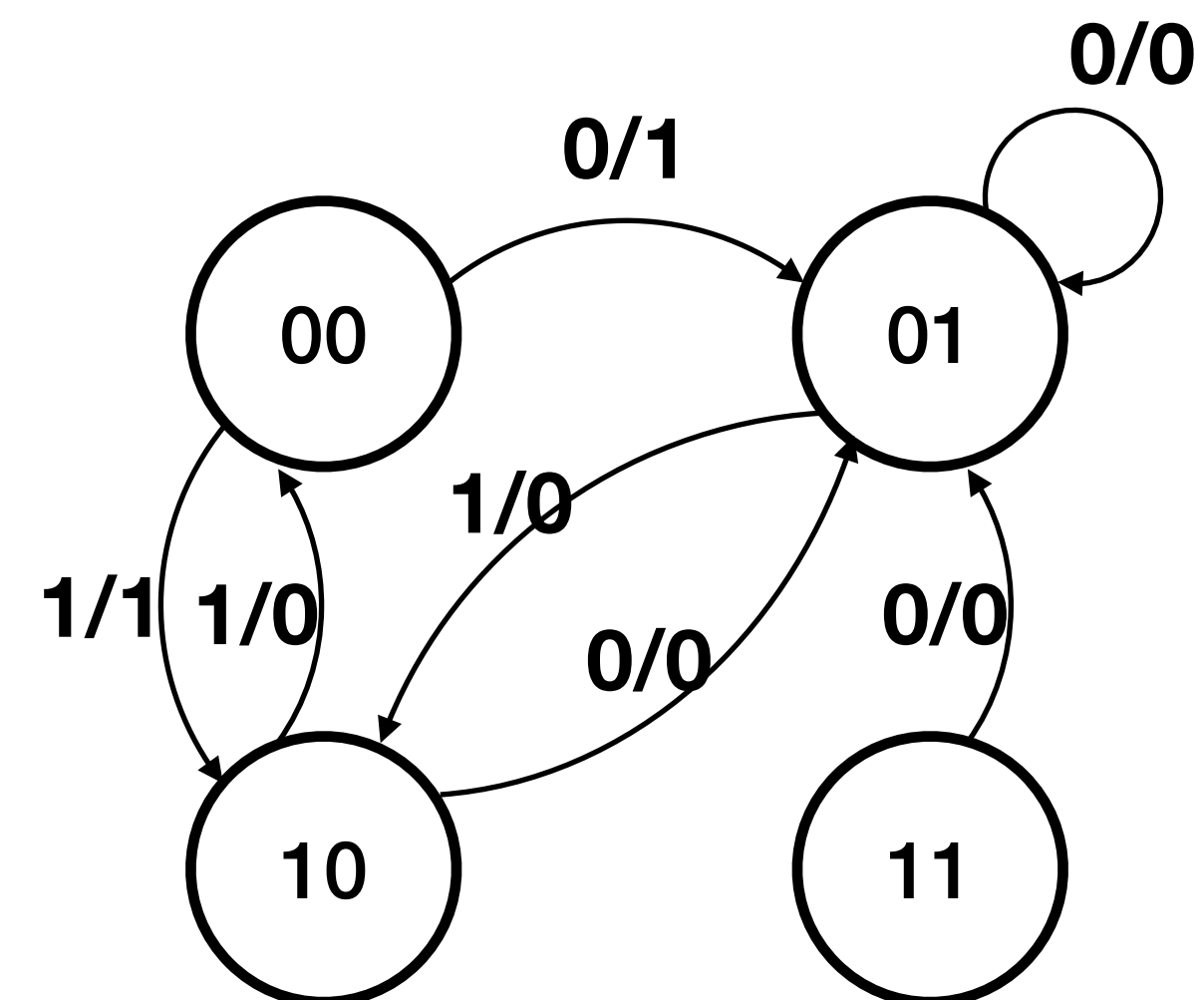

Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$


Present state		Input	Next state		Output
A	B		A	B	
0	0	0	0	1	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	1	0
1	1	1	1	0	0

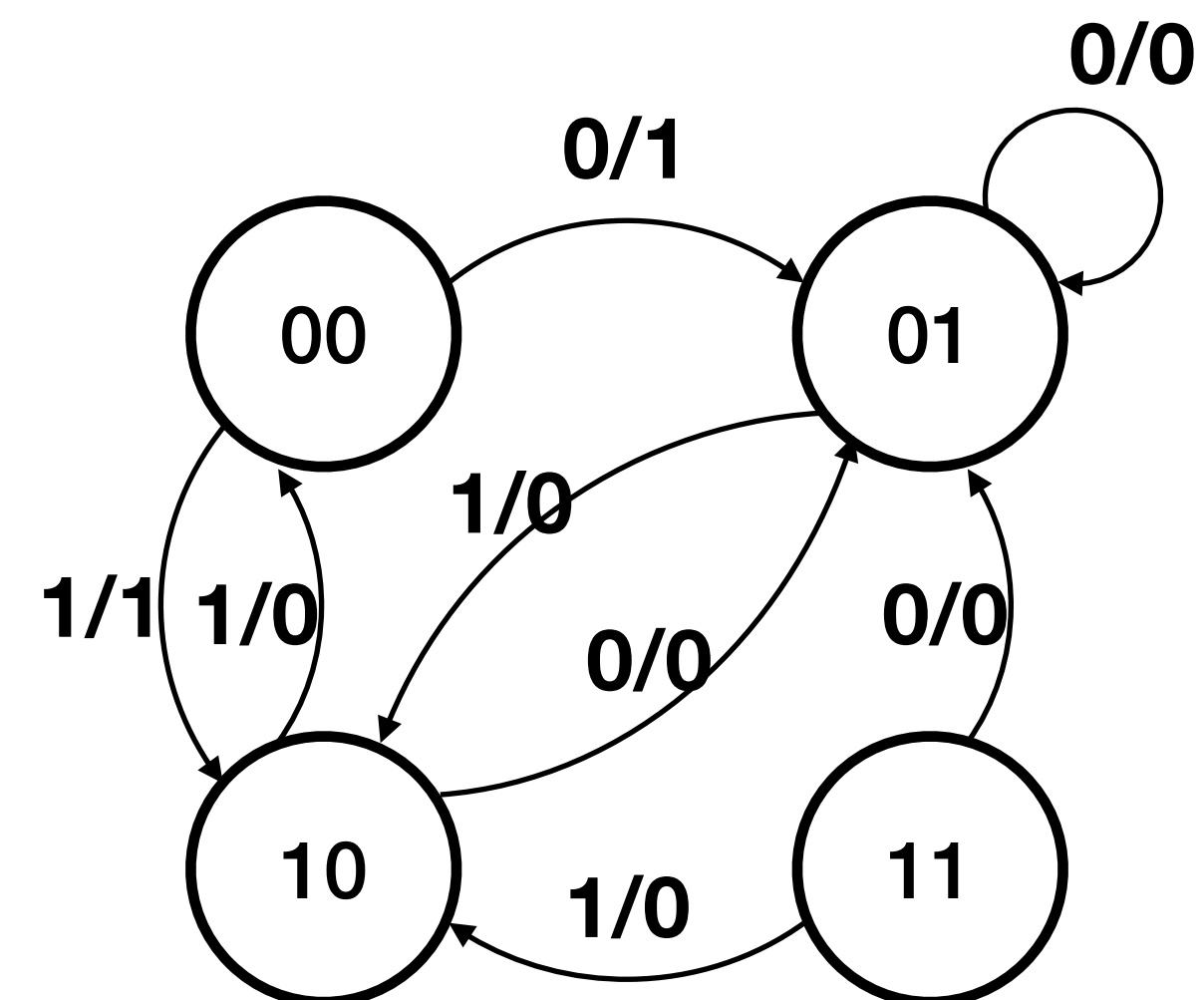

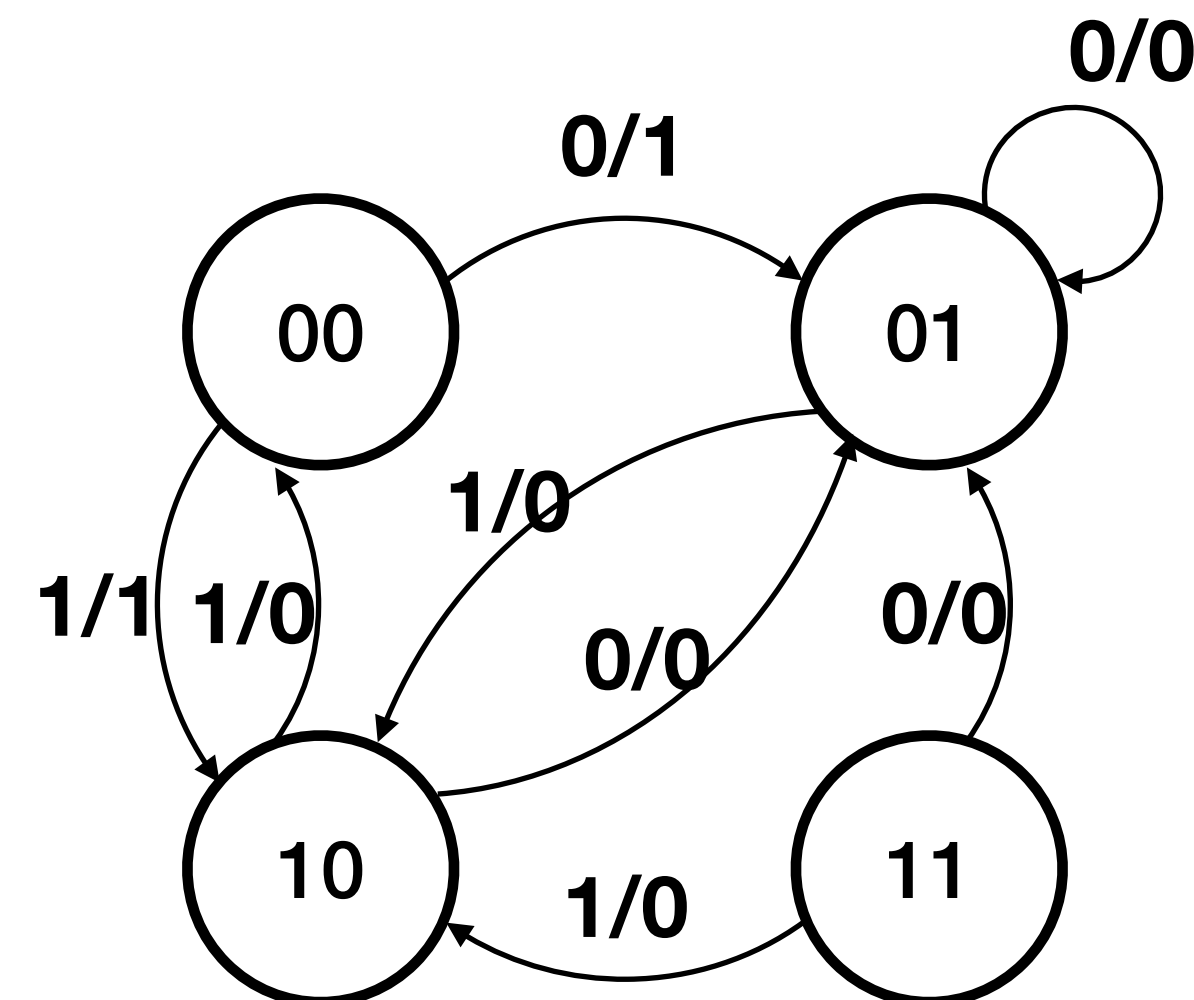Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$


- Initial state 00
- Write down the state transition from input 0101
- 00
- Write down the output
-



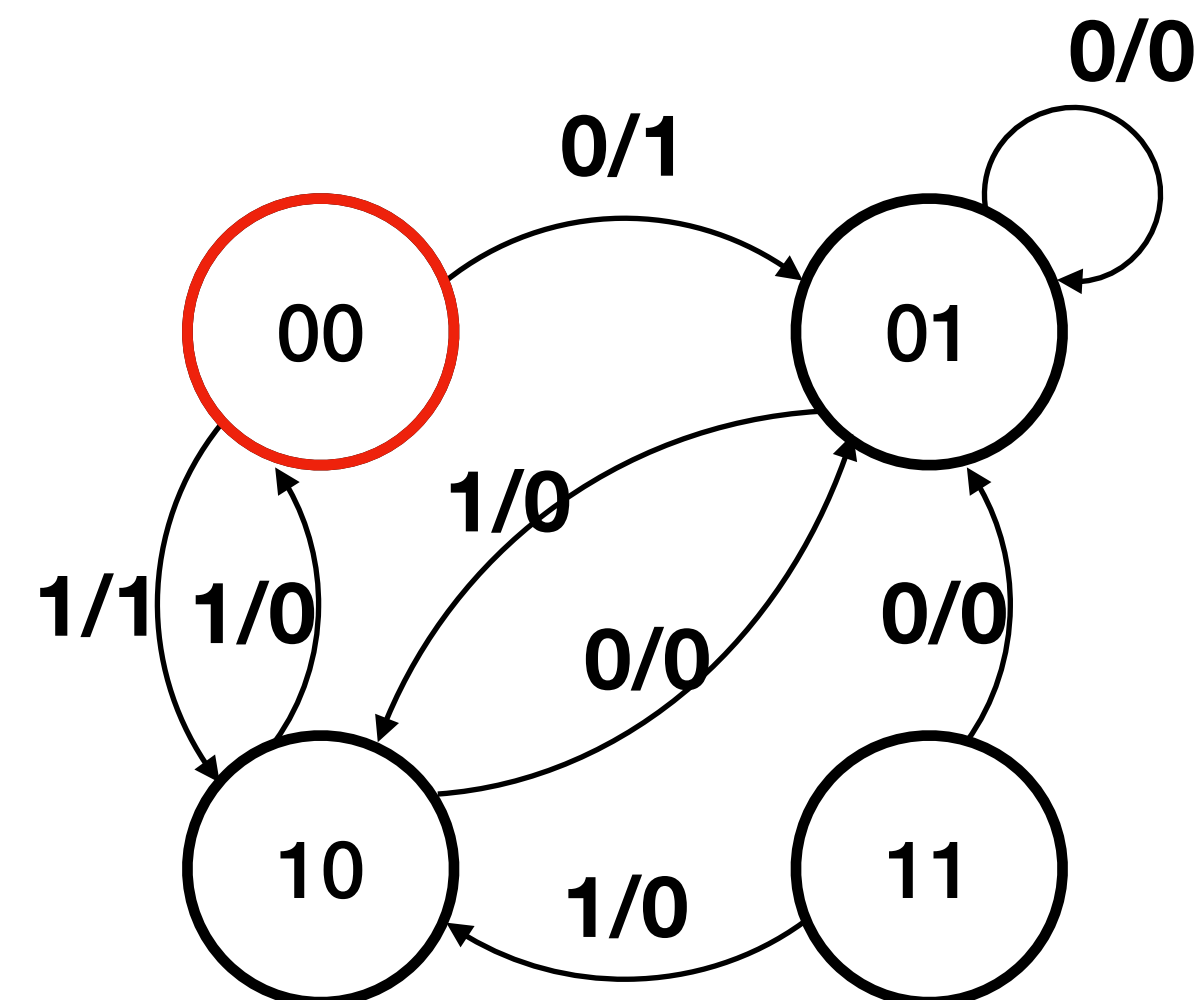Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$


- Initial state 00
- Write down the state transition from input 0101
- 00
- Write down the output
-



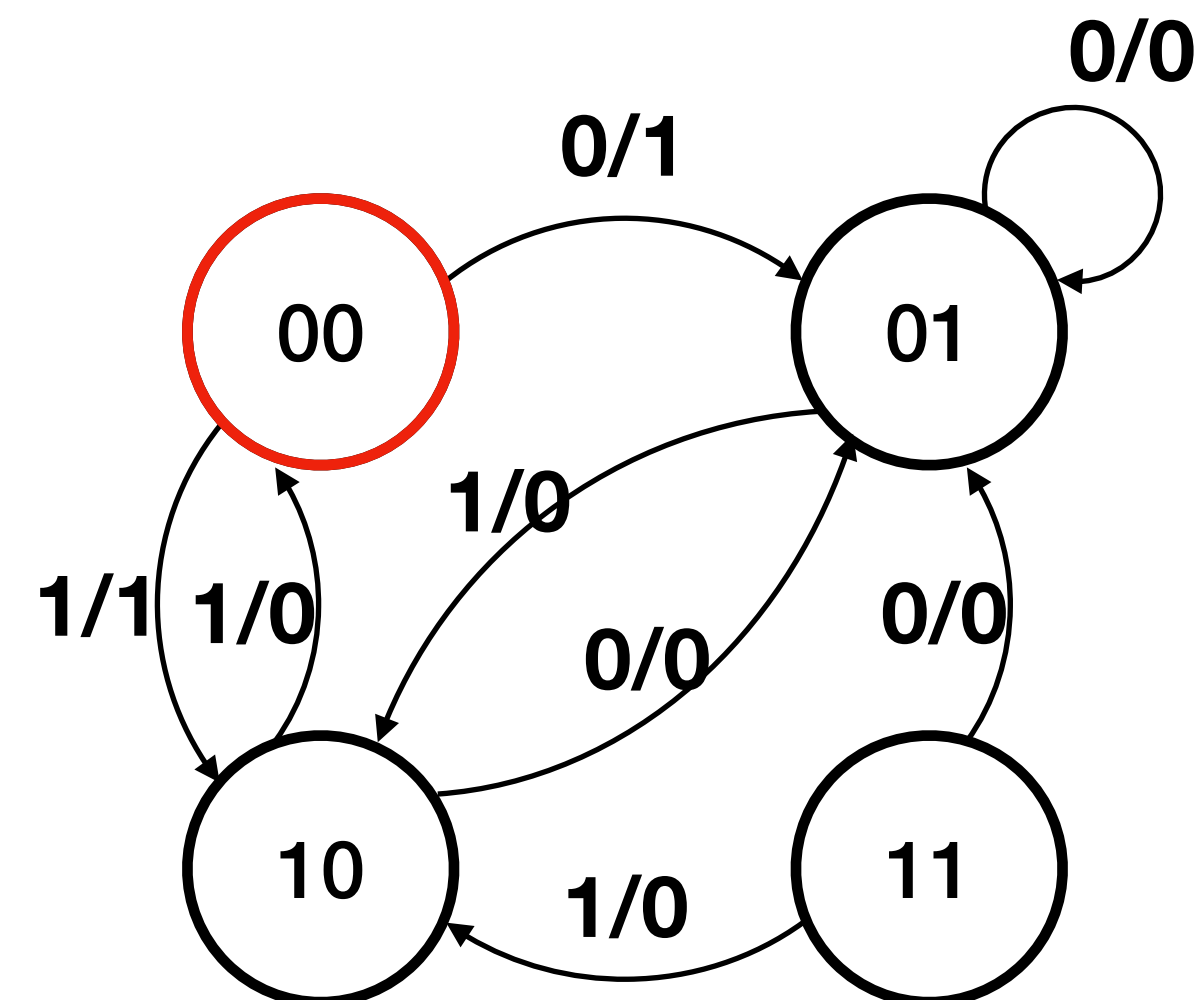Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$


- Initial state 00
- Write down the state transition from input 0101
- 00
- Write down the output
-



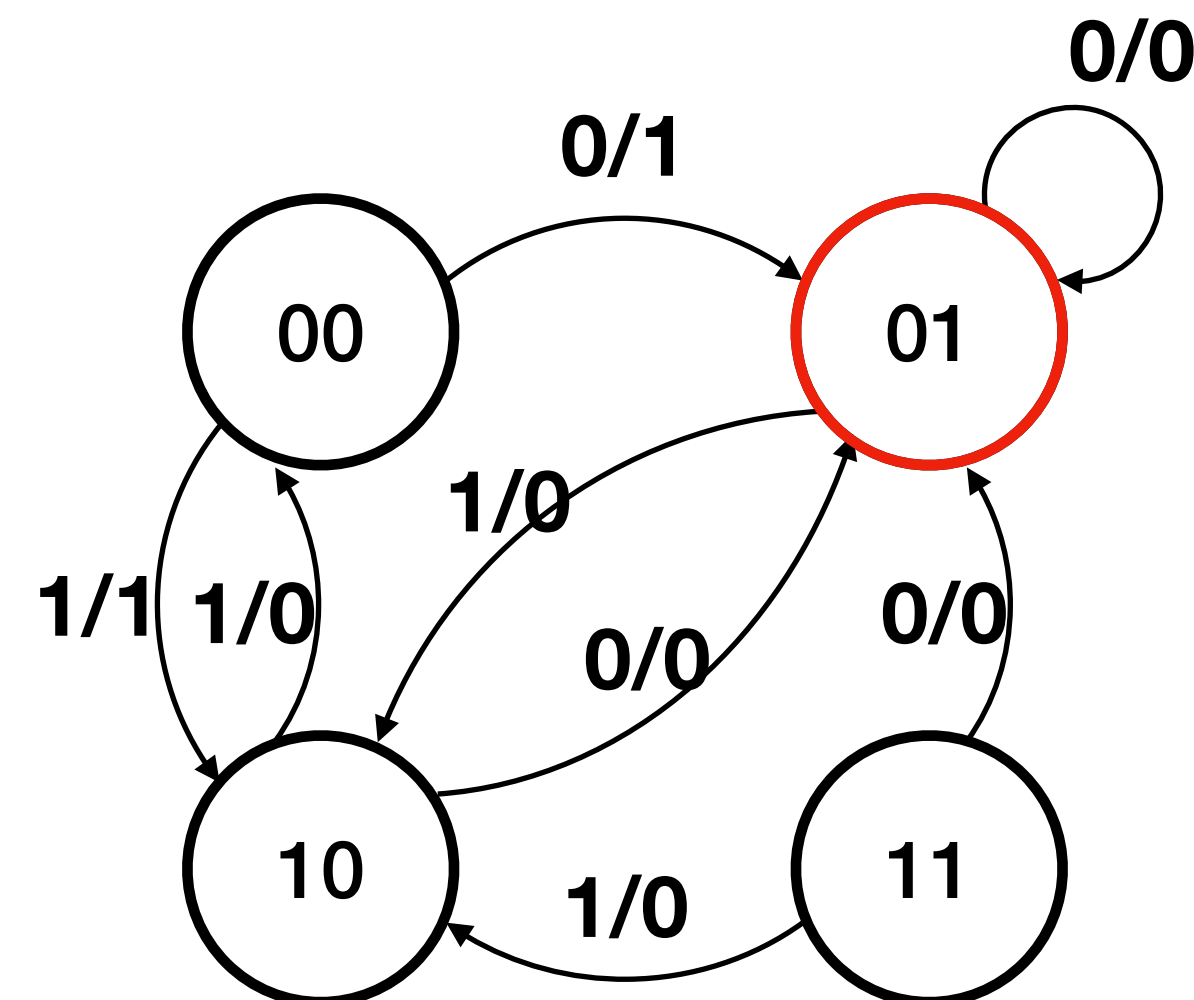Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$


- Initial state 00
- Write down the state transition from input 0101
- $00 \rightarrow 01$
- Write down the output
- 1



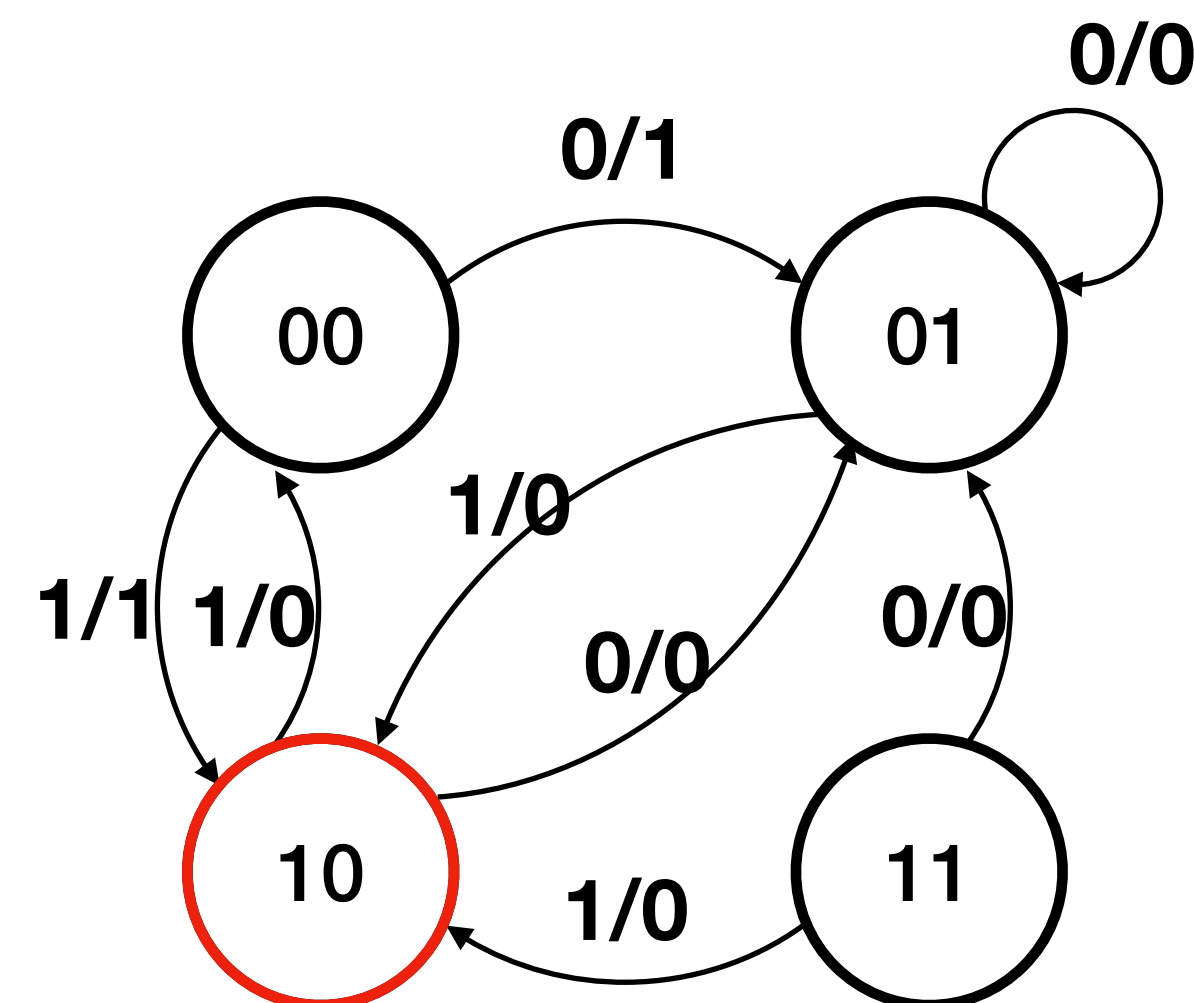Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$


- Initial state 00
- Write down the state transition from input 0101
 - $00 \rightarrow 01 \rightarrow 10$
- Write down the output
 - 10



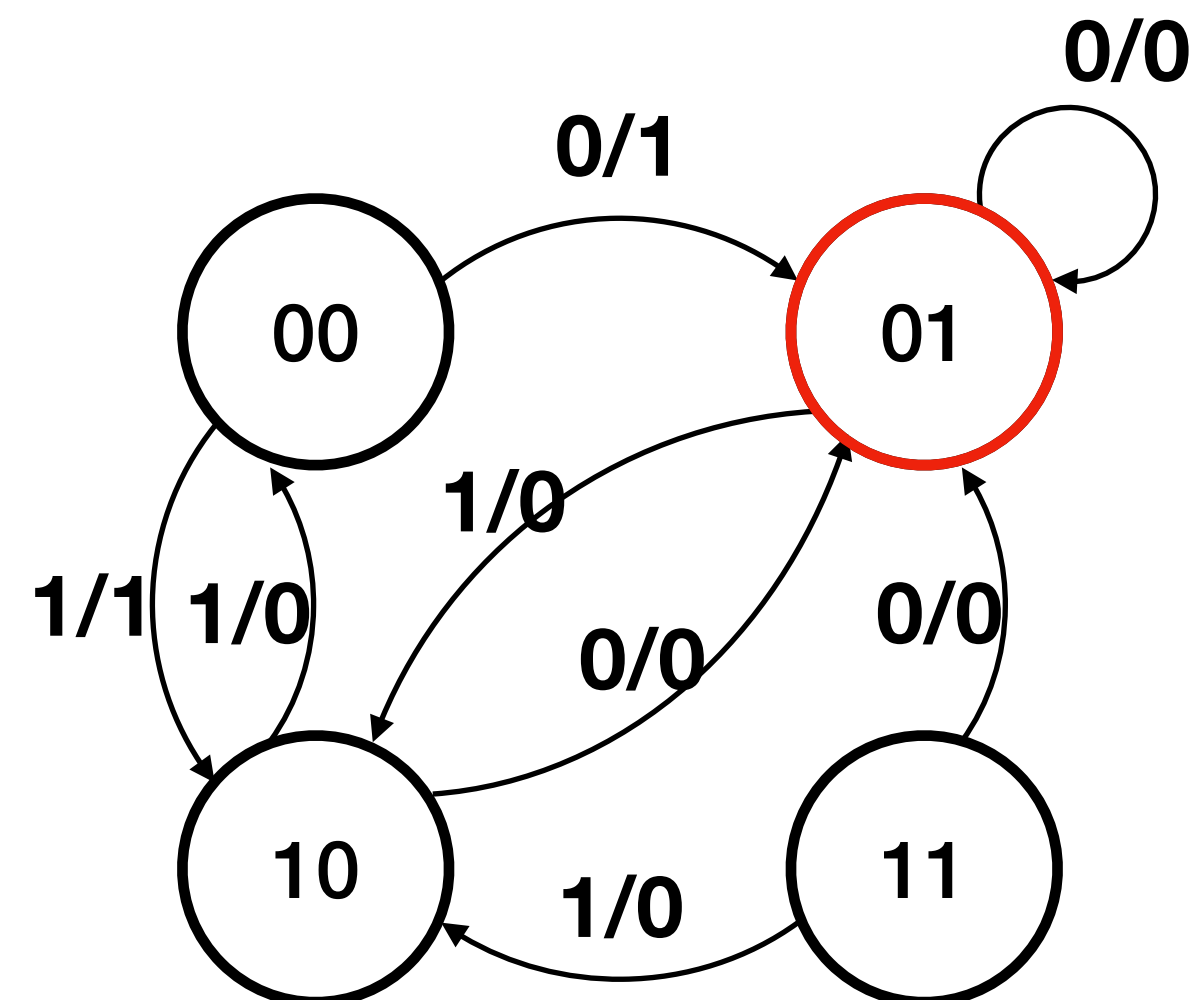Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$

- Initial state 00
- Write down the state transition from input 0101
- $00 \rightarrow 01 \rightarrow 10 \rightarrow 01$
- Write down the output
- 100



Question

$$D_A = BY + \bar{A}Y, D_B = \bar{Y}, Z = \bar{A}\bar{B}$$

- Initial state 00
- Write down the state transition from input 0101
- $00 \rightarrow 01 \rightarrow 10 \rightarrow 01 \rightarrow 10$
- Write down the output
- 1000

