



csci 150

Introduction to Digital and Computer System Design

Lecture 3: Combinational Logic Design VII



Jetic GU
2020 Fall Semester (S3)

Overview


- Focus: Arithmetic Functional Blocks
- Architecture: Combinatory Logical Circuits
- Textbook v4: Ch4 4.3, 4.4, 4.7; v5: Ch2 2.9, Ch3 3.10, 3.11
- Core Ideas:
 1. Subtraction II
 2. Subtraction III
 3. VHDL

Unsigned Binary Subtraction I

Review


Unsigned 1-bit Binary Subtraction

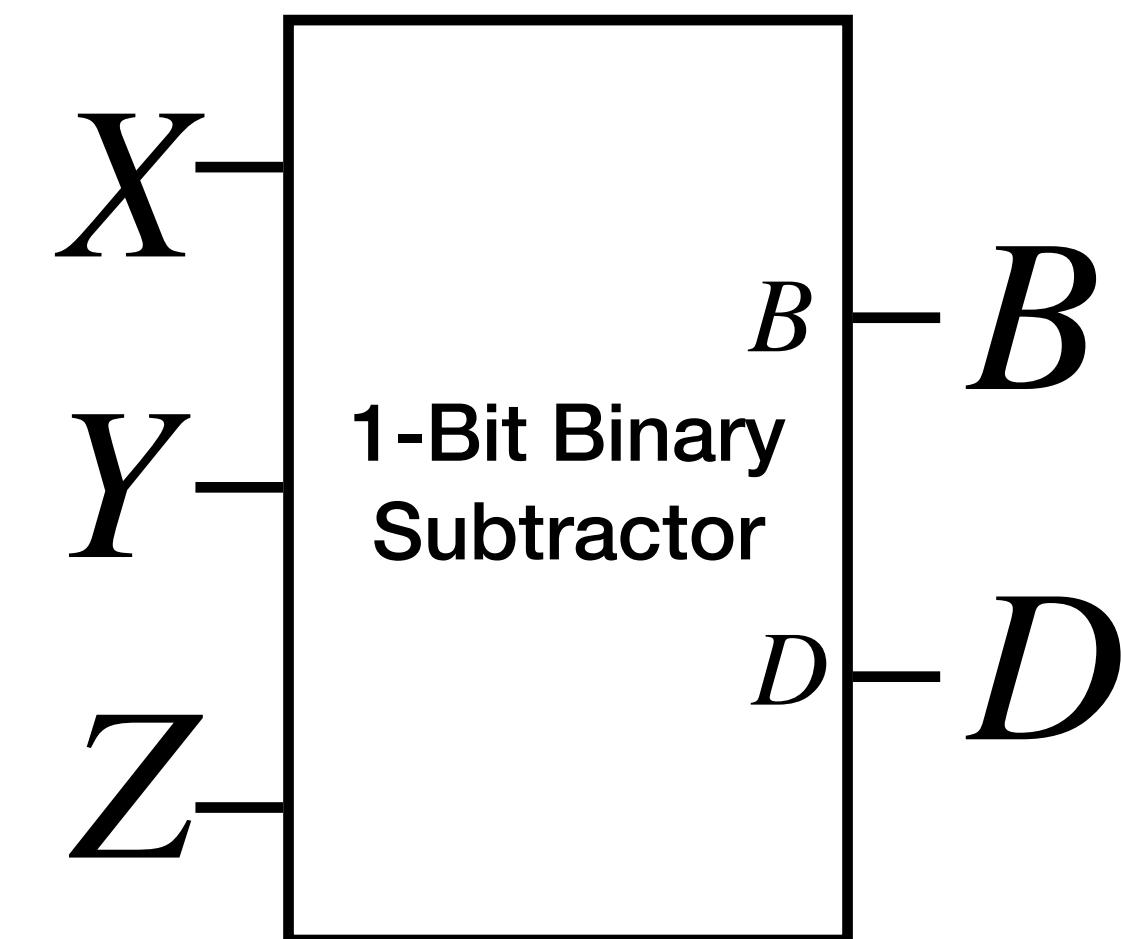- Implementation using 3-to-8 Decoder
 - $B = \Sigma m(1,2,3,7)$
 - $D = \Sigma m(1,2,4,7)$



Unsigned Binary Subtraction

P1
Subtraction

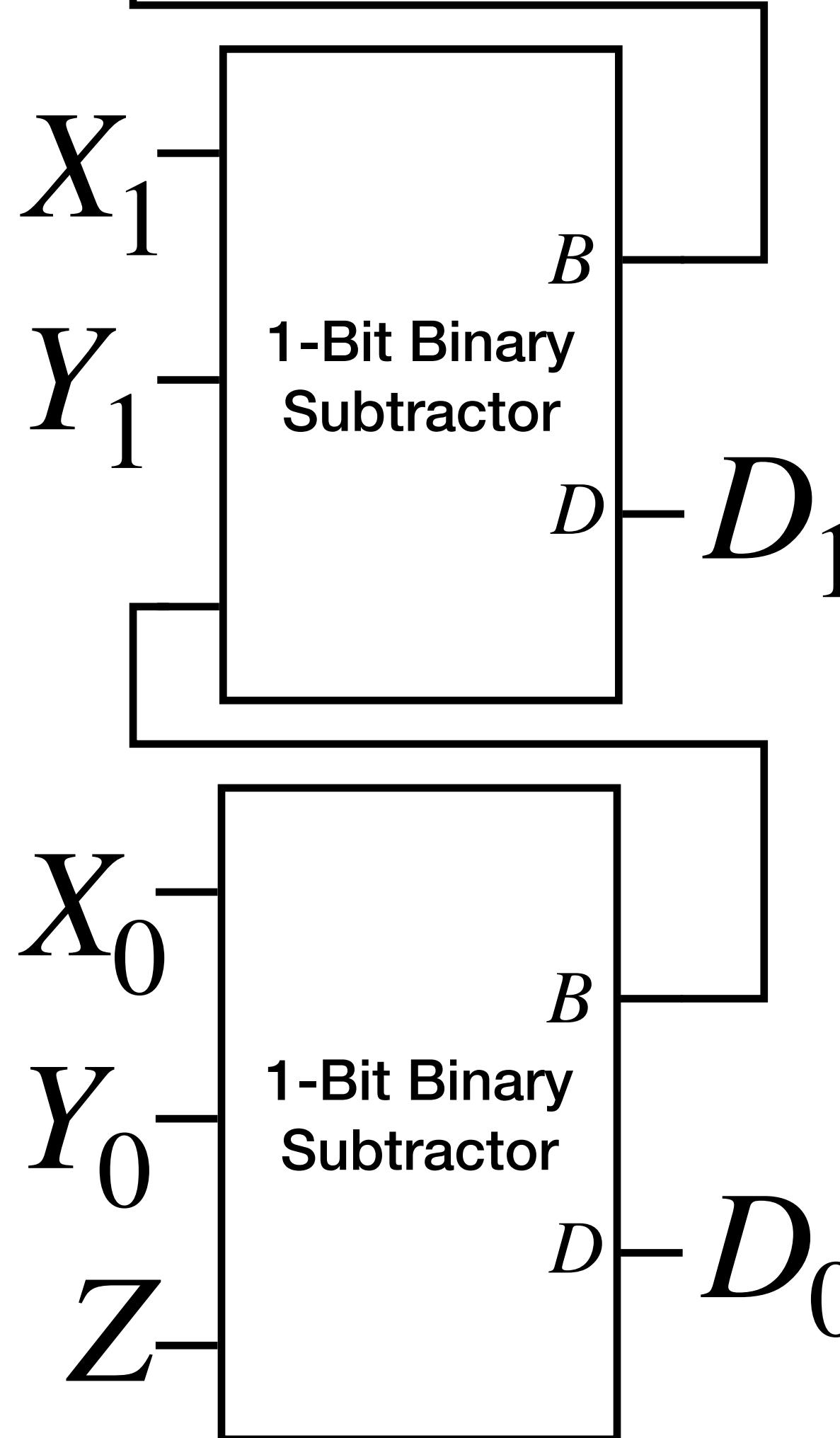

Borrows

Minuend $X_{0:n-1}$

Subtrahend $Y_{0:n-1}$

Difference $D_{0:n-1}$

$$\begin{array}{r} B \\ 000110 \\ 10110 \\ \hline - 10011 \\ \hline 00011 \end{array}$$

Input Output

Technology

- 1 bit Unsigned Subtractor

Review

Unsigned Binary Subtraction II

$X - Y$ when $Y > X$

What we have so far

- Binary Adder
- Binary Subtractor ($X - Y, X \geq Y$)

Unsigned Binary Subtraction

$$X > Y, F = X - Y$$

- We learned to perform subtraction, by subtracting the smaller number from the greater number
- What if it's the opposite? i.e. $X < Y, F = X - Y?$

Unsigned Binary Subtraction

Borrows

Minuend	10011
Subtrahend	- 00110
Difference	<hr/>

Borrows

Minuend	00110
Subtrahend	- 10011
Difference	<hr/>

Unsigned Binary Subtraction

Borrows

Minuend	10011
Subtrahend	- 00110
Difference	<hr/>

Borrows

Minuend	00110
Subtrahend	- 10011
Difference	<hr/>

Unsigned Binary Subtraction

Borrows	011000
Minuend	10011
Subtrahend	-00110
Difference	<hr/> 01101

Borrows	100110
Minuend	00110
Subtrahend	-10011
Difference	<hr/> 10011

Unsigned Binary Subtraction

Borrows	011000
Minuend	10011
Subtrahend	-00110
Difference	$\overline{01101}$

Borrows	100110
Minuend	00110
Subtrahend	-10011
Difference	$\overline{10011}$

This is correct

Unsigned Binary Subtraction

Borrows

011000

Minuend

10011

Subtrahend

-00110

Difference

01101

This is correct

Borrows

100110

Minuend

00110

Subtrahend

-10011

Difference

10011

This is incorrect

Unsigned Binary Subtraction

- Standard subtraction module works if the Minuend is bigger than the Subtrahend

Borrows

011000

Minuend

100111

Subtrahend

-00110

Difference

01101

Borrows

100110

Minuend

00110

Subtrahend

-10011

Difference

10011

This is correct

This is incorrect

Concept

Unsigned Binary Subtraction

- Standard subtraction module works if the Minuend is bigger than the Subtrahend

(2's compliment)

Borrows	100110
Minuend X	00110
Subtrahend Y	-10011
Difference D	<hr/> 10011
Corrected D'	-01101

This is incorrect

Concept

Unsigned Binary Subtraction

- Standard subtraction module works if the Minuend is bigger than the Subtrahend

- Incorrect output $D = 2^n + X - Y$

(2's compliment)

Borrows	1	00110
Minuend X	00110	
Subtrahend Y	- 10011	
<hr/>		
Difference D	10011	
Corrected D'	- 01101	

This is incorrect

Concept

Unsigned Binary Subtraction

- Standard subtraction module works if the Minuend is bigger than the Subtrahend
- Incorrect output $D = 2^n + X - Y$
- Correct output $D' = -(Y - X) = -(2^n - D) = -(\bar{D} + 1)$ (2's compliment)

Borrows	1	00110
Minuend X	0	0110
Subtrahend Y	$- 10011$	
Difference D	<hr/>	
Corrected D'	$- 01101$	

This is incorrect

Concept

2s compliment

- Given binary unsigned integer of n bits D , its 2s compliment

$$2^n - D = \overline{D} + 1$$

- Proof

- Biggest number represented in n bit: $(11\dots1)_2 = 2^n - 1$

$$2^n - D = [(11\dots1)_2 + 1] - D = (11\dots1)_2 - D + 1 = \overline{D} + 1$$

- Implementation

- Inversion and plus 1, easily doable as completer

Subtraction

Example

Subtraction

1. Compute $20-15=5$ using 6-bit binary

Subtraction

1. Compute $20-15=5$ using 6-bit binary
 - $20 = (010100)_2$, $15 = (001111)_2$

Subtraction

1. Compute $20-15=5$ using 6-bit binary

- $20 = (010100)_2, 15 = (001111)_2$

Borrows 001110
 010100
 -001111
 000101

Example

Subtraction

1. Compute $20-15=5$ using 6-bit binary

- $20 = (010100)_2, 15 = (001111)_2$

2. Compute $15-20=-5$ using 6-bit binary and 2s complement

Borrows

001110
010100
-001111
<hr/>
000101

Subtraction

1. Compute $20-15=5$ using 6-bit binary

- $20 = (010100)_2, 15 = (001111)_2$

2. Compute $15-20=-5$ using 6-bit binary and 2s complement

Borrows

001110
010100
-001111
<hr/>
000101

Subtraction

1. Compute $20-15=5$ using 6-bit binary

Borrows

1 100000

- $20 = (010100)_2, 15 = (001111)_2$

001111

2. Compute $15-20=-5$ using 6-bit binary and 2s complement

-010100

- Correction: $(111011)_2$ 2s complement: $(000101)_2$

111011

000101

Example

Subtraction

1. Compute $20-15=5$ using 6-bit binary

- $20 = (010100)_2, 15 = (001111)_2$

2. Compute $15-20=-5$ using 6-bit binary and 2s complement

-

Borrows

$$\begin{array}{r} \textcolor{red}{1} \ 100000 \\ 001111 \\ - 010100 \\ \hline 111011 \end{array}$$

Example


Subtraction

1. Compute $7-15=-8$ using 6-bit binary and 2s complement



Full Unsigned Subtraction

- Solution 1
 - Compare the Minuend and Subtrahend, switch places if the Subtrahend is greater, then add negative sign
- Solution 2
 - Use 2s compliment


Full Unsigned Subtraction

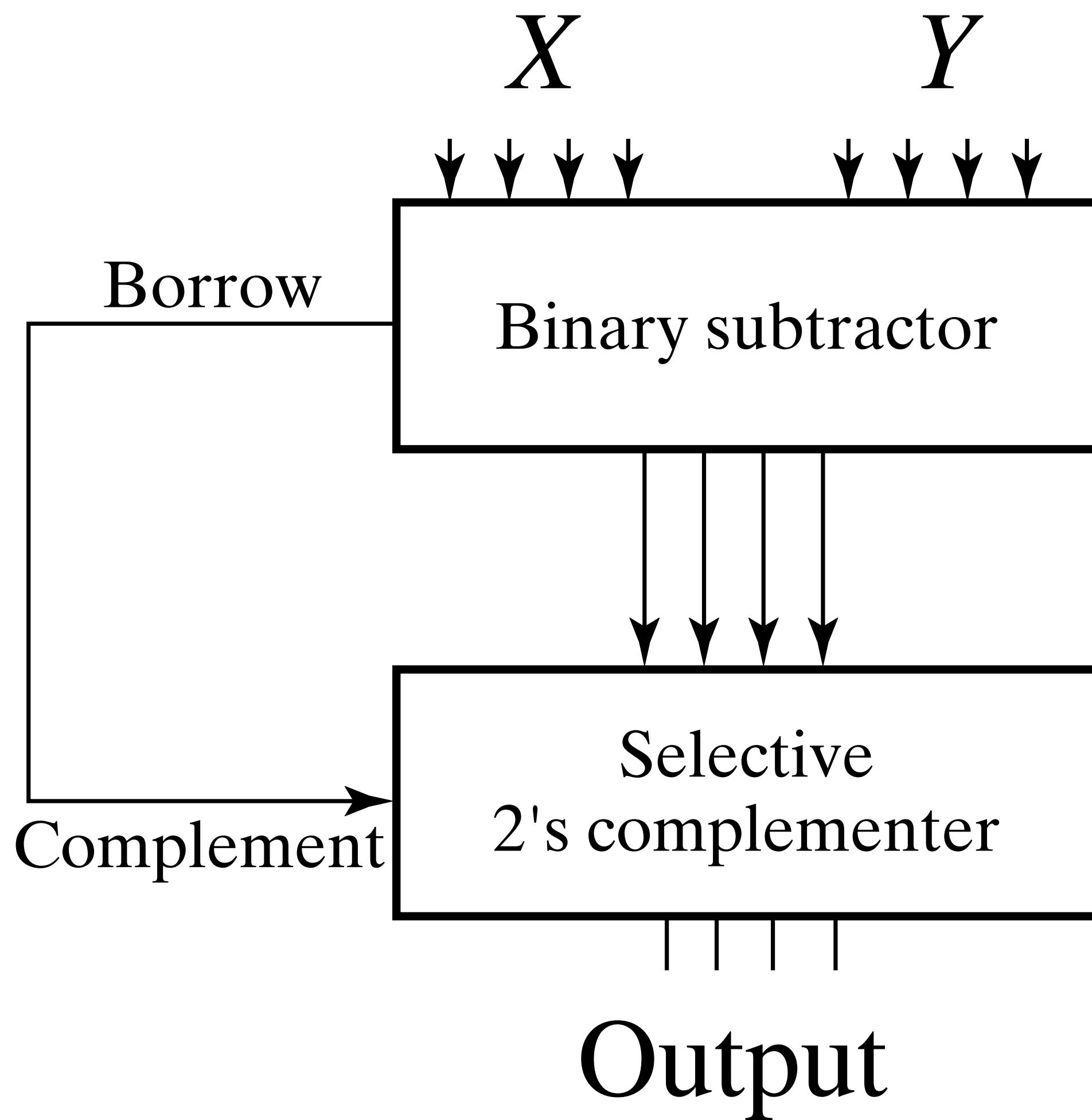

Full Unsigned Subtraction

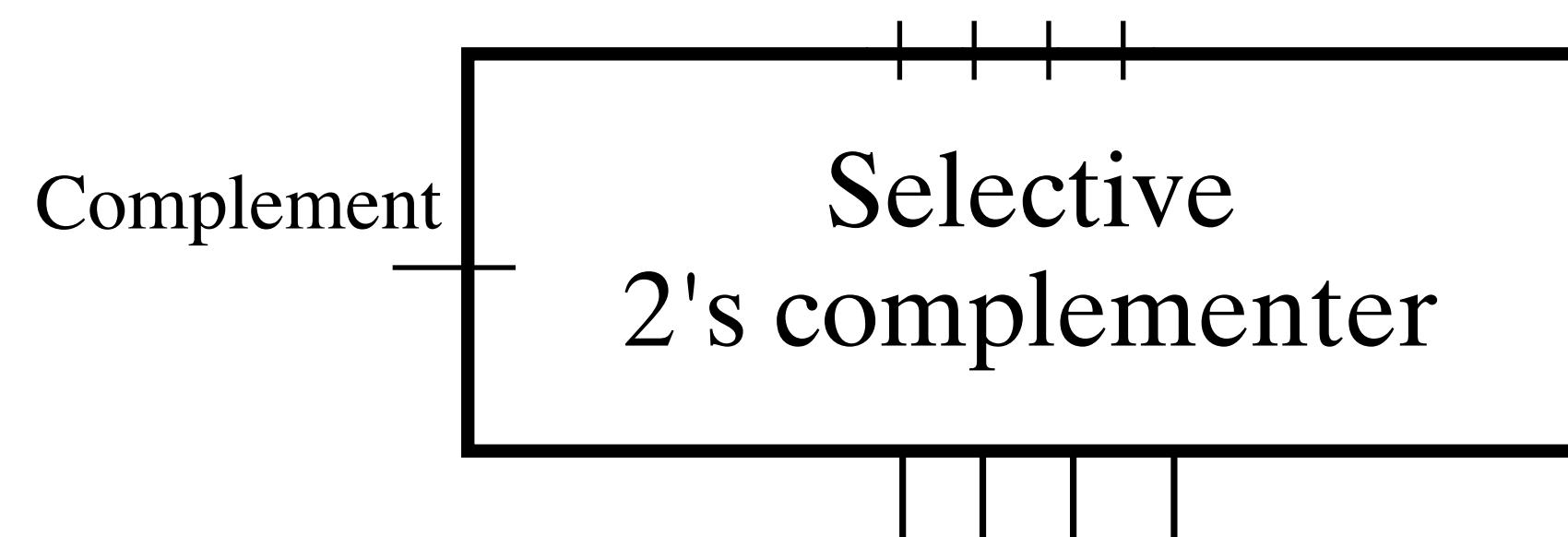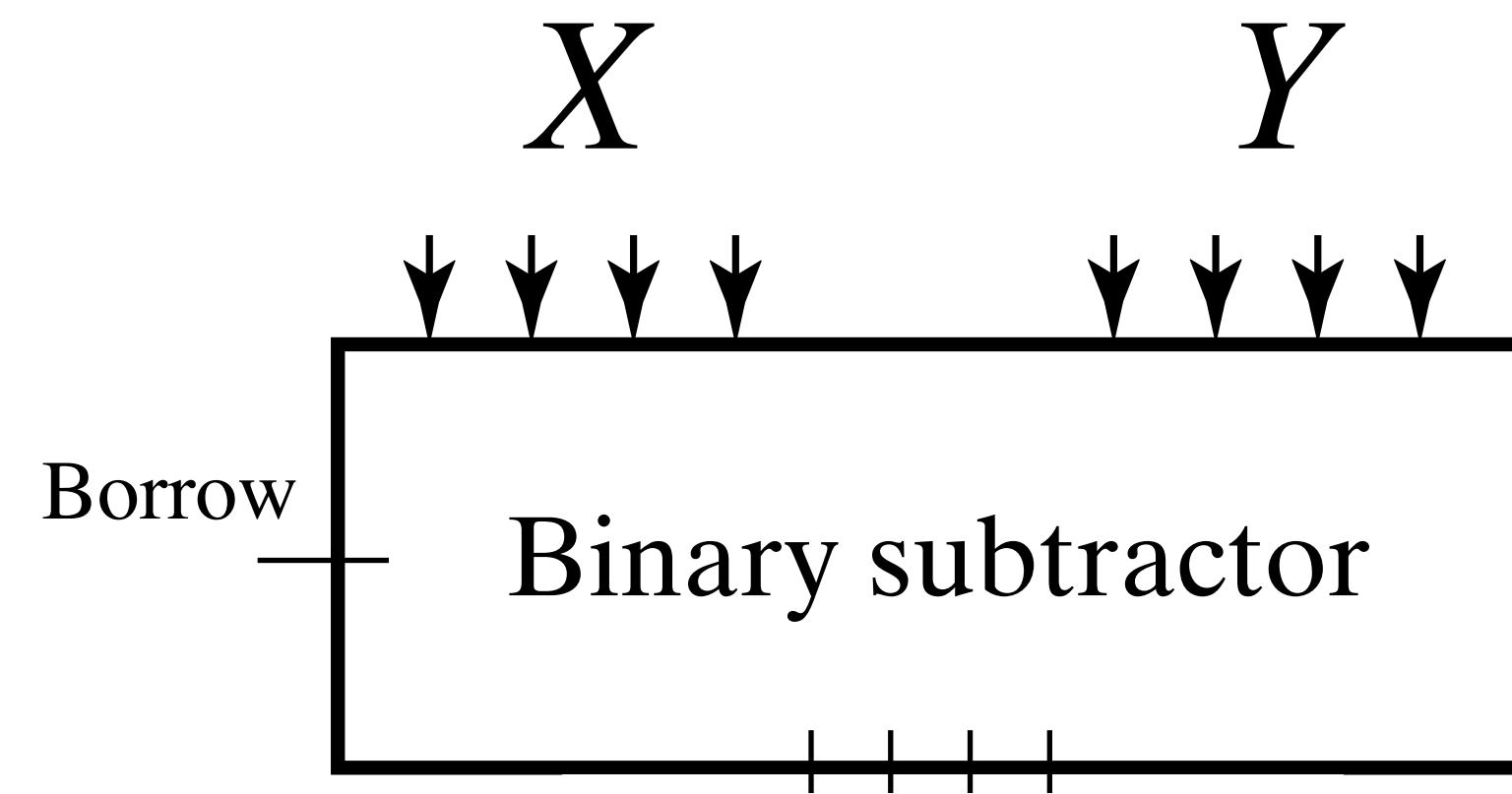

Adder-Subtractor

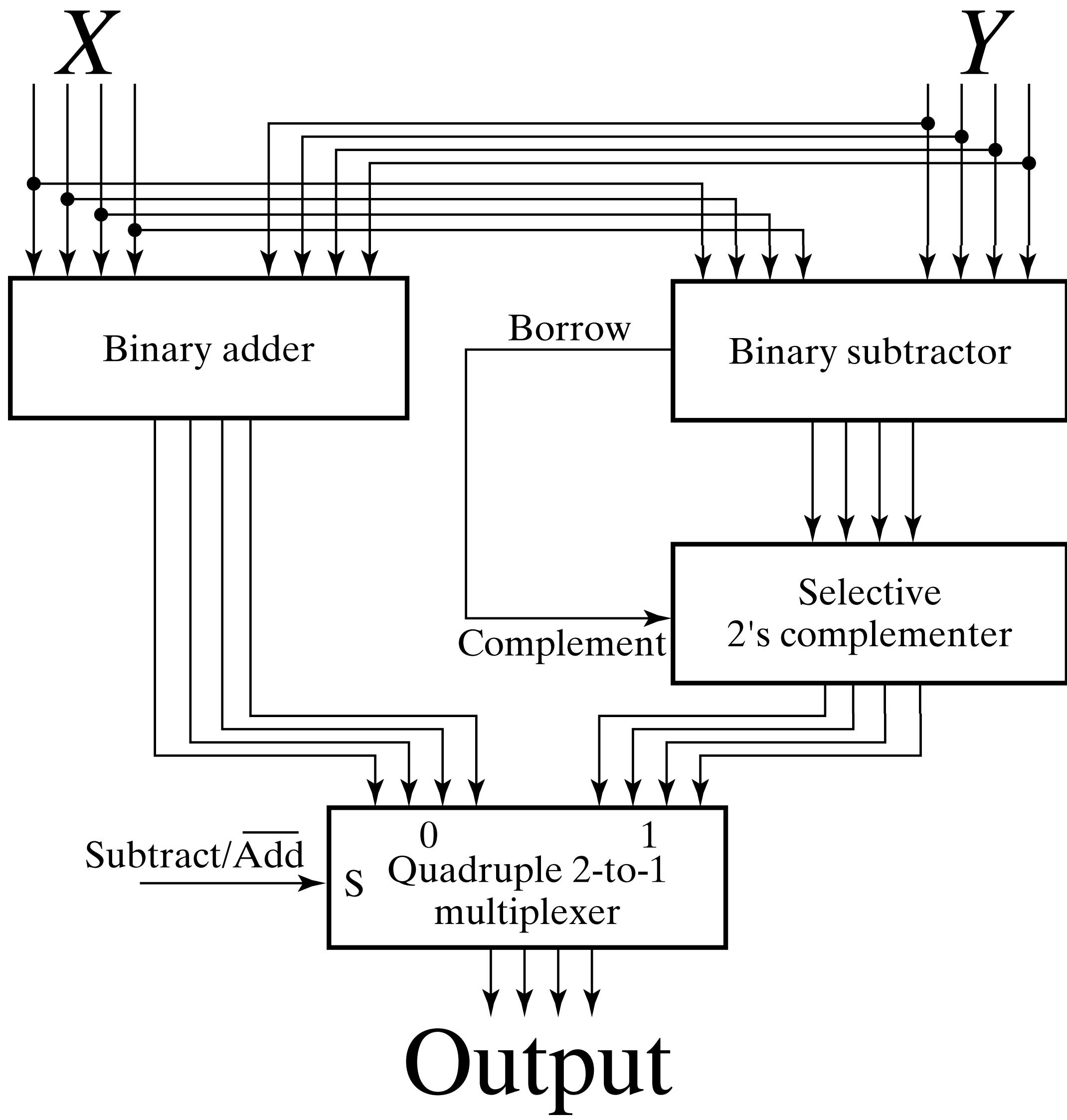

Unsigned Binary Subtraction III

What do you mean we can do subtraction using an adder?

2s compliment

$$2^n - D = \overline{D} + 1$$

Subtraction using 2s Complement

- Input: X and Y
- Y : 2s complement $Y' = \bar{Y} + 1$ ($\bar{Y} + 1 = 2^n - Y$)
- $X - Y = X + (2^n - Y) - 2^n = X + Y' - 2^n$
- Since $2^n = (10\dots0)_2$, and we only output n -bits, it can be discarded

Subtraction using 2s Complement

- $84 - 67$ (10bit)

Subtraction using 2s Complement

- 84 - 67 (10bit)

$$X = 0001010100$$

Subtraction using 2s Complement

- 84 - 67 (10bit)

$$X = 0001010100$$
$$Y = 0001000011$$

Subtraction using 2s Complement

- 84 - 67 (10bit)

2s complement

$$X = 0001010100$$

$$Y = 0001000011$$

$$Y' = 1110111101$$

Subtraction using 2s Complement

- 84 - 67 (10bit)

2s complement

$$X = 0001010100$$

$$Y = 0001000011$$

$$Y' = 1110111101$$

$$X + Y' = 10000010001$$

Subtraction using 2s Complement

- 84 - 67 (10bit)

$$X = 0001010100$$

$$Y = 0001000011$$

2s complement

$$Y' = 1110111101$$

$$X + Y' = 10000010001$$

discard carry

$$X + Y' - 2^{10} = 0000010001$$

Subtraction using 2s Complement

- 84 - 67 (10bit)

2s complement

$$X = 0001010100$$

$$Y = 0001000011$$

$$Y' = 1110111101$$

$$X + Y' = 10000010001$$

discard carry

$$X + Y' - 2^{10} = 0000010001$$

verify

$$(84 - 67)_{10} = 17_{10} = 10001 = 0000010001$$

Example

Subtraction using 2s Complement

- 84 - 67 (10bit)

2s complement

$$X = 0001010100$$

$$Y = 0001000011$$

$$Y' = 1110111101$$

$$X + Y' = 10000010001$$

discard carry

$$X + Y' - 2^{10} = 0000010001$$

correct!

verify

$$(84 - 67)_{10} = 17_{10} = 10001 = 0000010001$$

Example


P2
Subtraction

Adder-Subtractor Unit

Concept


Adder-Subtractor Unit

1. Adder

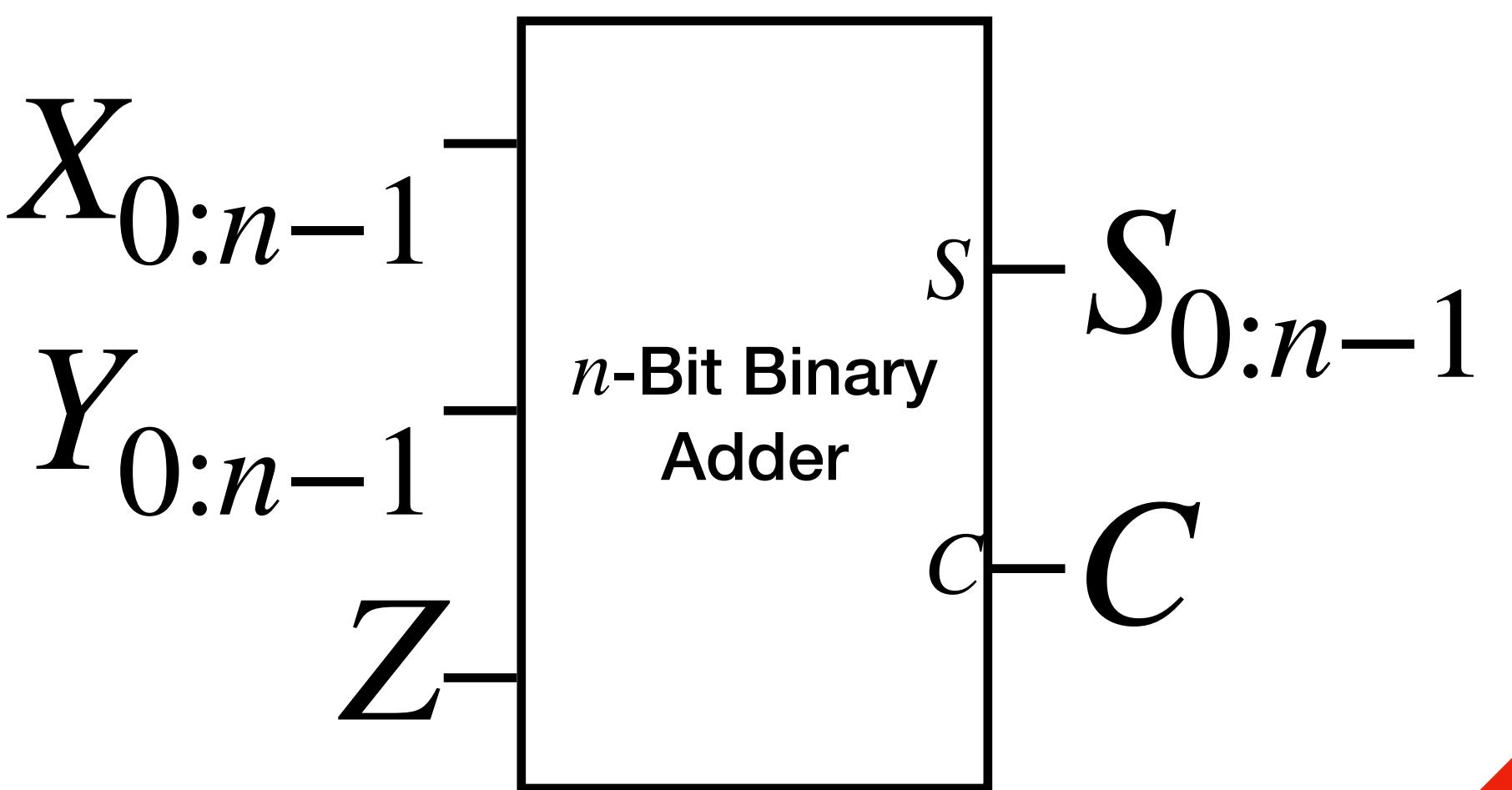


Adder-Subtractor Unit

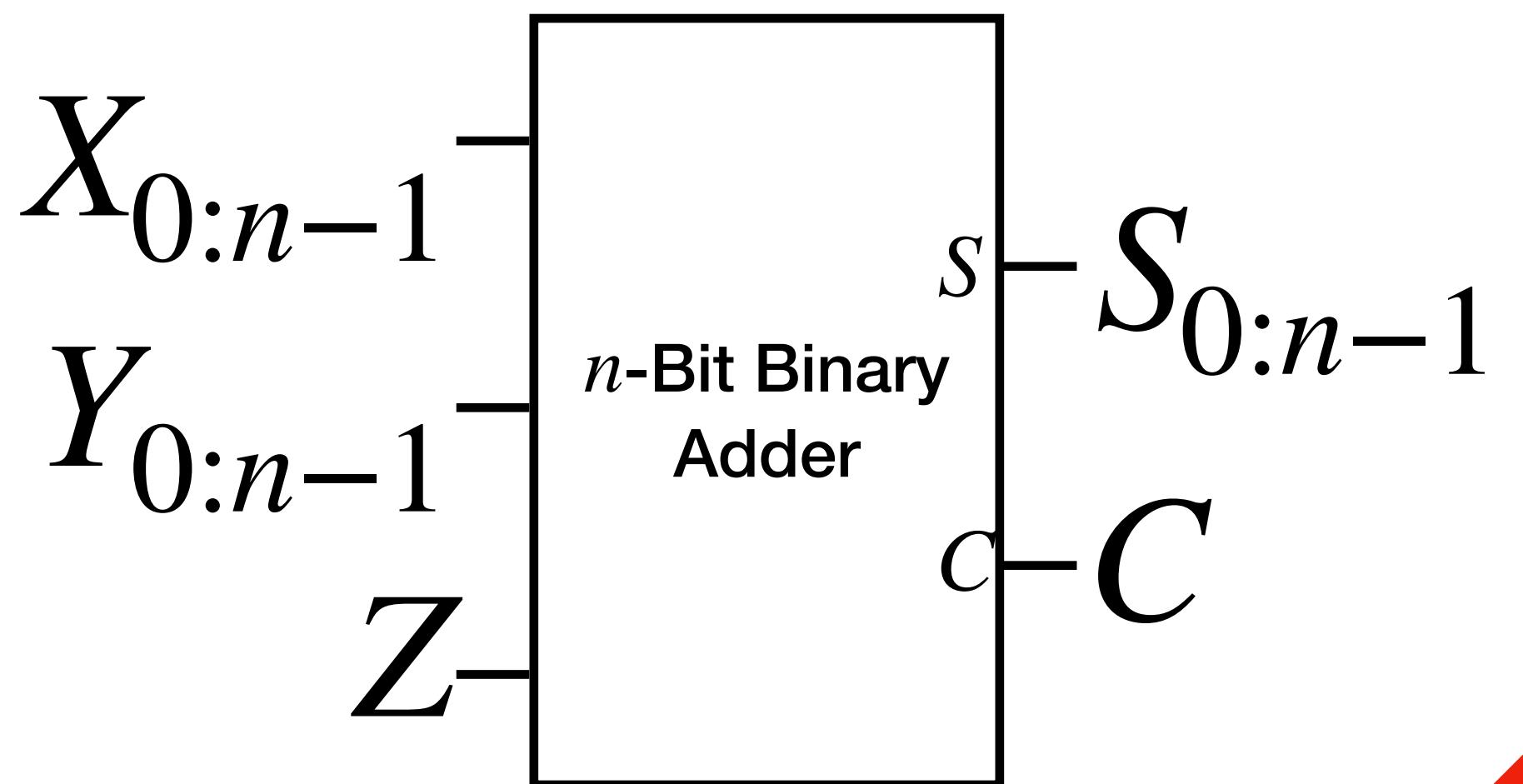1. Adder
2. Complementer (Inverting and add 1)




Adder-Subtractor Unit

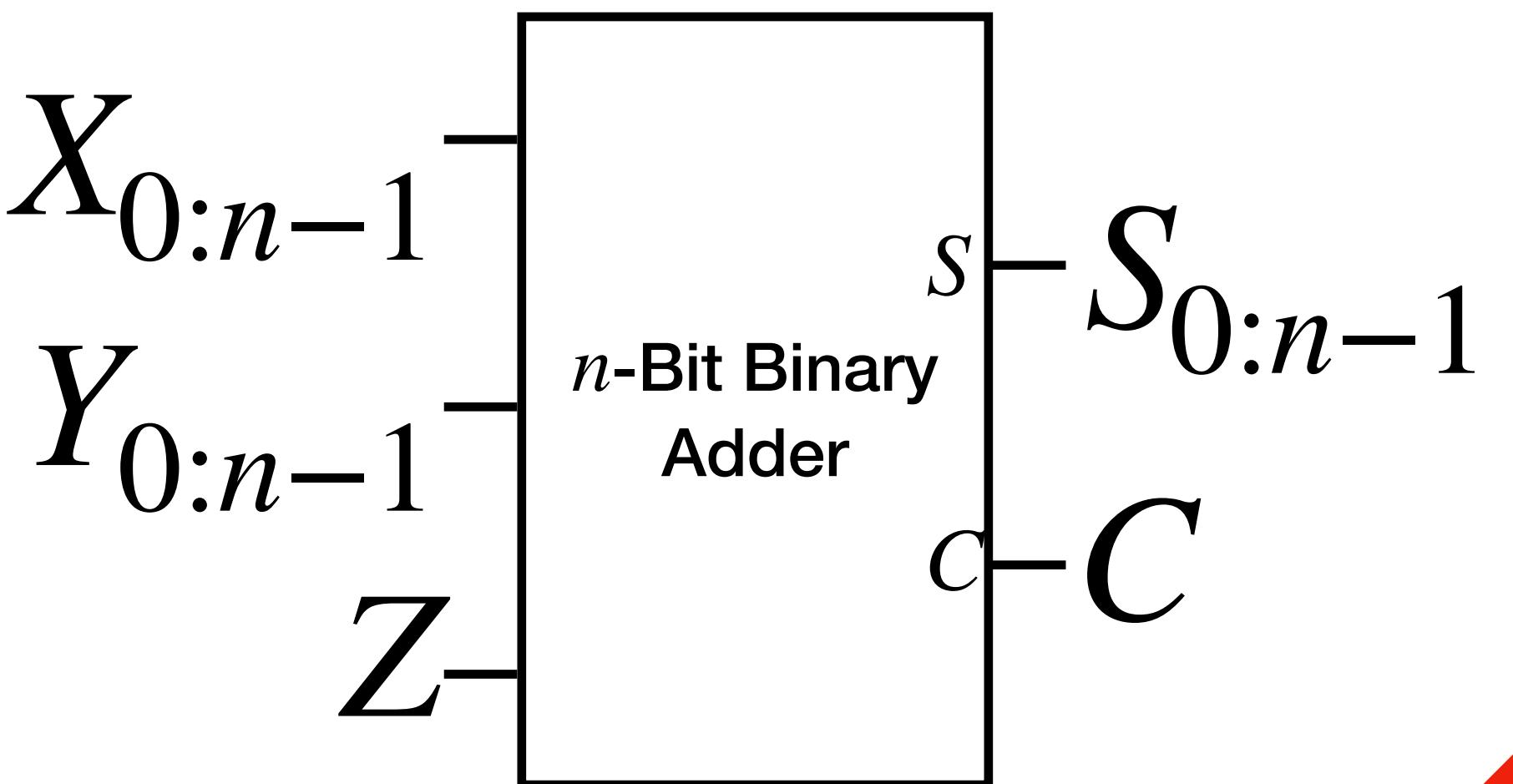1. Adder
2. Complementer (Inverting and add 1)
 - Or just inverting, and then plus one




Adder-Subtractor Unit

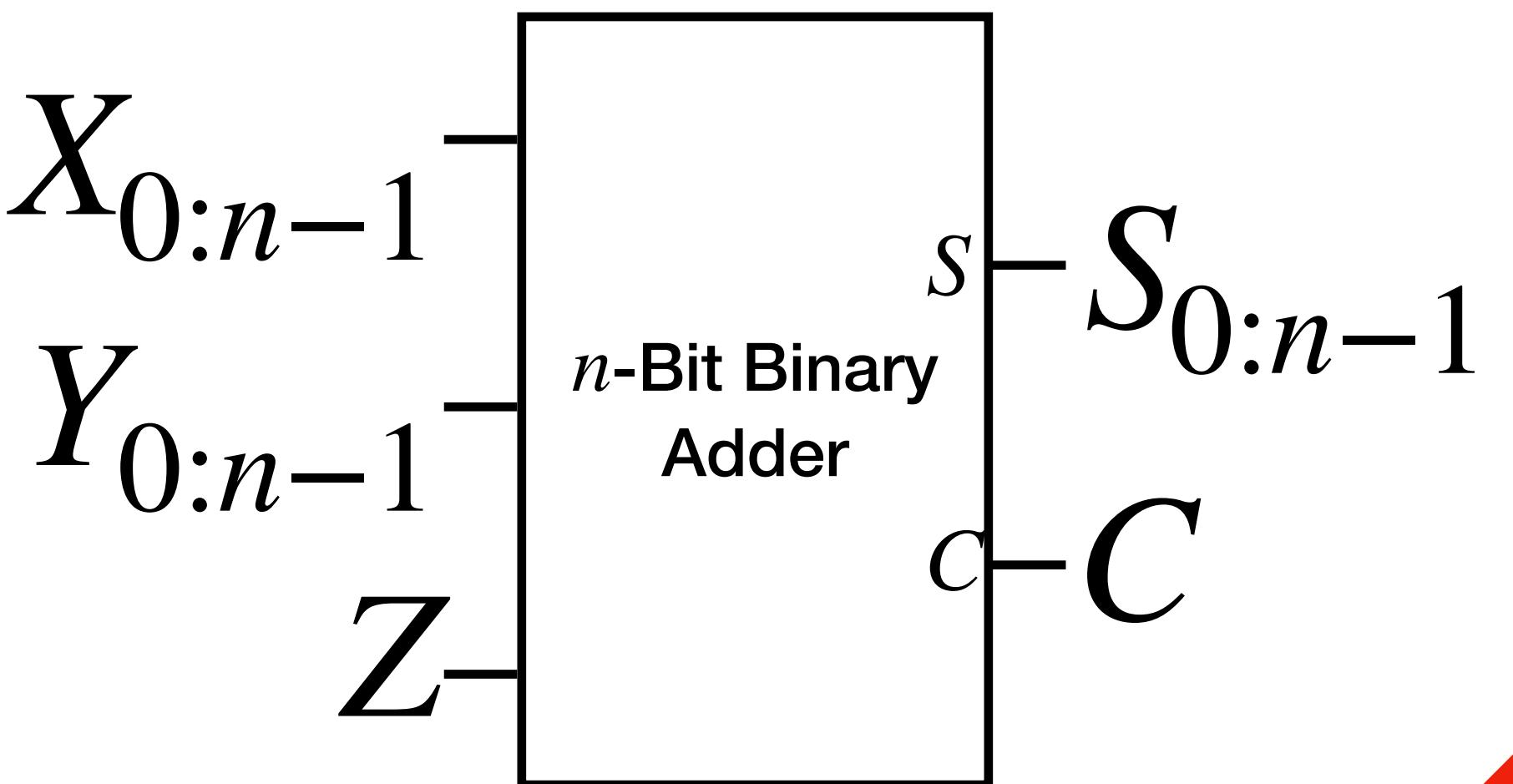1. Adder
2. Complementer (Inverting and add 1)
 - Or just inverting, and then plus one
 - Addition: $X + Y$




Adder-Subtractor Unit

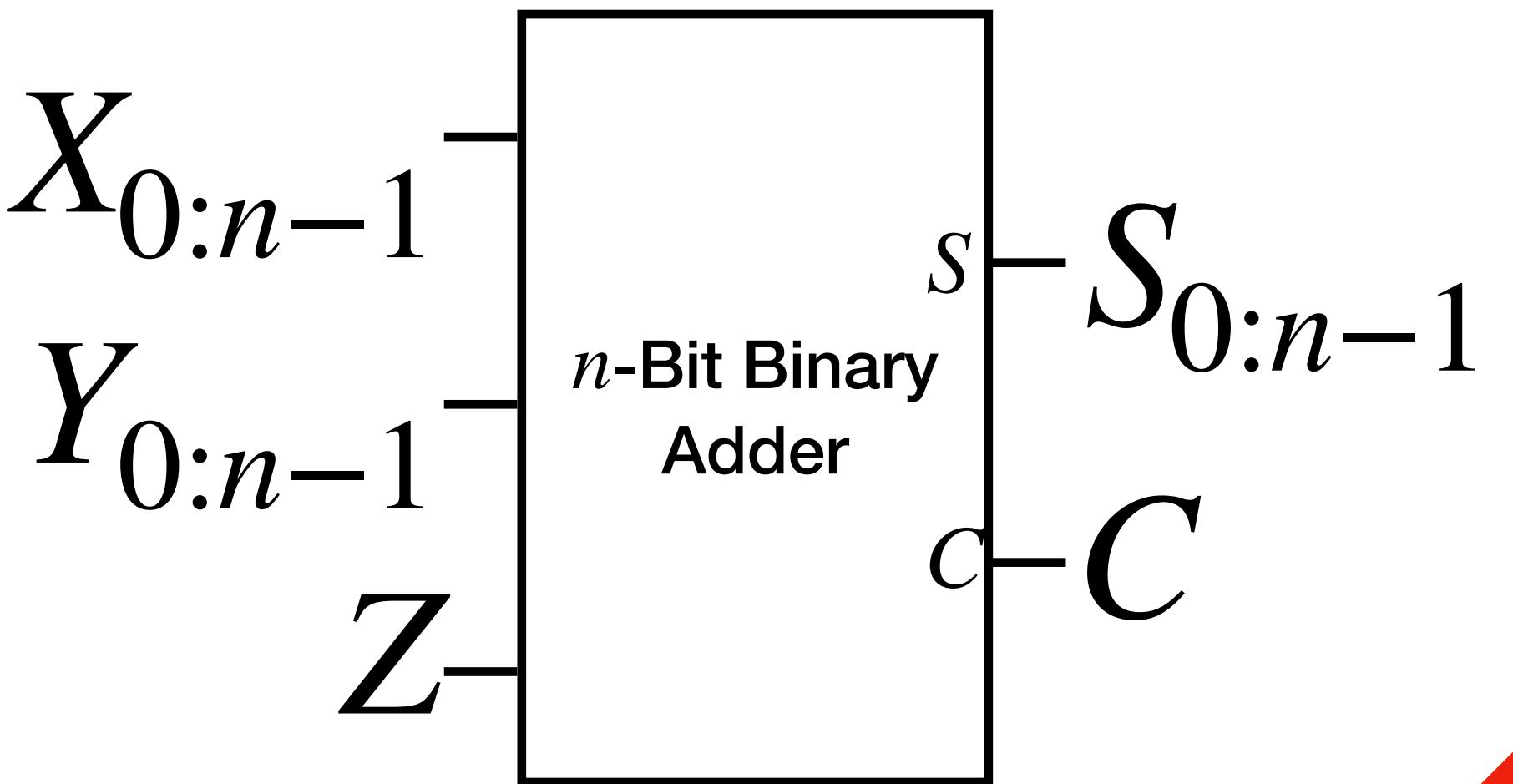1. Adder
2. Complementer (Inverting and add 1)
 - Or just inverting, and then plus one
 - Addition: $X + Y$
 - Subtraction: $X - Y = X + \bar{Y} + 1 - 2^n$




Adder-Subtractor Unit

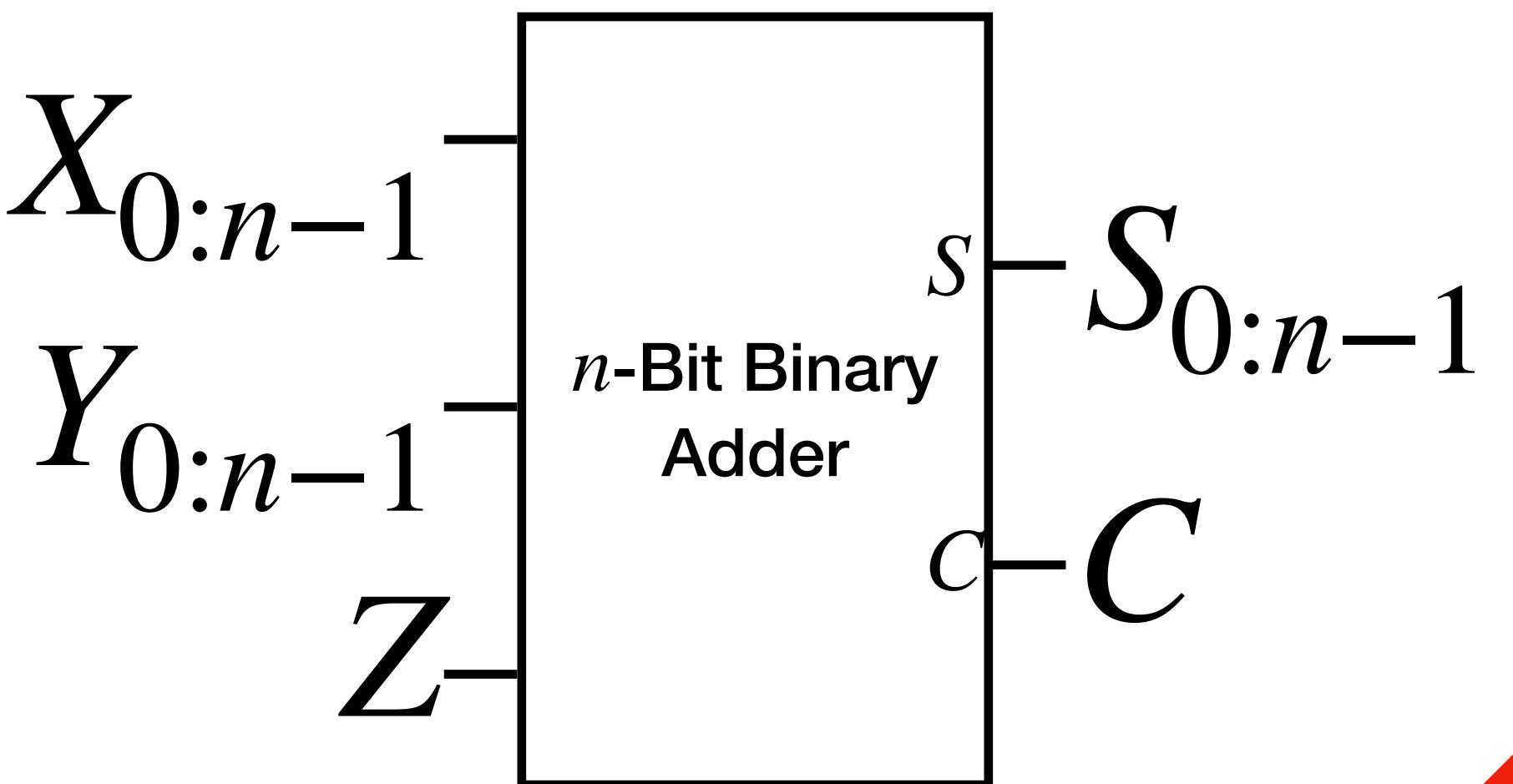1. Adder
2. Complementer (Inverting and add 1)
 - Or just inverting, and then plus one
 - Addition: $X + Y$
 - Subtraction: $X - Y = X + \bar{Y} + 1 - 2^n$
 - We are using n -bit adder, 2^n can be disregarded




Adder-Subtractor Unit

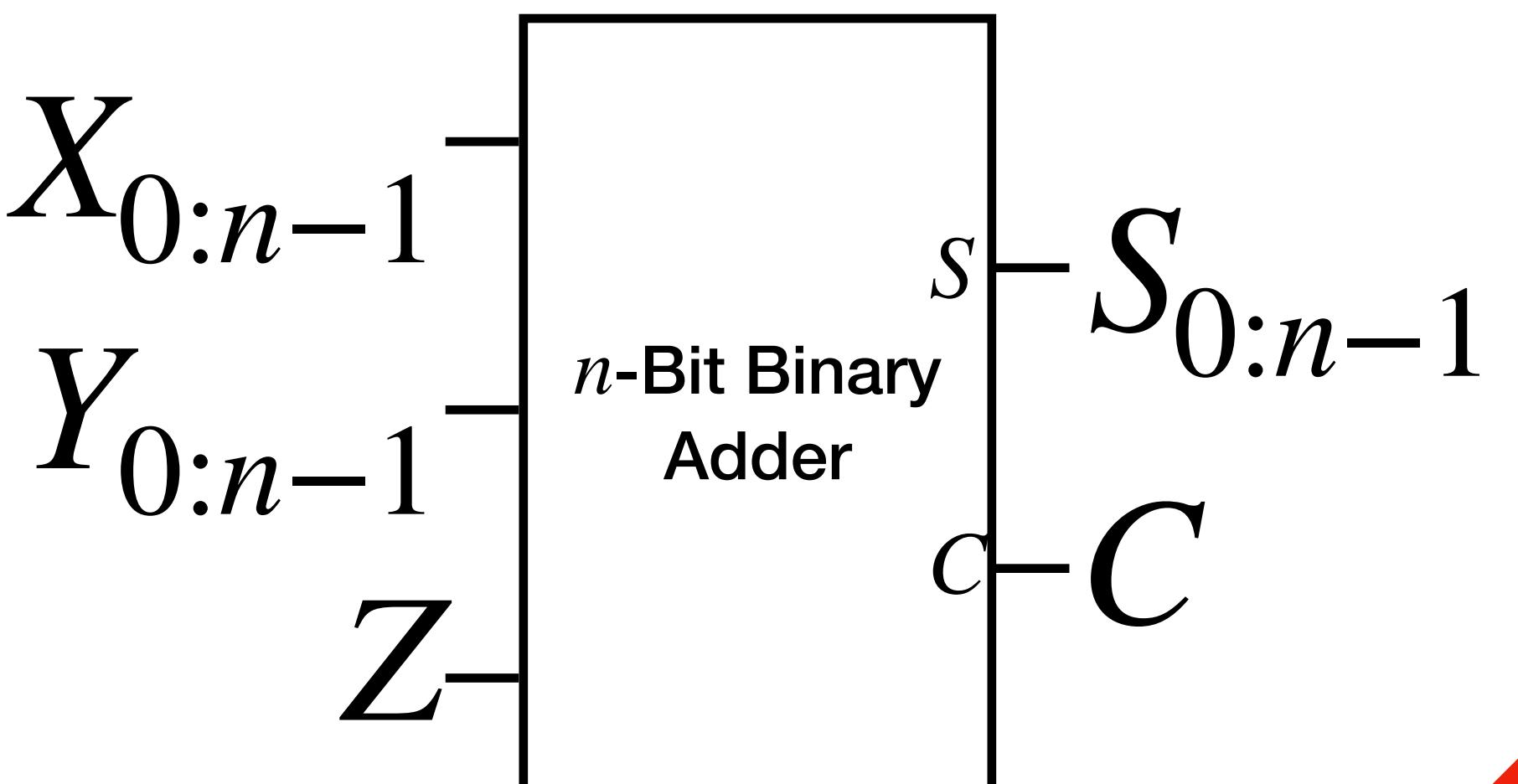1. Adder
2. Complementer (Inverting and add 1)
 - Or just inverting, and then plus one
 - Addition: $X + Y$
 - Subtraction: $X - Y = X + \bar{Y} + 1 - 2^n$
 - We are using n -bit adder, 2^n can be disregarded
 - The plus 1 here can be Z input to the adder



Adder-Subtractor Unit

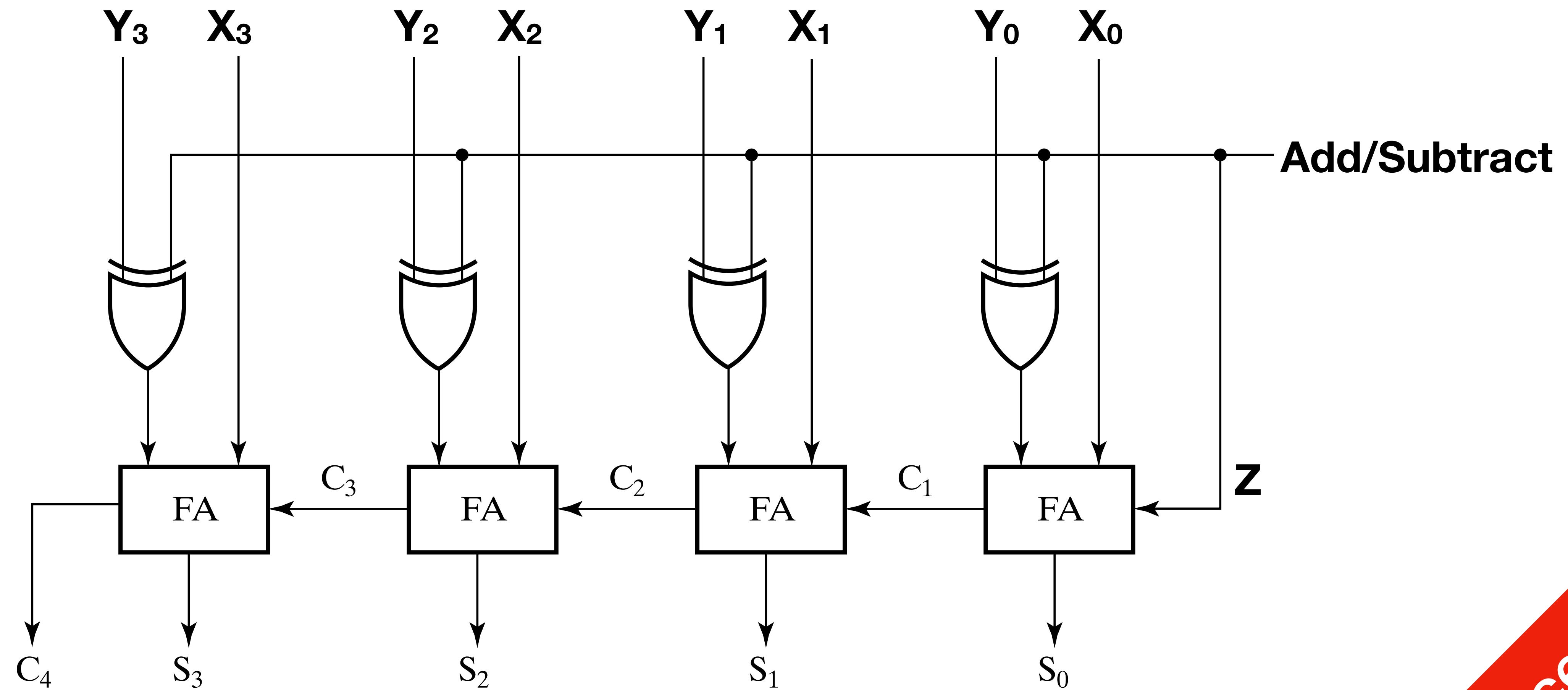

Adder Subtractor Units (Unsigned)

- Binary Adder
- Binary Subtractor
- Binary Adder-Subtractor Unit, using Adder, Subtractor, Complementer and Multiplexer
- Binary Adder-Subtractor Unit using Adder and XOR

Excercises

2s Complement
Subtraction using 2s Complement

P1
Subtraction

Subtraction

Exercise

Subtraction

- Compute $10 - 7$ using 4-bit binary using Adder and 2s complement

Subtraction

Subtraction


- Compute $24 - 17$ using 8-bit binary using Adder and 2s complement

Hardware Description Language

VHDL (VHSIC-HDL): Very High Speed Integrated Circuit Hardware Description Language


Previous: 1-bit Half Adder

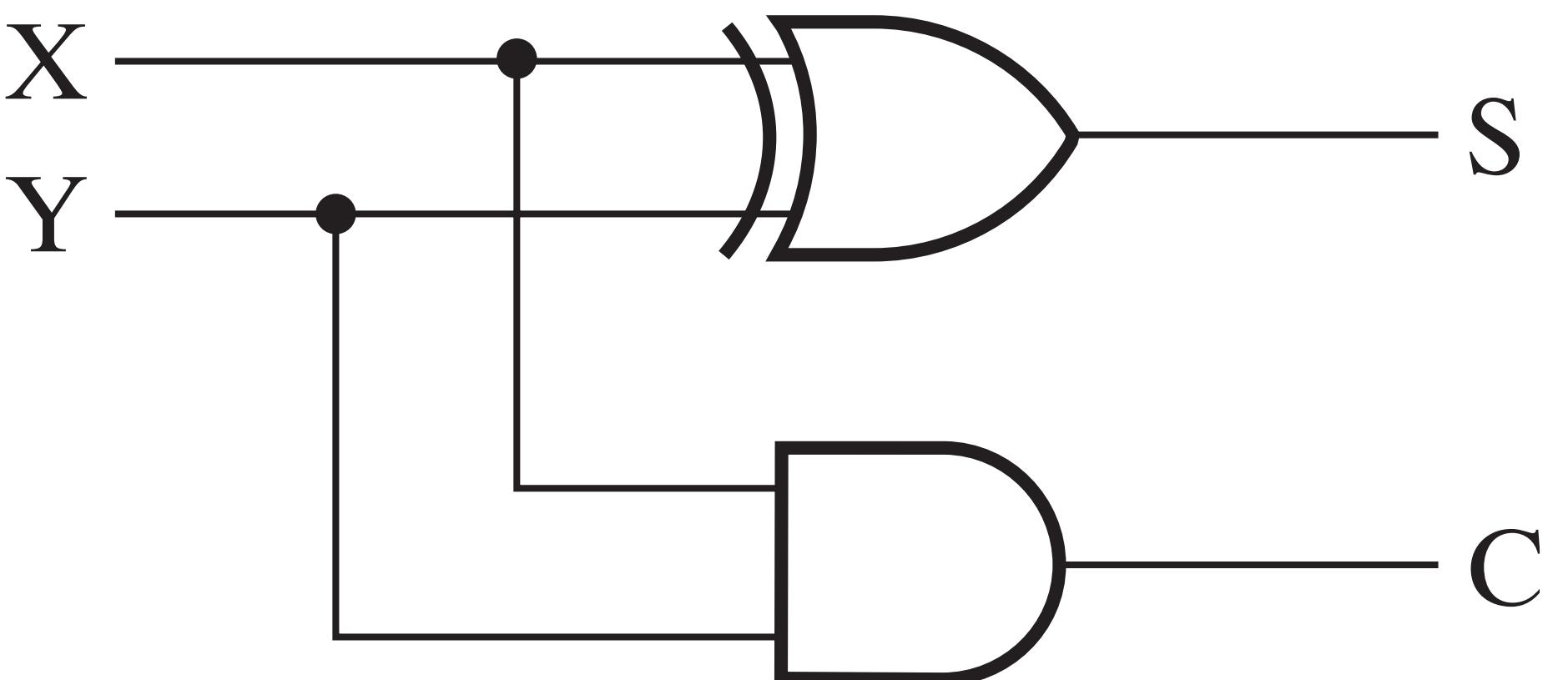- Create a new component in VHDL called HalfAdder1
 - Input: X, Y
 - Output: S, C
 - Don't use AFTER



Previous: 1-bit Half Adder
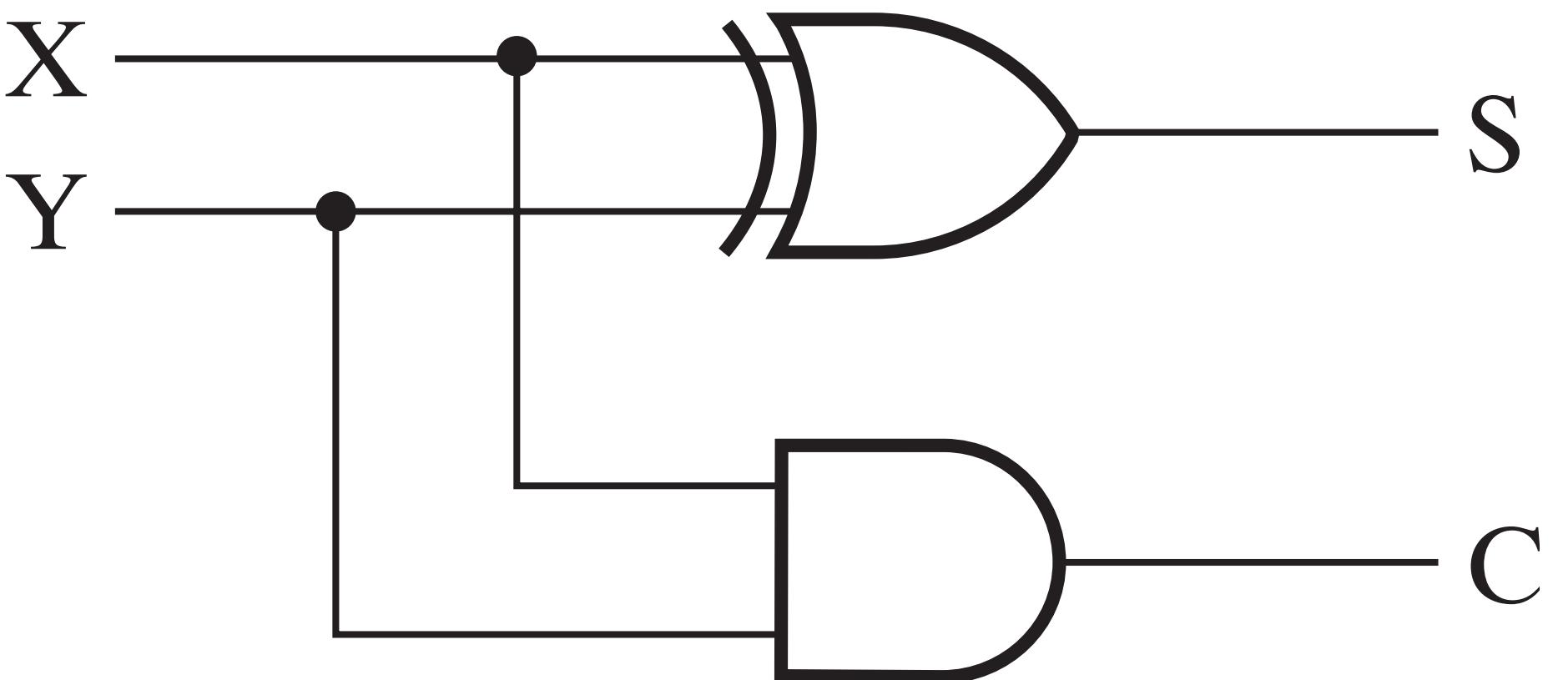
```
architecture arch1 of HalfAdder is
begin
    S <= X XOR Y;
    C <= X AND Y;
end arch1;
```



Today's Tasks

Today's Tasks

- 1-bit Half Adder

Today's Tasks

- 1-bit Half Adder
- 1-bit Full Adder using Schema Diagram (Logic Circuit Diagram)

Today's Tasks

- 1-bit Half Adder
- 1-bit Full Adder using Schema Diagram (Logic Circuit Diagram)
- 4-bit Full Adder using Schema Diagram (Logic Circuit Diagram)

Today's Tasks

- 1-bit Half Adder
- 1-bit Full Adder using Schema Diagram (Logic Circuit Diagram)
- 4-bit Full Adder using Schema Diagram (Logic Circuit Diagram)
- 4-bit Adder-Subtractor using Schema Diagram (Logic Circuit Diagram)