



02.11.20 11:58

CSCI 150

Introduction to Digital and Computer System Design

Lecture 4: Sequential Circuit I




Jetic Gū
2020 Fall Semester (S3)

Overview

- Focus: Basic Information Retaining Blocks
- Architecture: Sequential Circuit
- Textbook v4: Ch5 5.1, 5.2; v5: Ch4 4.1 4.2
- Core Ideas:
 1. Introduction
 2. SR and \overline{SR} Latches, D Latch


Combinational Logic Circuit Design

 - Design Principles
 - Knows: fixed-Length input and output
 - Knows: input/output mapping relations
 - Optimisation: Minimise overall delay




Combinational Logic Circuit Design

 - Features
 - Fixed-Length input and output
 - The same input will always give the same output
 - Operations are simultaneous with minimum delay



Combinational Logic Circuit Design

 
- Cannot handle variable length input
- Cannot store information
- Cannot perform multi-step tasks



Introduction to Sequential Circuit


Solution

 - Cannot handle variable length input
- Cannot store information
- Cannot perform multi-step tasks




Solution: Storage!

 - Cannot handle variable length input
- Cannot store information
- Cannot perform multi-step tasks




Solution: Storage!

 

- Cannot handle variable length input
- Cannot store information
- Cannot perform multi-step tasks
- Storage of partial input
- Storage of partial results and states
- Storage of instructions


Sequential Circuits

 - Handle variable-length input
- Store information
- Multi-step tasks
- **State Transition** from time t to $t + 1$



Definitions

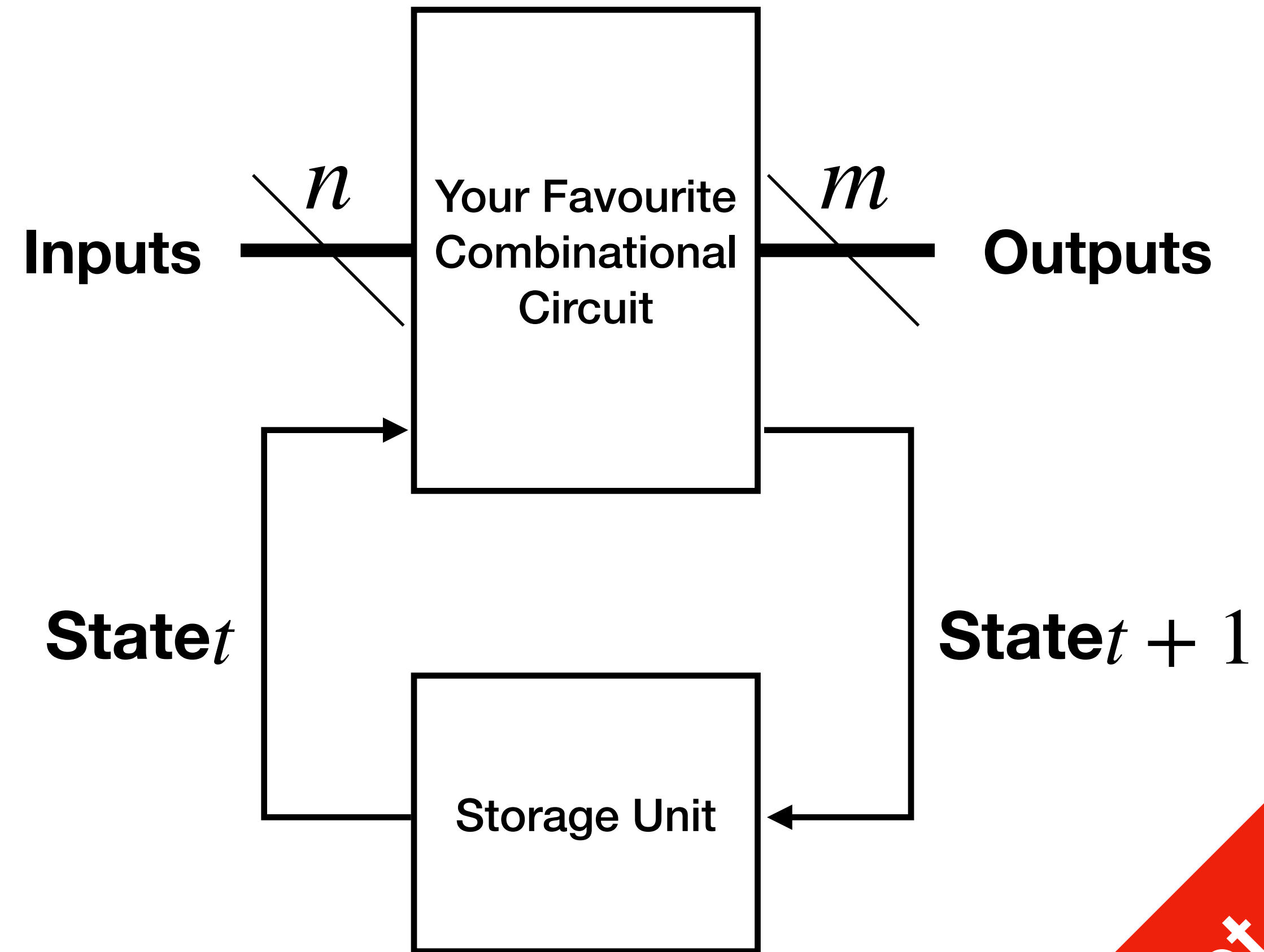1. **Storage Elements**
circuits that can store binary information
2. **State**
partial results, instructions, etc.
3. **Synchronous Sequential Circuit**
Signals arrive at discrete instants of time,
outputs at next time step
4. **Asynchronous Sequential Circuit**
Signals arrive at any instant of time,
outputs when ready



Definitions

3. Synchronous Sequential Circuit


Signals arrive at discrete instants of time, outputs at next time step

- Has Clock

4. Asynchronous Sequential Circuit

Signals arrive at any instant of time, outputs when ready

- May not have Clock

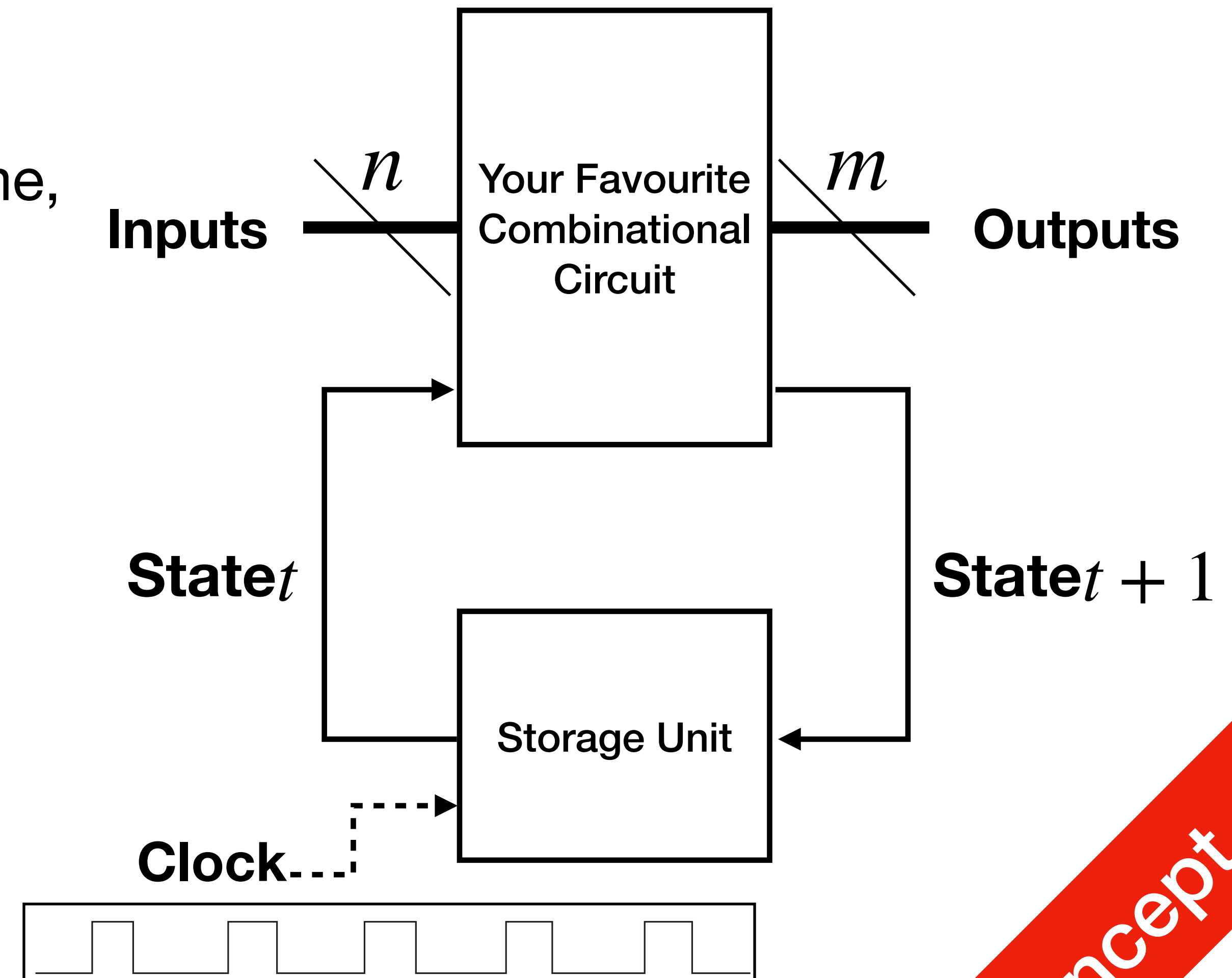

Question

1. Are calculators designed using **Combinational Circuits** or **Sequential Circuits**?
 - What about your microwave and toaster?
 - What about your digital watch (not smart)?
 - What about computers/smartphones?

Question



Question

2. Is this calculator using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?



Question

2. Is this calculator using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?
- What are the states for this calculator?



Question

2. Is this calculator using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?
- What are the states for this calculator?
 - What kind of information is stored?




Question




Question

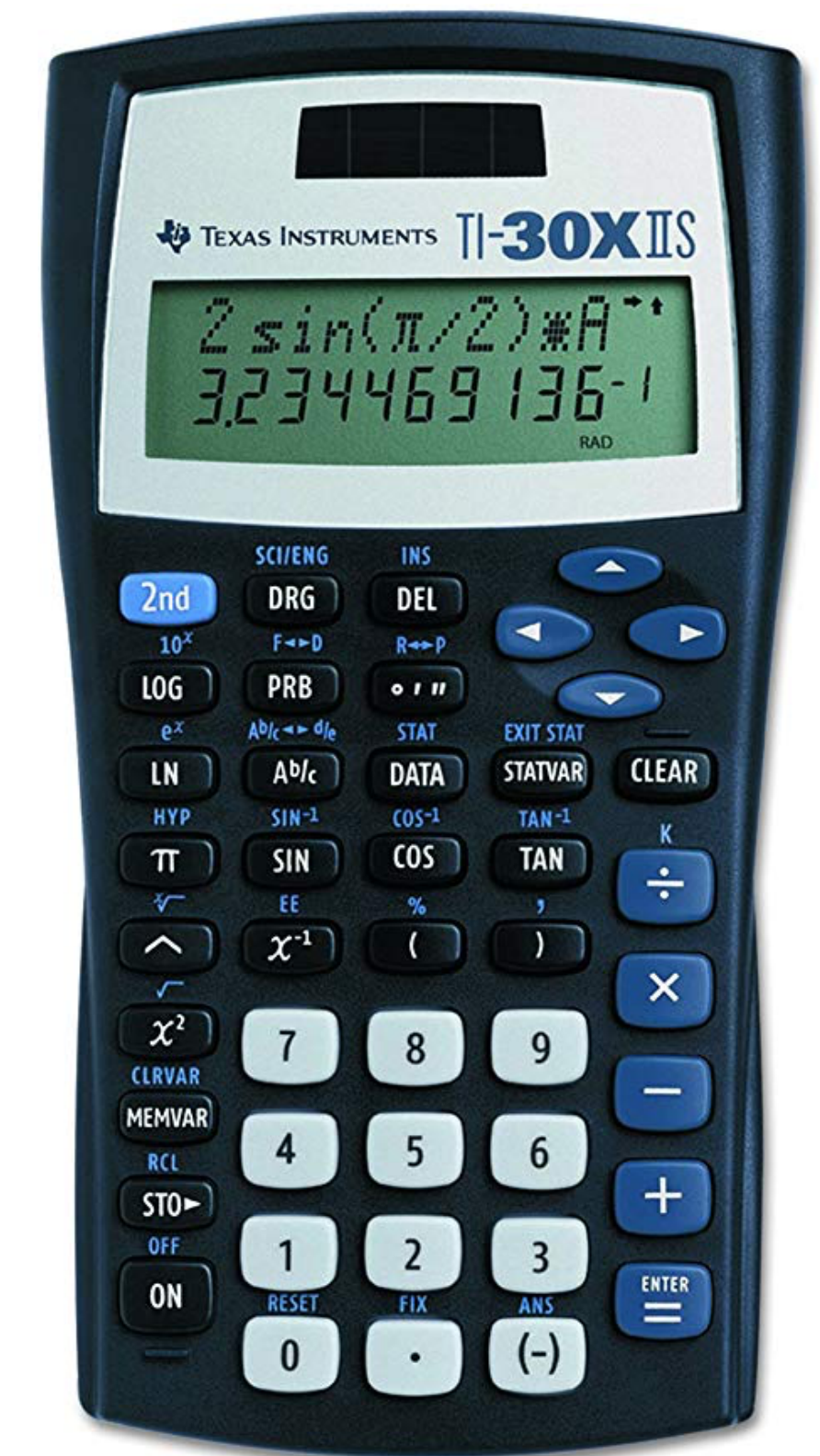3. Is this calculator using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?




Question

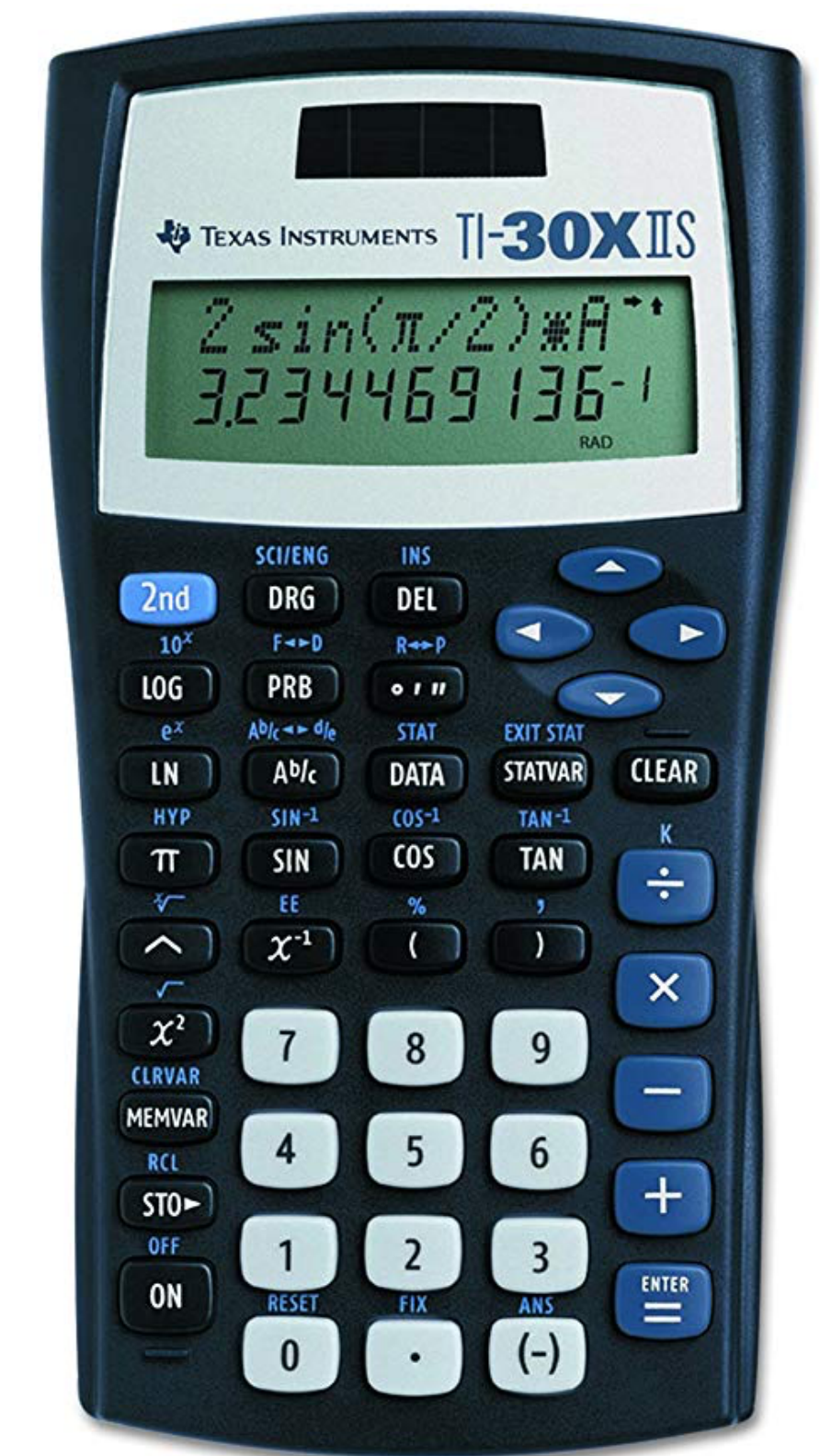3. Is this calculator using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?
- What are the states for this calculator?




Question

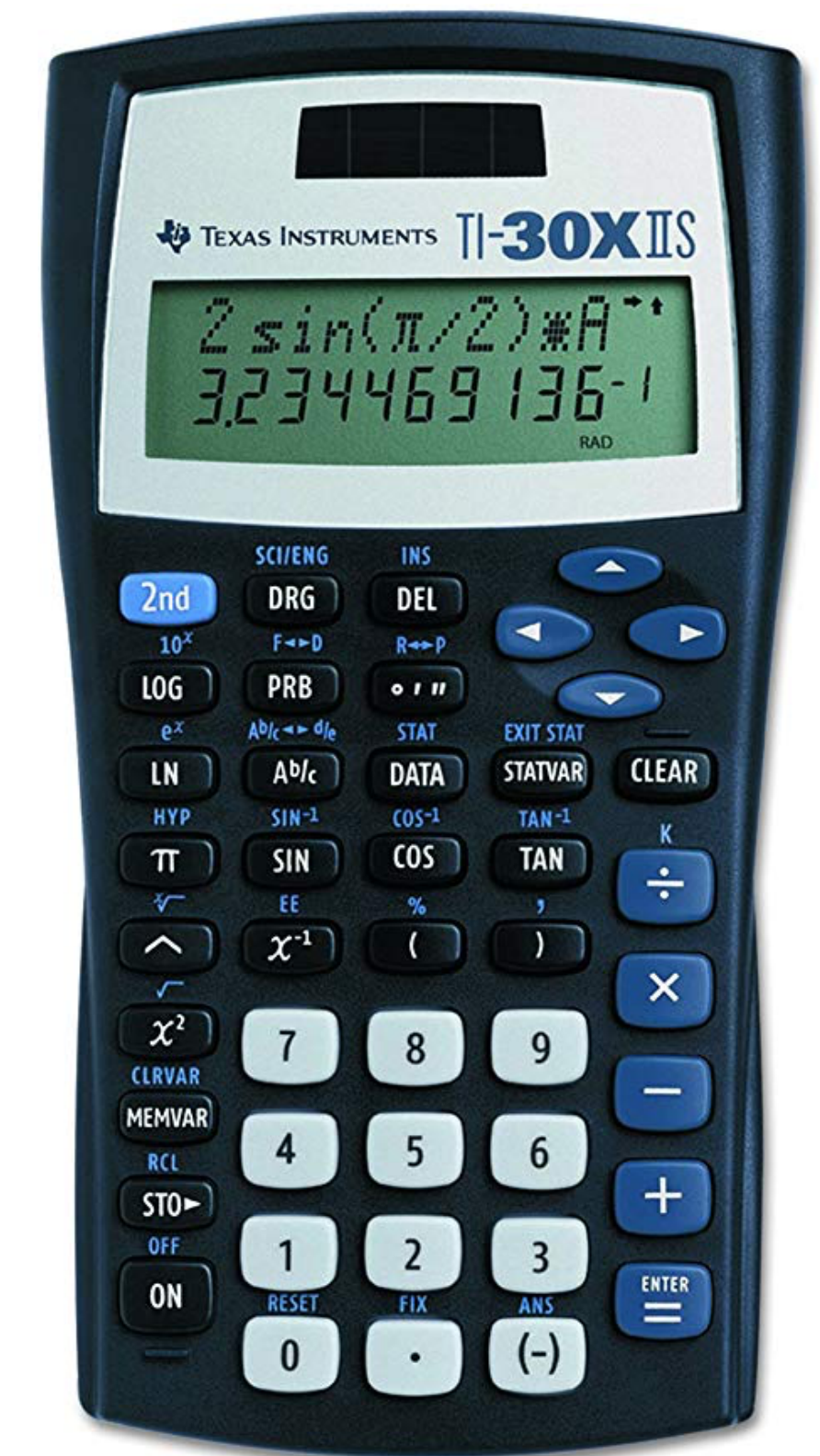3. Is this calculator using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?
- What are the states for this calculator?
 - What kind of information is stored?




Question

 


Question

 4. Is your laptop/PC/smartphone using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?




Question

 4. Is your laptop/PC/smartphone using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?
- What are the Input/Output devices of these computers?




Question

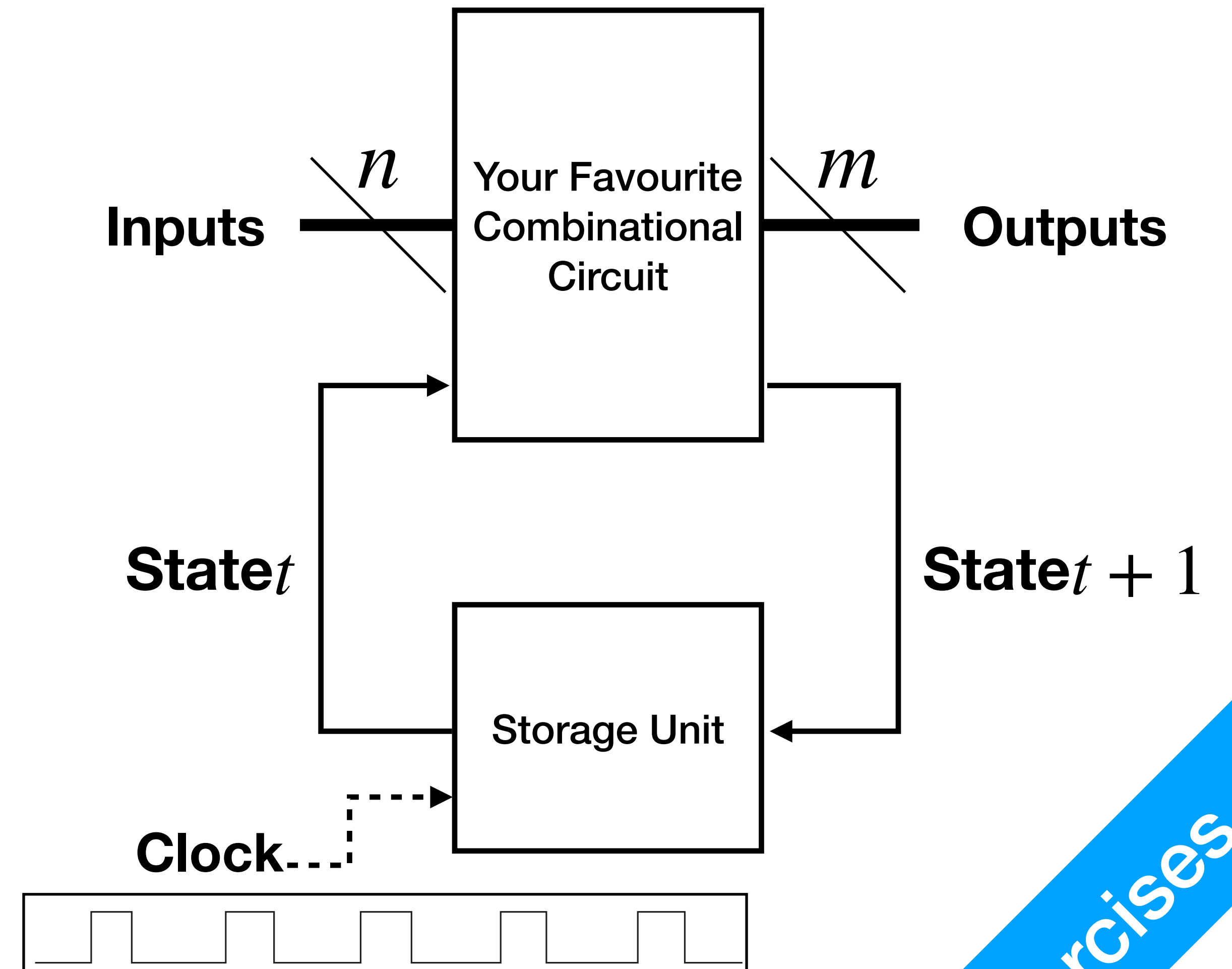4. Is your laptop/PC/smartphone using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?
- What are the Input/Output devices of these computers?
 - What are the storage devices?



Question

 4. Is your laptop/PC/smartphone using **Asynchronous Sequential Circuit** or **Synchronous Sequential Circuit**?
- What are the Input/Output devices of these computers?
 - What are the storage devices?
 - What about CPU?




Latches

SR and \overline{SR} Latches, D Latch


Stability

 - Stable State: the values in a circuit after brief changing due to delay in passing information, reaches a state where it doesn't change anymore -




Stability

 - Stable State: the values in a circuit after brief changing due to delay in passing information, reaches a state where it doesn't change anymore -




Stability

 - Stable State: the values in a circuit after brief changing due to delay in passing information, reaches a state where it doesn't change anymore -




Stability

 - Stable State: all values in a circuit after some changes due to delay in passing signals, reach a state where they don't anymore




Stability

 - Stable State: all values in a circuit after some changes due to delay in passing signals, reach a state where they don't anymore




Stability

 - Stable State: all values in a circuit after some changes due to delay in passing signals, reach a state where they don't anymore



Stability

 - Stable State: all values in a circuit after some changes due to delay in passing signals, reach a state where they don't anymore



- What other scenarios might bring about these instabilities?

Latches


- Basic Storage Elements
 - Maintain a binary state indefinitely, as long as there's power
 - The binary state inside can be changed




Summary

- SR Latches and \overline{SR} Latches
- D Latches


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 0

 


SR Latch: Stored value = 1

 


SR Latch: Stored value = 1

 


SR Latch: Stored value = 1

 


SR Latch: Stored value = 1

 


SR Latch: Stored value = 1

 


SR Latch: Stored value = 1

 


SR Latch: Stored value = 1

 


SR Latch: Stored value = 1

 


SR Latch: Stored value = 1

 


SR Latch: Stored value = 1

 


SR Latch: Stored value = 1

 


SR Latch: Stored value = 1

 


SR Latch: Stored value = 1

 


SR Latch: Stored value = 1

 


SR Latch: Stored value = 1

 


SR Latch: Stored value = 1

 

SR Latch: Stored value = 1

 


SR Latch: Stored value = 1

 


 Exercise

- Draw the SR Latch in LogicWorks as below, make sure it works as intended




\overline{SR} Latch

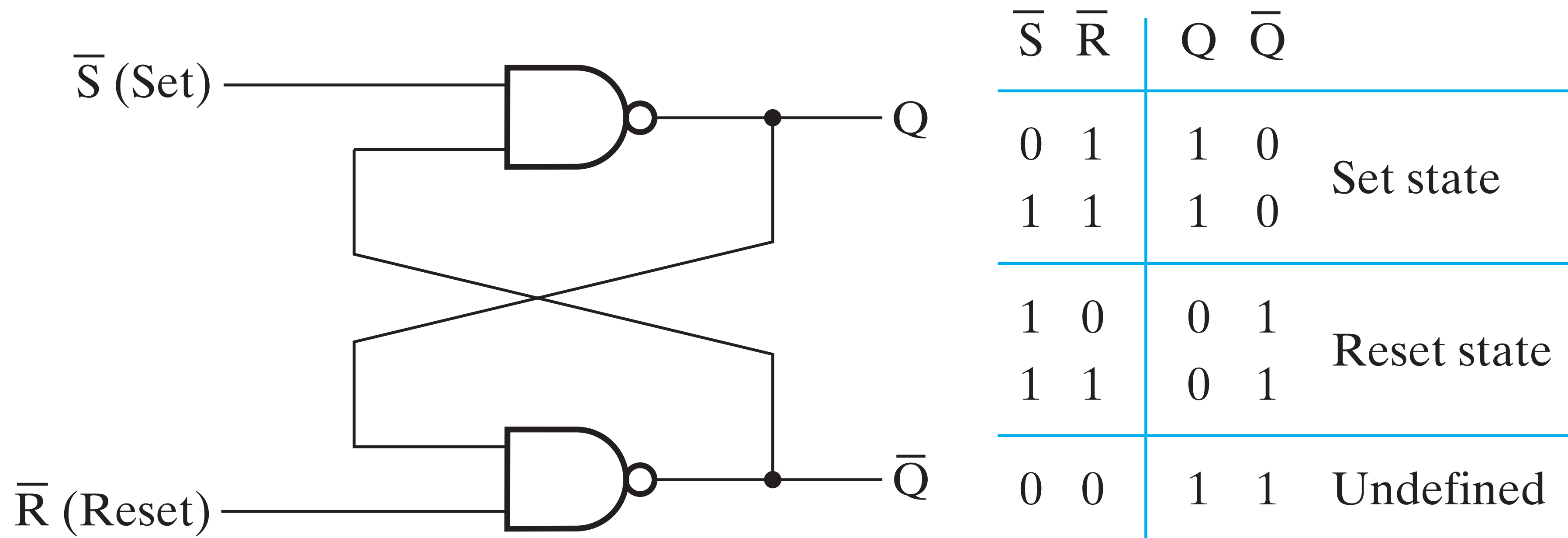

- Design similar to SR latches, but with NANDS
- Functions equivalent to SR latches with S and R inverted

D Latch

 

C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

- Implemented using \overline{SR} latches
- *C*: Signals changes to the stored states; *D* the value to change to

Latches

- Implement \overline{SR} latch, save as a component in your library
- Implement D latch, save as a component in your library

