



04.11.20 12:01

CSCI 150

Introduction to Digital and Computer System Design

Lecture 4: Sequential Circuit II




Jetic Gū
2020 Fall Semester (S3)


Overview

- Focus: Basic Information Retaining Blocks
- Architecture: Sequential Circuit
- Textbook v4: Ch5 5.2, 5.3; v5: Ch4 4.2, 5.3
- Core Ideas:
 1. Flip-Flops

SR Latch

 


\overline{SR} Latch

 

- Design similar to SR latches, but with NANDS
- Functions equivalent to SR latches with S and R inverted


D Latch

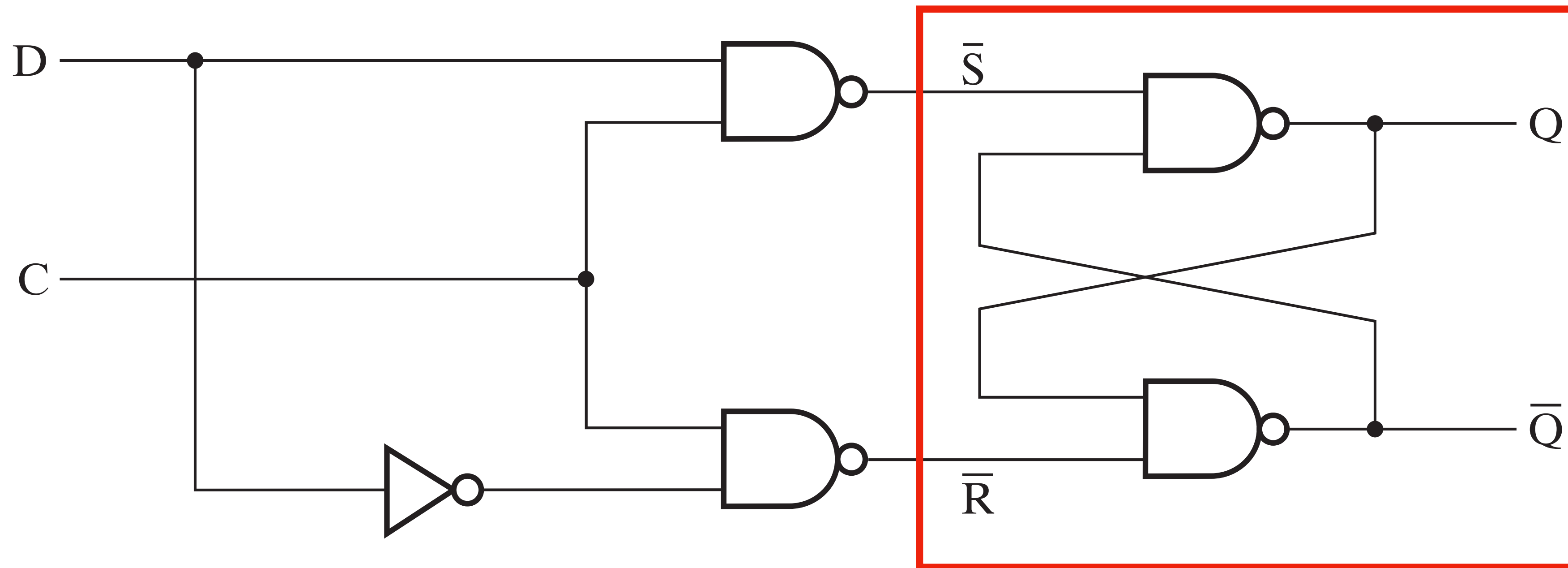

C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

- Implemented using $\overline{S}\overline{R}$ latches
- *C*: Signals changes to the stored states; *D* the value to change to


Latches

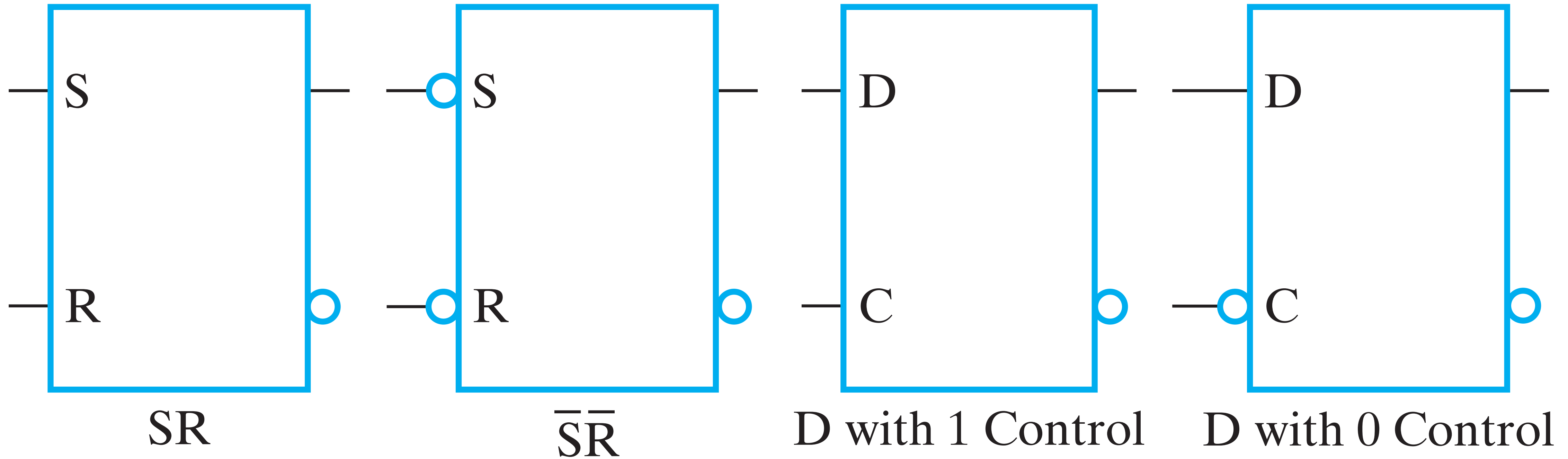

Flip-Flops

No, flip-flops are not proper shoes, nor shoes


SR Latch with Control Input

 

C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; Reset state
1	1	0	$Q = 1$; Set state
1	1	1	Undefined

- Implemented using \overline{SR} latches
- C acts as an enabler; otherwise the entire circuit functions as an SR latch

SR Latch with Control Input

 

C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	Q = 0; Reset state
1	1	0	Q = 1; Set state
1	1	1	Undefined


- Implemented using \overline{SR} latches
- C acts as an enabler; otherwise the entire circuit functions as an SR latch

Latches

- What happens if the control pulse remains active?
 - any changes in the data input will change the state of the latch immediately!
- latches are **transparent**
input can be seen from outputs while control pulse is 1

 Problems with Latches

- Transparent: changes happen instantly
- Time t , input changes
- Time $(t, t + 1)$, output stabilises
- Time $t + 1$, output stored in Storage Unit




Problems with Latches

- Transparent: changes happen
- Time t , input changes
- Time $(t, t + 1)$, output stabilises
- Time $t + 1$, output stored in Storage Unit

During this period, storage unit must keep outputting State_t , otherwise output may not stabilise

Latches cannot accomplish this!

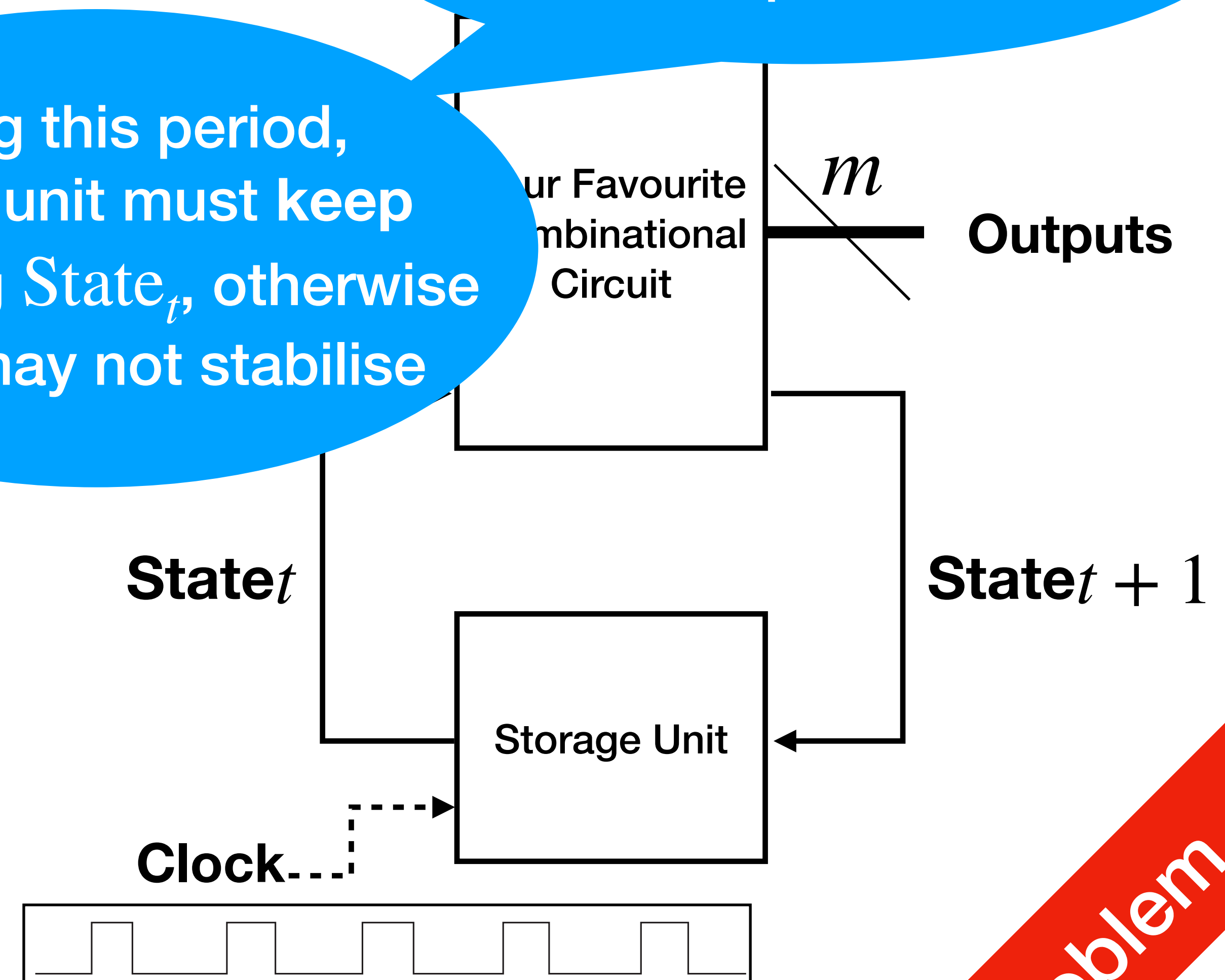


Flip-Flops


- Time t , clock flips, new input arrives
- Time $(t, t + 1)$: output State_t
 - meanwhile, new inputs arrives;
 State_{t+1} stabilises
- Time $t + 1$, clock flips, storage rewritten as State_{t+1} , new input arrives
- Time $(t + 1, t + 2)$: output State_{t+1}
- ...

Flip-Flops

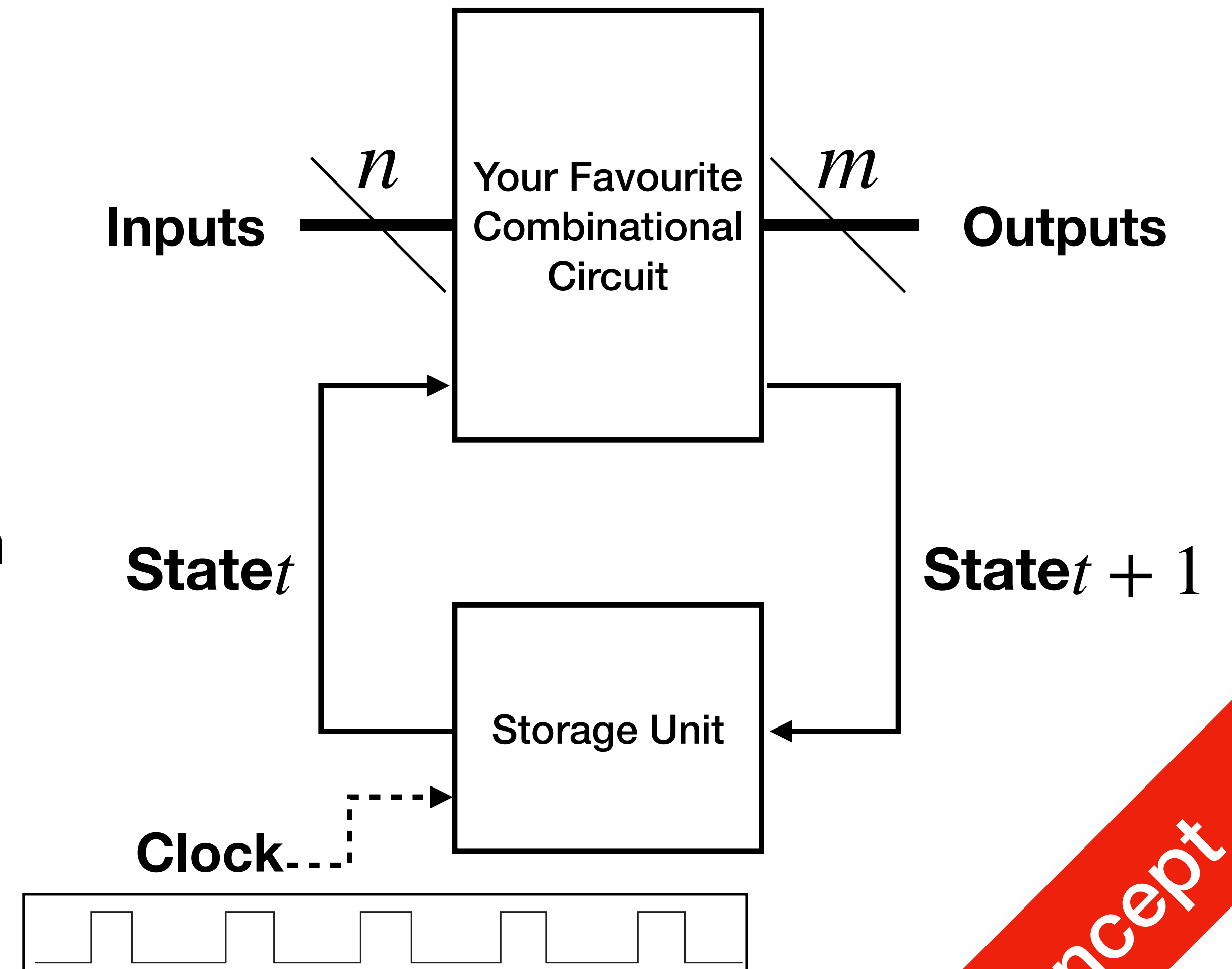- Time t , clock flips, new input arrives
- Time $(t, t + 1)$: output State_t
 - meanwhile, new inputs arrives;
 State_{t+1} stabilises
- Time $t + 1$, clock flips, storage rewritten as State_{t+1} , new input arrives
- Time $(t + 1, t + 2)$: output State_{t+1}
- ...




SR Master-Slave Flip-Flop

 


- Constructed using *SR* latches, left Master, right Slave
- Output state changes require $C = 0 \rightarrow C = 1 \rightarrow C = 0$ (Positive Pulse)

SR Master-Slave Flip-Flop

 


- Constructed using *SR* latches, left Master, right Slave
- Output state changes require $C = 0 \rightarrow C = 1 \rightarrow C = 0$ (Positive Pulse)

SR Master-Slave Flip-Flop

 


- Constructed using *SR* latches, left Master, right Slave
- Output state changes require $C = 0 \rightarrow C = 1 \rightarrow C = 0$ (Positive Pulse)

SR Master-Slave Flip-Flop

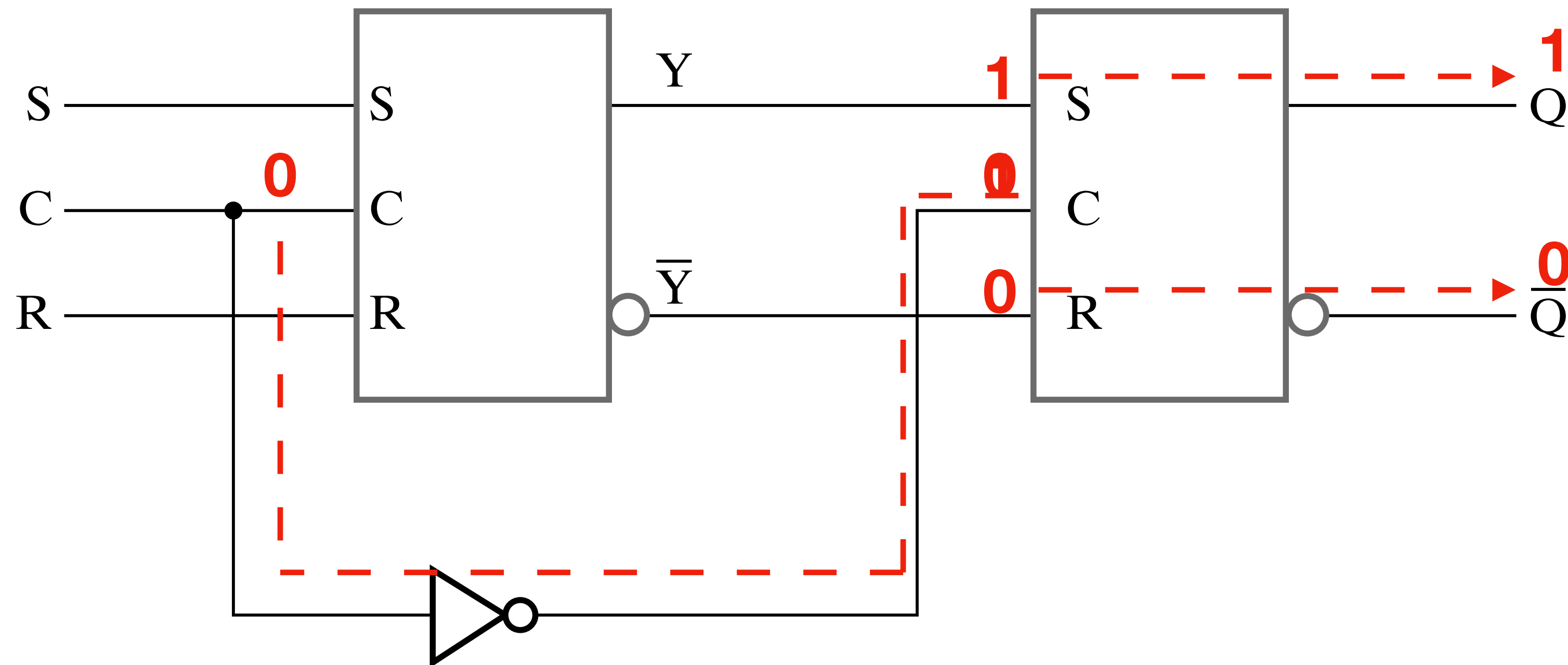


- Constructed using *SR* latches, left Master, right Slave
- Output state changes require $C = 0 \rightarrow C = 1 \rightarrow C = 0$ (Positive Pulse)

SR Master-Slave Flip-Flop

 

- Constructed using *SR* latches, left Master, right Slave
- Output state changes require $C = 0 \rightarrow C = 1 \rightarrow C = 0$ (Positive Pulse)
- Also called: **Positive Pulse Triggered *SR*** (Flip-Flop)



SR Master-Slave Flip-Flop

 


- Output state changes require $C = 1 \rightarrow C = 0 \rightarrow C = 1$ (Negative Pulse)
- **Negative Pulse Triggered *SR* (Flip-Flop)**

Implement Positive Pulse Triggered SR

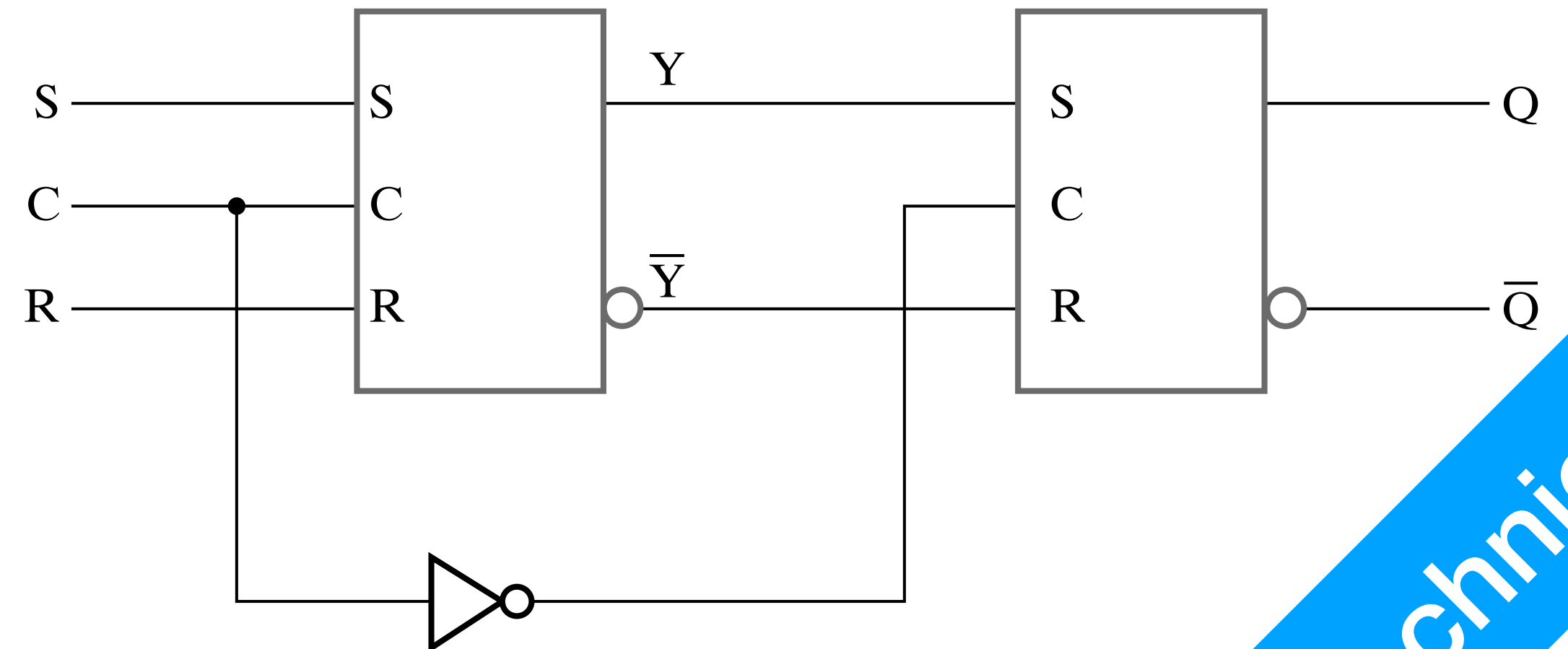 - Implement SR Latch with Control Input using $\overline{S}\overline{R}$ Latch
- Implement **Positive Pulse Triggered SR** using SR latch with Control Input




D Flip-Flop

 


- Replaces *SR* master in *SR* Master-Slave with *D* master Latch
- **Negative Edge Triggered *D*** (Flip-Flop): $C = 1 \rightarrow C = 0$

D Flip-Flop

 


- Replaces SR master in SR Master-Slave with D master Latch
- **Negative Edge Triggered D (Flip-Flop):** $C = 1 \rightarrow C = 0$

D Flip-Flop

 


- Replaces *SR* master in *SR* Master-Slave with *D* master Latch
- **Negative Edge Triggered *D*** (Flip-Flop): $C = 1 \rightarrow C = 0$

D Flip-Flop

 


- Replaces SR master in SR Master-Slave with D master Latch
- **Negative Edge Triggered D** (Flip-Flop): $C = 1 \rightarrow C = 0$


Flip Flops

 


Triggered SR

 

Triggered SR

 


Triggered D

 


Triggered D


Flip Flops

 


┐┐ Triggered SR

 

┐┐ Triggered SR

 

┐┐ Triggered D
┐┐ Triggered D

 

┐┐ Triggered D
┐┐ Triggered D

Summary

