



12.11.20 14:09

CSCI 150

Introduction to Digital and Computer System Design

Lecture 4: Sequential Circuit IV



Jetic Gū
2020 Fall Semester (S3)

Announcement

- No class this Wednesday (Remembrance Day)
- Assignment 4 will be released this week (instead of last week)




Overview

- Focus: Basic Information Retaining Blocks
- Architecture: Sequential Circuit
- Textbook v4: Ch5 5.3, 5.4; v5: Ch4 4.2 4.3
- Core Ideas:
 1. Sequential Circuit Design Procedures

Definitions

 1. **Storage Elements**
circuits that can store binary information
2. **State**
partial results, instructions, etc.
3. **Synchronous Sequential Circuit**
Signals arrive at discrete instants of time,
outputs at next time step
4. **Asynchronous Sequential Circuit**
Signals arrive at any instant of time,
outputs when ready



Definitions

3. Synchronous Sequential Circuit


Signals arrive at discrete instants of time, outputs at next time step

- Has Clock

4. Asynchronous Sequential Circuit


Signals arrive at any instant of time, outputs when ready

- May not have Clock

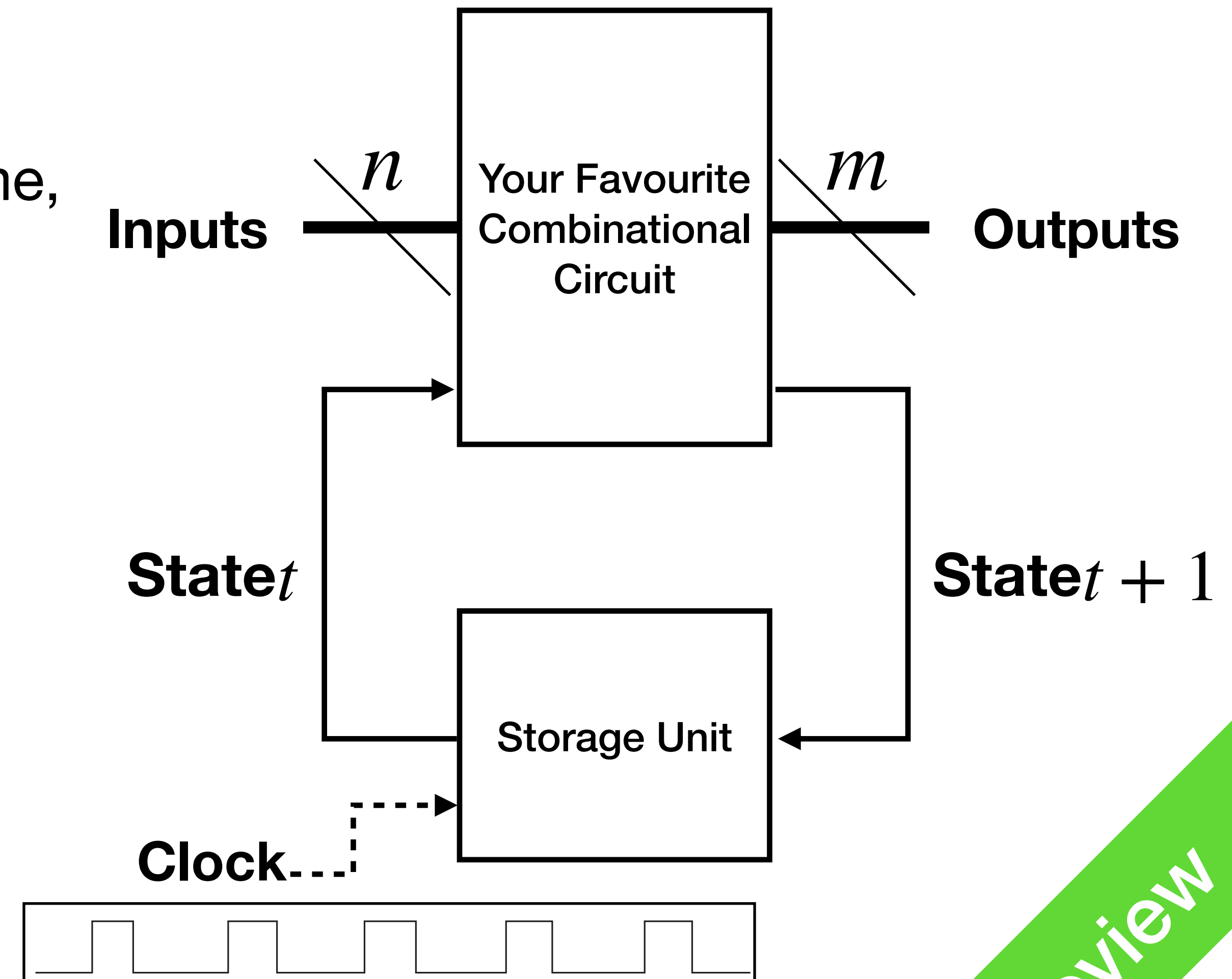


Summary

Latches

 


SR

 

D with 1 Control

Flip-Flops

 

┐ Triggered D

Sequential Circuit Design I

8 Step Design Procedures; Formulation

Systematic Design Procedures

Combinational Circuits

1. **Specification**
2. **Formulation**
3. **Optimisation**
4. **Technology Mapping**
5. **Verification**

Systematic Design Procedures

Sequential Circuits

1. **Specification**

2. **Formulation**

e.g. using **state table** or **state diagram**

TODAY'S FOCUS

3. **State Assignment**: assign binary codes to states

4. **Flip-Flop Input Equation Determination**: Select flip-flop types, derive input equations from next-state entries

5. **Output Equation Determination**: Derive output equations from the output entries


6. **Optimisation**

7. **Technology Mapping**


8. **Verification**

 0. Reset

- When the power was first turned on, the states in flip-flops are all unknown
This requires resetting!
- Flip-Flops with Reset



(a) Asynchronous Reset

 

(b) Synchronous Reset

0. Reset


- In reality, all storage devices in a computer has a Reset mode for easy resetting to all 1s or all 0s
- e.g. C: `memset(void* ptr, int value, size_t num);`
Fill blocks of memory

1. Specification

- Same as combinational

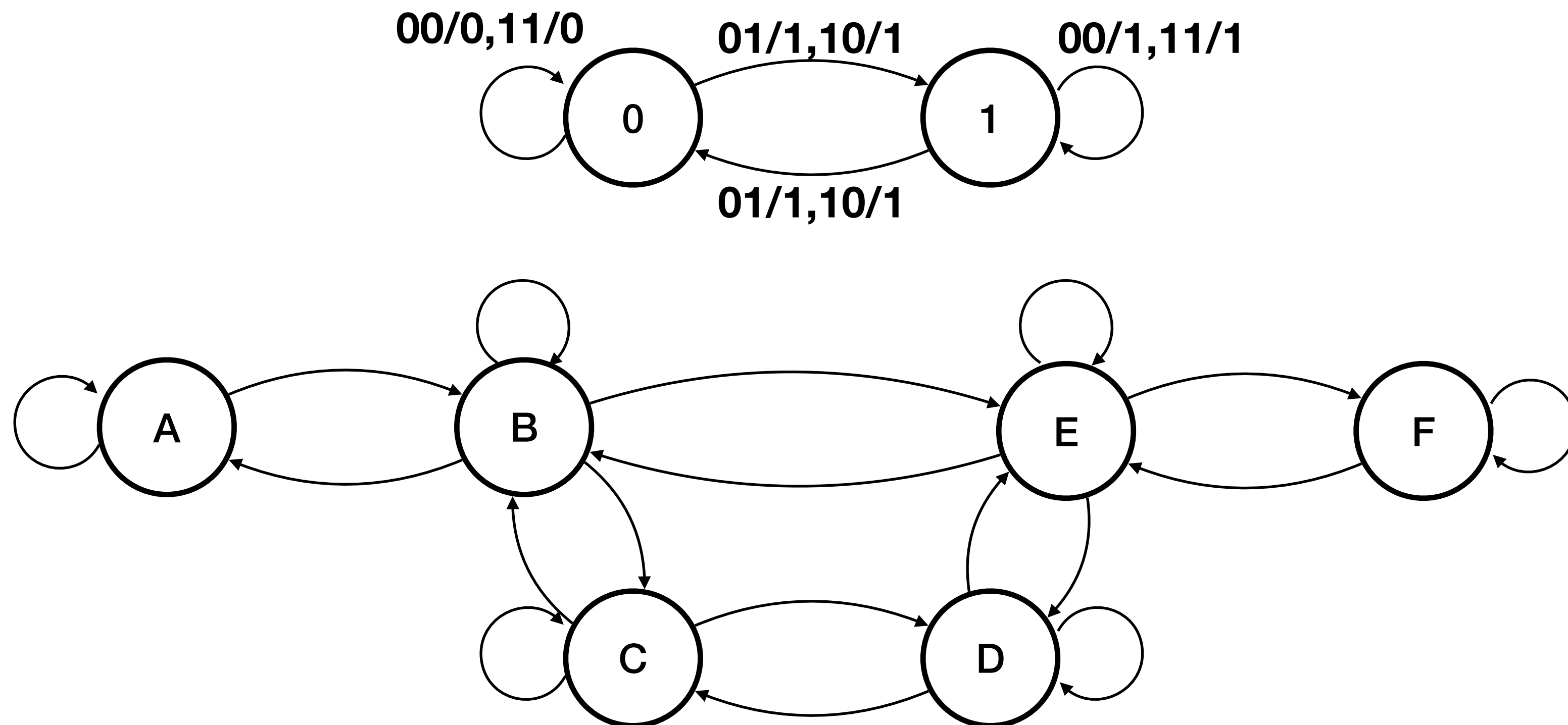
2. Formulation

- Sometimes it is more intuitive to describe state transitions then defining the states



 
2. Formulation

- Incrementer: perform $+1$ operation every CLK on 3-bit




 2. Formulation

- Simple 1-bit binary calculator
- Input: 0 button, 1 button, Add button, Equ button
- Storage: A, B: variables; I: operator




First Input

 


Example

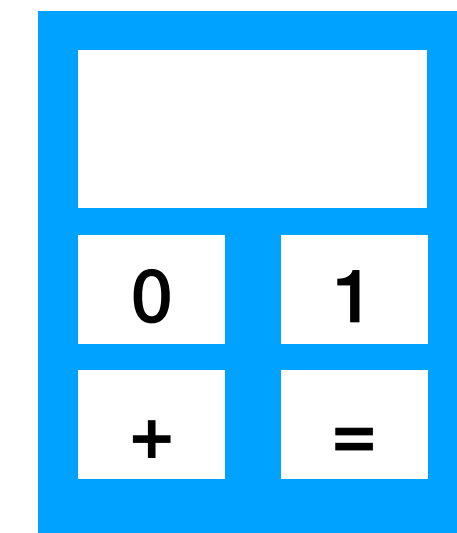2. Formulation

- Simple 1-bit binary calculator
- Input: 0 button, 1 button, Add button, Equ button
- Storage: A, B: variables; I: operator




First Input

 


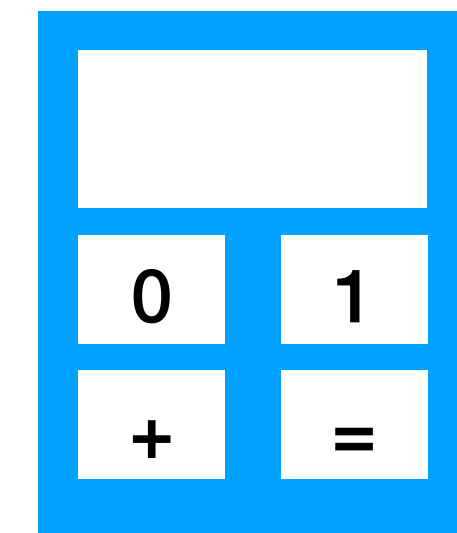2. Formulation

- Simple 1-bit binary calculator
- Input: 0 button, 1 button, Add button, Equ button
- Storage: A, B: variables; I: operator




After first input, press add

 


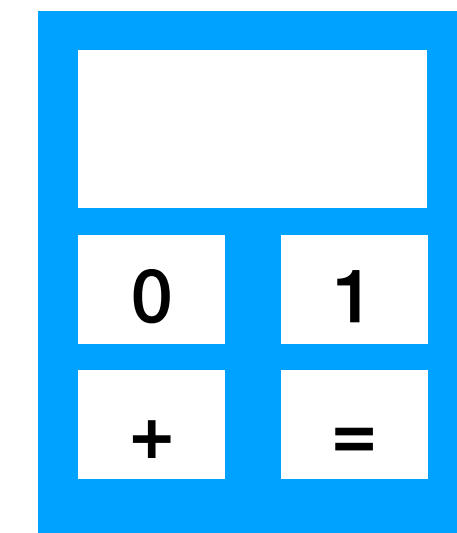2. Formulation

- Simple 1-bit binary calculator
- Input: 0 button, 1 button, Add button, Equ button
- Storage: A, B: variables; I: operator




Second input

 


Example

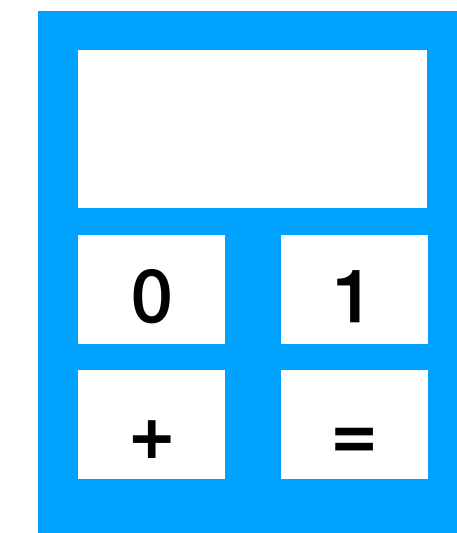2. Formulation

- Simple 1-bit binary calculator
- Input: 0 button, 1 button, Add button, Equ button
- Storage: A, B: variables; I: operator




Get result

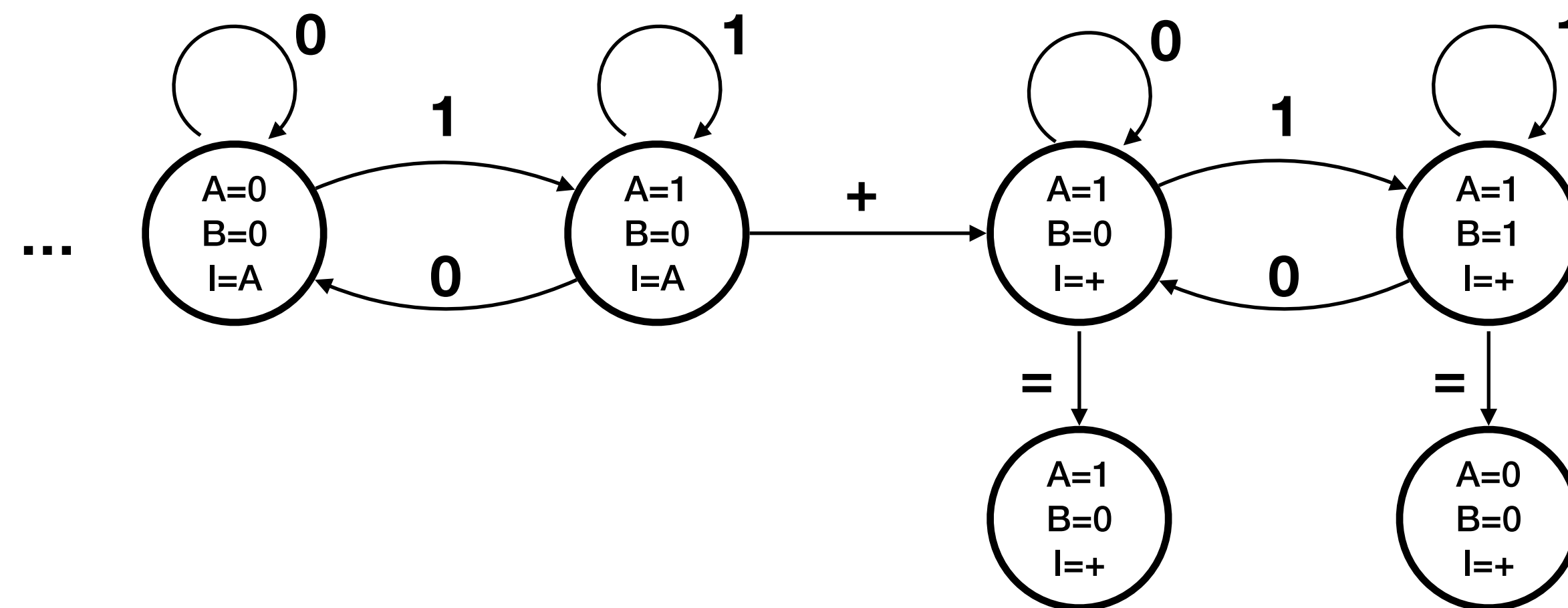


 2. Formulation

- Simple 1-bit binary calculator
- Input: 0 button, 1 button, Add button, Equ button
- Storage: A, B: variables; I: operator




Next calculation

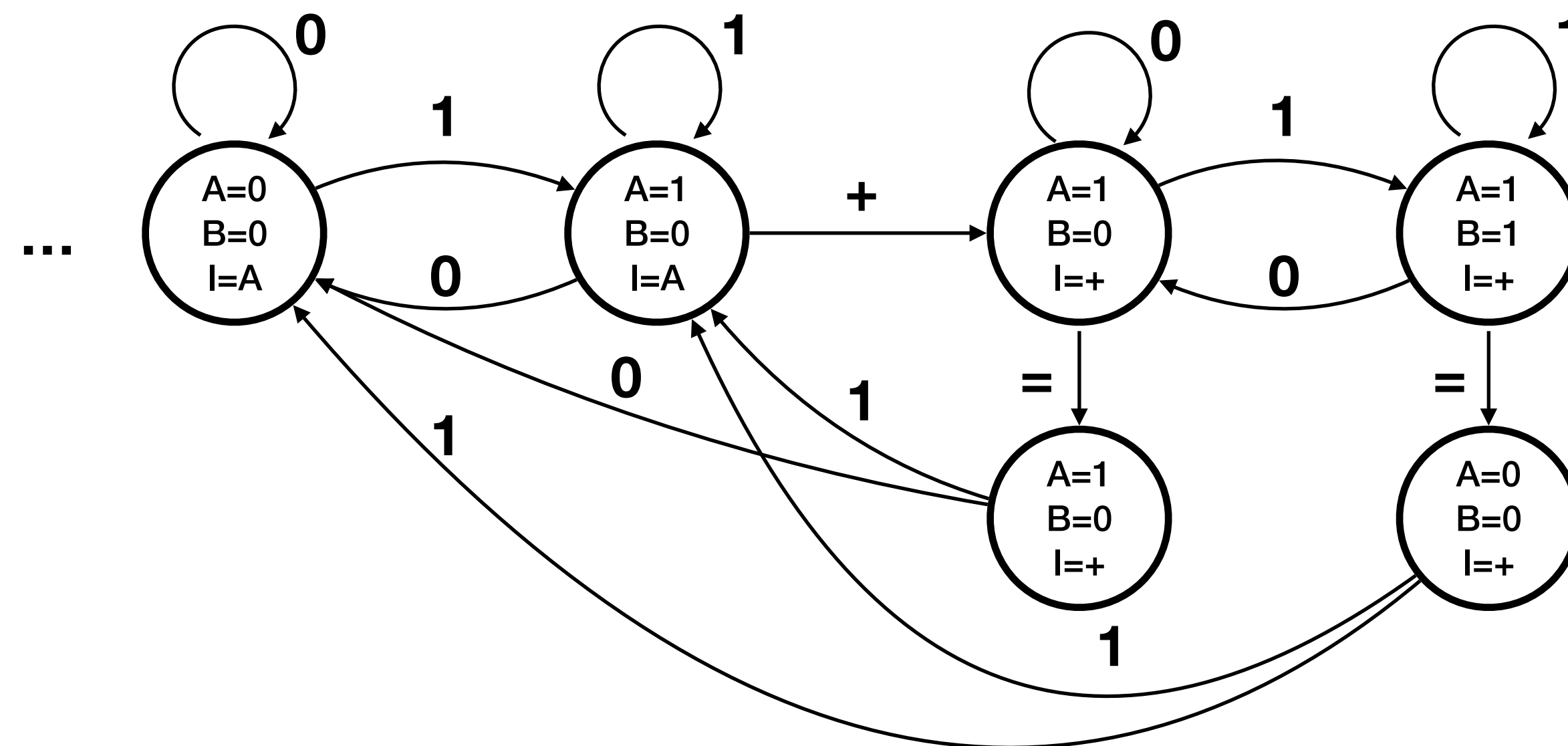

Example

 
Exercise

- Draw the state diagram of 3-bit incrementer/decrementer
- Input X : 0 for increment, 1 for decrement
- Do the state table



 
Exercise

- Draw the state diagram of rotator
 - Start state $X_3X_2X_1X_0$: original 4-bit
 - Input Y :
 - 0 for left rotation (output $X_2X_1X_0X_3$);
 - 1 for right rotation (output $X_0X_3X_2X_1$);
 - Every CLK triggers a shift



 Exercise

- Draw the state diagram of rotator
 - Start state $X_3X_2X_1X_0$: original 4-bit
 - Input Y :
 - 0 for left rotation (output $X_2X_1X_0X_3$);
 - 1 for right rotation (output $X_0X_3X_2X_1$);
 - Every CLK triggers a shift
- Try to write down the equations for each flip-flop, treat X_i as constants. Implement in LogicWorks



LogicWorks Exercise

- Implement D flip flop using D latch and SR latch
Save it as a component in your library
- Implement circuit $D_S = X \oplus Y \oplus S$, where D_S is a D flip flop
- Implement $D_A = \bar{X}A + XY$, $D_B = \bar{X}B + XA$, $Z = XB$
- Draw the state table and diagram, and verify your table with LogicWorks

