



03.02.21 10:05

CSCI 150

Introduction to Digital and Computer System Design

Lecture 2: Combinational Logical Circuits V



Jetic Gū

Overview

- Focus: Boolean Algebra
- Architecture: Combinatory Logical Circuits
- Textbook v4: Ch2 2.8, 2.9. 2.10; v5: Ch2 2.6, 2.7
- Core Ideas:
 1. Other Gate Types: XOR, NAND, NOR, Buffer, High-Impedance, Odd Function
 2. Lecture 2 Review

Boolean Algebra I-III

I. AND, OR, NOT Operators and Gates

- Simple digital circuit implementation
- Algebraic manipulation using Binary Identities

II. Standard Forms

- Minterm & Maxterm
- Sum of Products & Product of Sums



III. Optimisation Using K-Map (For 2,3,4 Variables)

Other Gate Types

Delay Propagation
XOR, NAND, NOR, Buffer



Gate Delay

Timing Diagram (**REALITY**)

  



Gate Delay

Timing Diagram (**REALITY**)

  

Gate Delay


Timing Diagram (**REALITY**)

  

Delays


- Gate Delay
 - The time required for a change in value of a signal to propagate from input to output (of a Gate)
- Propagation Delay
 - The time required for a change in value of a signal to propagate from input to output (of a Circuit)

Delays

 


- t_{pd} : Propagation Delay: longest time for propagating from input to output
- t_{PHL} : Hight2Low propagation time; t_{PLH} : Low2High propagation time;


Transport and Inertial Delays

 


Transport and Inertial Delays

 

Transport and Inertial Delays

 


Transport and Inertial Delays

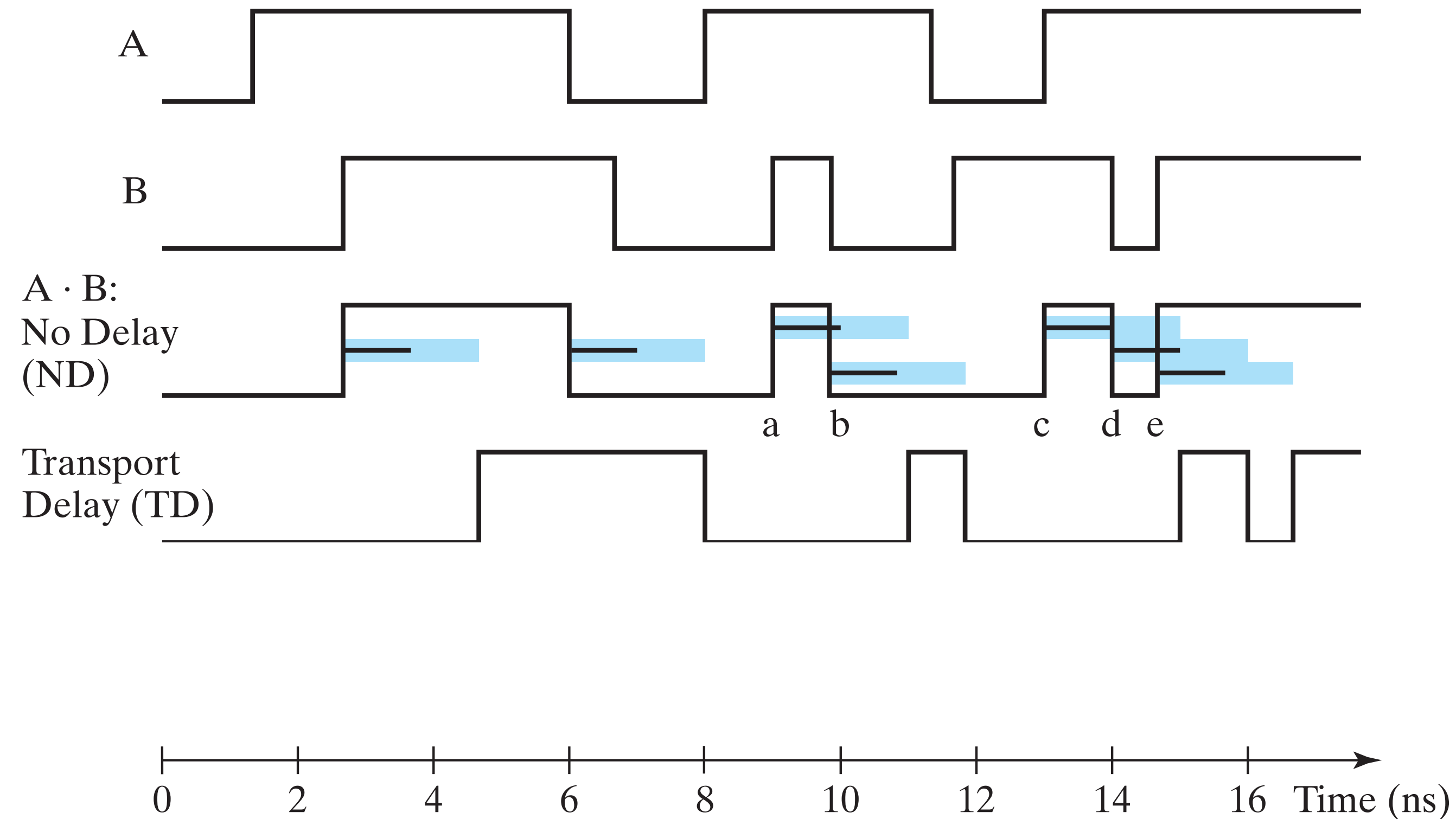

- **Transport Delay:** output in response to input changes after propagation delay

Transport and Inertial Delays

 

- **Transport Delay:** output in response to input changes after propagation delay
- **Inertial Delay:** if a value changes twice in a short time (**rejection time**), ignore

Parameters of Gate Delay


Parameters of Gate Delay

- Fan-in
number of inputs of a logic gate

Parameters of Gate Delay


- Fan-in
number of inputs of a logic gate
- Fan-out (standard load)
number of gates that each logic gate can drive while providing voltage levels in the guaranteed range is called the standard load or fan-out

Standard Load

 


- Digital circuits are driven by power, each component also takes power

Standard Load

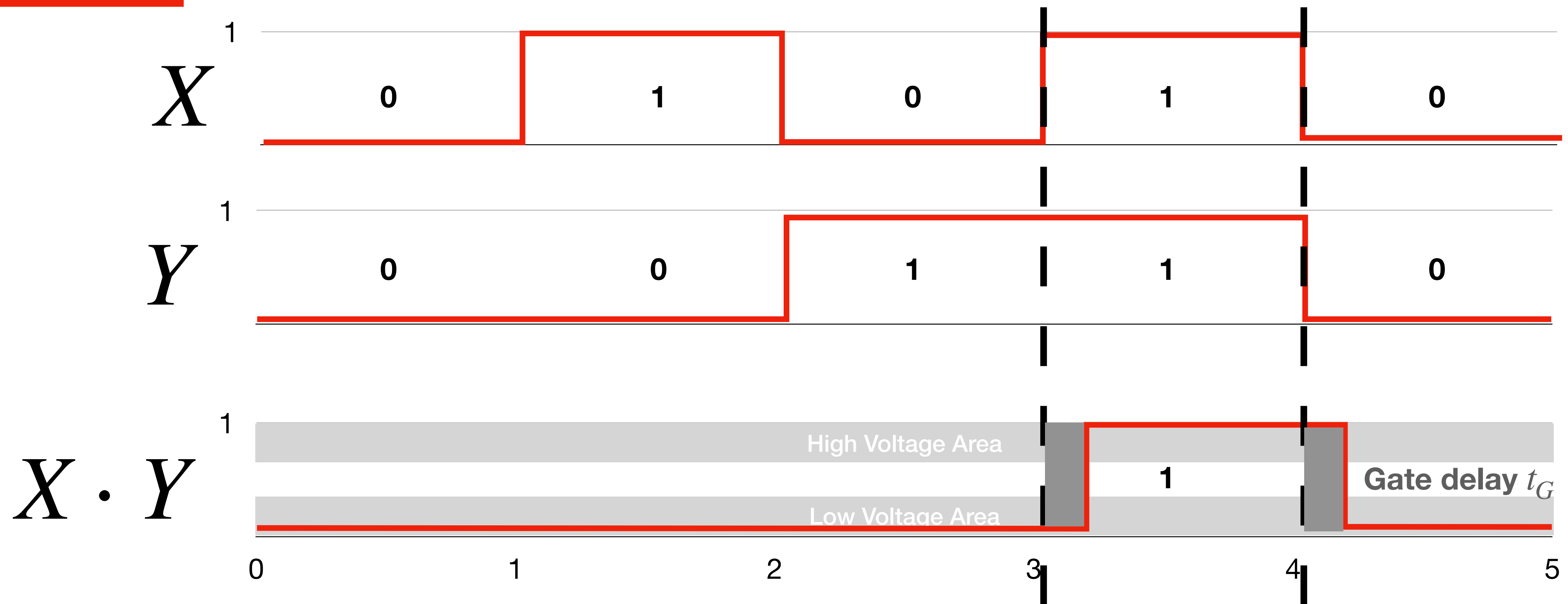


- Digital circuits are driven by power, each component also takes power

Standard Load

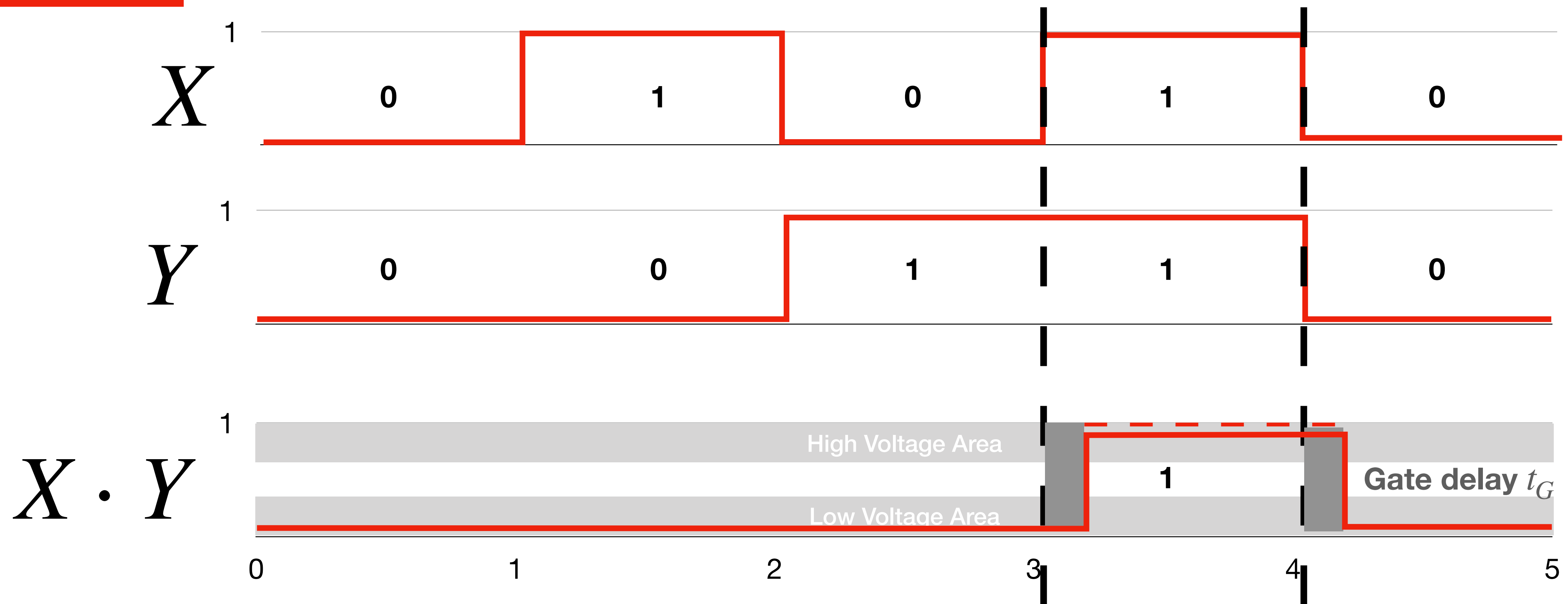


- Digital circuits are driven by power, each component also takes power

Standard Load

 


- Changes in input voltage can also affect output voltage

Standard Load

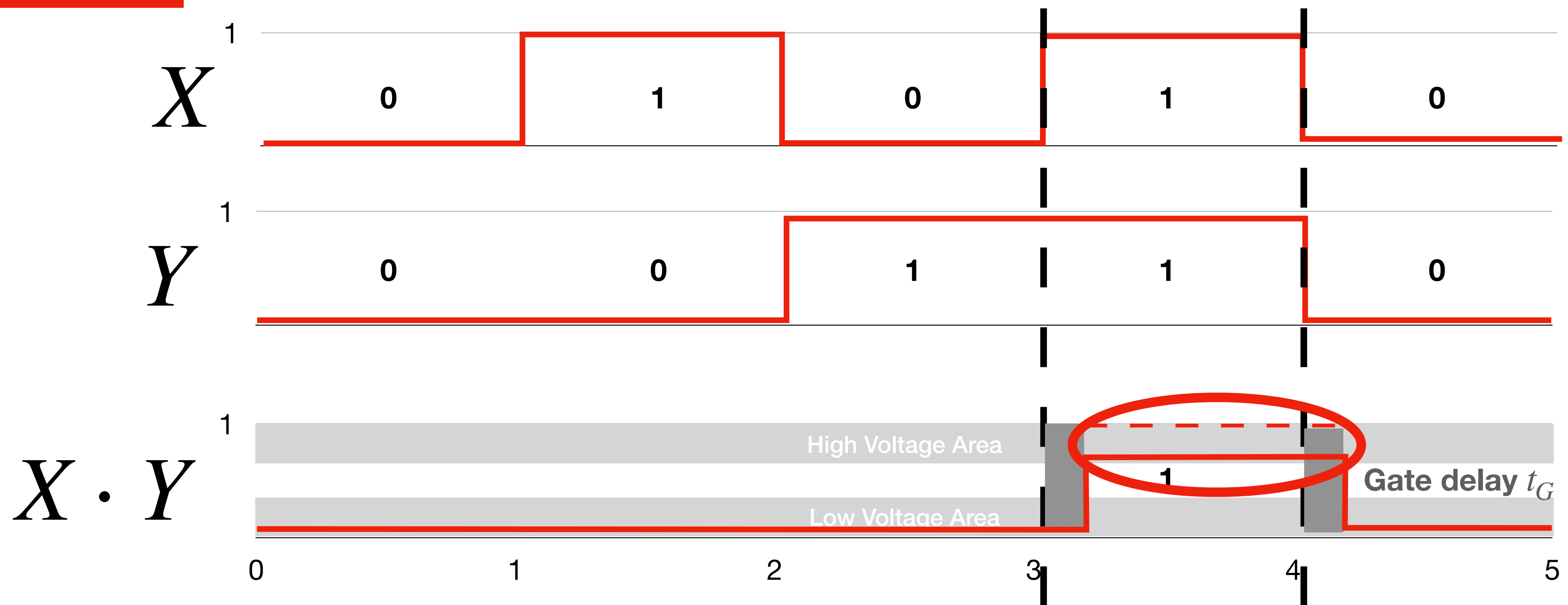

- If it takes too much power, it will not be able to guarantee output voltage
- Standard load is defining that power consumption, which also affect delay

Standard Load

 

- OR Gate: 0.8 SL; AND Gate: 1.00 SL;


- Delay for AND:

$$t_{pd} = 0.07 + 0.021 \times \sum InputSL$$

- Delay for OR:

$$t_{pd} = 0.05 + 0.02 \times \sum InputSL$$


Standard Load

 


- OR Gate: 0.8 SL; AND Gate: 1.00 SL;
- Estimation for OR2
$$t_{pd} = 0.05 + 0.02 \times (0.8 + 1.00) = 0.086\text{ns}$$
- Delay for AND:
$$t_{pd} = 0.07 + 0.021 \times \sum \text{InputSL}$$
- Precise estimation is very hard, since we lack a lot of these information
- Delay for OR:
$$t_{pd} = 0.05 + 0.02 \times \sum \text{InputSL}$$
- We can ignore this computation, but you should know roughly

Other Gates


XOR Gate
Exclusive-OR

 

Buffer

 


3-State Buffer

 


Buffer


XOR Gate
Exclusive-OR

 

Buffer

 


3-State Buffer

 


- Has delay
- Increases output Voltage
e.g.: input 0.8 V, output 1.0 V

3-State Buffer


XOR Gate
Exclusive-OR

 

Buffer

 


3-State Buffer

 


- Has delay
- Increases output Voltage
e.g.: input 0.8 V, output 1.0 V
- When $E = 0$, outputs no electricity
(Open circuit/Hi-Z/High Impedance)

3-State Buffer


XOR Gate
Exclusive-OR

 

Buffer

 

3-State Buffer

 


- Has delay
- Increases output Voltage
e.g.: input 0.8 V, output 1.0 V
- When $E = 0$, outputs no electricity
(Open circuit/Hi-Z/High Impedance)




3-State Buffer


XOR Gate
Exclusive-OR

 


Buffer

 

3-State Buffer

 


 - Has delay
- Increases output Voltage
e.g.: input 0.8 V, output 1.0 V
- When $E = 0$, outputs no electricity
(Open circuit/Hi-Z/High Impedance)




3-State Buffer


XOR Gate
Exclusive-OR

 

Buffer

 

3-State Buffer

 


3-State Buffer Truth Table

E	X	Z
0	0	Hi-Z
0	1	Hi-Z
1	0	0
1	1	1

XOR Gate

XOR Gate
Exclusive-OR

 


XOR Truth Table

X	Y	$Z = X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

XOR Gate

XOR Gate
Exclusive-OR

 

XOR Truth Table

X	Y	$Z = X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

XOR Gate

- $X \oplus 0 = X$

- $X \oplus X = 0$

- $X \oplus \bar{Y} = \overline{X \oplus Y}$

- $X \oplus 1 = \bar{X}$

- $X \oplus \bar{X} = 1$

- $\bar{X} \oplus Y = \overline{X \oplus Y}$

Odd and Even Functions

- Odd Functions
 - Outputs 1 if the **number of 1s** in the input is an **Odd** number
 - 2 variables: XOR
- Even Functions
 - Outputs 1 if the **number of 1s** in the input is an **Even** number
 - 2 variables: XNOR

Odd Function K-Map


		Y			
		00	01	11	10
X	0		1		1
	1	1		1	

(a) $X \oplus Y \oplus Z$


		C			
		00	01	11	10
A	00		1		1
	01	1		1	
	11		1		1
	10	1		1	

(b) $A \oplus B \oplus C \oplus D$

Odd Function Boolean Expressions

 


(a) $P = X \oplus Y \oplus Z$

 


(b) $C = X \oplus Y \oplus Z \oplus P$

N-Gates


NOT Gate

 


NAND Gate

 

NOR Gate

 

XNOR Gate

 

Summary

Summary

- Delay: Remember the Definitions!

Summary

- Delay: Remember the Definitions!
- Gate Delay and Propagation Delay

Summary

- Delay: Remember the Definitions!
- Gate Delay and Propagation Delay
- Transport and Inertial Delays

Summary

- Delay: Remember the Definitions!
 - Gate Delay and Propagation Delay
 - Transport and Inertial Delays
 - Standard Load

Summary

- Delay: Remember the Definitions!
 - Gate Delay and Propagation Delay
 - Transport and Inertial Delays
 - Standard Load
- Other Gates: Remember the Definitions!

Summary

- Delay: Remember the Definitions!
 - Gate Delay and Propagation Delay
 - Transport and Inertial Delays
 - Standard Load
- Other Gates: Remember the Definitions!
 - XOR, Buffer, 3-State, NAND, NOR