

Jetic Gū

Columbia College

This assignment is due on 26 June 2020

Please remember to write your name and student number.

You must complete the following assignment and submit a PDF of relevant questions. Handwritten submissions and proprietary formats (e.g. Pages or MS Word) will not be accepted. You will also need to upload LogicWork circuit design file. Then upload a single ZIP file to Moodle.

Submission File structure:

```
submission.zip
  - answer.pdf
  - circuit1-1.cct
  - circuit1-2.cct
  - circuit1-3.cct
  - circuit1-4.cct
  - circuit1-5.cct
  - circuit2-1.cct
  - circuit2-2.cct
  - circuit2-3.cct
  - circuit2-4.cct
  - circuit3.cct
  - circuit4.cct
  - circuit5.cct
  - lib.clf
```

The first 4 circuit files (1-1, 1-2, 1-3, 1-4) are 0.5pt each, the rest are 1pt each.

Lab 2

1. Save the library and circuit files we created in class containing the following designs in the final ZIP file:
 1. 2-to-4 Decoder (`circuit1-1.cct`);
 2. 3-to-8 Decoder implemented using the 2-to-4 Decoder (`circuit1-2.cct`);
 3. 4-to-2 priority encoder with validity bit (`circuit1-3.cct`);
 4. 4 channel 1bit Multiplexer implemented using the 2-to-4 Decoder (`circuit1-4.cct`);
 5. 4 channel 4bit Multiplexer implemented using the 4 channel 1bit Multiplexers (`circuit1-5.cct`);
 6. Include the above designs in your library file (`lib.clf`), I must be able to use these components in your library file, or 50% of the points will be lost.
2. Save the library and circuit files we created in class containing the following designs in the final ZIP file:
 1. 1-bit binary adder (`circuit2-1.cct`);
 2. 4-bit binary adder (`circuit2-2.cct`);

- 3. 4-bit binary adder-subtractor with XOR and Adder (`circuit2-3.cct`);
- 4. 4-bit binary plus 1 incremter (`circuit2-4.cct`);
- 5. Include the above designs in your library file (`lib.clt`), I must be able to use these components in your library file, or 50% of the points will be lost.

- 3. Implement the following Boolean function with an 4-to-1 1bit multiplexer and optionally, a single inverter:

$$F(A, B, C) = \Sigma m(2,4,6)$$

You must ONLY use value-fixing and the components stated above. Save the circuit as `circuit3.cct` .

- 4. You are commissioned to design the light controller for a Mr. Rob Banks. Mr. Rob Banks' house has a proximity sensor (S_1) near the entrance controlling the light (L_1) there, 2 switches (S_2, S_3) inside the house controlling (L_2, L_3). In addition, a master switch M can be used to turn both L_2 and L_3 off, regardless of the states of S_2 and S_3 .

A. Perform formulation and optimisation, include the truth table and boolean expressions in the PDF (2.5pt).

B. Perform Technology mapping. Use `binary switches` in LogicWorks for S_1, S_2, S_3 , and M , use `binary probs` as L_1, L_2, L_3 , save the circuit as `circuit4.cct` .

- 5. You are commissioned to design a simple petrol gauge for Mr. Rob Banks' volume controller. Volume control is realised though the use of a turning wheel, and you need to convert the degree of rotation to a binary integer indicating volume levels. As the user rotates the wheel into fixed positions, one of the inputs I_0, I_1, I_2, I_3 will receive a positive signal, while the rest remain 0. Your output $O_1 O_0$ should be a binary number, indicating the current level, with 00 being Min, 11 being Max.

A. Perform formulation and optimisation, include the steps in the PDF (2.5pt).

B. Perform Technology mapping using a priority encoder, save as `circuit5.cct`

