

Jetic Gū

Columbia College

This assignment is due on 8 Aug 2022.

Please remember to write your name and student number.

You must complete the following assignment and submit a PDF of relevant questions. Handwritten submissions and proprietary formats (e.g. Pages or MS Word) will not be accepted. You will also need to upload LogicWork circuit design file. Then upload a single ZIP file to Moodle.

Submission File structure:

```

submission.zip
  - answer.pdf
  - circuit1-1.cct
  - circuit1-2.cct
  - circuit2.cct
  - circuit3.cct
  - circuit4.cct
  - lib.clf

```

The files `circuit1-1`, `circuit1-2`, `circuit3` are 1pt each, `circuit2` 2pt, `circuit3` 3pt, `answer.pdf` 2pt.

## Lab 4

- (PDF) Datapath conceptual question: assume a datapath with a 4-bit register array (4 GPRs inside) that can perform certain functions. The datapath takes input `Func2:0` from the control unit for function selection, `reg1:0` and `reg_21:0` for register selection, `Func_in3:0` for value input.

<code>Func2:0</code>	Register Operation
000	No change
001	Clear a single register to 0, selected by <code>reg1:0</code>
010	Perform register transferring, assign the value of register at address <code>reg_21:0</code> to register at <code>reg1:0</code> .
011	Load value from <code>Func_in3:0</code> into a single register, selected by <code>reg1:0</code>
110	Perform addition of 2 register values, selected by <code>reg1:0</code> and <code>reg_21:0</code> , store the output to register with address <code>reg1:0</code> . (Use the adder-subtractor functional block)
111	Perform subtraction of 2 register values, selected by <code>reg1:0</code> and <code>reg_21:0</code> , store the output to register with address <code>reg1:0</code> . (Use the adder-subtractor functional block)

Write down the sequence for all necessary inputs for computing  $4 + 5 - 7$ . You will need to load number 4, 5, 7 into the datapath, then perform the necessary calculation, and finally store the result in register number 0. (2pt)

Hint: here's a sample for loading value 4 into register number 0, and 5 into register 1 (one line per):

`Func2:0 = 011, reg1:0 = 00, Func_in3:0 = 0100`

`Func2:0 = 011, reg1:0 = 01, Func_in3:0 = 0101`

2. Register design:
  - A. Draw the circuit diagram of a D Flip-Flop with EN, using the `D flip-flop wo/SQ` component in the system library. Save it as a component in your library, as well as in a circuit file (`circuit1-1.cct`).
  - B. Draw the circuit diagram of a 4bit Register using the above D Flip-Flop with EN, your register must have  $D_3D_2D_1D_0$ ,  $EN$ ,  $C$ , and  $R$  as input ports, and  $Q_3Q_2Q_1Q_0$  as output (`circuit1-2.cct`).
3. Register array: draw the circuit diagram of a Register array with 4 registers, that meets the following specification (`circuit2.cct`):
  - A. the register array will have one 4bit `data_in` bus providing new values to be stored, 2bit `reg_in` bus specifying the register to take in new values;
  - B. one 4bit `data_out` bus outputting values from the register array, selected by the 2bit `reg_out` bus;
  - C. a single `Clear` switch that can clear all registers to 0; and
  - D. a single `CLK` switch simulating the clock unit.
  - E. you should use your own register in Q1, 2-to-4 decoder, 4channel 4bit multiplexer. I also recommend using the HEX display and keyboards to help run simulations.
4. Datapath functional block: implement a 4bit Bitwise NOT component (`circuit3.cct`).
5. Final assembly:
  - A. Copy your design from `circuit2.cct`, name it `circuit4.cct`.
  - B. Overall Inputs:
    - I. `func_in`, a hex keyboard
    - II. `mode`, a switch for functional block mode
    - III. `func`, a hex keyboard, using least significant 2bits for function selection
    - IV. `reg_in`, a hex keyboard, using least significant 2bits
    - V. `reg_out`, a hex keyboard, using least significant 2bits
    - VI. `reg_out_2`, a hex keyboard, using least significant 2bits
    - VII. `CLK`, a switch for simulating clock
    - VIII. `Clear`, a switch for clearing all registers

- C. You should have 4 functional blocks, selected by 2bit input bus `func`:
- I. Function 0: register assignment, takes input from a HEX keyboard (`func_in`);
  - II. Function 1: register transferring, takes input from the register output bus (`data_out`);
  - III. Function 2: Bitwise NOT, takes input from the register output bus (`data_out`), outputs its bitwise complement.
  - IV. Function 3: Adder-Subtract, takes input from the register output bus (`data_out`), and another register (`data_out_2`), specified by 2bit `reg_out_2` bus. There should also be a mode switch input, selecting between performing addition and subtraction.
- D. The output from the functional block selected by `func` will be fed back into the register array on `data_in`, replacing the keyboard in `circuit2.cct`.