Jetic Gū

Columbia College

Please remember to write your name and student number.

You must complete the following assignment and submit a PDF of relevant questions. Handwritten submissions and proprietary formats (e.g. Pages or MS Word) will not be accepted. You will also need to upload LogicWork circuit design file. Then upload a single ZIP file to Moodle.

Submission File structure:

All circuit files are 1pt each.

Lab 2

- 1. Save the library and circuit files we created in class containing the following designs in the final ZIP file:
 - 1. 3-to-8 Decoder implemented using the 2-to-4 Decoder (circuit1-1.cct);
 - 2. 4-to-2 priority encoder with validity bit (circuit1-2.cct);
 - 3. 4 channel 4bit Multiplexer implemented using the 4 channel 1bit Multiplexers (circuit1-3.cct);
 - 4. Include the above designs in your library file (lib.clt), I must be able to use these components in your library file, or 50% of the points will be lost.
- 2. Save the library and circuit files we created in class containing the following designs in the final ZIP file:
 - 1. 4-bit binary adder (circuit2-1.cct);
 - 2. 4-bit binary adder-subtractor with XOR and Adder (circuit2-2.cct);
 - 3. 4-bit binary plus 1 incrementer (circuit2-3.cct);
 - 4. Include the above designs in your library file (lib.clt), I must be able to use these components in your library file, or 50% of the points will be lost.

3. Implement the following Boolean function with an 1bit 4-to-1 multiplexer and optionally, a single inverter:

$$F(A, B, C) = \Sigma m(2,4,6)$$

You must ONLY use value-fixing and the components stated above. Save the circuit as circuit3.cct.

4. Implement the following Boolean function with a 3-to-8 decoder:

$$F(A, B, C) = \Sigma m(1, 2, 3, 6)$$

You must ONLY use value-fixing and the components stated above. Save the circuit as circuit4.cct.

- 5. A parity checker is a component that verifies the parity of the entire input. For example, a 9bit even parity checker would be able to tell that 100010001 contains error, while 000110000 does not. Given 9bit input $A_8 \dots A_0$, design an even parity checker that outputs 0 when no error is found, and 1 when there is. You should store the implemented component as a 9bit Parity Checker in your library, and circuit as circuit5.cct.
- 6. Implement an unsigned selective 2s complementer. It should take 4bits $A = A_3 \dots A_0$ and C as input, $D = D_3 \dots D_0$ as output. It should output A when C = 0, the unsigned 2s complement of A when C = 1. You should store the component as a 4bit 2s Comp in your library, and circuit as circuit6.cct.