

Jetic Gū

1. Handwritten submissions and proprietary formats (e.g. Pages or MS Word) **will not be graded**.
2. Mathematical expressions must be written entirely using LaTeX, otherwise **50%-100%** of marks will be deducted.
3. Circuits must be **tested** using switches/probs against a truth table. Untested circuits will receive 0.

Submission File structure:

```

submission.zip
  - myfloat.py
  - Adder16bit.dvw
  - AddSub16bit.dvw
  - circuit1.cct
  - circuit2.cct
  - csci250.clf

```

The dwv files are 2.5pt each, myfloat.py is worth 5pt.

## Lab 1

1. Float point conversion. In this question, you are required to programme a custom float point converter/adder in python (5pt). Here are the instructions:
  1. Download [jetic.org/dl/myfloat.py](http://jetic.org/dl/myfloat.py) and [jetic.org/dl/myfloat\\_test.py](http://jetic.org/dl/myfloat_test.py)
  2. You should modify the `add` and `todec` methods in `myfloat.py`, such that your float class can accept any number of bits for exponent and mantissa.
  3. You can test your implementation by using the provided `myfloat_test.py`. You should add more test cases, and do not change the interface of the `MyFloat` class.
  4. Only normal float numbers will be tested, not subnormal numbers. The exponent offset is set to  $-2^{e-1} + 1$ , where  $e$  is the number of bits for the exponent.
  5. Submit `myfloat.py` only for this question.
2. Implement a 16bit Unsigned Binary Adder (2.5pt).
  1. Use Model Wizard to create a component called `Adder16bit`;
  2. Put input `X`, `Y` as 16bit buses, input `Z` as single bit; put output `S` as a 16bit bus, output `C` as single bit;
  3. Use `std_logic_arith` to implement the addition (1pt);
  4. Make sure `C` outputs the correct value (1.5pt). (Hint: use concatenation and vector signals)
  5. Show your component working in `circuit1.cct` using HEX keyboards and switch.
3. Implement a 16bit Unsigned Binary Adder-Subtractor (2.5pt).
  1. Use Model Wizard to create a component called `AddSub16bit`;
  2. Put input `X`, `Y` as 16bit buses, input `AS` as 1bit; put output `O` as a 16bit bus, output `C` as single bit;

3. Use similar code from Q2 to implement addition, then modify the code so `AS` switches between addition (0) and subtraction (1) (2.5pt)
4. Show your component working in `circuit2.cct` using HEX keyboards and switch.